

Lessons and Challenges for Future Mixed-Signal, RF, and Memory Circuits

Akira Matsuzawa




Tokyo Institute of Technology

**Can we verify the analog circuits perfectly
by circuit simulator?**

- **Bugs of system level design**
- **Lack of well device models**
- **Wrong circuit simulation**
- **Effects of parasitic components**
 - **Not only in IC but also external components (package, PCB, etc.)**
- **Influences of EM fields**

Ex.1 Hung-up: wrong system level design 3

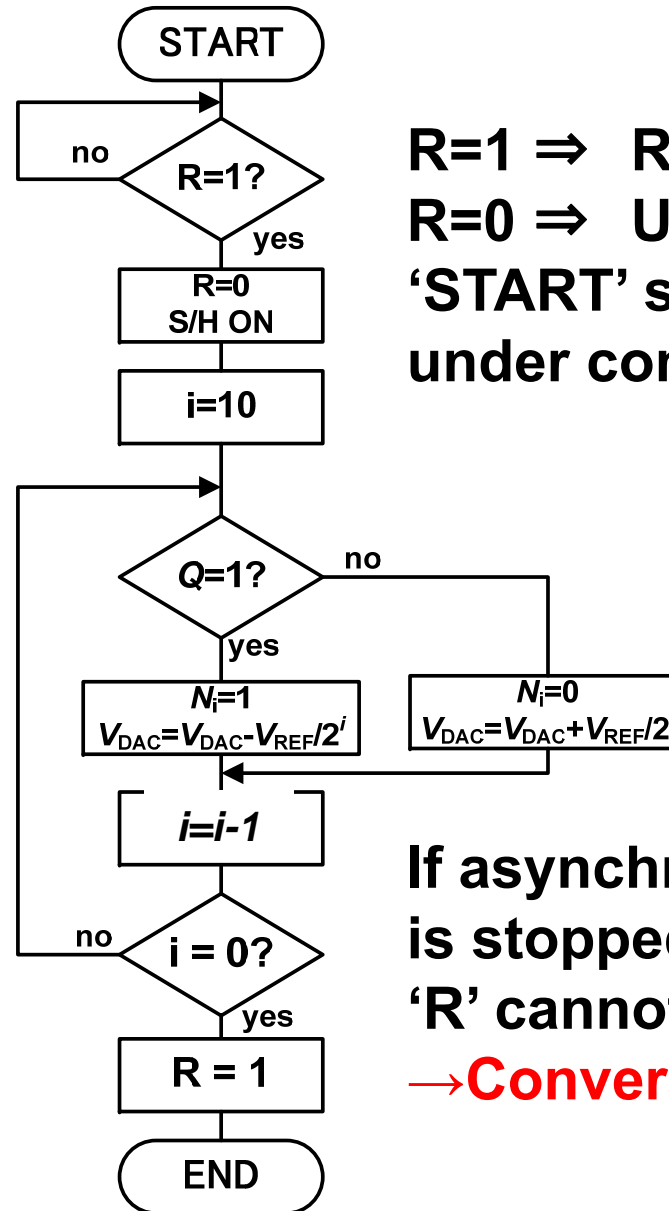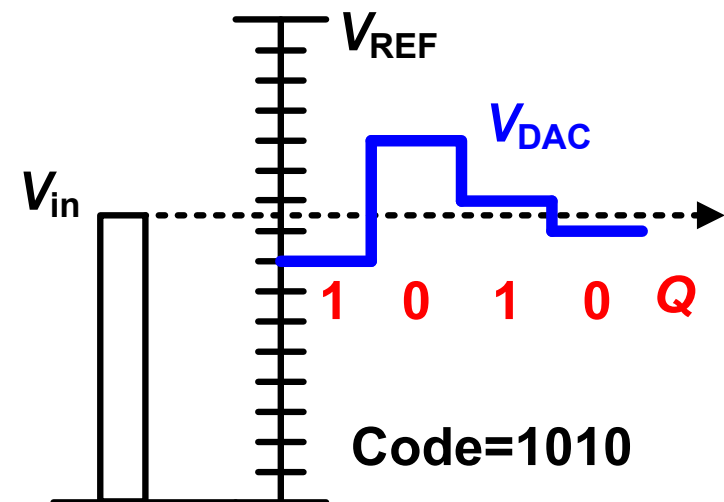 50MS/s SAR ADC suddenly stopped after 1 hour from power-on .
 Error rate: 10^{-11} ← Can we simulate?




R=1 ⇒ Ready
 R=0 ⇒ Under Conversion
 ‘START’ signal is ignored under conversion.

If asynchronous operation is stopped,
 ‘R’ cannot be ‘1’ .
 → Conversion is stopped.


Ex.2 Wrong circuit simulation

4

 Sometimes circuits have two steady-states.
Designers have to set a initial condition carefully.





CMOS oscillator with
DC-cut LC tank

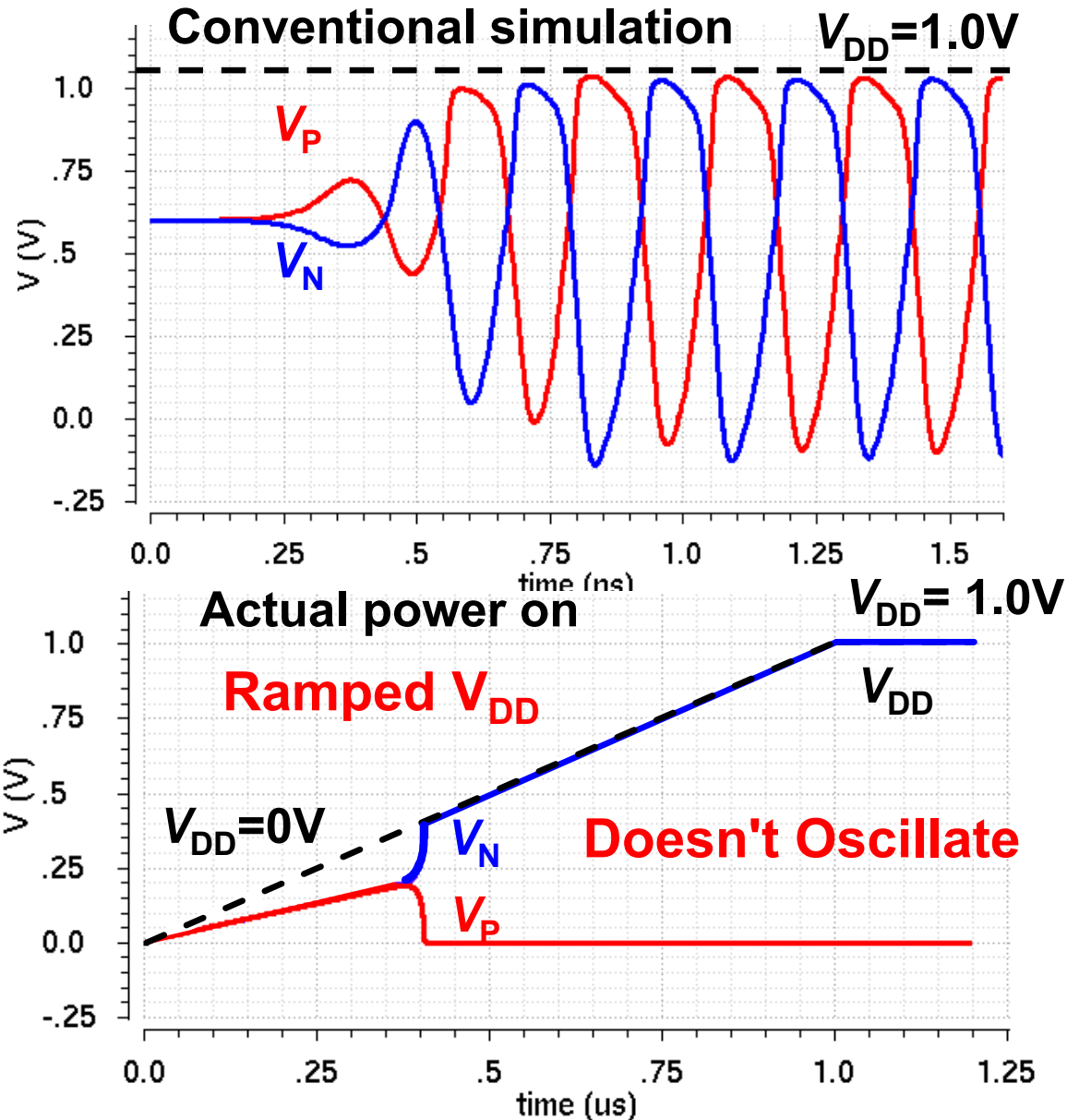


Ex.3 Different result: Effect of inductance 5

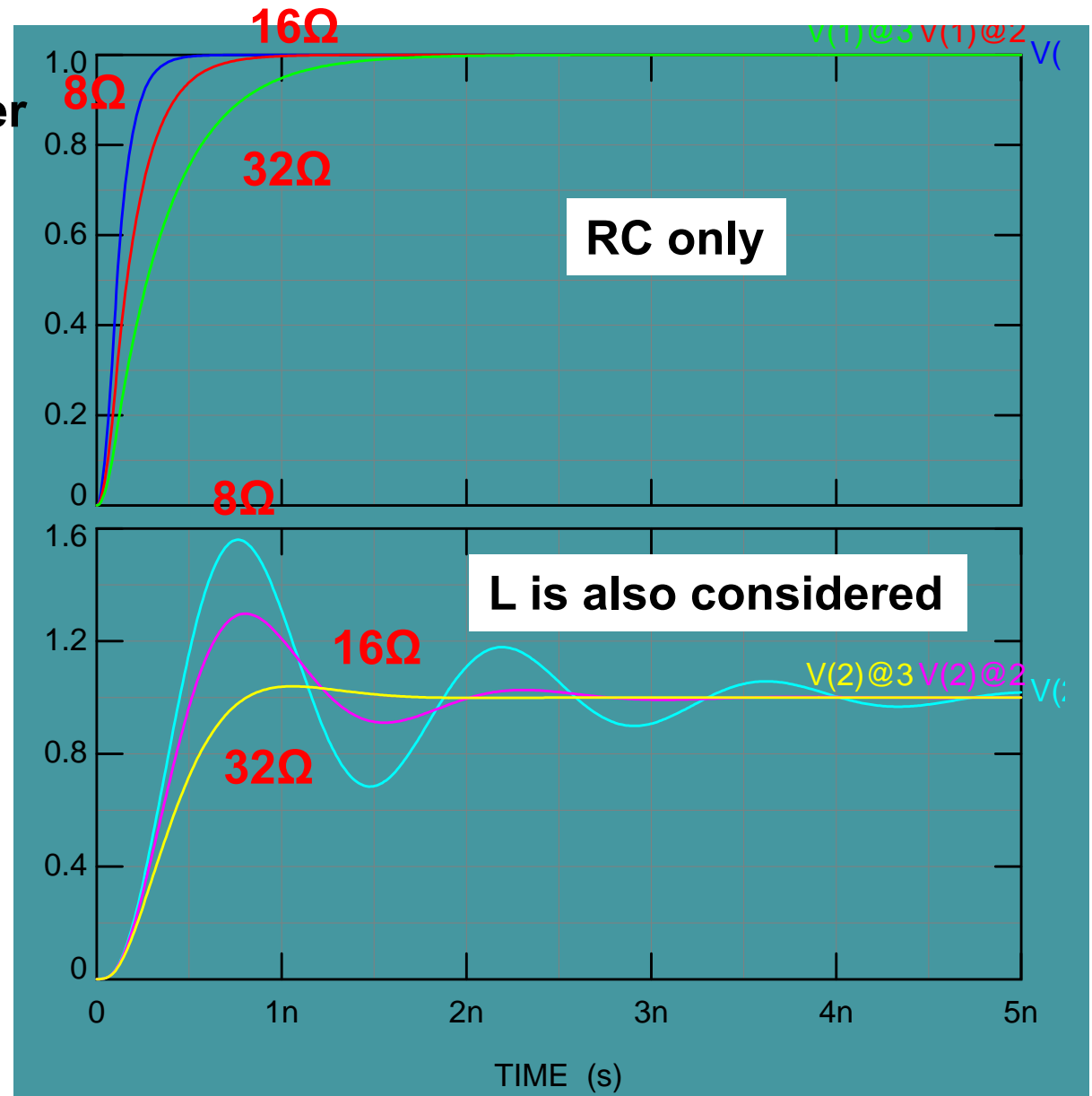 If inductance is neglected,
The smaller resistance is the better
for fast settling.
However, actual circuit contains
Inductive component; wires.
If it is considered,
Smaller resistance makes large
Ringing. The optimum resistance
exists.




Ex.4 Parasitic components


Mutual inductance between wires

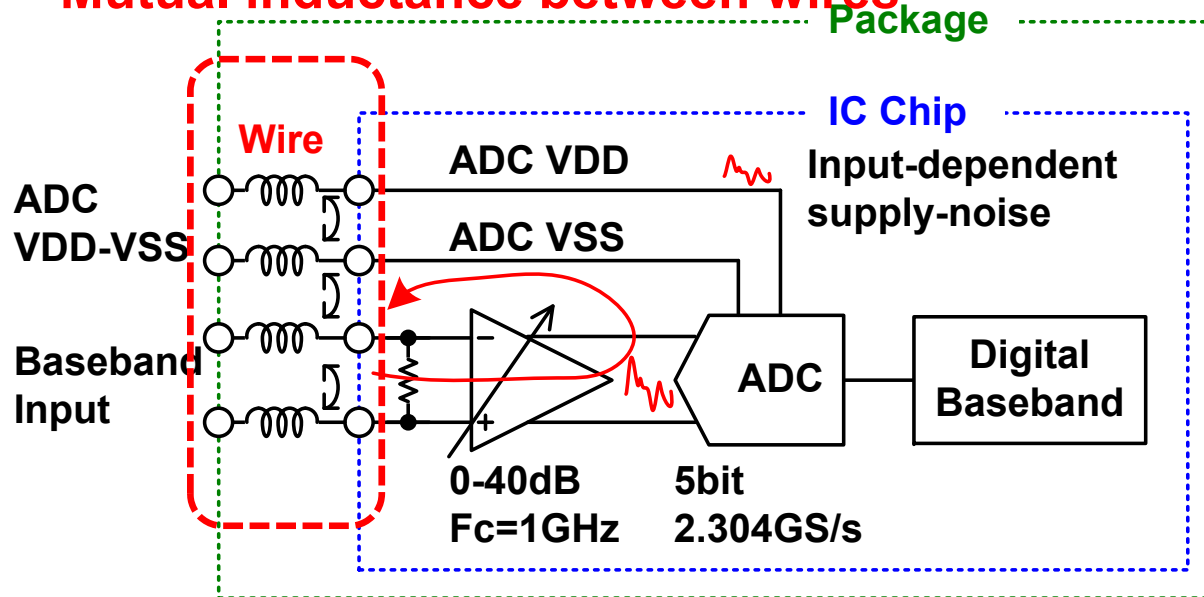

 Mutual inductance of package wire often forms feedback loop resulting in oscillation.



Wire coupling effect

 


Revised version

Small design margin: V_T of transistor 7

V_T of 40nm CMOS transistor is quite high of 0.6V. ($V_{GS}=0.8V$)

PVT variation is 220-240mW.

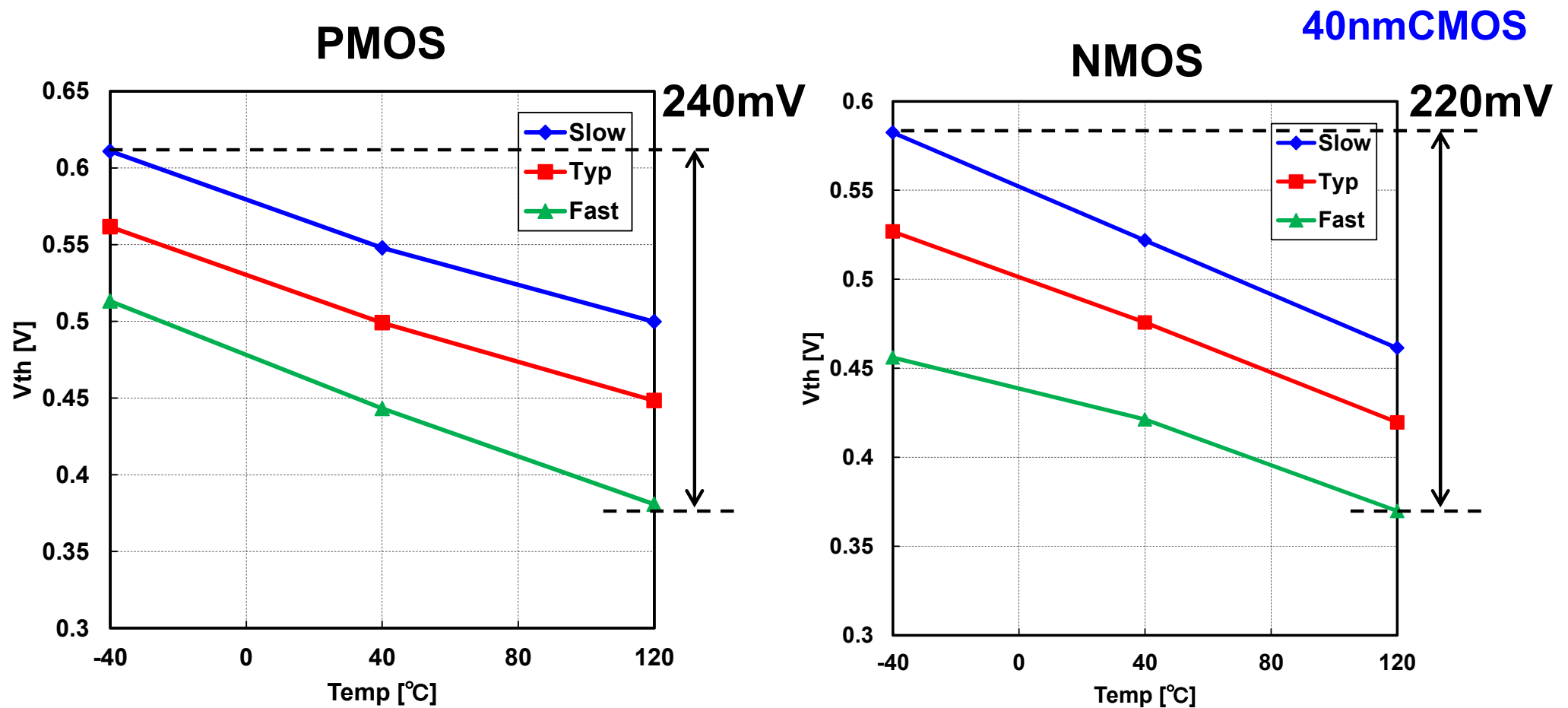Therefore it is quite difficult to realize 1V operation with 40nm CMOS.




- **Circuit design**
 - Almost no margin for low voltage design.
 - Can't simulate every performance with every condition.
 - Calibration technique is needed, however it can't guarantee the optimum performance.
- **Layout design**
 - Analog performance is strongly affected by layout design.
 - Package and board design affects the performance.
 - Not acceptable time for LPE simulation.
- **Testing and embedding**
 - No testing method for perfect verification.
 - Strongly affected by package or probe.
 - Affected by embedding to Mixed signal LSI.


TEG test and rework are necessary before embedding to the M/S SoC.

Circuit design

Layout design

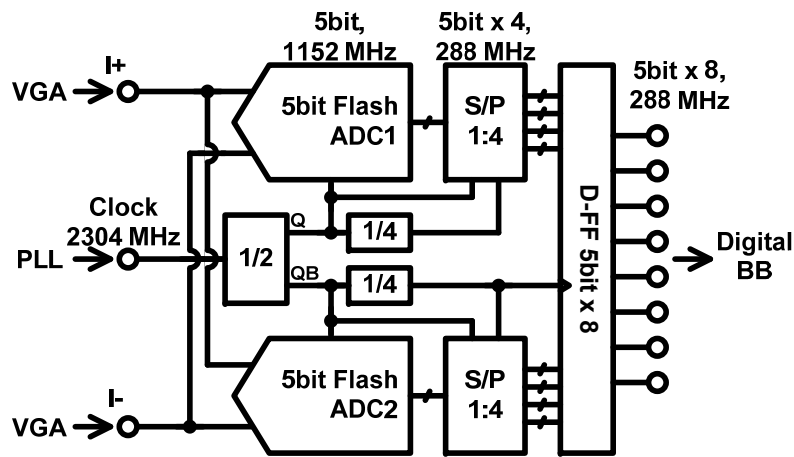


TEG Test & Rework

 

5b, 2.3GSps ADC

Simulation with package

Embedding to the SoC

 

BB SoC for 60GHz CMOS Transceiver