

# Current and future of analog and RF circuits technology

**Akira Matsuzawa**

**Tokyo Institute of Technology**

- **RF circuits**
  - **Challenge for ultra-high speed data transfer using millimeter wave technology**
    - 60GHz CMOS transceiver attained 28Gbps
    - Toward 300Gbps
- **ADC**
  - Performance trend
  - Scalable 12bit SAR ADC
  - 7bit 2.2GHz ADC using time-domain signal processing
- **PLL**
- **Layout-driven circuit design and programmable analog circuit technique**
- **Summary**

# Analog & RF circuits

2

TOKYO TECH  
Pursuing Excellence

Data rate  $\propto$  BW  $\times$  SNR(dB)

**Low power**

- Dynamic circuits
- Charge base
- Low energy loss

$$C = BW \log_2 \left( 1 + \frac{P_S}{P_N} \right)$$

Shannon's theorem

**Wide BW**

- Small cap.

**High SNDR**

- Scaled transistor
- Frequency compensation
- Distributed circuit

- Low noise
- Low jitter
- Low distortion
- Linearization
- High power

Wide BW and high SNDR are essentially important for the progress of analog circuits

Communication

$$D_{rate} \approx N \cdot BW$$

N: # of bits

BW: Signal bandwidth

ADC performance

$$D_{rate} \approx N \cdot f_s$$

N: Resolution

f<sub>s</sub>: Conversion frequency

Shannon's theorem

$$C = BW \log_2 \left( 1 + \frac{P_S}{P_N} \right)$$


Higher SNR is required for higher data rate

BW and SNR in ADC

$$BW < \frac{f_s}{2}$$

$$\frac{P_S}{P_N} \Big|_{ADC} = 1.5 \cdot 2^{2N}$$

$$C \approx N f_s$$

 

# RF circuits



**Challenge for ultra-high speed data transfer using millimeter wave technology**

Wider BW and high # of bits are required

16QAM

- BPSK: 1.7 Gbps
- QPSK: 3.5 Gbps
- 16QAM: 7 Gbps
- 64QAM: 10.5Gbps


$$D_{rate} \approx N \cdot BW$$

  

# 60GHz CMOS transceiver attained 28Gbps 6

## Direct conversion 60GHz CMOS transceiver

\*K. Okada, , A. Matsuzawa., ISSCC 2014

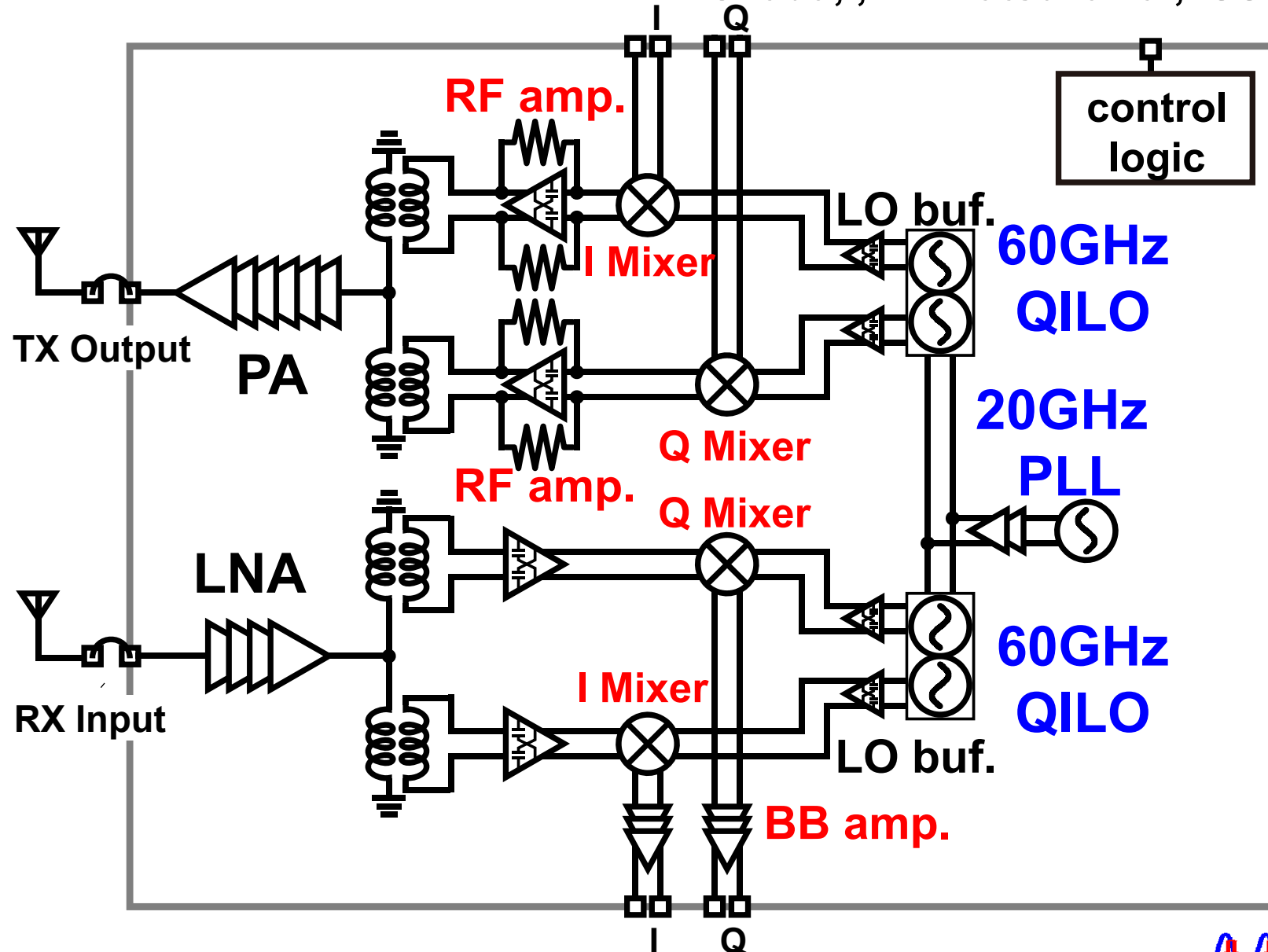


# Chip photo

FUJITSU 65nm CMOS

4.2mm

TX BB in  
↓ ↓ ↓ ↓

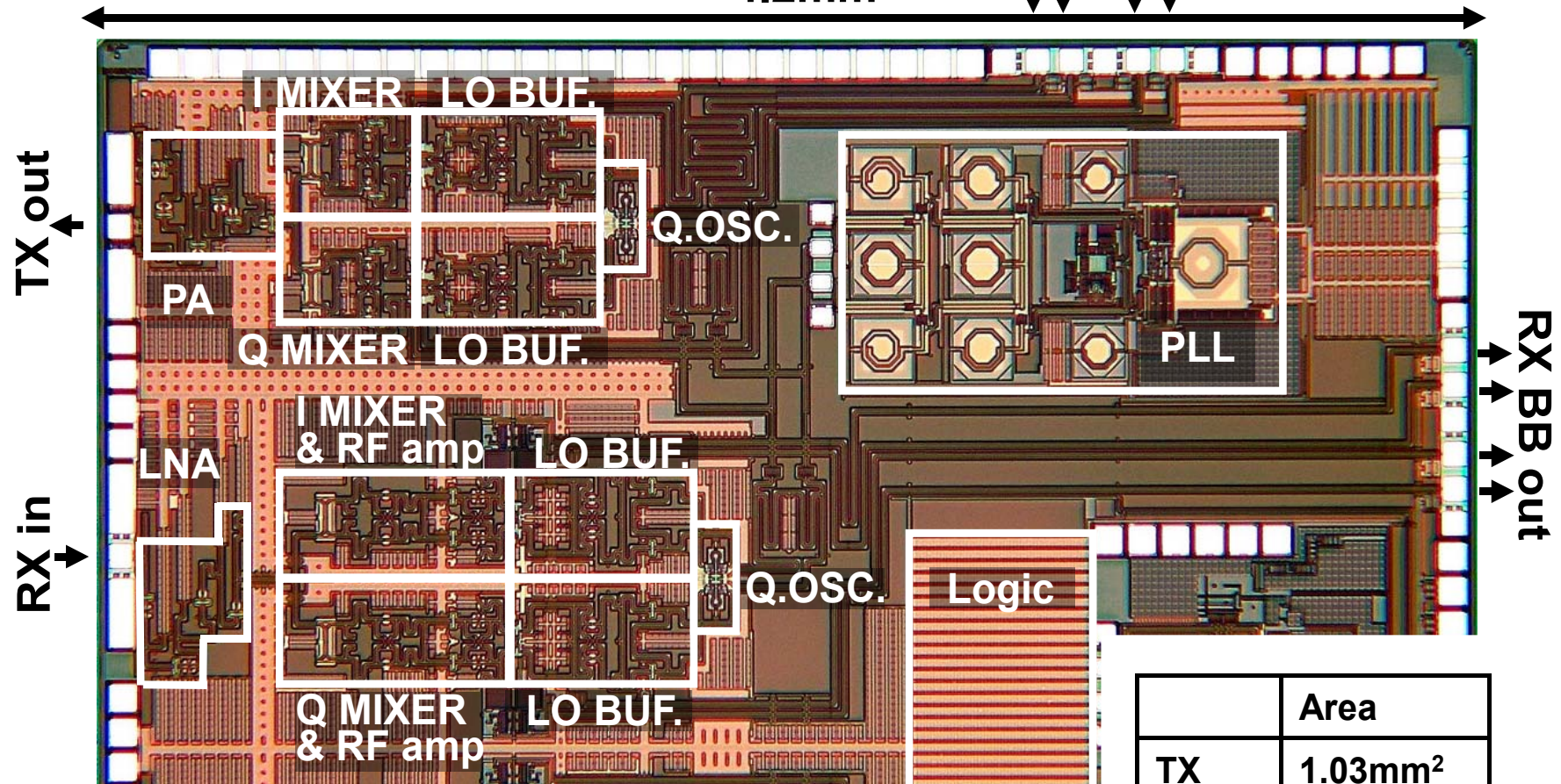

**TX: 186m**



**WRX: 155mW**

**PLL: 64mW**

	Area
TX	1.03mm <sup>2</sup>
RX	1.25mm <sup>2</sup>
PLL	0.90mm <sup>2</sup>
Logic	0.67mm <sup>2</sup>











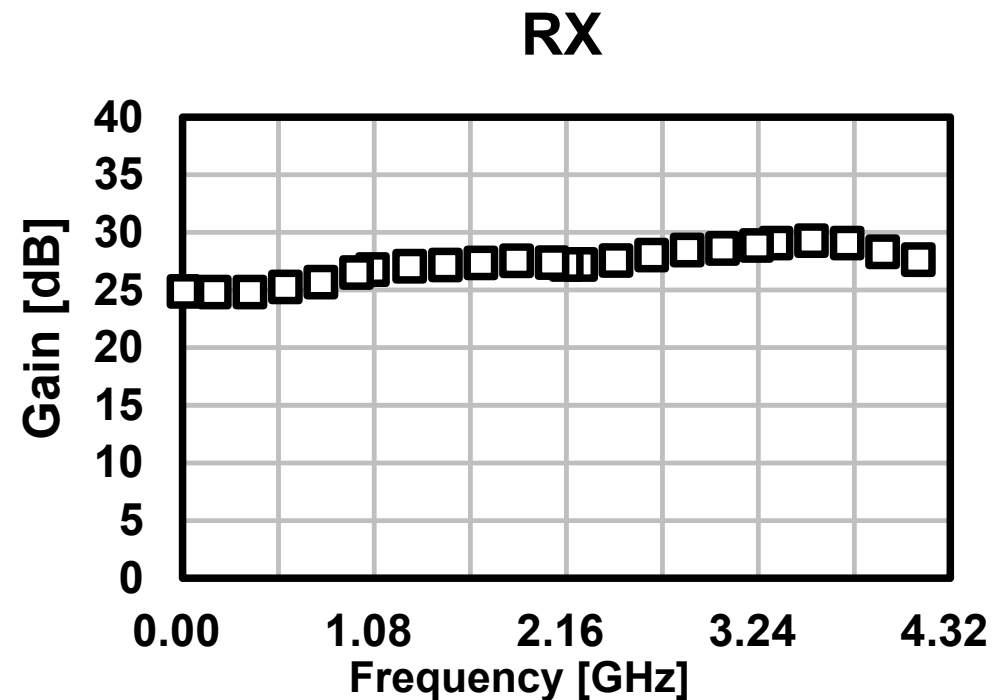
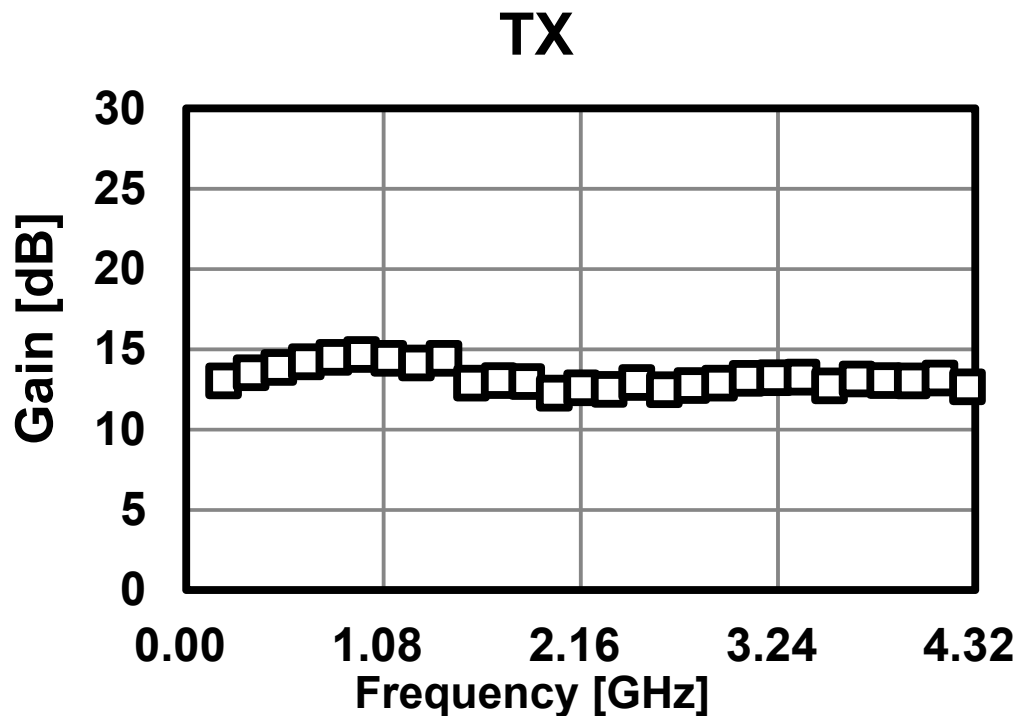
Flat frequency characteristics in wide bandwidth  
(DC~4.32GHz) for the channel bonding




# Measured characteristics

**World's first 64QAM**

**World's fastest 28Gbps**

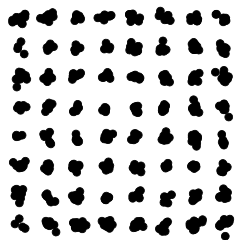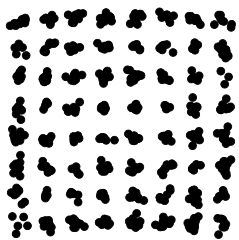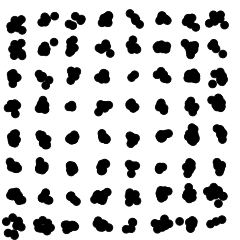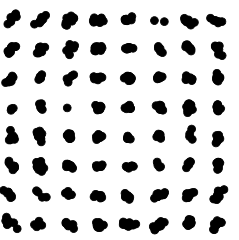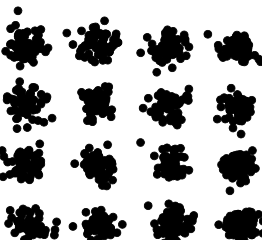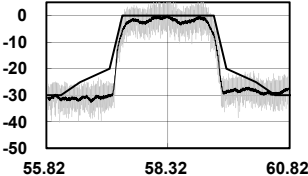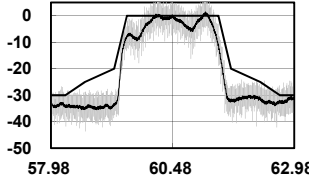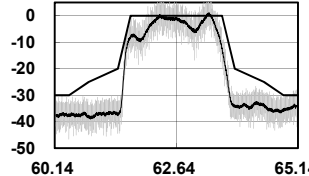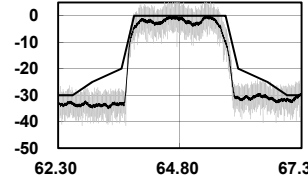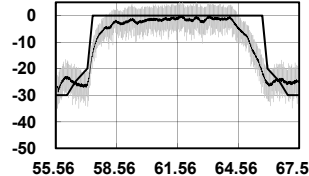Channel/ Carrier freq.	ch.1 58.32GHz	ch.2 60.48GHz	ch.3 62.64GHz	ch.4 64.80GHz	ch.1-ch.4 Channel bond
Modulation	64QAM				16QAM
Data rate*	10.56Gb/s	10.56Gb/s	10.56Gb/s	10.56Gb/s	28.16Gb/s
Constellation**					
Spectrum**					
TX EVM**	-27.1dB	-27.5dB	-28.0dB	-28.8dB	-20.0dB
TX-to-RX EVM***	-24.6dB	-23.9dB	-24.4dB	-26.3dB	-17.2dB

# Progress of data rate in 60 GHz band

 

$$D = BW \log_2 \left( 1 + \frac{P_S}{P_N + P_D} \right)$$


- **Wider BW**

- Reduction of parasitic comp.
- Neutralization of parasitic comp.
- Wide-band impedance matching

- **Higher SNR**

- Increase of signal power
- Reduction of power loss
- Decrease of thermal noise
- Decrease of phase noise
- Reduction of distortion

 
$$(P_S + P_{NT}) e^{j(\omega t + \phi_N)}$$


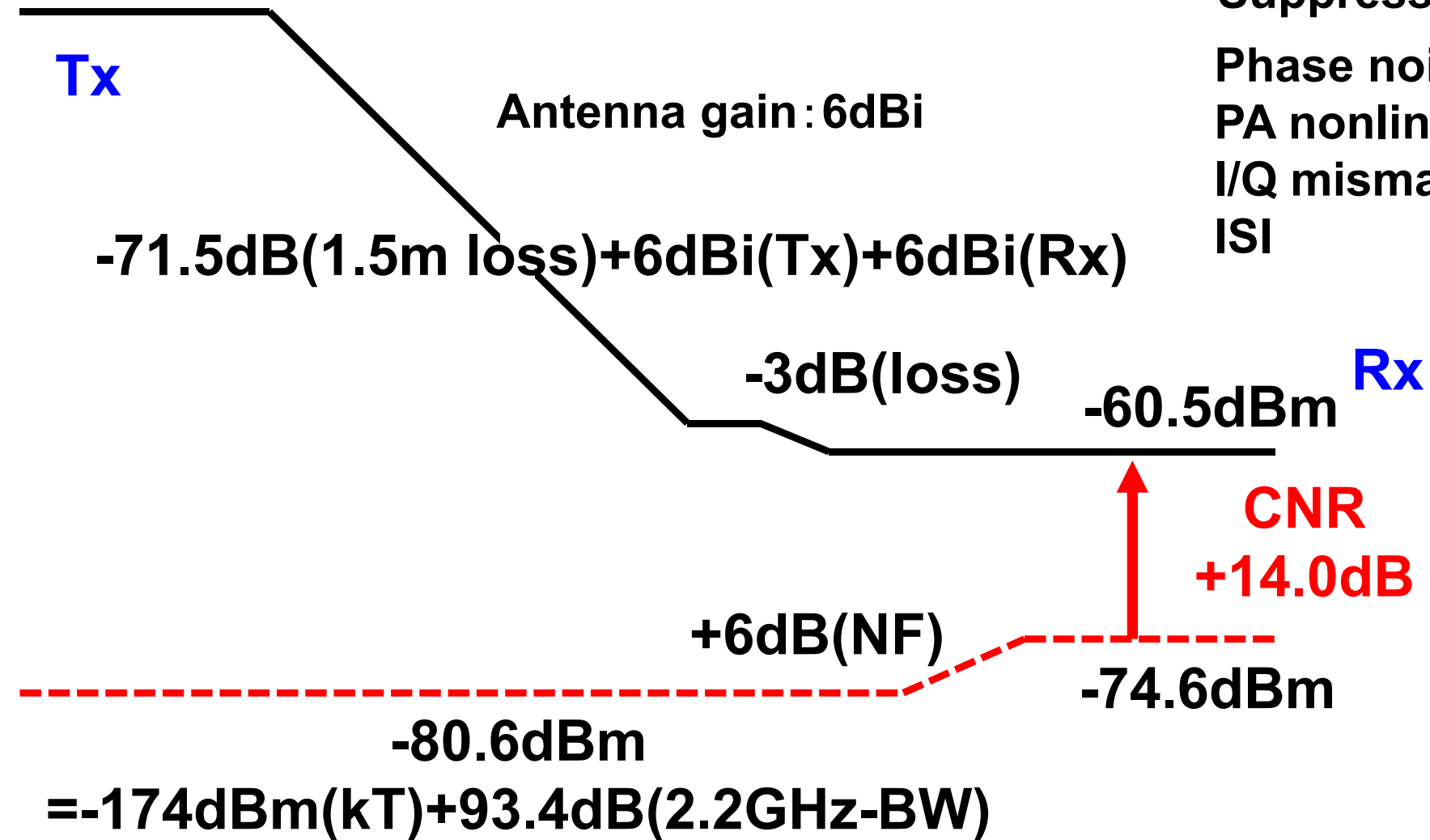
# 60GHz Link budget (QPSK)

Required CNR: 9.8dB

$6\text{dBm}(P_{\text{out}}) - 4\text{dB}(\text{back-off}) = 2\text{dBm}$



Suppress  
Phase noise  
PA nonlinearity  
I/Q mismatch  
ISI

# Friis's equation

Higher frequency does not mean higher data rate

Received signal is inversely proportional to square of frequency

$$P_r = \left( \frac{\lambda}{4\pi d} \right)^2 P_t G_t G_r = \left( \frac{c}{4\pi d f_c} \right)^2 P_t G_t G_r$$

Labels for Friis's equation:  
RX power:  $P_r$   
TX power:  $P_t$   
Antenna gains:  $G_t$  and  $G_r$   
Distance:  $d$   
Carrier frequency:  $f_c$

(Fixed carrier frequency)

$$P_{\text{eff}} = P_t + G_t + G_r - NF - IL - 20 \log_{10} \frac{d}{1\text{m}} \text{ [dBm]}$$


Labels for effective power equation:  
Received power:  $P_{\text{eff}}$   
TX power:  $P_t$   
Antenna gains:  $G_t$  and  $G_r$   
Noise figure:  $NF$   
Implementation loss:  $IL$   
Distance:  $d$

# Estimated data rate

Higher data rate can be expected up to the certain frequency, however it is reduced after that frequency.

Higher power is required for increasing the data rate.

16QAM is the most promising method

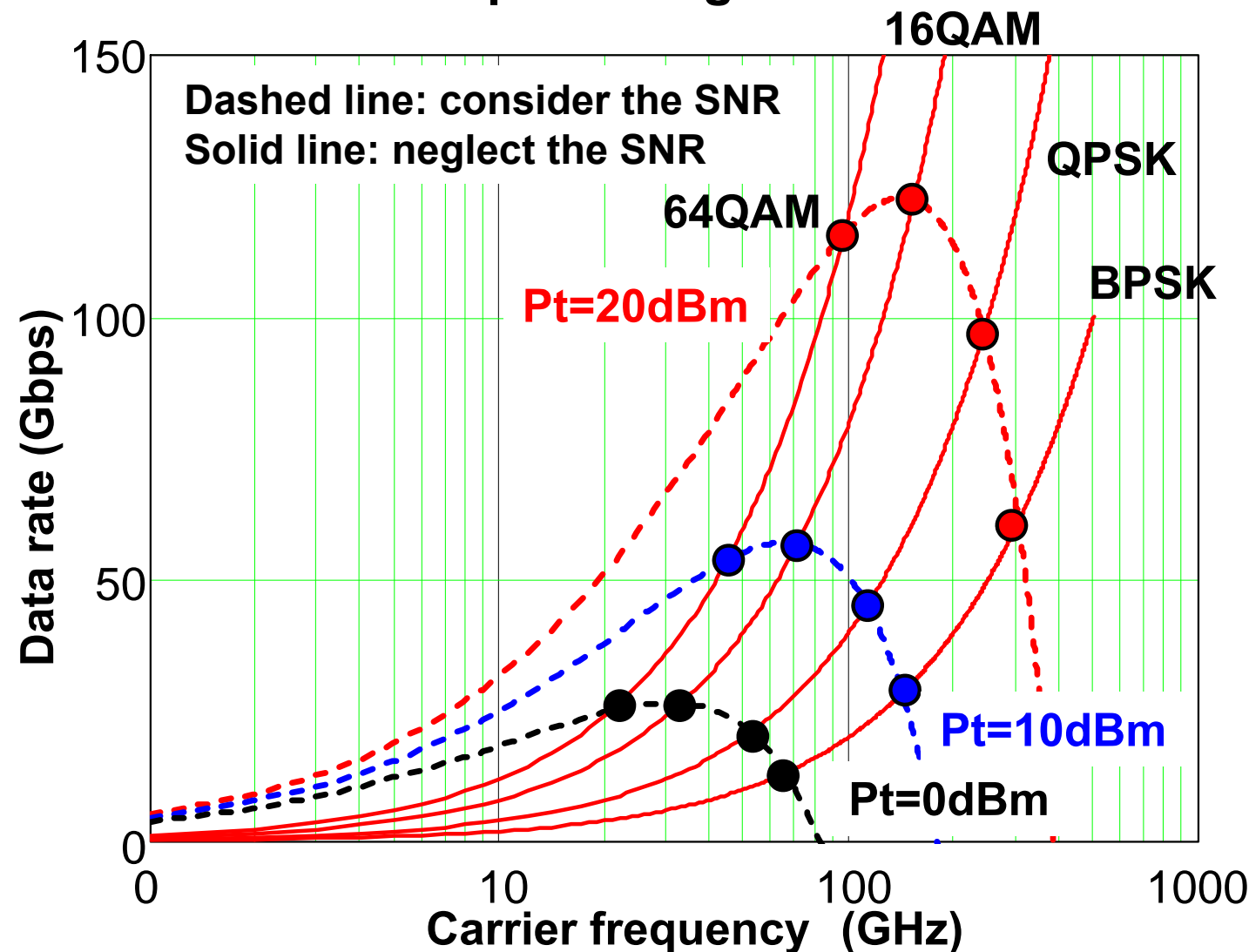

Distance: 1m


Antenna gain: 6dBi

NF: 6dB

Back off: 4dB

Power loss: 3dB

# Roadmap for 300Gbps data transfer / 15

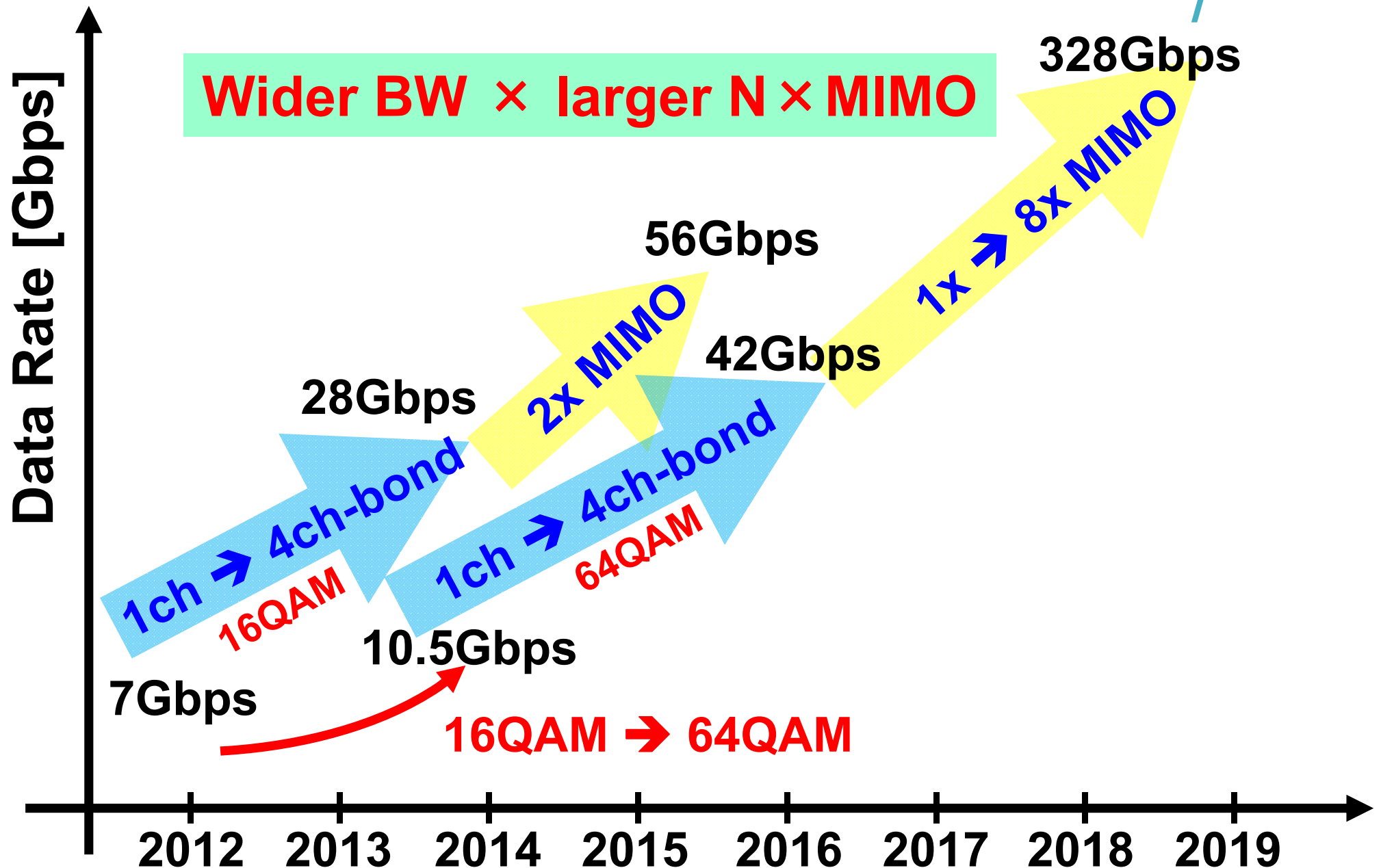



# ADC


**Requirement for ADC development is still high.  
Begin with ADC development and end with it ?**

# Begin with ADC development and end with it? / 17


I developed the world's first video-rate 10b ADC in 1981.  
I have been developing many ADCs during 35 years.  
The development of ADC will not end.

Bipolar (3um)  
10b, 20MS/s, 2W  
\$ 800

 
HDTV broad casting for Seoul Olympic game T. Takemoto and A. Matsuzawa,  
JSC, pp.1133-1138, 1982.




# Progress of ADCs

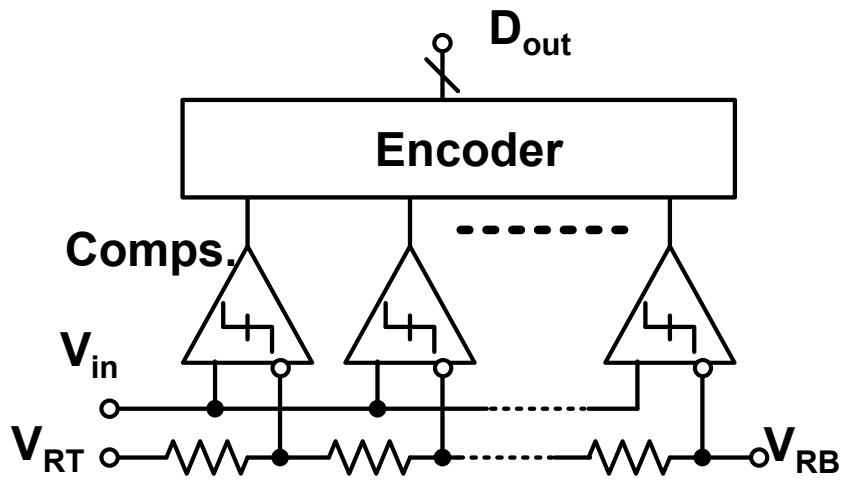


(a) Flash

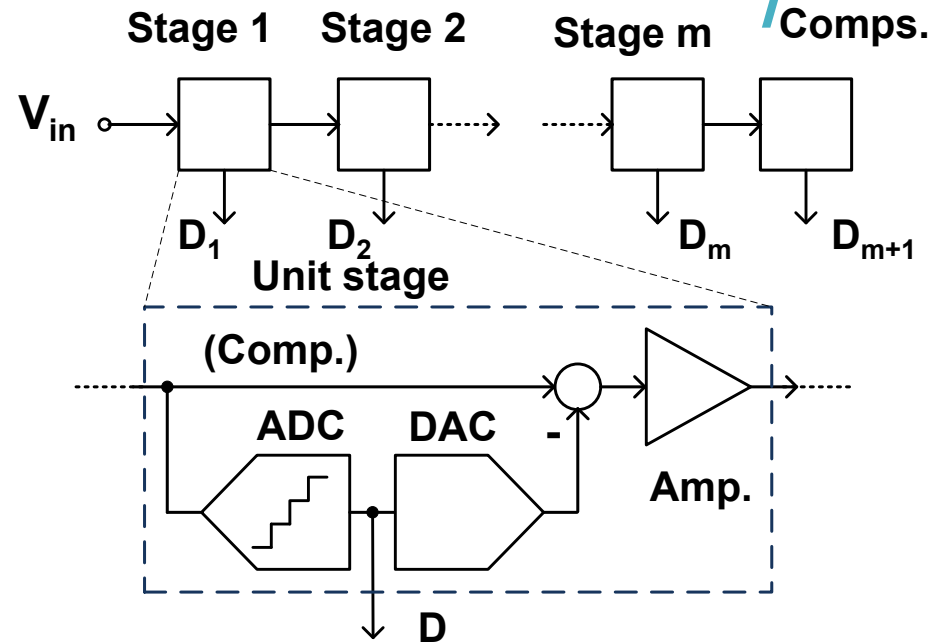

(c) Pipelined ADC

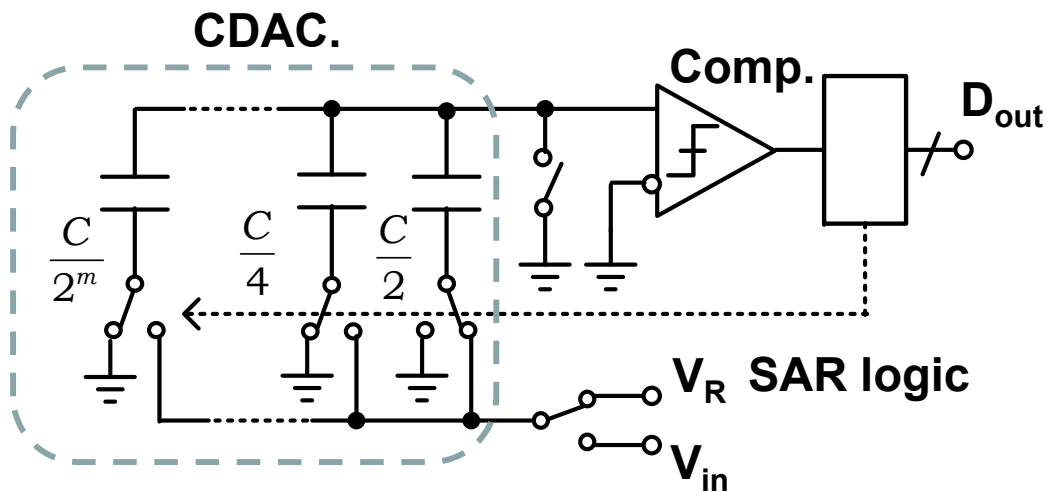


(b) SAR

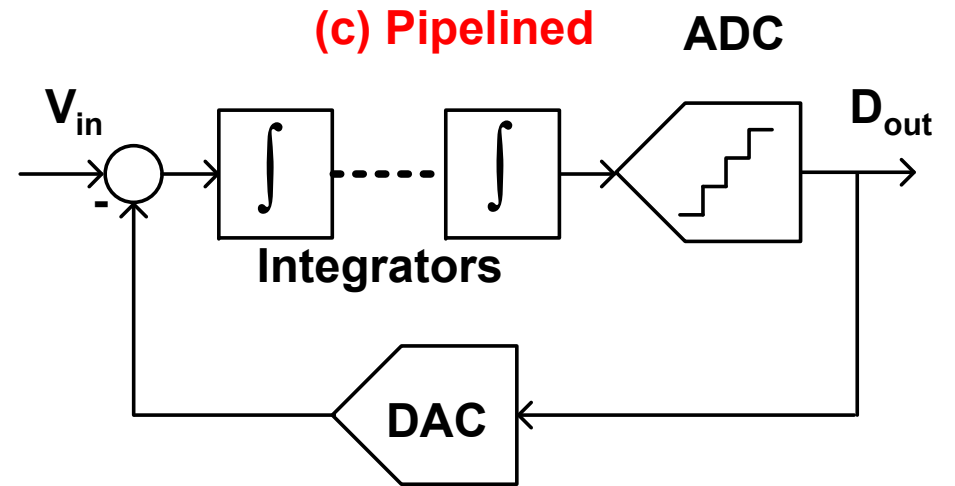

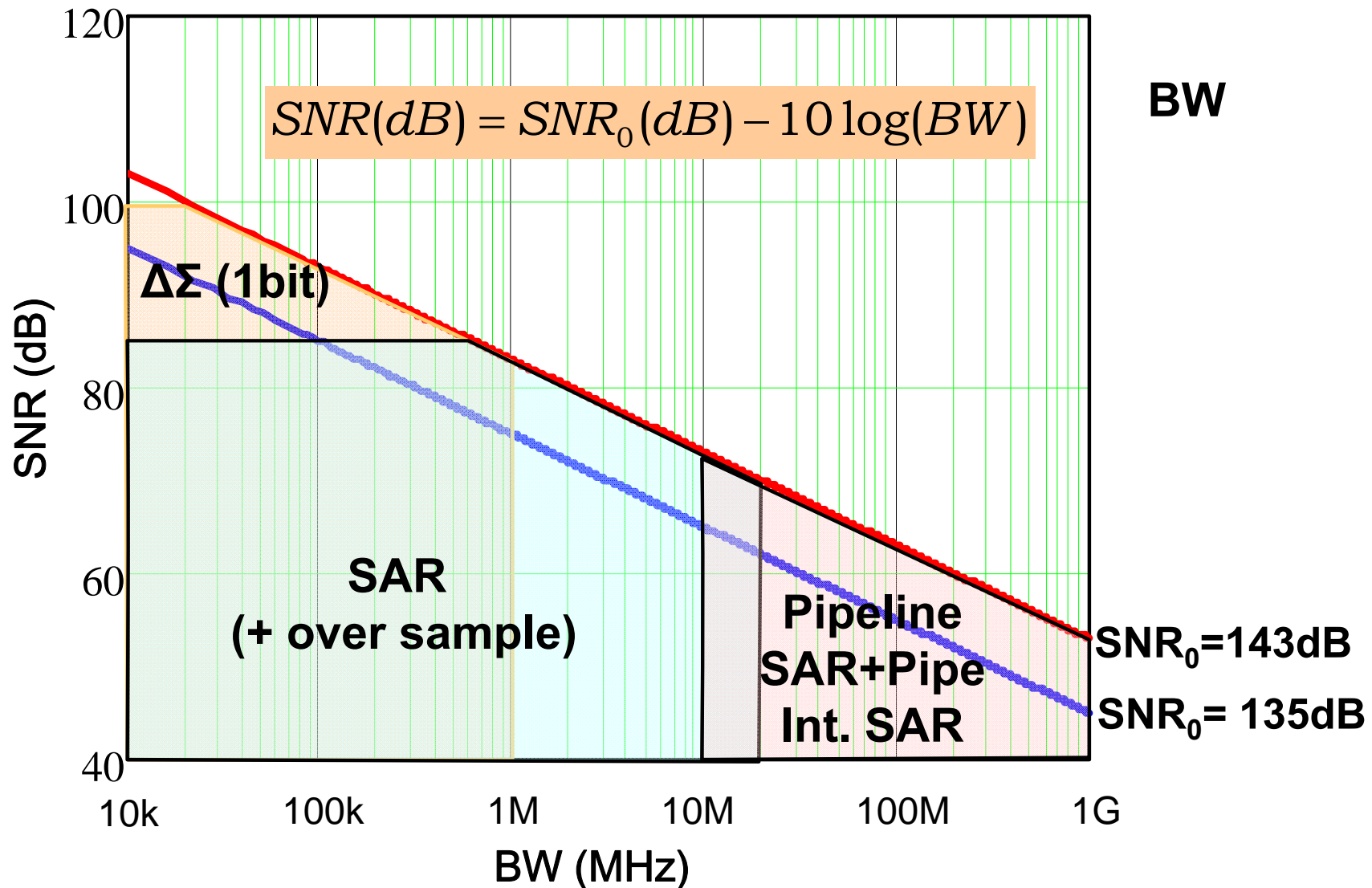(d) Sigma-Delta


SAR ADC is major. DS ADC is for higher SNR than 80 dB.  
Pipelined ADC is for wider BW than 40MHz.


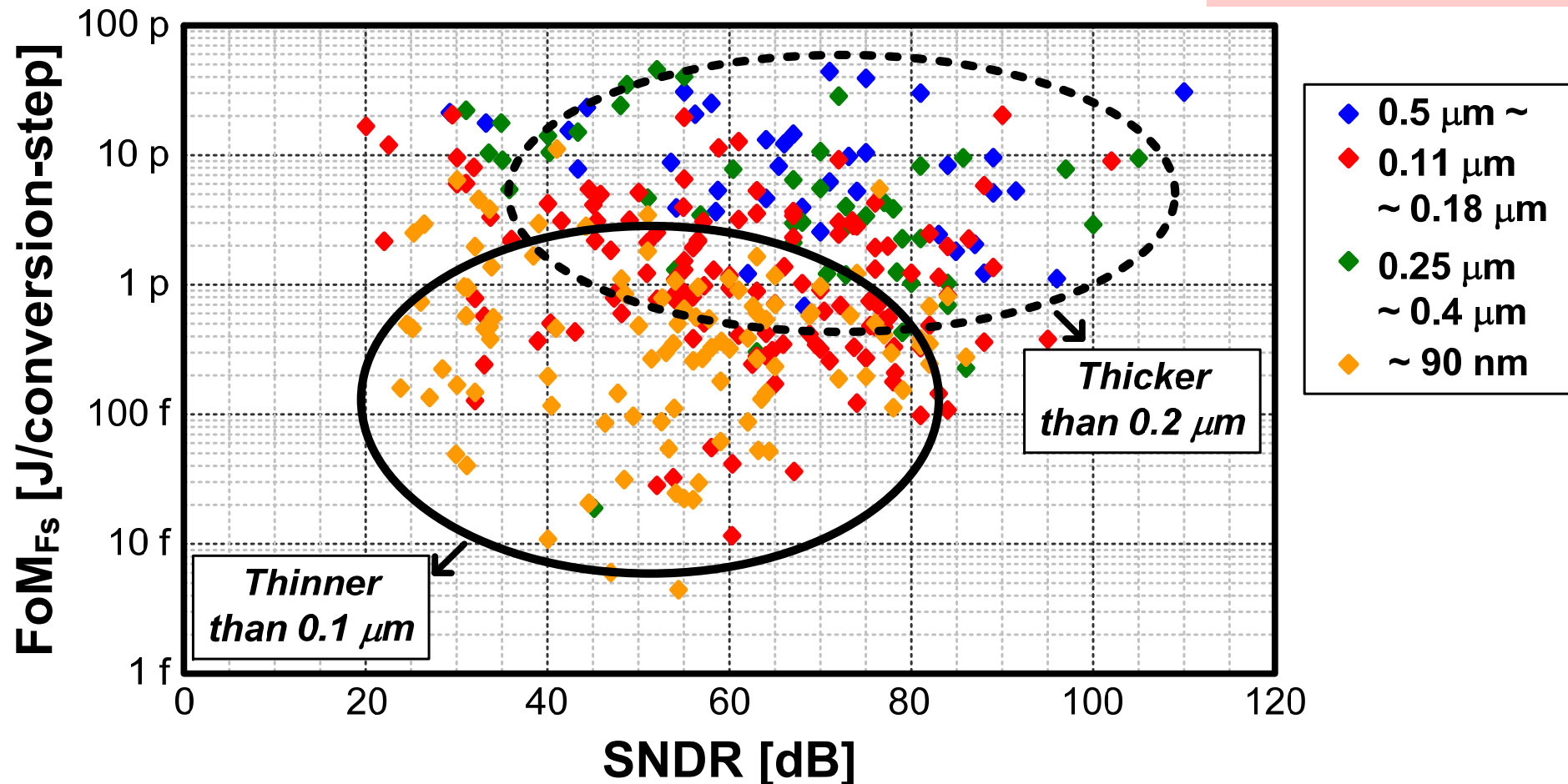
# Technology scaling and ADC performance 21

Technology scaling is effective to lower the FOM for low SNR ADC, however not effective to higher SNR ADC.


$$FoM = \frac{P_d}{f_s \times 2^{ENOB}}$$



B. Murmann, "ADC Performance Survey 1997-2011," [Online].

Longer technology node is needed for higher SNR

$$SNR(dB) = SNR_0(dB) - 10 \log(BW)$$

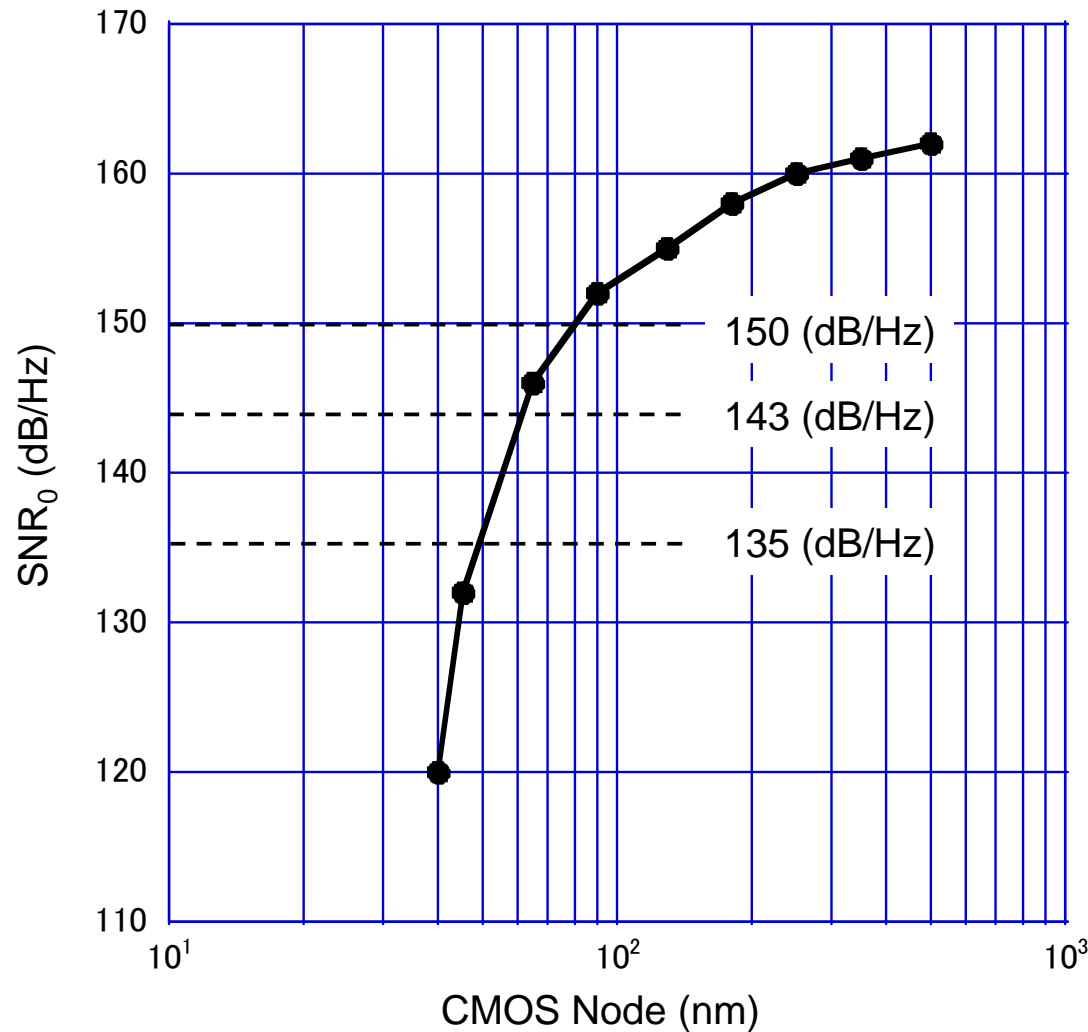

Jonsson, B., ICECS 2010.


# Fundamental Energy of sampling circuit 23

Fundamental energy of sampling is often used.

However this neglects the power for comparison.

$$E_{ADC} \approx N \times E_s = 24kT \cdot N \cdot 2^{2N}$$

Sampling circuit

 

Quantization voltage

$$V_q = \frac{V_{FS}}{2^N}$$

Quantization noise power

$$\overline{V_q^2} = \frac{V_q^2}{12} = \frac{V_{FS}^2}{12 \cdot 2^{2N}}$$

Noise balance

$$\overline{V_n^2} = \overline{V_q^2}$$

**Electrical energy=Thermal energy**

$$\frac{1}{2} CV_n^2 = \frac{1}{2} kT \quad \therefore V_n^2 = \frac{kT}{C}$$

Capacitance

$$C = 12kT \frac{2^{2N}}{V_{FS}^2}$$

$P_d$  of sampling circuit



$$E_S = 2CV_{FS}^2 = 24kT2^{2N}$$





# Transient noise simulation

Input noise is increased with frequency bandwidth, if  $C_p$  is very small.  
If  $C_p$  exists, it determines noise voltage.

$C_p=0$

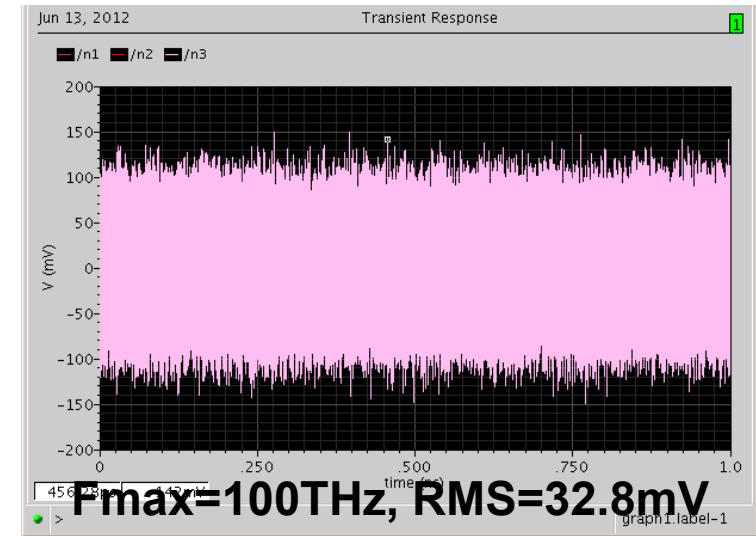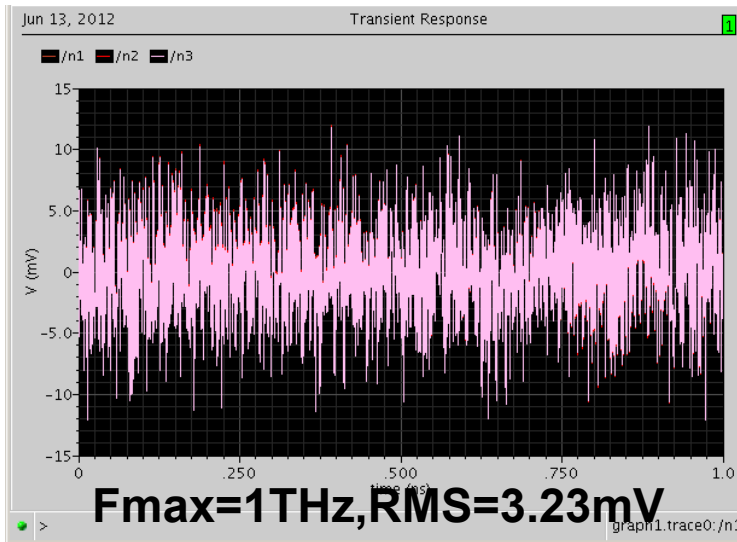


$C_p=100fF$

  

 
## $P/f_s$ is proportional to SNDR theoretically

Theoretical limit

$$E_{ADC} = N \times 2^{2N} \times 10^{-19}$$



 SNDR is reduced with increasing BW.  
Required timing jitter is less than 0.1 ps order.



# Scalable 12bit SAR ADC

# Scalable ADC



SNR can be increased by the reduction of BW, up to 84 dB.

SNR<sub>0</sub> should be higher than 143 dB.

P<sub>d</sub> should be minimized and can be reduced by the reduction of BW.

$$SNR \approx SNR_0 - 10 \log(BW)$$
  
$$P_d \approx K_1 \cdot BW \quad K_1: 0.2 \text{ -- } 3 \text{ (mW/MHz)}$$




Matsuzawa, A. "Digitally-Assisted Analog and RF CMOS Circuit Design for Software-Defined Radio," Chapter 7, Springer 2011.

Conventional analog circuit consumes continuous current and results in larger energy consumption. **Not scalable  $P_d$**  for operating frequency.

Dynamic circuits doesn't consume larger energy.

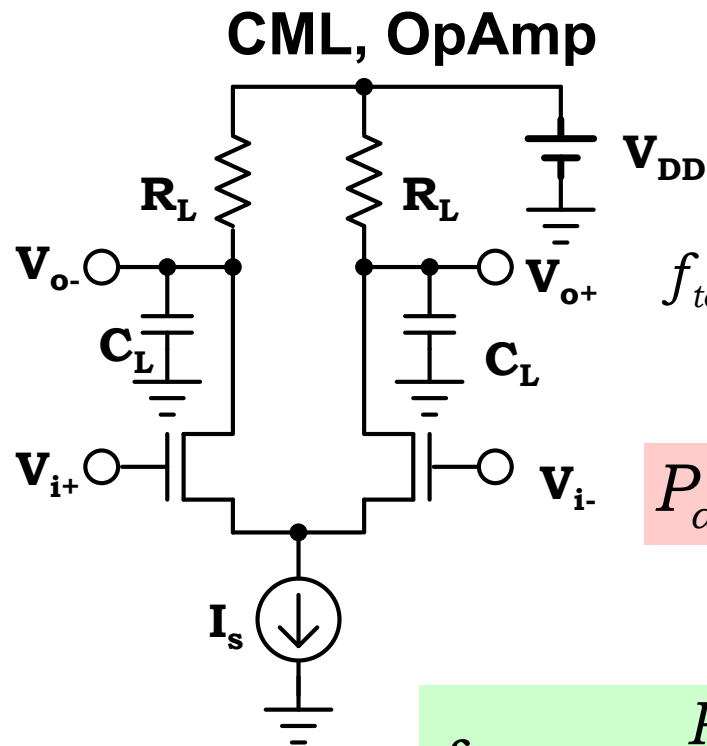CMOS: Consumed energy is **independent** of the delay time.  
**Scalable power consumption** for the operating frequency.




$$f_{toggle} \propto \frac{I_s}{V_{DD} C_L}$$

$$P_d = V_{DD} I_s$$

$$f_{toggle} \propto \frac{P_d}{C_L V_{DD}^2}$$

$$f_{toggle} \propto \frac{1}{R_o C_L}$$

 


$$f_{toggle} \propto \frac{1}{T_r} \propto \frac{1}{R_o C_L}$$

$$E_d = \frac{1}{2} C_L V_{DD}^2$$


$$P_d = f_{clk} E_d = \frac{1}{2} f_{clk} C_L V_{DD}^2$$

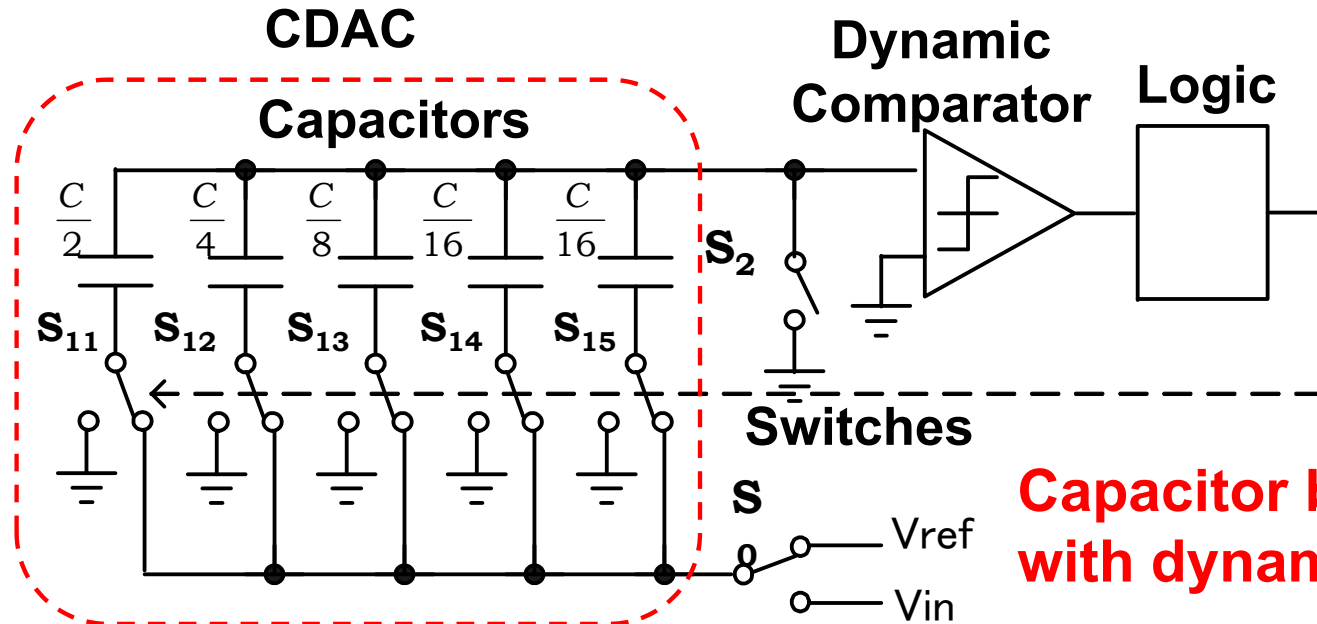SAR ADC doesn't consume any static power and has no tradeoff between the speed and the energy consumption.




No resistors  
No amplifier  
No static current !  
Potentially full swing

 Capacitor based analog processing with dynamic comparator



$$Q = -CV_{in}$$

Generating subtracted signal

 


$$V_x = -(V_{sig} - a \cdot V_{ref})$$

$$0 < a < 1$$

$$E_d \approx \frac{1}{2} CV_{ref}^2$$
 
# SAR ADC : Versatile ADC

SAR ADC is the most energy efficient ADC.  
It can be used for versatile applications.




Mismatch CAL.

Parasitic CAL.

12bit, 65nmCMOS, 0.03mm<sup>2</sup>

420μm

S. Lee, A. Matsuzawa, SSDM 2013


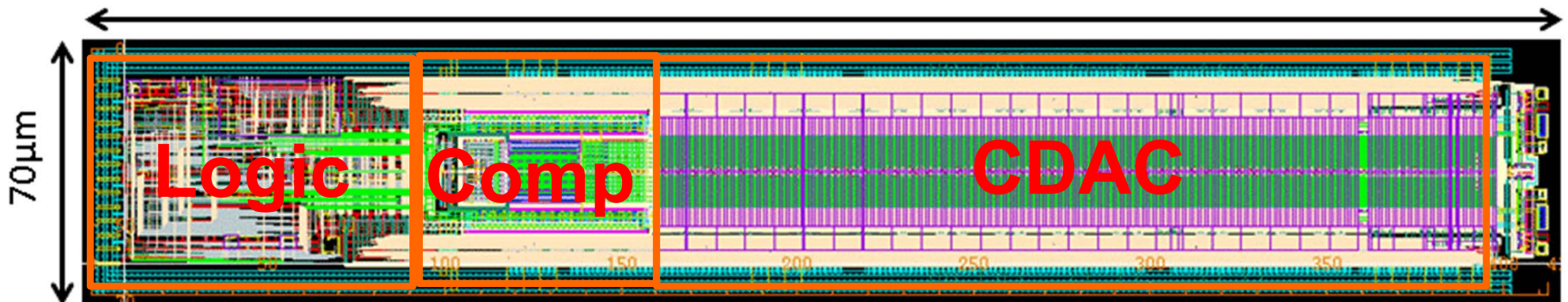



 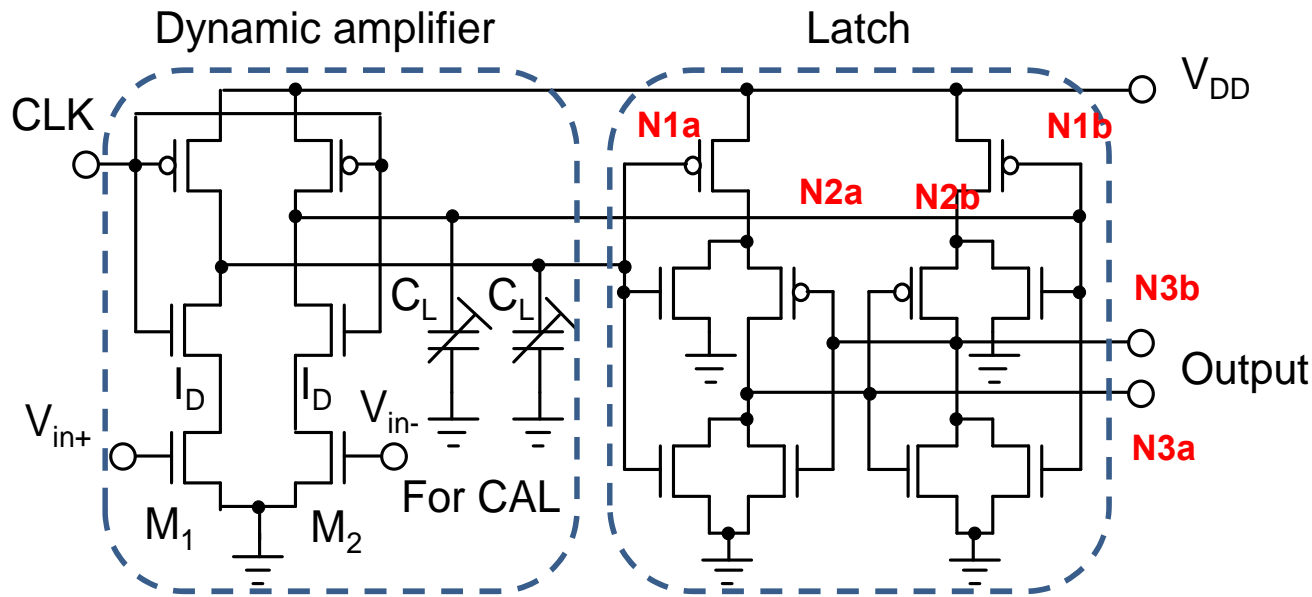
# Dynamic comparator

32

Dynamic comparator doesn't consume any static power.  
Large noise was an issue, however improved by our proposed  
Circuit using CMOS inter-stage amplifier.




M. Miyahara, Y. Asada, D. Paik, and A. Matsuzawa, "A Low-Noise Self-Calibrating Dynamic Comparator for High-Speed ADCs," A-SSCC, Nov. 2008.


Yusuke Asada, Kei Yoshihara, Tatsuya Urano, Masaya Miyahara, and Akira Matsuzawa, "A 6bit, 7mW, 250fJ, 700MS/s Subranging ADC," A-SSCC, 5-3, pp. 141-144, Taiwan, Taipei, Nov. 2009.

Noise in dynamic comparator can be improved by CMOS inter-stage amplifier and it is basically determined by the output capacitance of the dynamic amplifier.
 
$$\overline{v_{ni}^2} = \frac{kT\gamma}{C_L} \frac{V_{eff}}{V_{os}}$$



Resolution,  $C_L$ , and  $E_c$

 


A. Matsuzawa, ASICON 2009, pp. 218-221, Oct. 2009.



Successive comparison with binary search is started after the sampling period. The end flag becomes high when 12 conversion is completed. The conversion period is about 12 ns. The leakage current can be blocked by using power gating.

$P_d$  is proportional to the sampling frequency.


$$P_d = f_s \times E_d$$

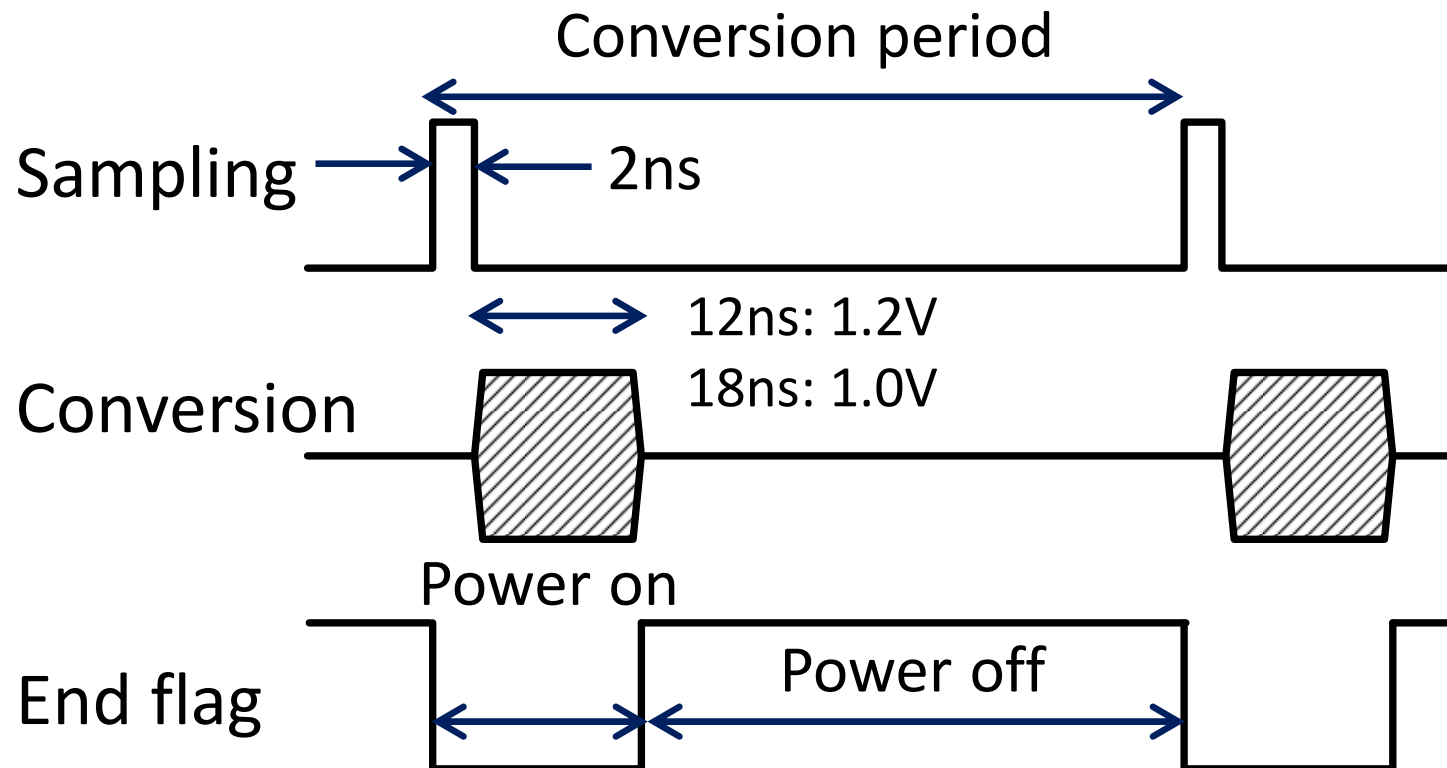

  MOM capacitor uses the capacitance between the lateral interconnection. The capacitor density can be increased by technology scaling. Smaller occupied area (same C) can be expected by technology scaling. Furthermore, parasitic capacitance can be controlled.



 $P_d$  is completely proportional to the sampling frequency.  
Therefore an ultra-low power is possible at low speed operation.  
Further low power is possible by using low voltage operation.



50MSps: 2mW  
5MSps: 200uW  
500KSps: 20uW  
50KSps: 2uW  
5kSps: 0.2uW

S. Lee, A. Matsuzawa, et al., SSDM 2013

- Highest conversion rate: 70MSps
- Lowest voltage: 0.8V
- Lowest  $P_d$ : 2.2mW at 50MSps
- Smallest FoM: 28fJ
- Smallest area: 0.03mm<sup>2</sup>

## 12bit SAR ADCs

	This work			[3]	[4]
Resolution (bit)	12			12	12
V <sub>DD</sub> (V)	0.8	1	1.2	1.2	1.2
f <sub>sample</sub> (MHz)	30	50	70	45	50
P <sub>d</sub> (mW)	0.8	2.2	4.6	3	4.2
SNDR (dB)	62	64	65	67	71
FoM (fJ) Nyq/DC	81/28	62/33	100/45	36/31	36/29
Technology (nm)	65			130	90
Occupied area(mm <sup>2</sup> )	0.03			0.06	0.1

S. Lee, A. Matsuzawa, et al., SSDM 2013.

[3] W. Liu, P. Huang, Y. Chiu, ISSCC, pp. 380-381, Feb. 2010.

[4] T. Morie, et al., ISSCC, pp.272-273, Feb. 2013.



# Performance scalable ADC ?

SNR can be increased up to 78 dB by reducing BW.  
Smallest  $P_d$  among ADCs for wireless communication.

84 dB will be attained by dither and DEM method.  
 $SNR_0$  is 140 dB and it should be increased.

S. Lee, A. Matsuzawa, et al., SSDM 2013

1V, 50MSps Operation

  

# SAR ADC vs. SD ADC


SAR ADC must be better than the SD ADC

; Small area, low power, easy to design, and low voltage of LT. 1.0V.

SAR ADC: Area: 0.03mm<sup>2</sup> (65nm) f<sub>b</sub>=25MHz P<sub>d</sub>=2.0mW, SNDR=70dB

SDADC: Area: 0.05mm<sup>2</sup> (40nm) f<sub>b</sub>=10MHz P<sub>d</sub>=2.6mW, SNDR=70dB

Conference	Technology	Area (mm <sup>2</sup> )	Power (mW)	SNDR (dB)	DR (dB)	BW (MHz)	Fs (MHz)	FOM (fJ/conv.)	FOM2
Modulator-B	40nm	0.051	2.57	70.0	70.6	10	300	50	166.5
Modulator-A	65nm	0.060	1.36	68.8	69.3	3	186	101	162.0
VLSI2011[4]	40nm	0.085	2.80	78.0	83.0	1.92	246	112	171.4
ISSCC2006[5]	130nm	1.2	20.0	74.0	76.0	20	640	122	166.0
ISSCC2011[6]	90nm	0.15	8.0	63.5	70.0	25	500	125	164.9
ISSCC2009[7]	65nm	0.084	4.52	79.1	80.0	2	128	153	166.5
CICC2010[2]	65nm	0.16	3.6	69.8	70.2	4	140	178	160.7

 

(a) Modulator-A

(b) Modulator-B

K. Matsukawa,  
S. Doshio, VLSI 2012




Sigma-delta ADCs are widely used for wireless communications. But....

Sigma delta ADC can suppress only the quantization noise of ADC.

The performance is limited by the input error voltage.

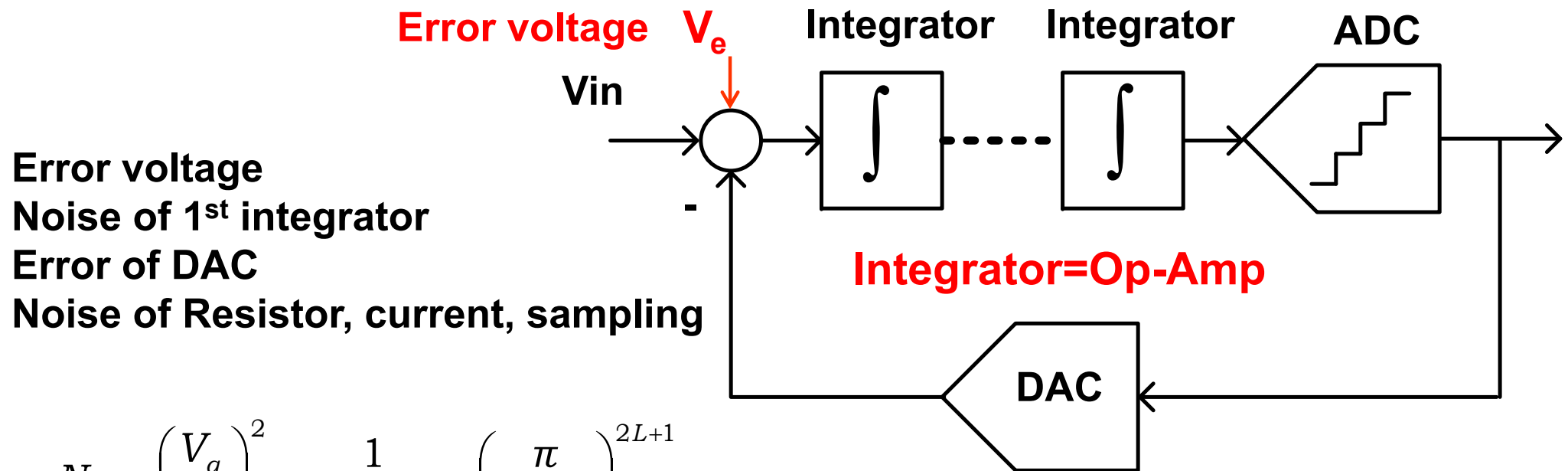Op-Amp is needed for the integrator and consumes static power.



$$N_q = \left(\frac{V_q}{2}\right)^2 \frac{1}{3\pi(2L+1)} \left(\frac{\pi}{OSR}\right)^{2L+1}$$

Quantization noise can be suppressed so much

$$V_{e\_eff} \approx \frac{V_e}{OSR}$$


Error voltage at input summing node can't be suppressed so much. Suppressed by only OSR.

# 7bit 2.2GSps ADC

using time-domain signal processing



- 7bit ADC for the 16QAM modulation
- Convert the voltage difference to the timing difference
- Folding and interpolation are realized by logic gates

M. Miyahara, A. Matsuzawa, ISSCC 2014

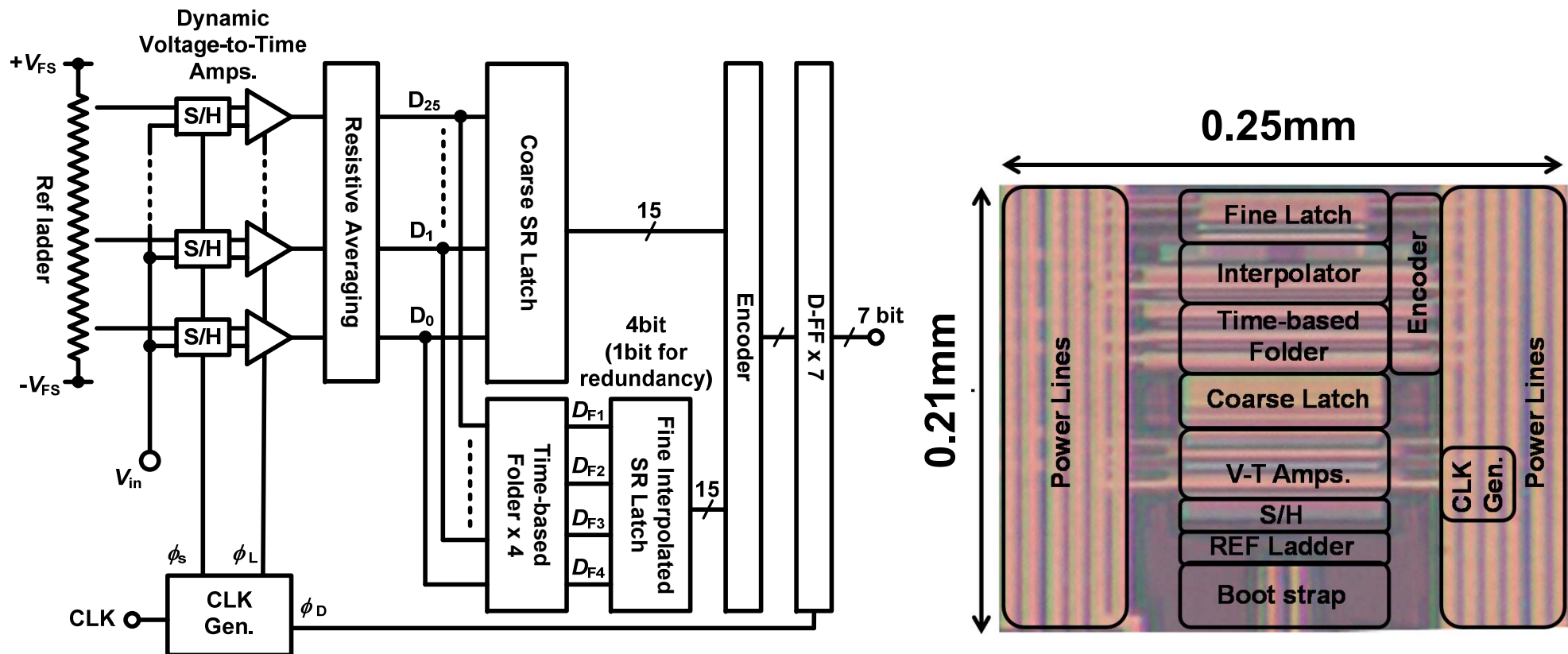

Voltage difference can be changed to time difference in a dynamic amplifier.


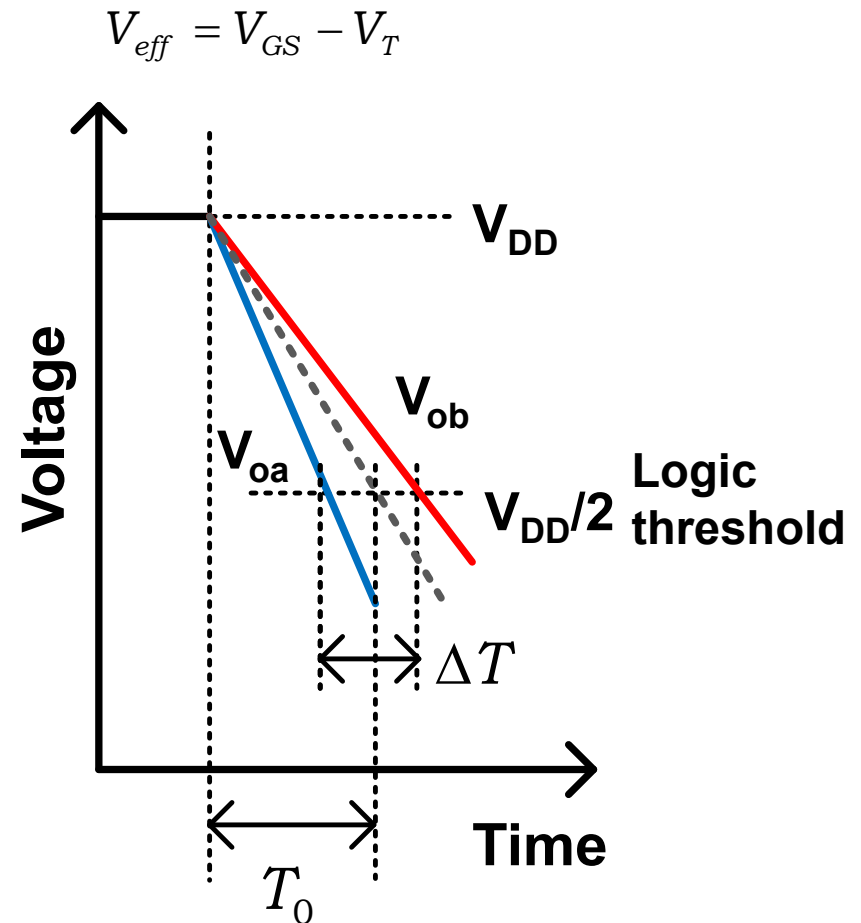
 
$$\Delta T \approx \frac{\Delta V_{in}}{V_{eff}} T_0$$



# Conversion from the voltage to the timing / 44

The signal generation of larger voltage difference is faster in the dynamic amplifier.



Dynamic Amps.

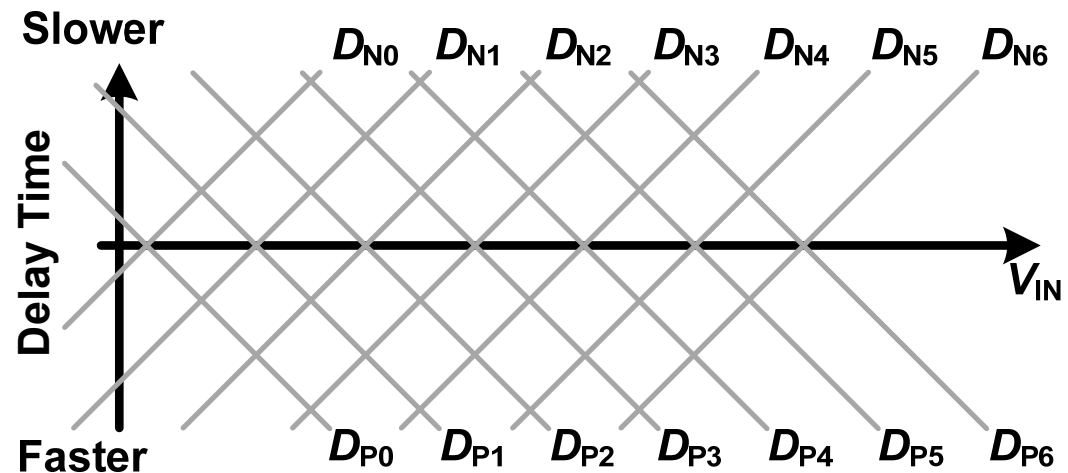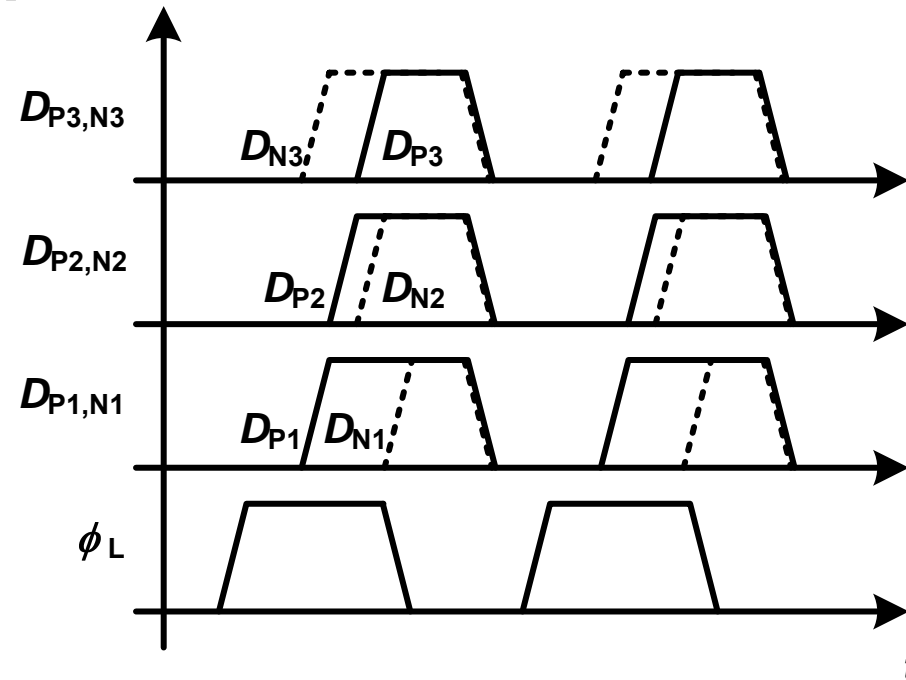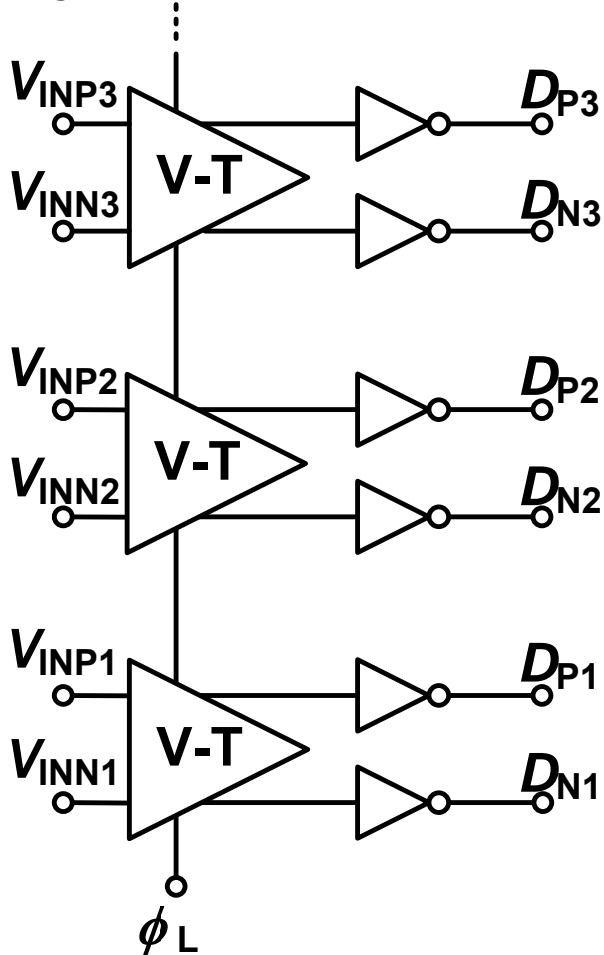



# Signal folding in time-domain

Signal folding in time-domain can be realized easily by simple logic gates.


AND: Select late pulse

  



OR: Select early pulse

  

 Higher resolution ADC can be realized by interpolating folded signals.



  Interpolation can be made with gate-weighted inverters.  
SR latch acts as a comparator by comparing pulse timing



SR-Latch response in the case of interpolation ratio of 5:3

[6] D. Miyashita, et al., VLSI symp. 2011



# Performance comparison

48

Highest SNDR of 37.4 dB is attained in flash ADCs

No calibration circuits are required.


This ADC will contribute increase of data rate of 60 GHz transceivers.

$P_d$  is large so far, however can be reduced by the optimization.


	ISSCC 2008 [3]	VLSI 2012 [8]	VLSI 2013 [9]	This work
Technology	90nm	40nm	32nm SOI	40nm LP
Resolution [bit]	5	6	6	7
Power Supply [V]	1	1.1	0.85	1.1
Sampling Frequency [GS/s]	1.75	3	5	2.2
Power Consumption [mW]	2.2	11	8.5	27.4
SNDR @Nyquist [dB]	27.6	33.1	30.9	<b>37.4</b>
FoMw [fJ/conv.-step]	64.5	99.3	59.4	210
FoMs [dB]	143.5	144.4	145.6	143.3
Core area [mm <sup>2</sup> ]	0.0165	0.021	0.02	0.052
Calibration	Off chip	Foreground	Off chip	<b>No need</b>

# PLL

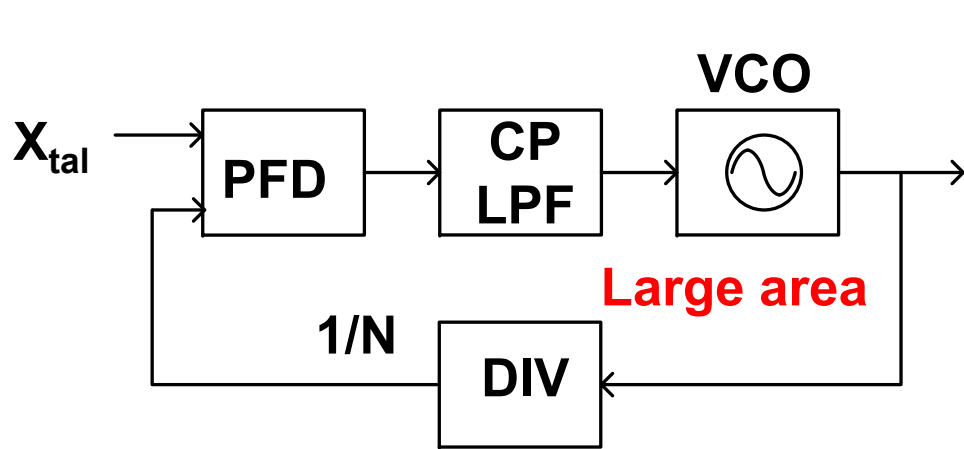**PLL that can generate accurate frequency and timing will be improved continuously.**




(a) Conventional Charge-pump PLL

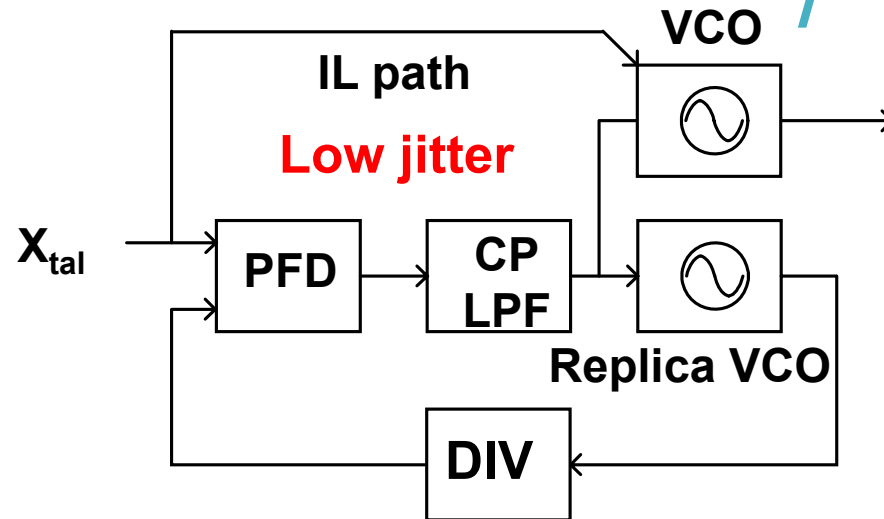


(b) Injection lock (IL) PLL  
(with replica VCO)

Small area  
Low power

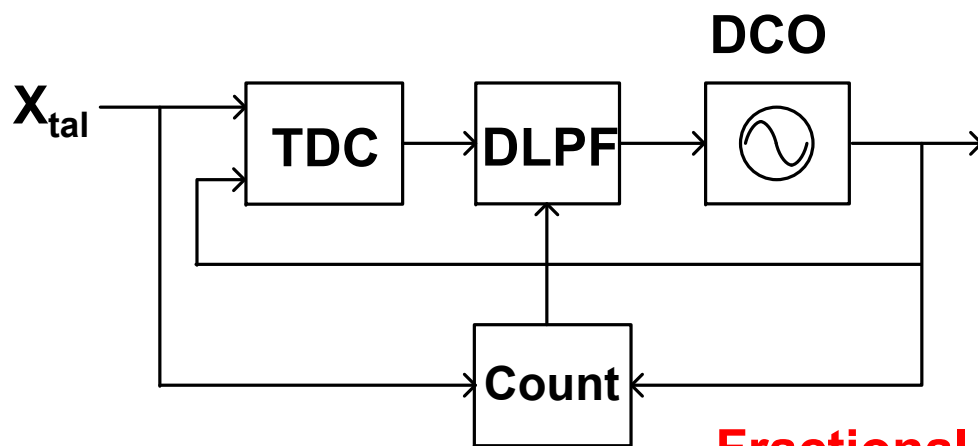



(d) Full digital PLL

Fractional  
Small area  
Low jitter

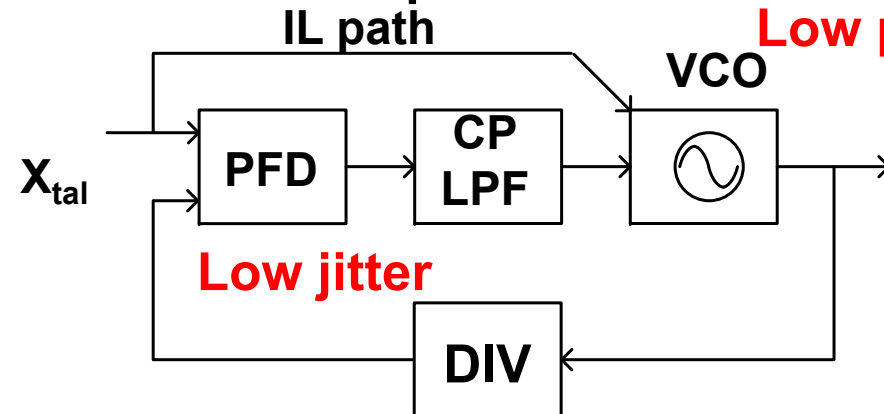

 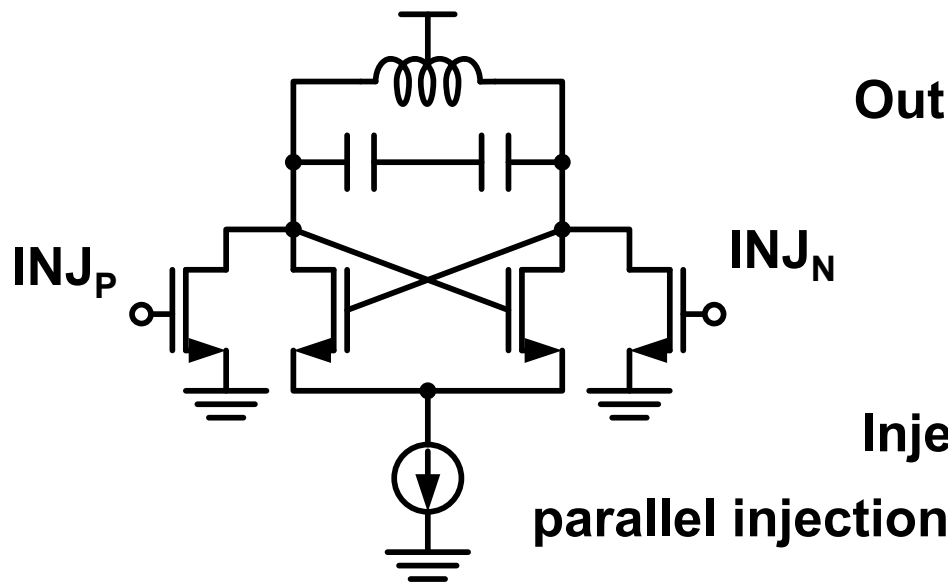(c) Injection lock (IL) PLL  
( without replica VCO )

Injection locking method can control the phase of higher frequency oscillator by that of lower frequency oscillator.



•Phase noise (jitter) is mandated by the IL pulse

Phase noise of frequency multiplier

$$PN_{ILO} = PN_{INJ} + 20 \log(N)$$

N: Multiply

Lock range


$$\Delta\omega_L = \frac{\omega_o}{Q} \cdot \frac{I_{inj}}{I_{osc}} \cdot \frac{1}{\sqrt{1 - \frac{I_{inj}^2}{I_{osc}^2}}}$$

N=3のとき 9.5dB

 
# Low phase noise 60GHz quadrature VCO / 52

Very low phase noise 60GHz Quadrature VCO has been developed.  
60GHz I/Q VCO is locked by low phase noise 20 GHz PLL.

-96dBc/Hz@1MHz is attained. Previous one is -76dBc/Hz@1MHz



 It can realize the direct conversion transceivers and 64 QAM.




A. Musa, K. Okada, A. Matsuzawa, in A-SSCC  
Dig. Tech. Papers, pp. 101–102, Nov. 2010.

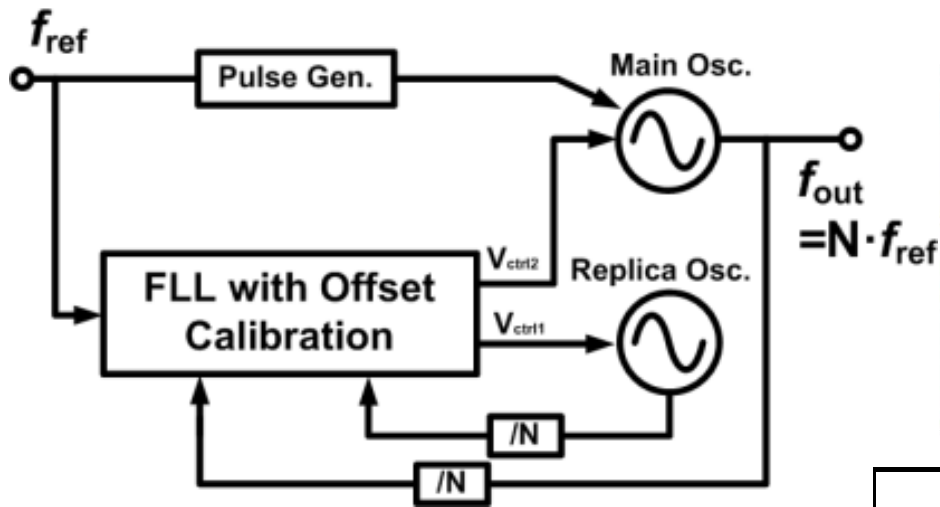
## Small, low jitter, and low power ring OSC for SoC by using IL method

$T_j=1.8\text{ps}$ , 1.0 mW, 0.02mm<sup>2</sup>

Automated circuit and layout design will be possible.




IL VCO Comparison

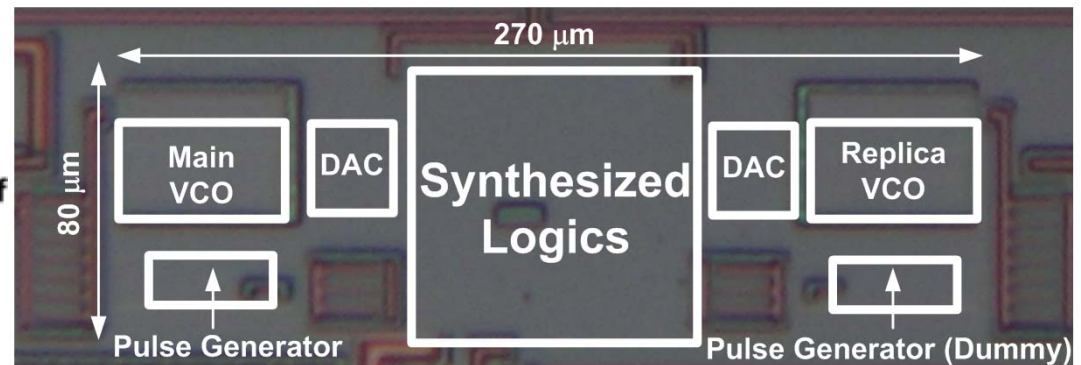

	This work	[1]		[2]	[5]
	IL-PLL	DMDLL	DPLL	MDLL	IL-PLL
Freq. [GHz]	1.2 (0.5-1.6)	1.5 (0.8-1.8)	1.5 (0.8-1.8)	1.6	0.216
Ref. [MHz]	300 (40-300)	375	375	50	27
Power [mW]	<b>0.97</b>	0.89	1.35	<b>12</b>	<b>6.9</b>
Area [mm <sup>2</sup> ]	<b>0.022</b>	<b>0.25</b>	0.25	0.058	0.03
Integ. Jitter [ps]	0.7	0.4	3.2	0.68	2.4
Jitter RMS/PP [ps]	1.81/19.4 10M hits	0.92/9.2 5M hits	4.2/33 5M hits	0.93/11.1 30M hits	N.A.
FOM [dB]	-243	-248.46	-228.59	-233.76	-225
CMOS Tech.	65nm	130nm	130nm	130nm	55nm

W. Deng, K. Okada, A. Matsuzawa,  
ISSCC 2013
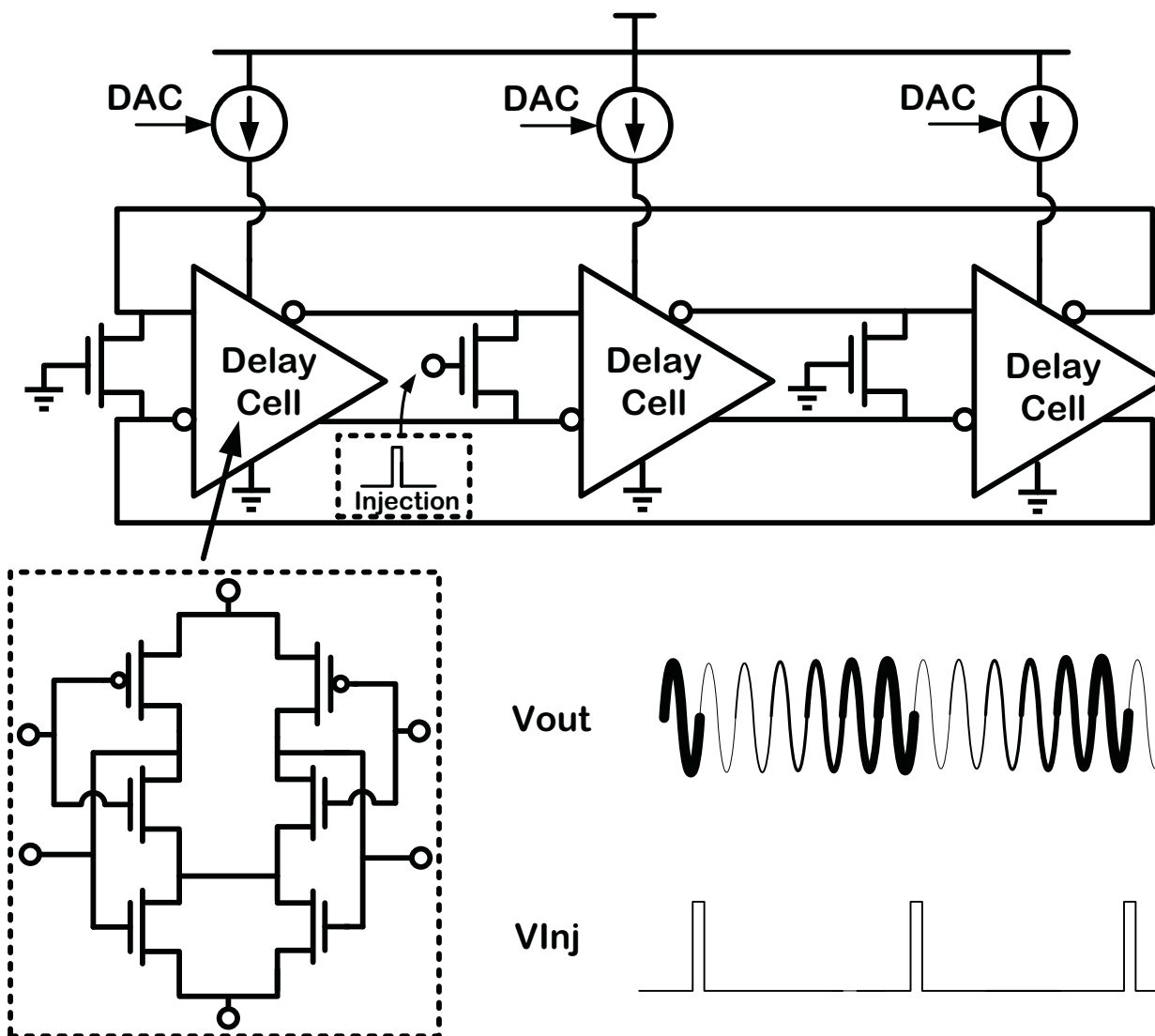
## Differential ring VCO with injection locking






W. Deng. ISSCC 2013

# Effect of the injection locking

55
   
## Phase noise is reduced so much by the injection locking




Ref.: 300MHz (40MHz-300MHz) Freq.: 1.2GHz (0.5-1.6GHz)  
Integrated jitter: 0.7ps (10kHz-40MHz) Pdc: 0.97mW (1.2GHz)





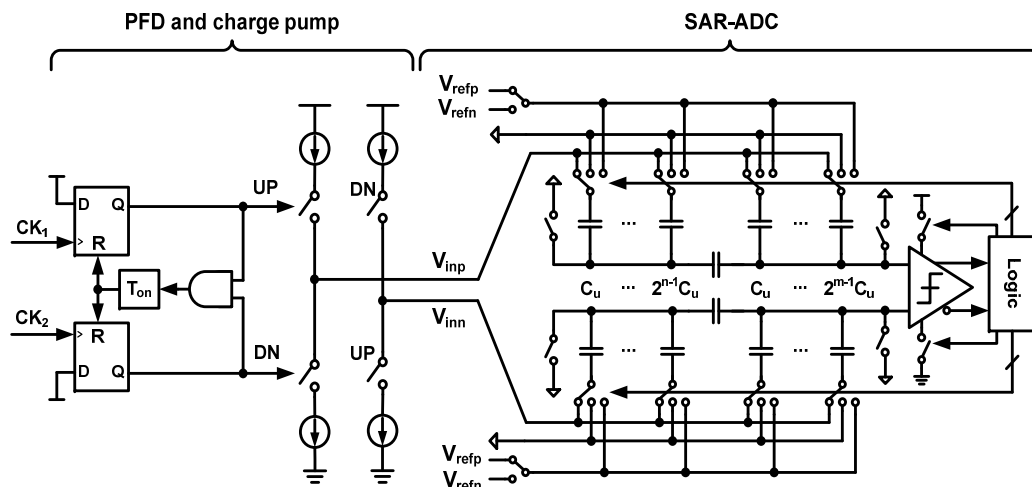
# High precision Time to Digital Converter / 56

Charge pump + SAR ADC realizes sub-ps TDC  
Resolution of conventional inverter based TDC is 10 ps at most.

Low phase noise fractional PLL  
On-chip jitter measurement  
Sub-mm laser radar



DNL and INL in 8-bit with 0.84ps/LSB

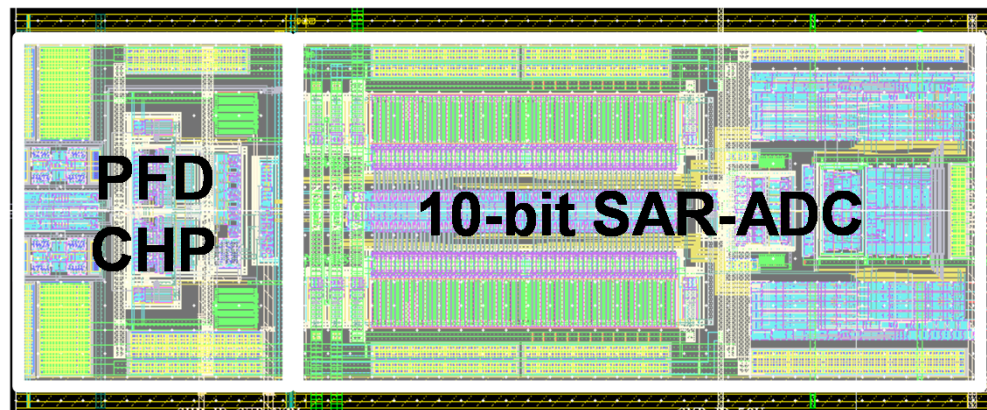  


0.8ps, 10bit, 100Msps, 4mW, 0.02mm<sup>2</sup>

Z. Xu, A. Matsuzawa, CICC 2013.

PLL is one of the rare area that digital technology is not used.


Conventional charge pump PLL has an essential limitation, however high precision TDC has not been developed.

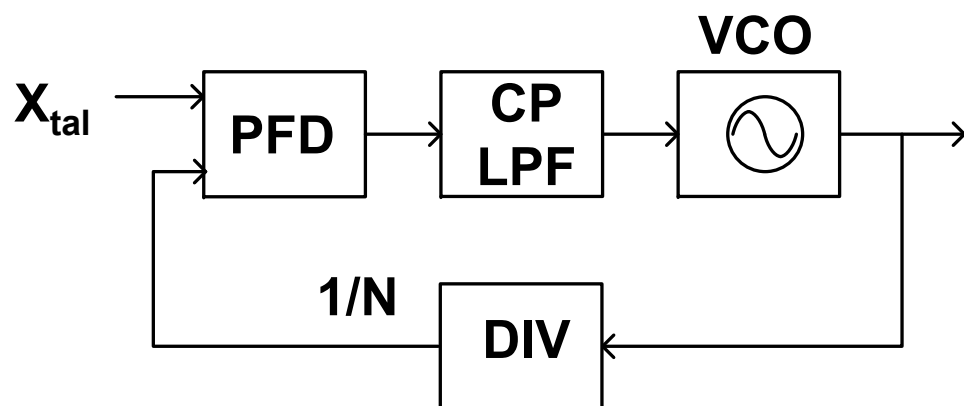The success of high precision TDC will realize high performance Full Digital PLL.



Large area  
Not adaptive

Conventional Charge-pump PLL

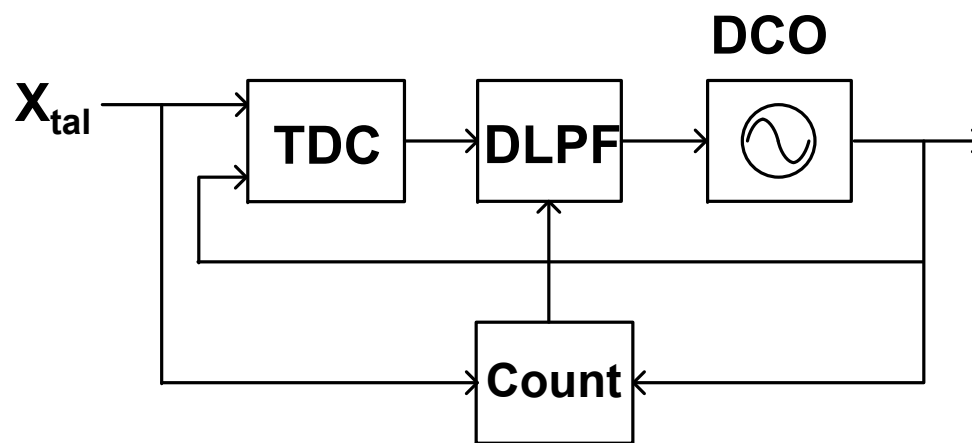

Full digital PLL

Fractional  
Small area  
Adaptive  
Low jitter

# Layout-driven circuit design and programmable analog circuit technique


- **Motivation**

- Lack of analog circuits designers
- Analog circuits design will continue to be difficult
  - Less margin for low voltage operation
- Short development time and cost saving are required

- **Solution**


- Regular structure layout
  - Can realize small area, low power, high speed
  - Can control parasitic components
  - Can use automated layout design
- Select circuits that have high robustness

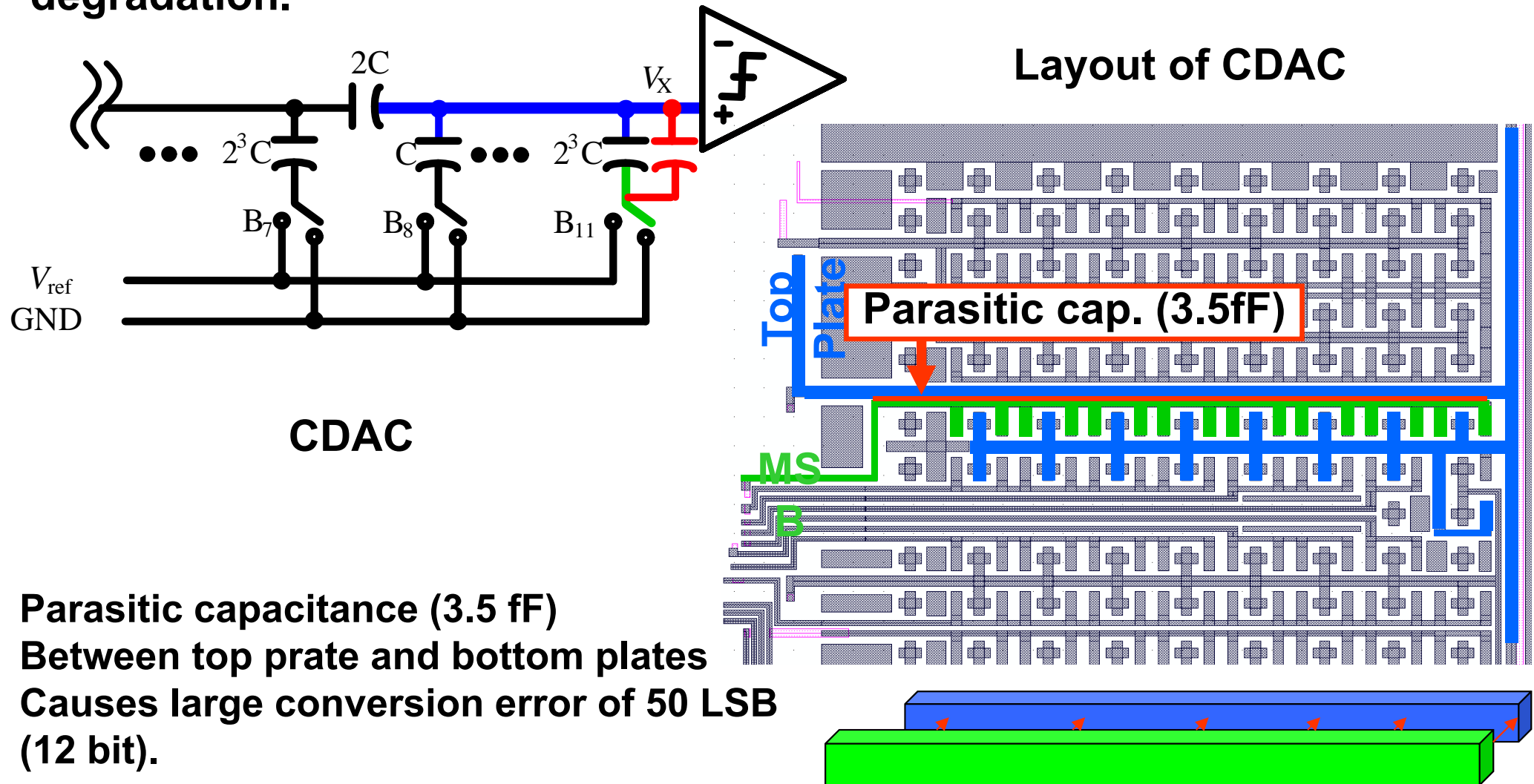A conventional layout idea of **Place** the components and **Route** them causes parasitic components essentially and it results in performance degradation.




# Regular layout driven design

61

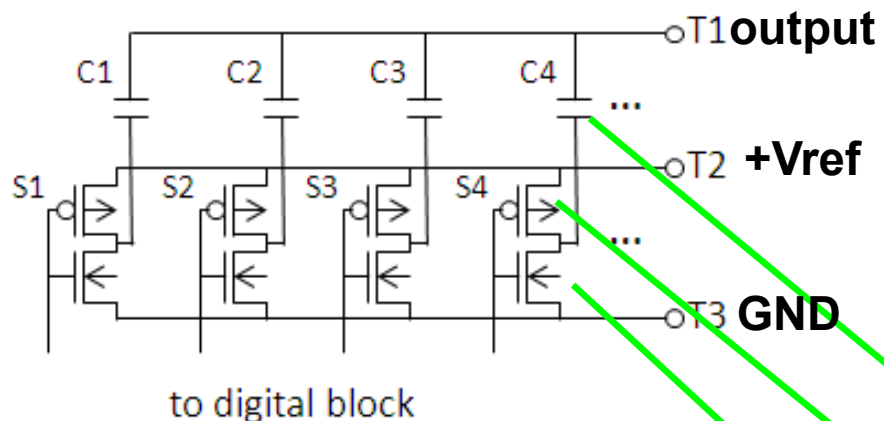

 Avoid wires between components  
Wire itself is the component  
Respect the regularity  
Pitch should be aligned



菅原, 松澤 他, アナログRF 研究会, 2013年11月


# Ideal layout design

62

Pitch is aligned.

It minimizes parasitic component, wire length, delay and capacitance.

 
Low power, high speed, small area, and high robustness can be realized.



SAR ADC


菅原, 松澤 他,  
アナログRF 研究会  
2013年11月

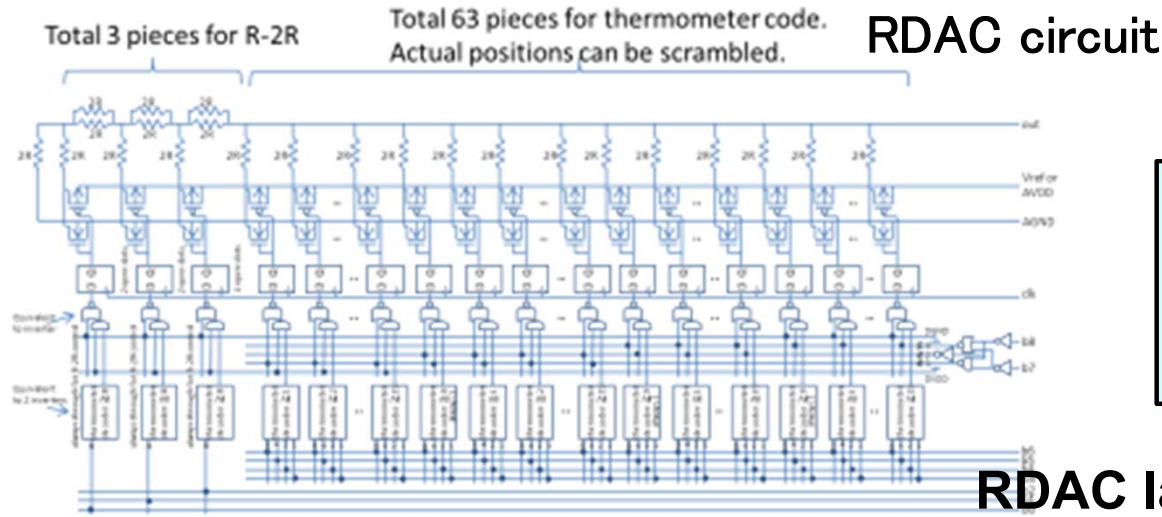We can compose analog layout automatically with SKILL language




盛, 松澤 他, "9ビットRDACの自動合成"  
アナログRF 研究会, 2013年8月

 Automated optimization  
Automated layout with SKILL  
language





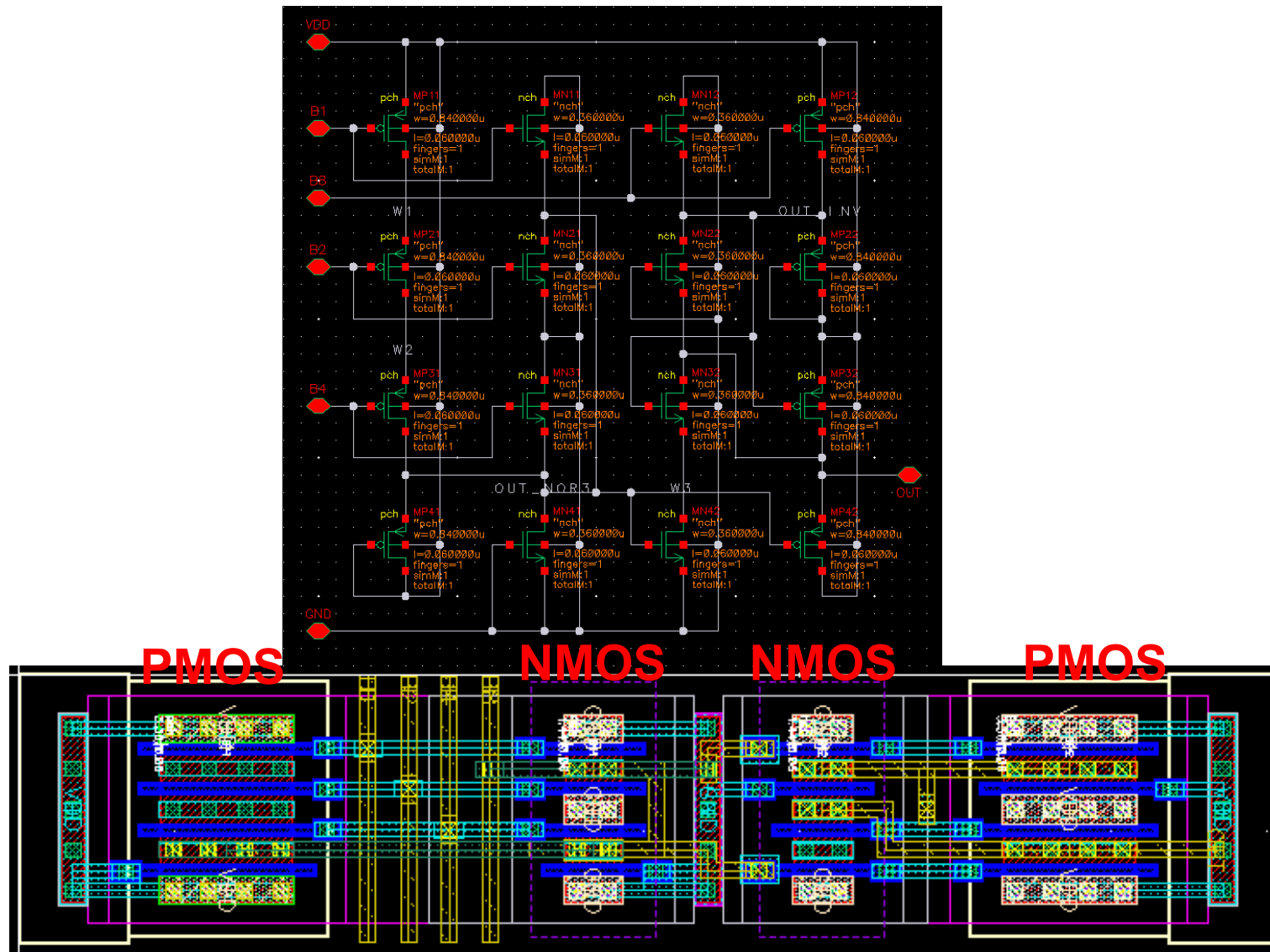Logic gates should have regularity and launch the automated layout.




# Align the layout pitch


65

TOKYO TECH  
Pursuing Excellence

 Logic gates, DFFs, switches, and resistors are aligned



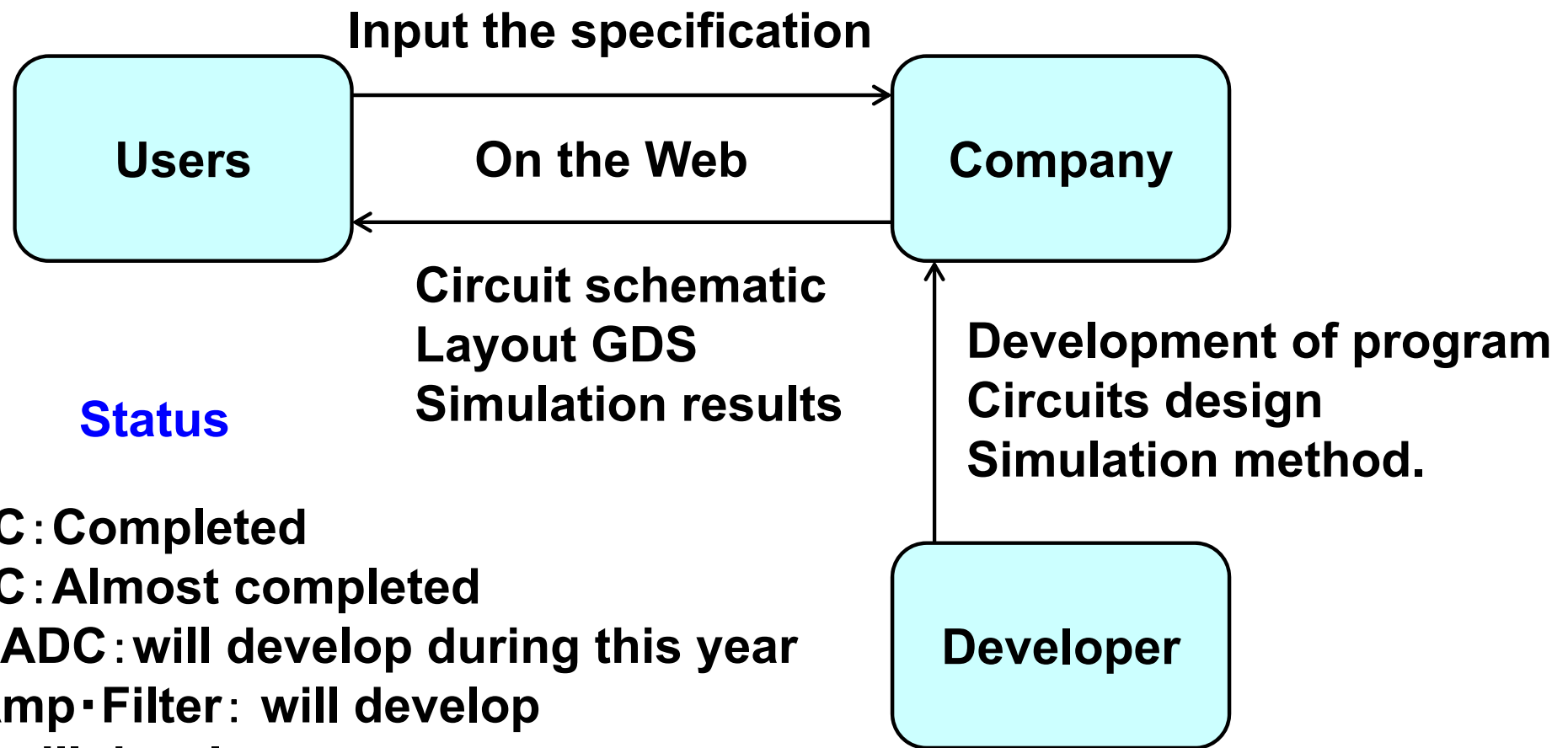**Circuit should be composed automatically.  
Developers develop the technology itself.**



- **We have realized the world's first 64QAM and attained the world's fastest 28Gbps.**
  - Not only increase BW but also increase SNDR
  - MIMO is the next step
- **Developed 12b SAR ADC can cover almost all the performance area for wireless communication with the lowest power.**
  - Dynamic capacitance and comparator
  - MOM capacitance
  - Over sampling, Dither, and DEM
- **7bit 2.2 GHz ADC with time-domain signal processing**
  - Time-domain processing can realize folding and interpolation with simple logic gates. Suitable for low voltage operation
- **PLL will be progressed and finally use digital techniques**
  - Injection locking method
  - Full digital PLL using fine TDC
- **Regular layout driven automated design will be developed.**