

Introduction to Embedded Data Converters

Akira Matsuzawa

Tokyo Institute of Technology

Contents

- 1. Introduction**
- 2. Characterization of data converters**
- 3. Overview of high-speed A/D converters**
- 4. Overview of high-speed D/A converters**
- 5. Overview of over-sampling sigma-delta data converters**
- 6. Basic design considerations**


1. Introduction

- **Mixed signal systems**
 - **Software defined radio**
 - **Digital read channel**
 - **Mixed Signal SoC**

- **Progress of ADC and DAC**
 - **Power and area**
 - **Embedding**

Basic mixed signal system

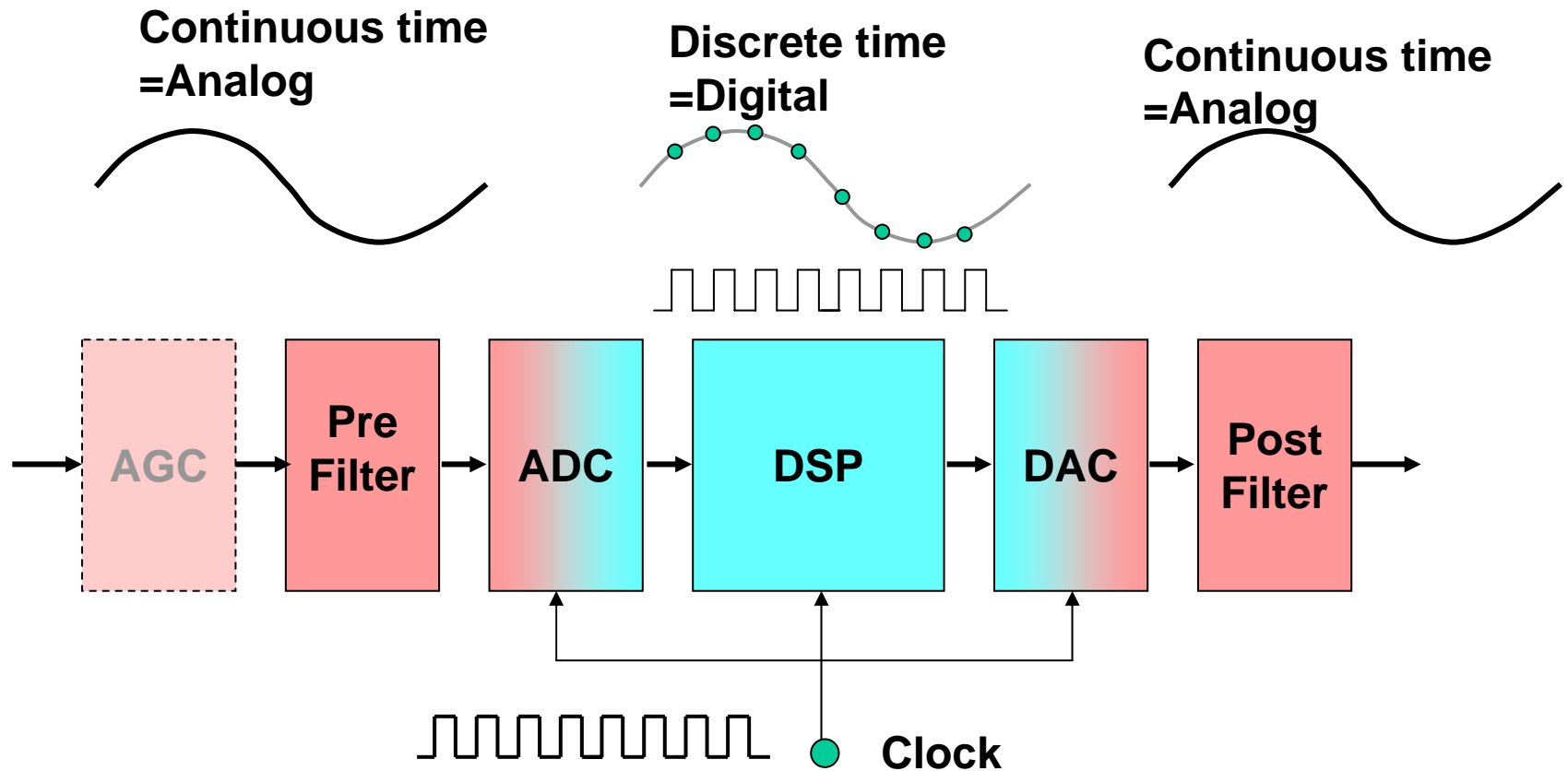
Mixed signal systems basically consist of DSP, ADC, DAC, and pre/post filters. The signals are converted between continuous time and discrete time.




Software defined radio

Future wireless systems need powerful ADC and DAC for software defined radio.

 
Future cellular phone needs 11 wireless standards!!



Multi-standards and multi chips

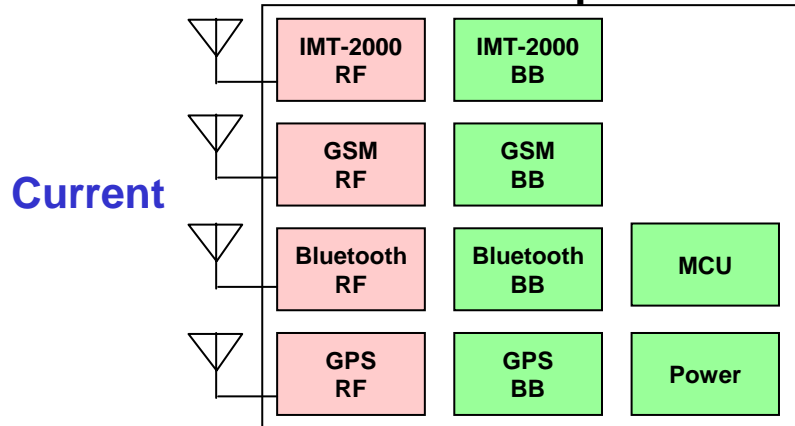

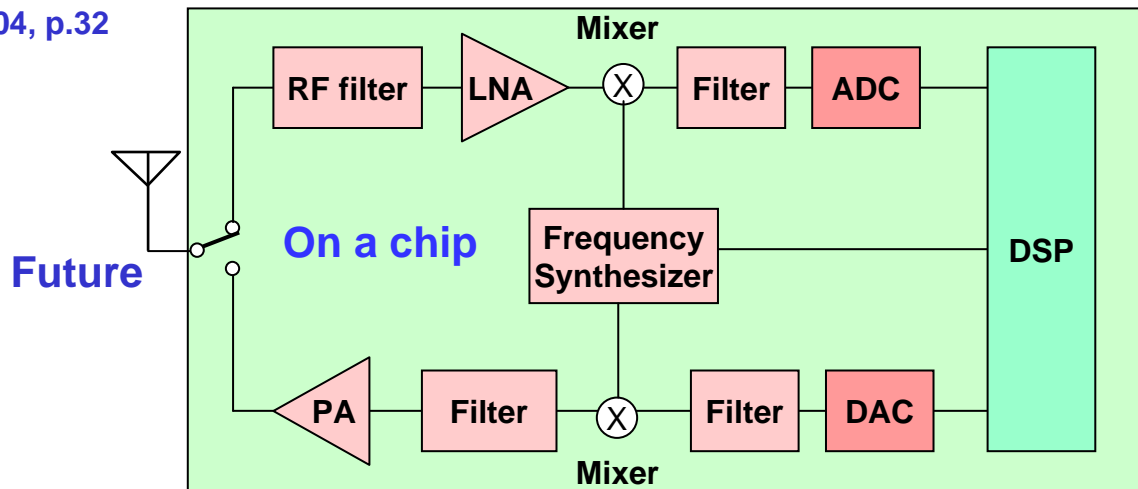
Multi-bands and Multi-standards on a single chip



Yrjo Neuvo, ISSCC 2004, p.32

Mixed signal tech. ; Digital read channel

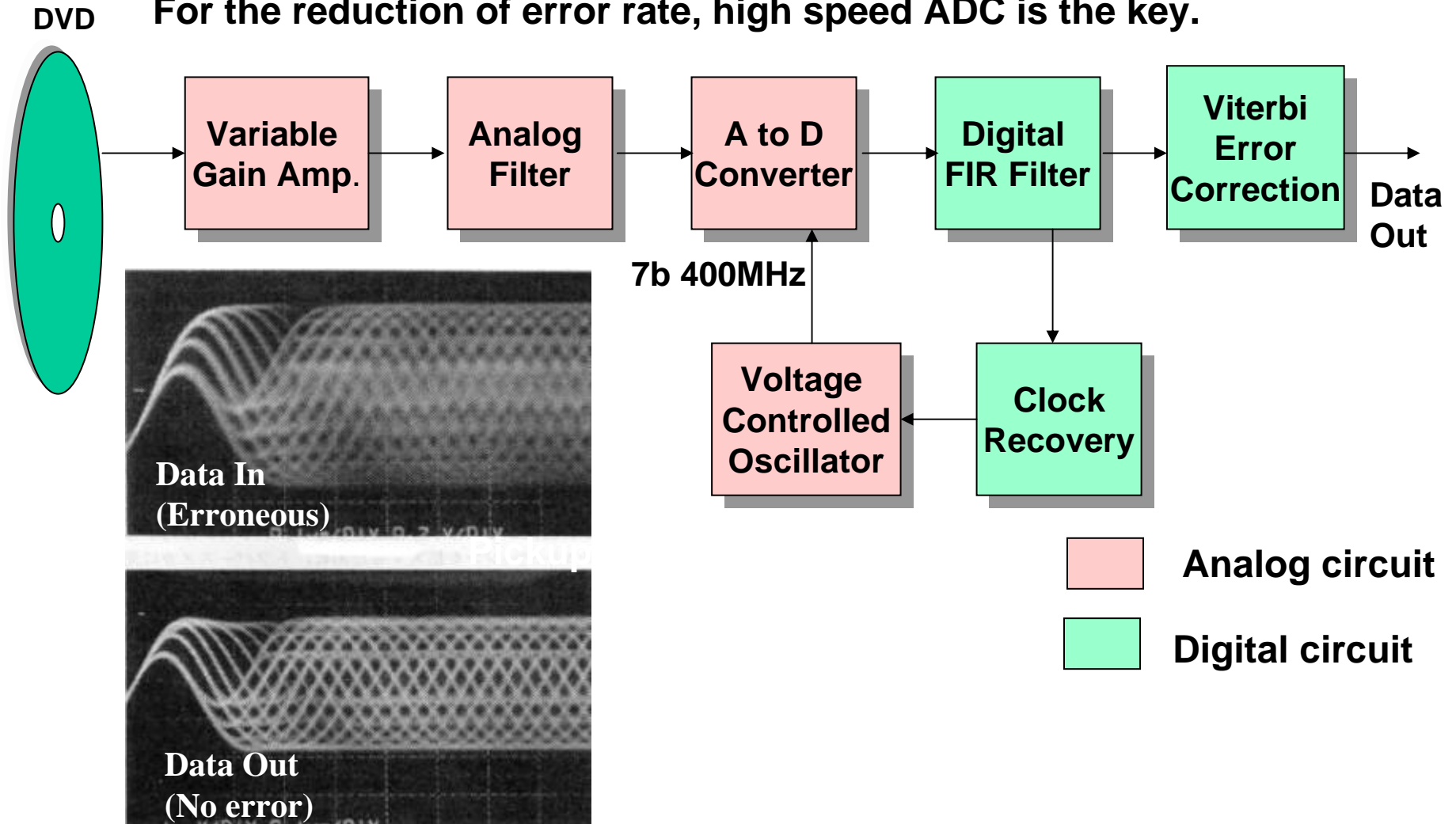
Digital storage needs high speed mixed signal technologies.
For the reduction of error rate, high speed ADC is the key.



Mixed signal SoC

Mixed signal SoC can realize full system integration for DVD application.
Embedded analog is the key.

0.13um, Cu 6Layer, 24MTr

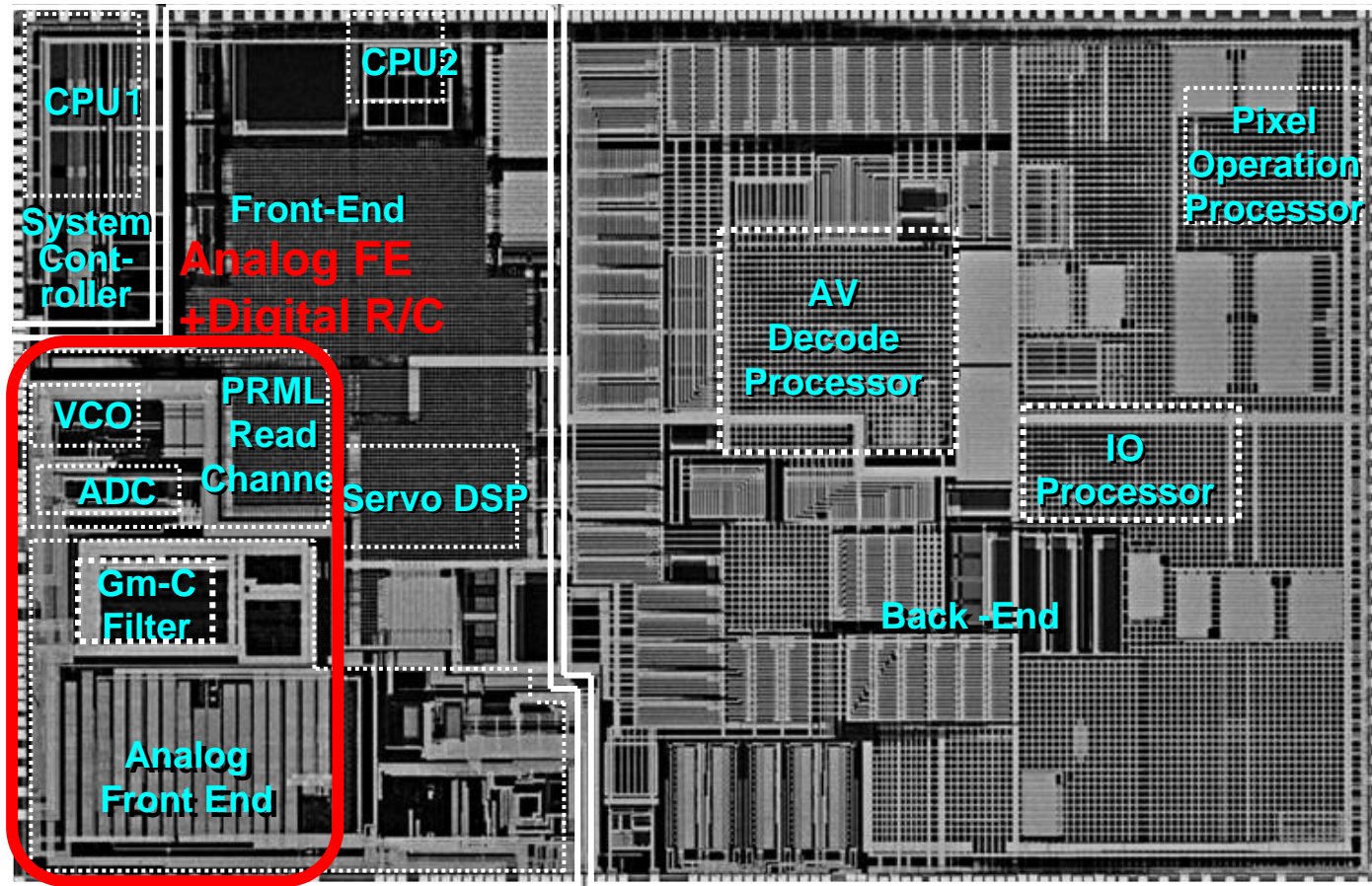


Okamoto, et al., ISSCC 2003

Progress of high-speed ADC

High speed ADC can be embedded in CMOS resulting in power reduction.


ISSCC 1991

 

6b, 1GHz ADC
2W,
1.5um Bipolar

Matsuzawa, ISSCC 1991

ISSCC 2000

 

6b, 800MHz ADC
400mW, 2mm²
0.25um CMOS

Sushihara, et al, ISSCC 2000

ISSCC 2002




Technology : 0.18um CMOS(3AL1P5)
Area : 0.88mm X 0.34mm

World lowest Pd HS ADC

7b, 400MHz ADC
50mW, 0.3mm²
0.18um CMOS

Sushihara and Matsuzawa, ISSCC 2002

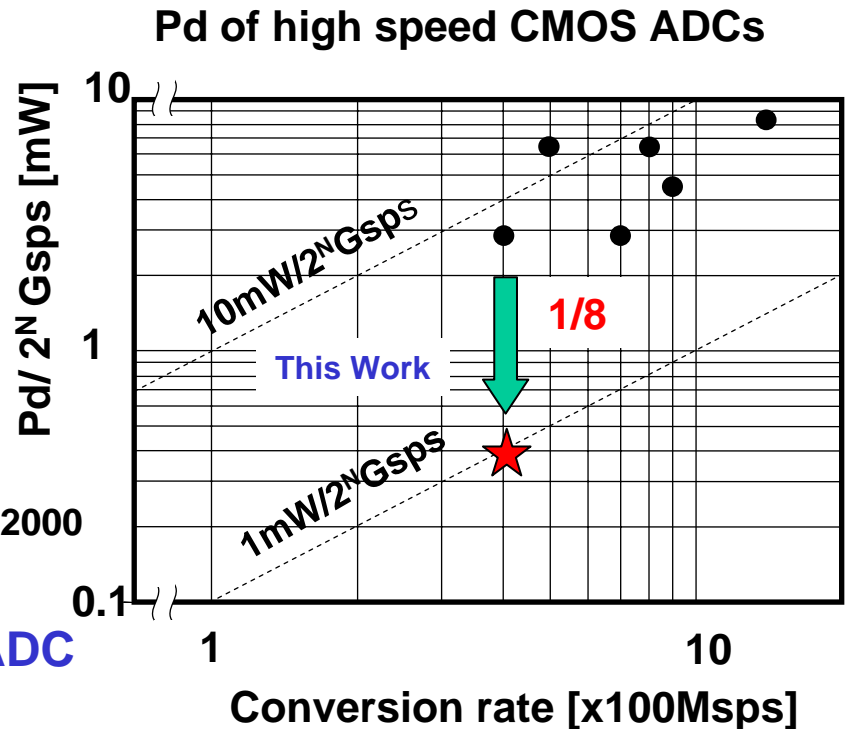


Progress of A/D converter; video-rate 10b ADC


1/2000 in Power and 1/200,000 in cost during past 20 years

ADC was the bottle-neck for the digital TV and Video systems
Technology progress has solved this problem.

1980	1982	1993	Now
Conventional product	World 1 st Monolithic	World lowest power	SoC Core
Board Level (Disc.+Bip)	Bipolar (3um)	CMOS (1.2um)	CMOS (0.15um)
20W	2W	30mW	10mW
\$ 8,000	\$ 800	\$ 2.00	\$0.04

 

 T. Takemoto and A. Matsuzawa,
JSC, pp.1133-1138, 1982.




K. Kusumoto and A. Matsuzawa,
ISSCC 1993.




Power and area reduction of video-rate 10b ADCs

Power and area of ADC have been reducing continuously.
Currently, ADC can be embedded on a chip



Power reduction

 

Area reduction

 

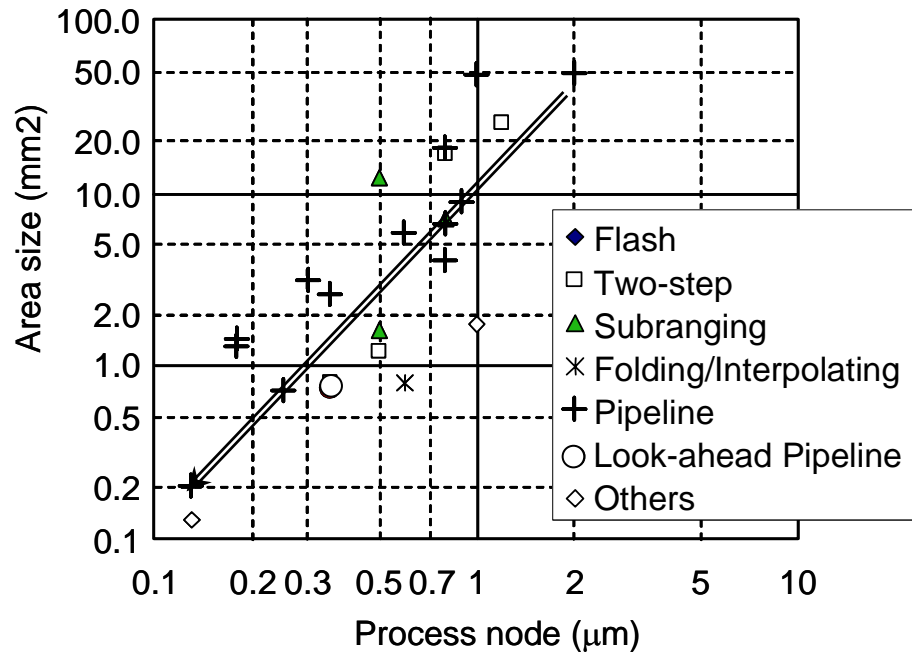 Power and area reduction of video-rate 10b ADCs



M. Hotta et al. IEICE 2006. June

Embedding ADC on a CMOS chip



CMOS ADC and DAC has been embedded on a CMOS chip.
This has realized low cost and low power digital portable AV products.

1993 Model: Portable VCR with digital image stabilizing



A. Matsuzawa, JSC, pp. 470-480, 1993.

System block diagram

  


2. Characterization of data converters

- **Basic functions of ADC and DAC**
- **Static performance**
 - INL, DNL, monotonicity
 - Quantization noise
- **Dynamic performance**
 - SNR, SFDR, THD, SNDR, ENOB
 - Sampling Jitter
 - ERB
 - Glitch
- **Figure Of Merit**
- **Performances and applications**
 - Needed performances for wireless systems

Basic functions of ADC

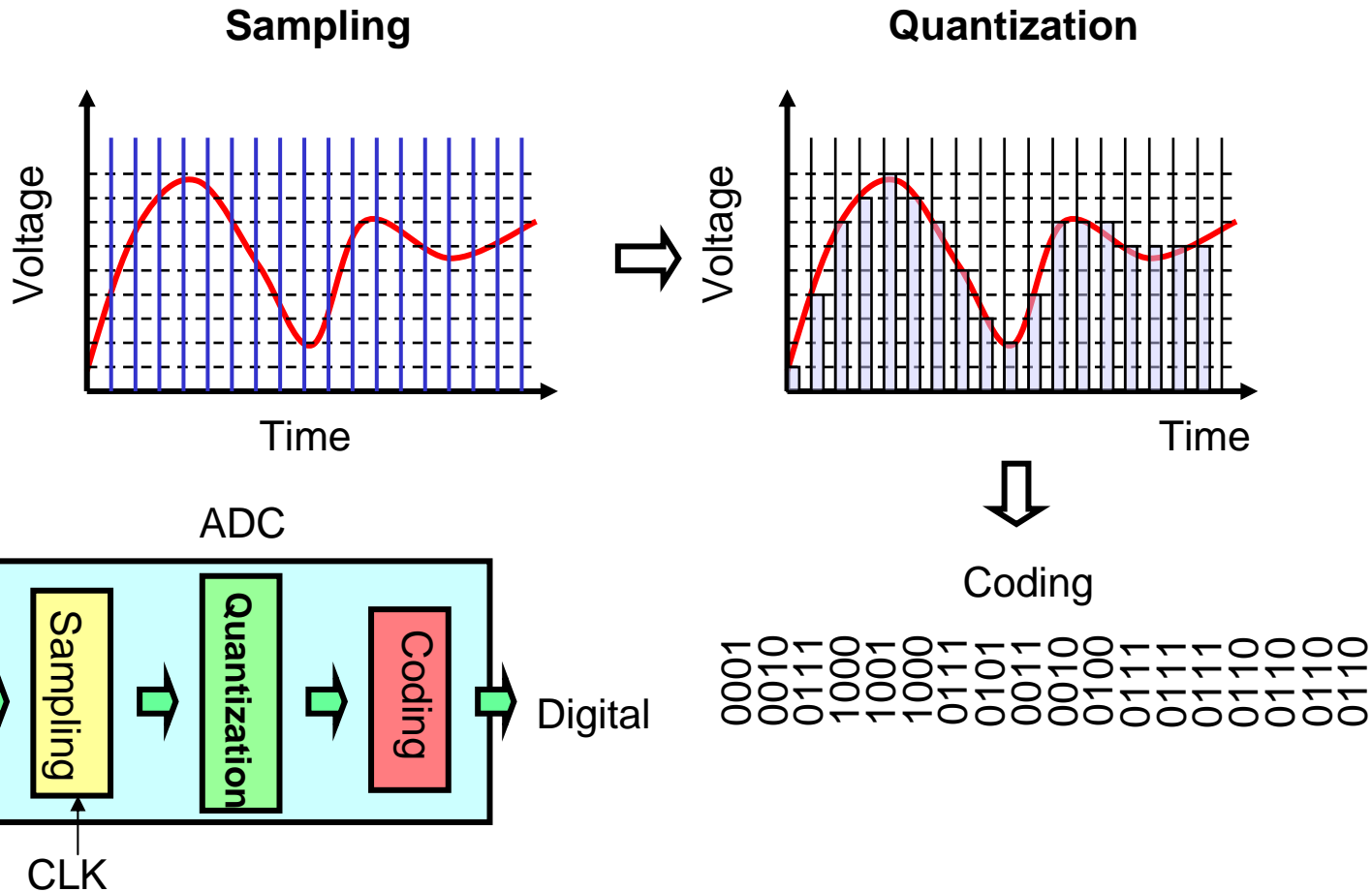Sampling: Sampling the analog signal with accurate timing.
Quantization: Express the converted data with certain accuracy.



Static performance


INL and DNL are the major static performance indicators of ADC and DAC.

DNL: Differential Non-Linearity $DNL_j \equiv \frac{Width_{ACTUAL,j} - Width_{IDEAL}}{Width_{IDEAL}}$

INL: Integrated Non-Linearity $INL_j \equiv Transfer\ function_{ACTUAL,j} - Transfer\ fuction_{IDEAL,j}$


$$INL_j = \sum_{k=0}^{k=j} DNL_k$$

$$DNL_j = INL_{j+1} - INL_j$$

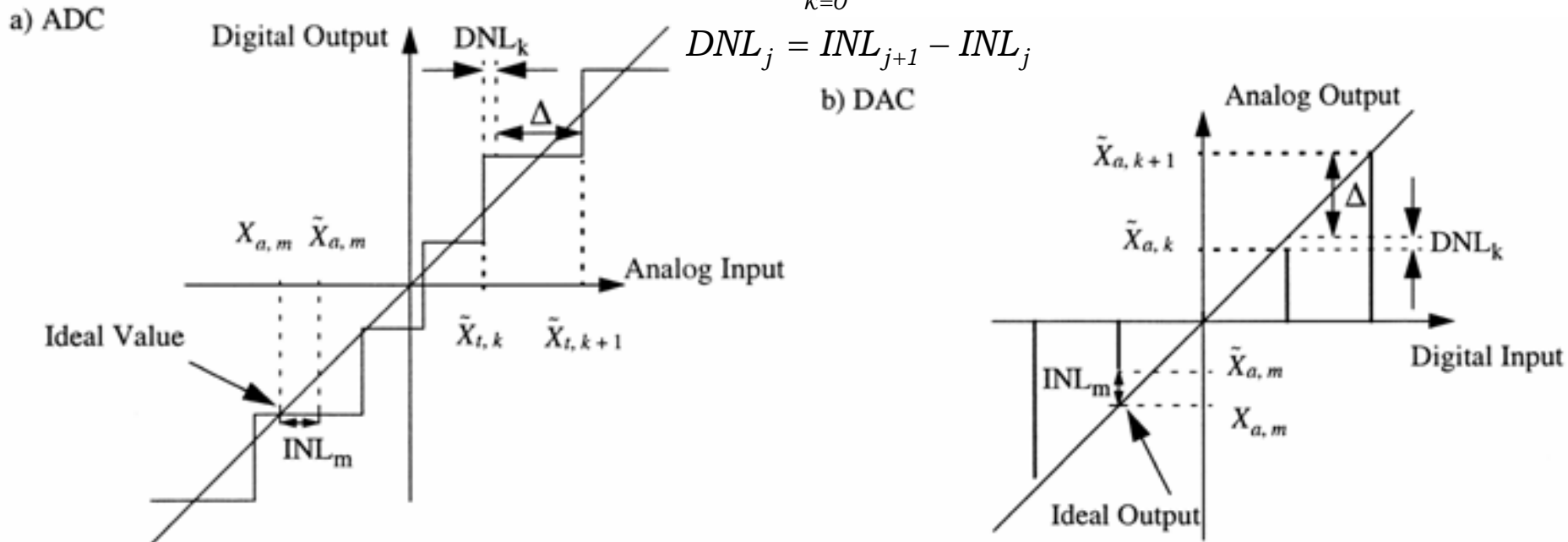


DNL and INL

DNL profile

 

INL profile

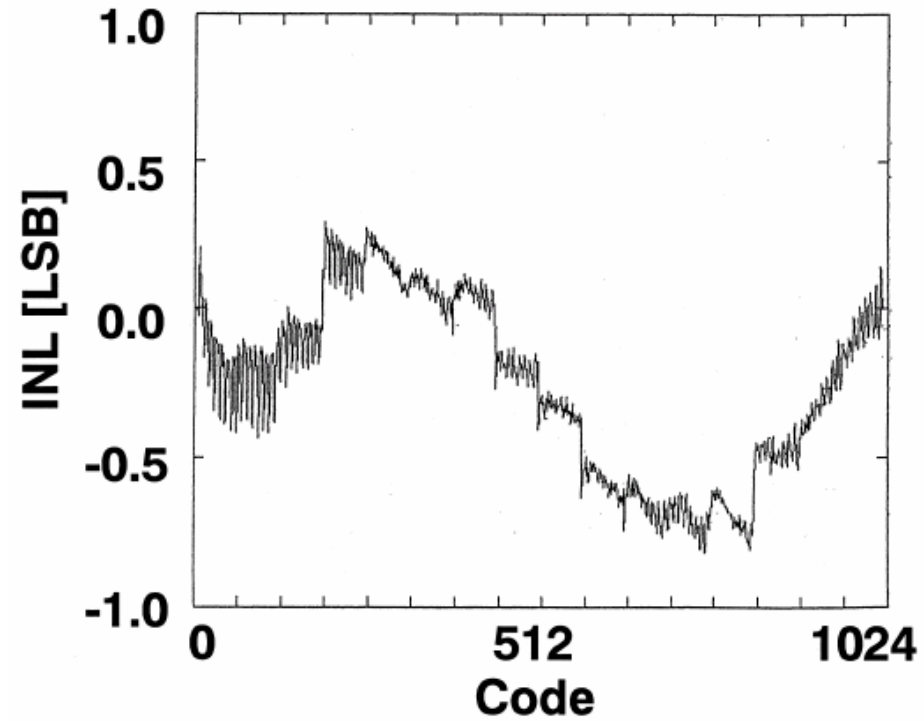



Monotonicity in DAC

Binary coded DAC often degrades monotonicity.

The monotonicity stands for the qualitative characteristics of data converters of which transfer function keep the monotonic increase or decrease.

At the change of MSB bit

 
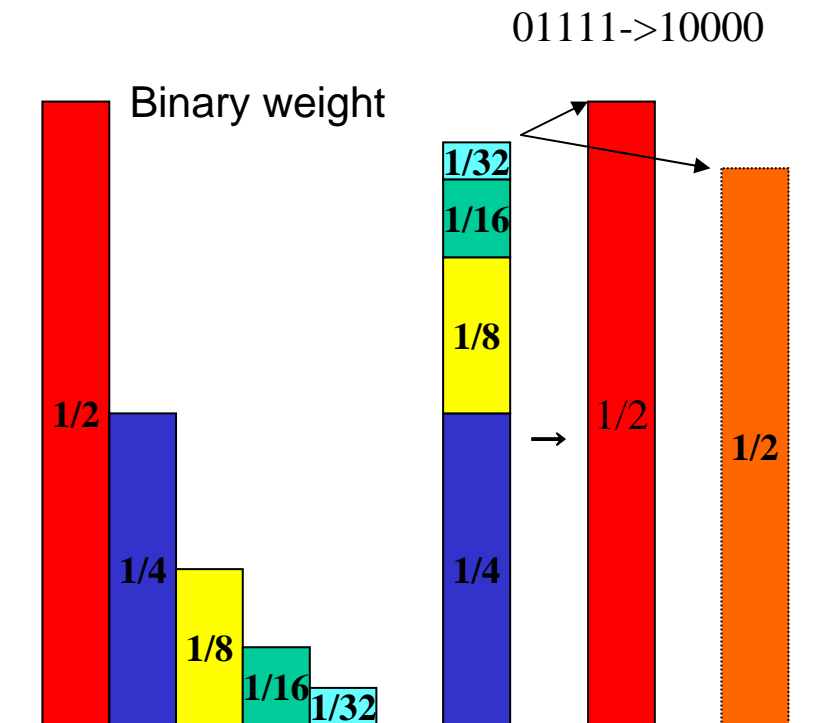
If the converter can not guarantee the monotonicity, The feedback loop doesn't work properly and results in backrush.



Quantization noise

Quantization causes noise

Higher SNR needs higher resolution

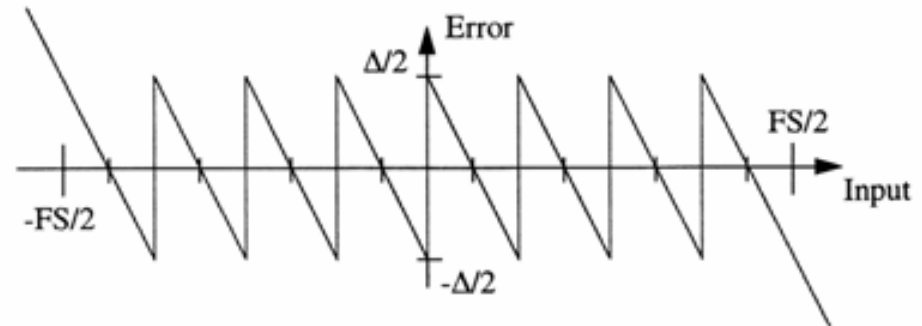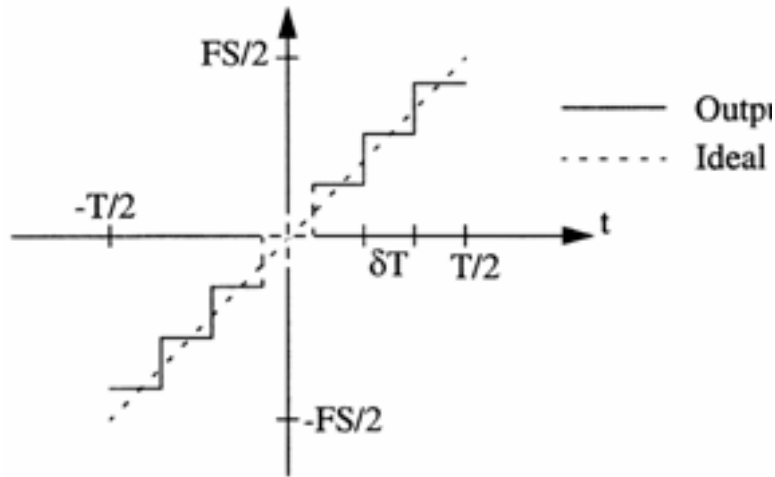

Quantization noise

Transfer characteristics

$$P_n = \int_{-\Delta/2}^{\Delta/2} e^2 P(e) de = \int_{-\Delta/2}^{\Delta/2} e^2 \frac{1}{\Delta} de = \frac{\Delta^2}{12}$$

$$\therefore P(e) = \begin{cases} \frac{1}{\Delta} & , |e| < \frac{\Delta}{2} \\ 0, & \text{all other } e \end{cases}$$

$$P_s = \frac{(\Delta \cdot 2^{N-1})^2}{2}$$

$$SNR \equiv \frac{P_s}{P_n} = \frac{(\Delta \cdot 2^{N-1})^2}{2} \cdot \frac{12}{\Delta^2} = 1.5 \cdot 2^{2N}$$

$$SNR_{dB} = 10 \log \left(\frac{P_s}{P_n} \right) = 6.02 \cdot N + 1.76$$

Dynamic performance

Dynamic performance indicates the ratio between signal and noise or distortion.

We should use the suitable terms depending upon the type of application.


$$SNR = 10 \log \frac{\text{Signal power}}{\text{Total noise floor power}}$$

$$SFDR = 10 \log \frac{\text{Signal power}}{\text{Largest spurious power}}$$

$$THD = 10 \log \frac{\text{Total harmonic distortion power}}{\text{Signal power}}$$

$$SNDR = 10 \log \frac{\text{Signal power}}{\text{Noise and distortion power}}$$

$$ENOB = \frac{SNDR - 1.76}{6.02}$$

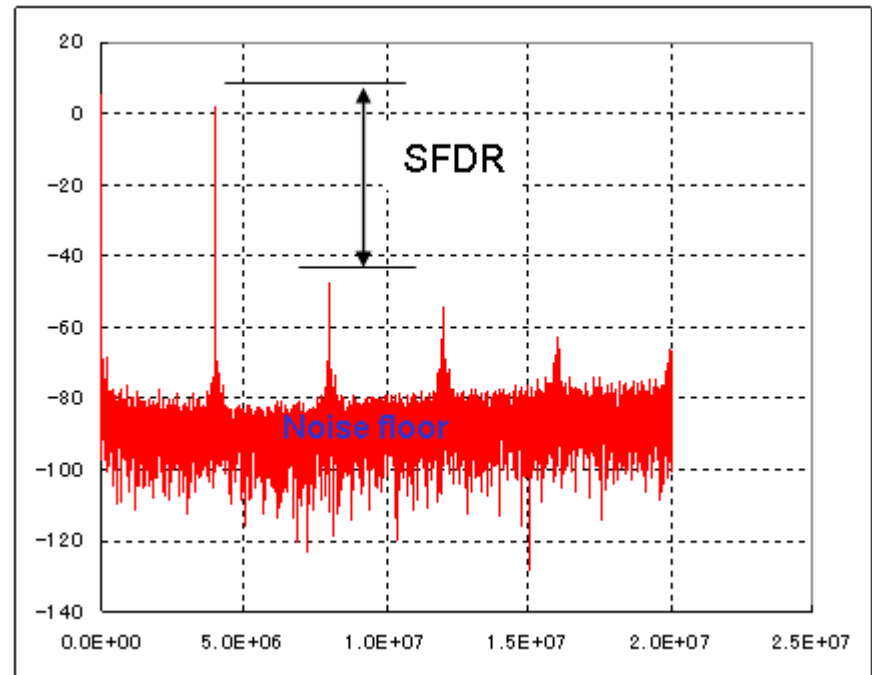

$F_c=40\text{MHz}$, $f_{in}=4\text{MHz}$

SFDR=49.8dB

SNDR=44.9dB, ENOB=7.17-bit



2ndHD=-49.8dB, 3rdHD=-56.7dB

Sampling jitter effect

Sampling jitter is converted to noise.


When the input frequency becomes higher, the SNR becomes lower.
  
$$SNDR(dB) = -10 \log \frac{1}{(2\pi f_{in} \sigma_t)^2}$$



Effective Resolution Bandwidth

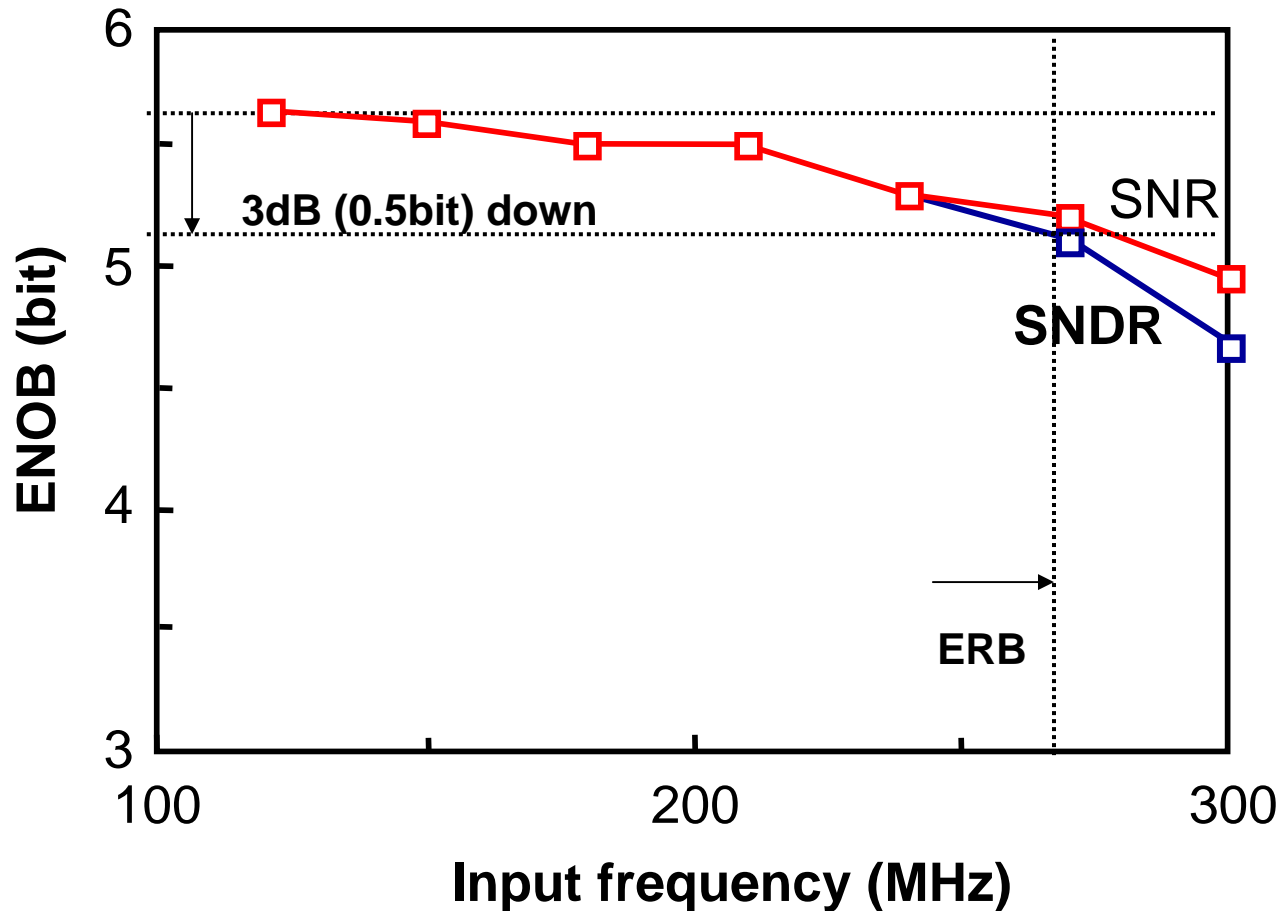
ERB is the input frequency where the SNDR has dropped 3dB (or ENOB 0.5 bit)




Glitch

Glitch is the spiky signal at code transition.


State 1: [1000]=8

 

State 2: [0111]=7

 

Intermediate: [1111]=15

 

Caused by overlapping of signals
This appears within a few psec,
However, energy is not negligible.
Glitch causes the distortion of signal

$$P_{g,max} = 2^{2N-2} \cdot \Delta^2 \cdot \frac{T_g}{T_s}$$

$$P_{g,max} < P_{QN} = \frac{\Delta^2}{12}$$


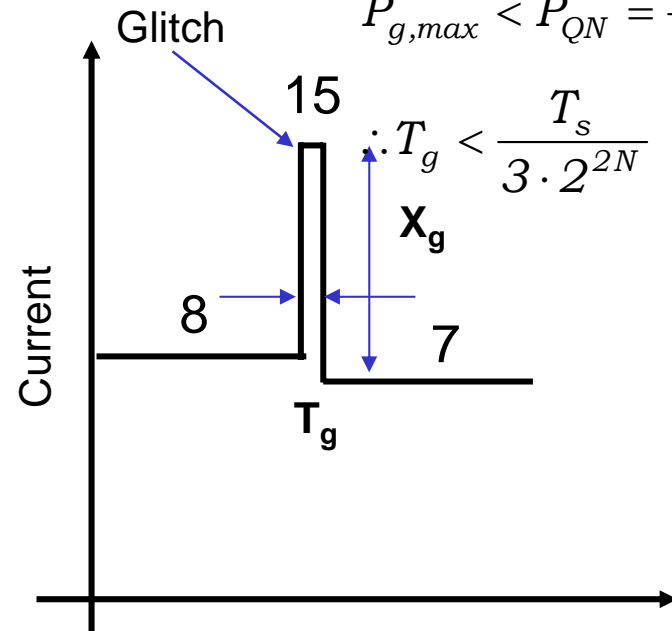


Figure Of Merit


Figure of merit shows energy efficiency for data conversion.
 
$$\begin{aligned}
 FOM &= \frac{\text{Energy}}{\text{Conversion step}} \\
 &= \frac{\text{Power}}{2^{ENOB} \times f_s} \\
 \text{or} &= \frac{\text{Power}}{2^{ENOB} \times 2BW}
 \end{aligned}$$




Performance and application

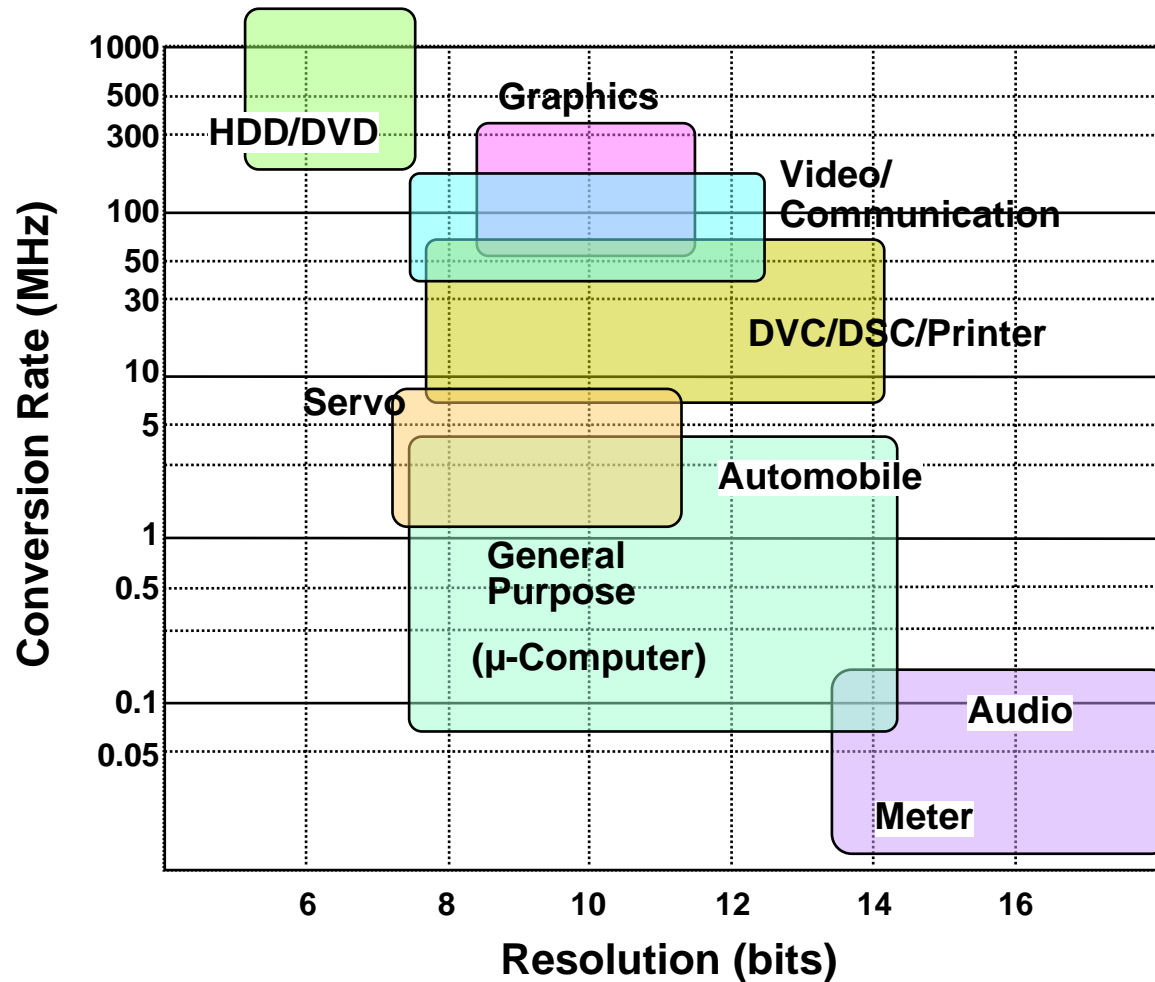Needed resolution and conversion rate depending upon the application.



Needed SNR for certain BER in wireless system

 Lower Bit Error Rate in the digital modulation needs higher SNR.




n-PSK

$$BER \approx \text{erfc} \left(\sqrt{SNR} \sin \frac{\pi}{n} \right)$$

n-QAM


$$BER \approx 2 \left(1 - \frac{1}{\sqrt{n}} \right) \text{erfc} \left(\frac{\sqrt{2 \cdot SNR}}{2(\sqrt{n} - 1)} \right)$$

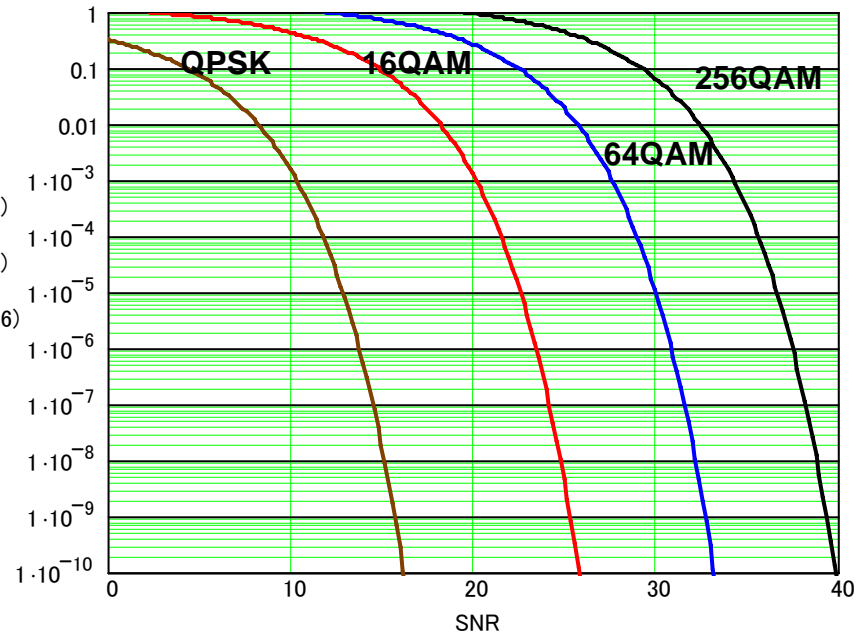$BER_q(SNR, 16)$
 $BER_q(SNR, 64)$
 $BER_q(SNR, 256)$
 $BER_p(SNR, 4)$




BER requirement

 The lower the bit error rate the higher the required ADC/DAC resolution.
Resolution (quantization noise) affects BER.




DAC requirement for QAM

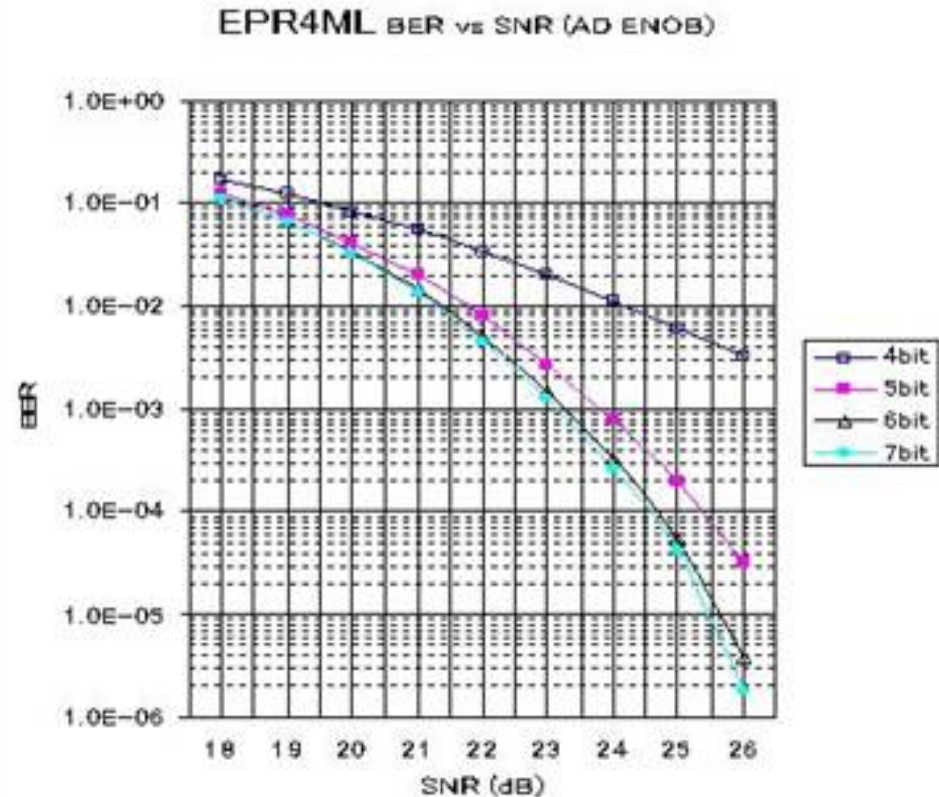

ADC requirement for digital read-channel


Signal intensity in wireless system

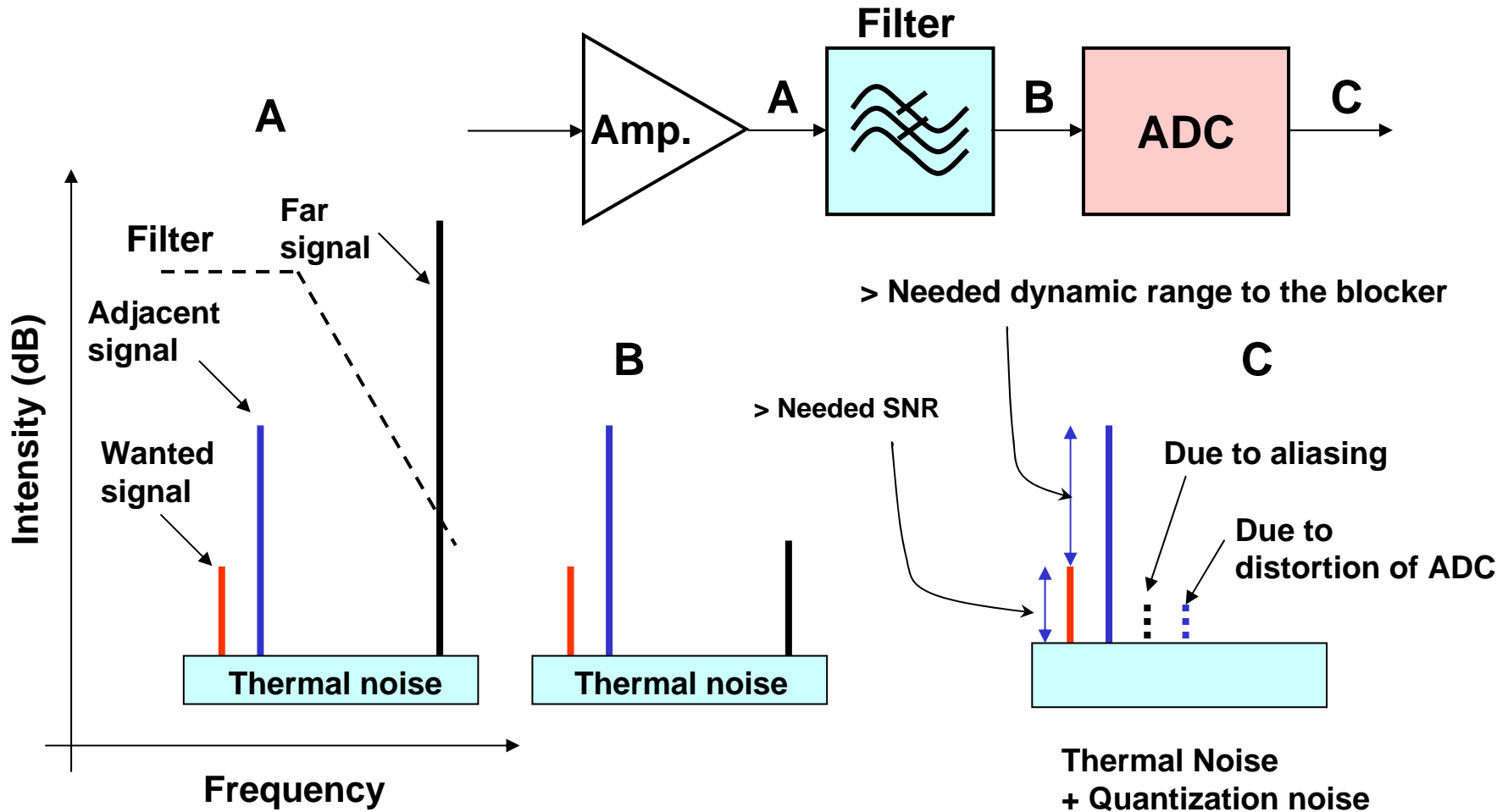Wireless system has strong unwanted signals.
Also, electric circuits generate distortion and noise.



Needed ADC dynamic range

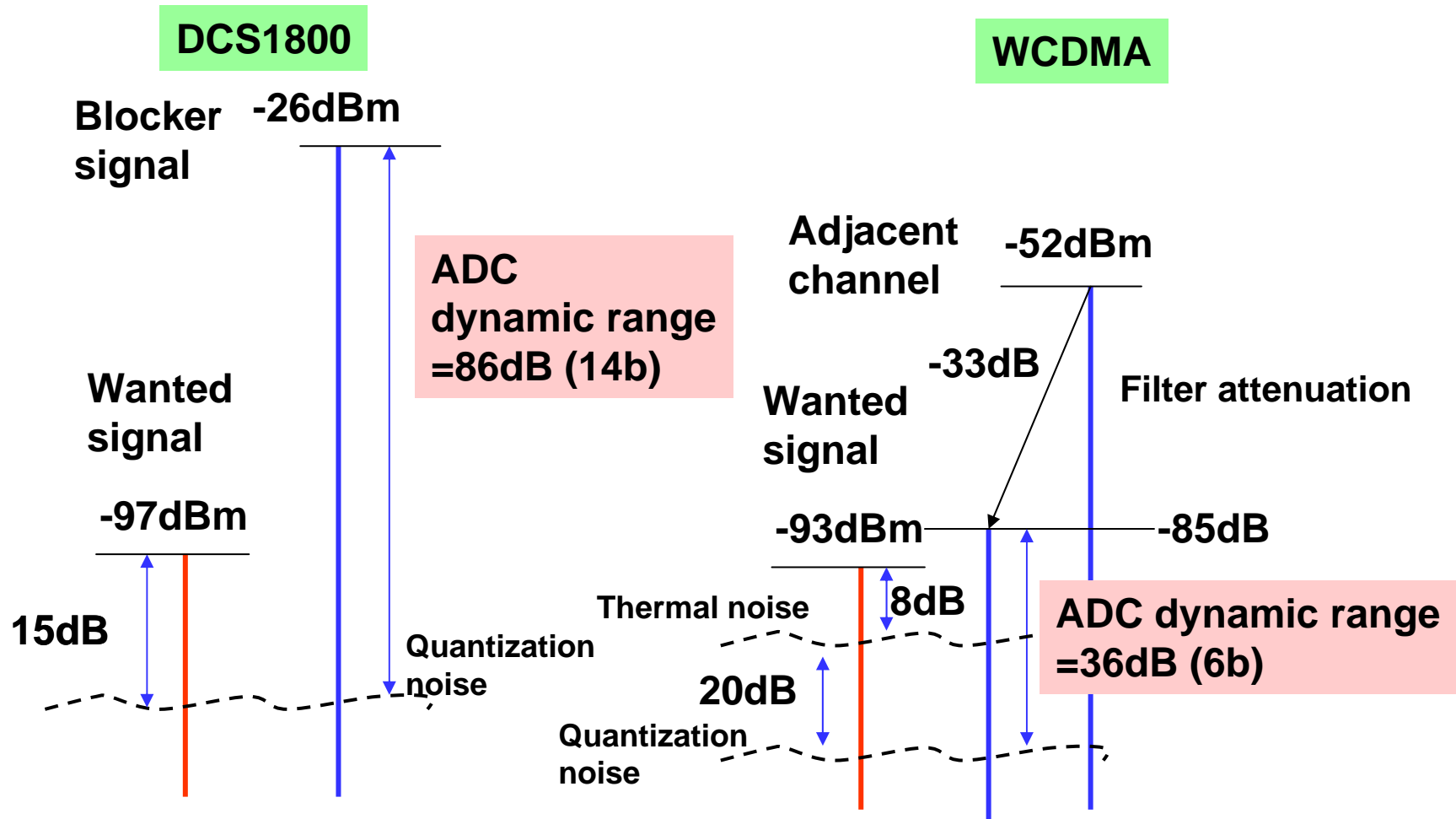Existence of strong blockers results in the need for high dynamic range ADC.




3. Overview of high-speed A/D converters

- **Performance and ADC architecture**
- **Integrating ADC**
- **Successive approximation ADC**
- **Flash ADC**
- **Sub-ranging ADC**
- **Interpolation method**
- **Folding ADC**
- **Pipelined ADC**


ADC performance and architectures

 There are many conversion architectures with varying performance parameters.




Integrating ADC

 Integrating ADC achieves high resolution, but at low speed. Recently it has been used as column-ADC in CMOS imager.



Water clock

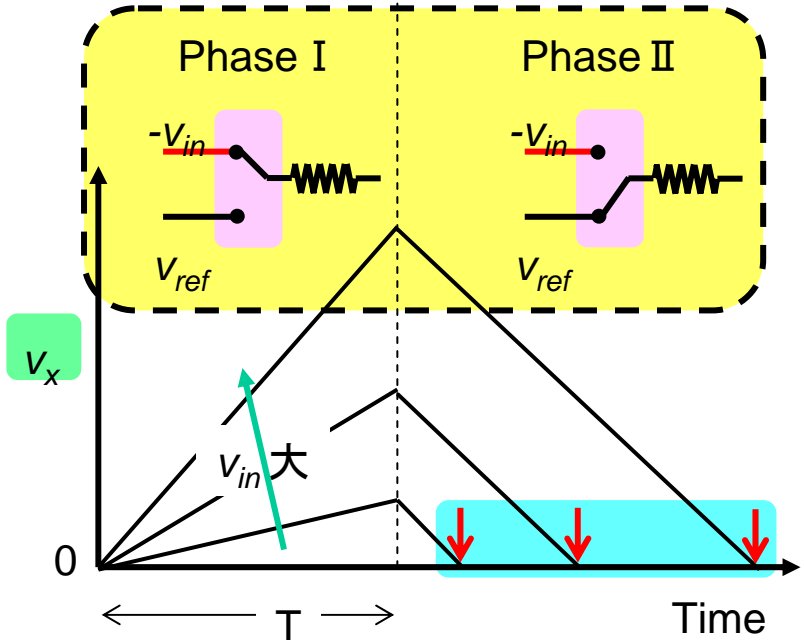- High resolution (20bit and more)
- Very low speed (DC measurement)
- Small DNL
- Can realize zero offset voltage
- Small analog elements and area






Going to 0 -> 1, when V_x becomes negative.

$$v_x(T) = -\int_0^T \frac{(-v_{in})}{RC} d\tau = \frac{v_{in}}{RC} T$$

Successive-approximation ADC

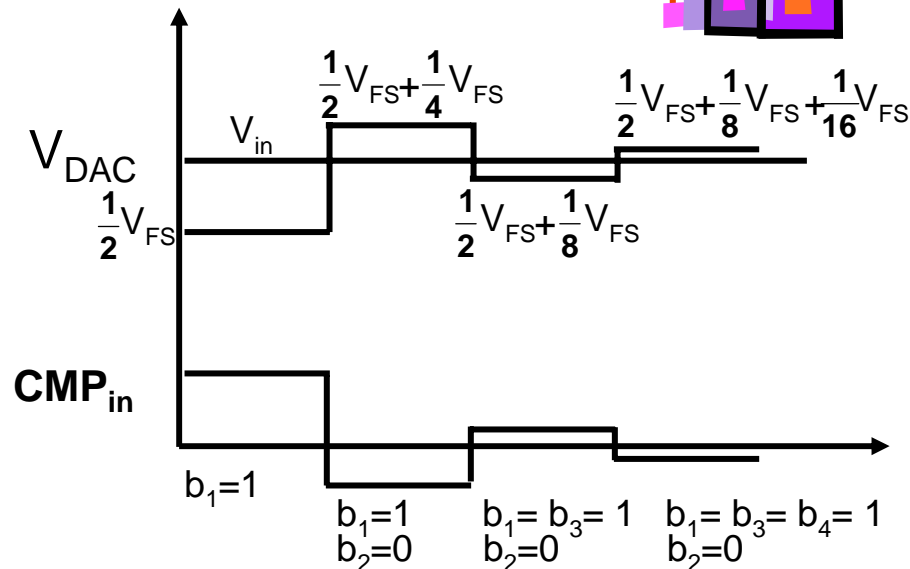 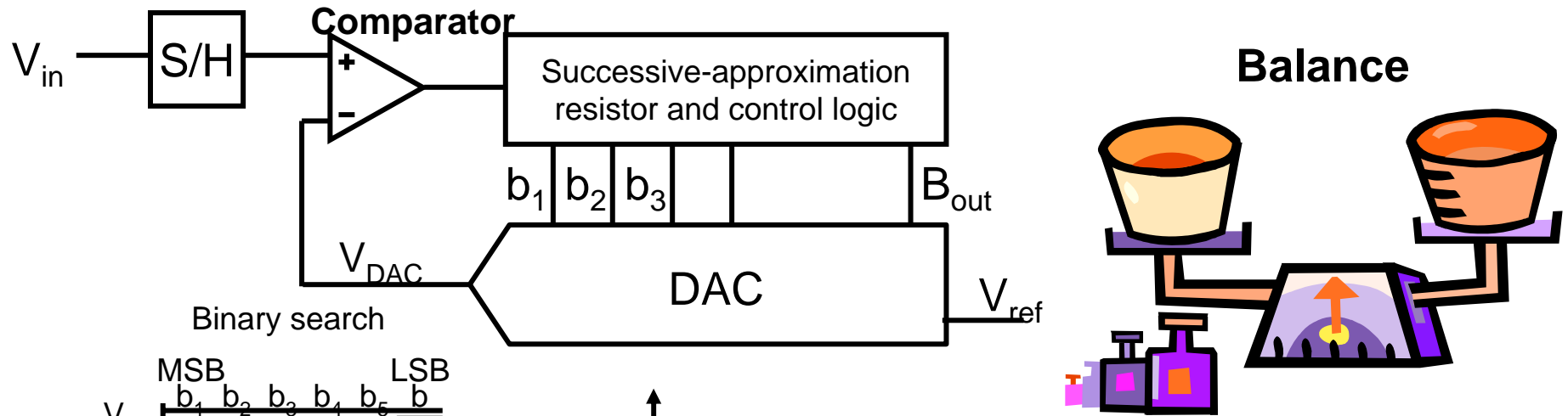
Successive-approximation method is based on a binary search.




Charge-redistribution ADC

Charge-redistribution ADC draws attention as a suitable ADC in the nano-meter CMOS era. Because it needs no OP-Amp, but just needs capacitors and comparator.

1) Sampling

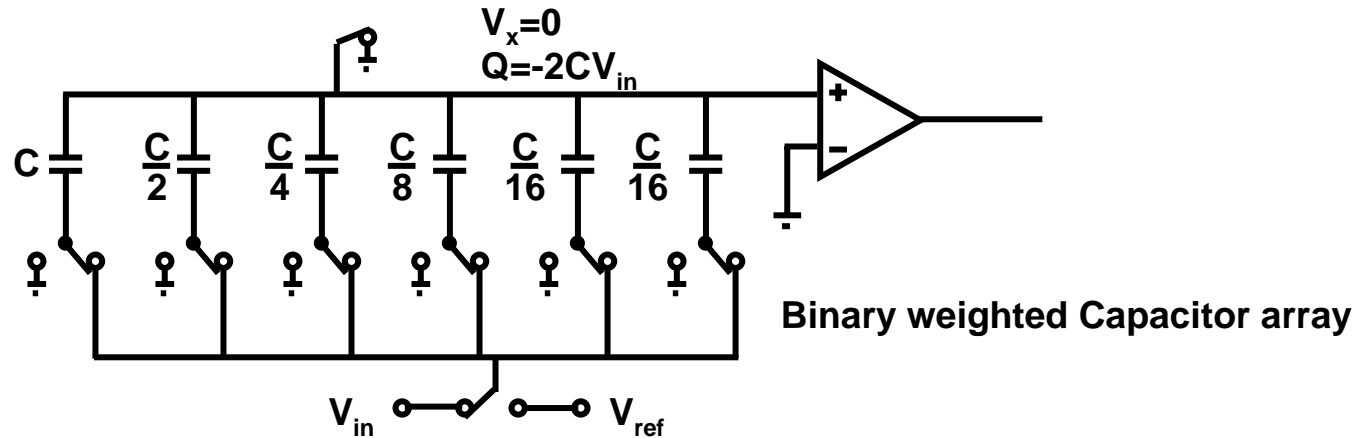


2) Hold

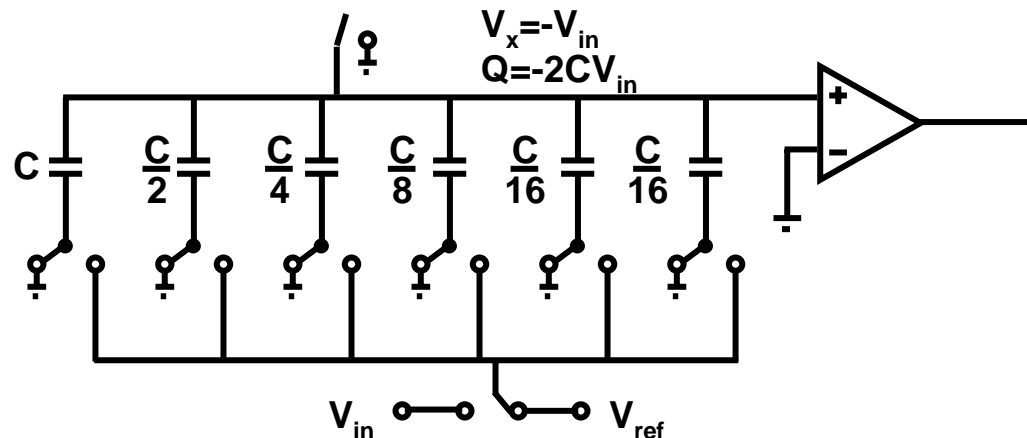


Charge-redistribution ADC

3) Charge redistribution

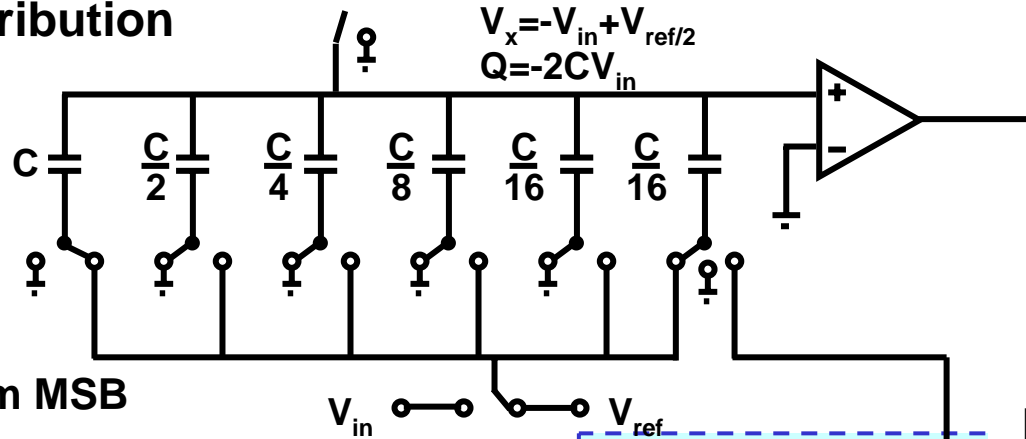

If needed

Resistor ladder for higher resolution

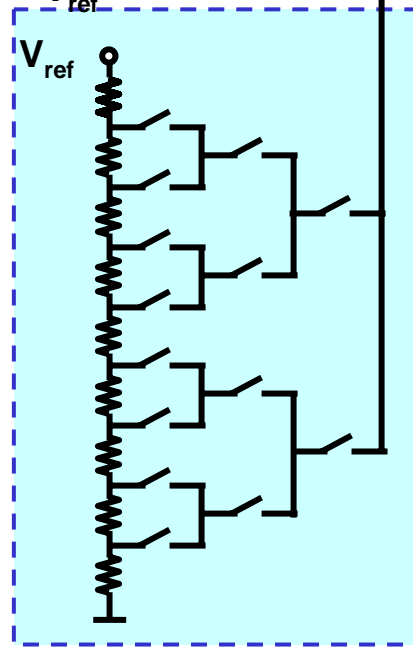

Higher resolution

Easy calibration

Ultra low power

No OP amp



Low conversion rate

Needs multi clock

Flash ADC

Flash ADC is very fast, but area and power increase exponentially with resolution.

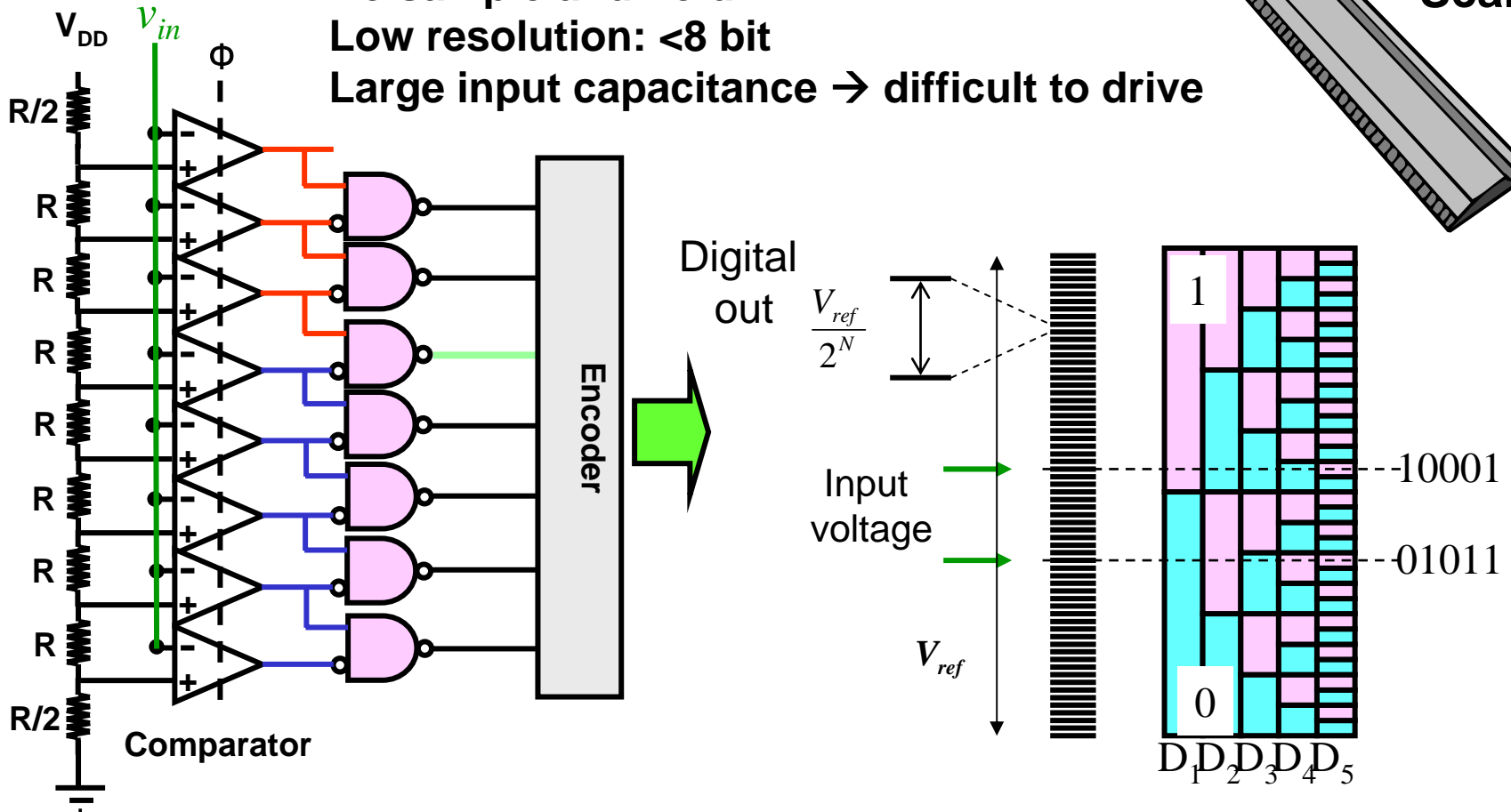 Ultra fast operation: Several GHz
No sample and hold
Low resolution: <8 bit
Large input capacitance → difficult to drive



Sub-ranging ADC



Multi-step conversion can reduce the # of comparators.
 However, it needs high precision comparators.
 As a result, small power and area.

10bits: Flash; $2^N - 1 = 1023$

two step; $2 \left(2^{\frac{N}{2}} - 1 \right) = 62$




Slide gauge

 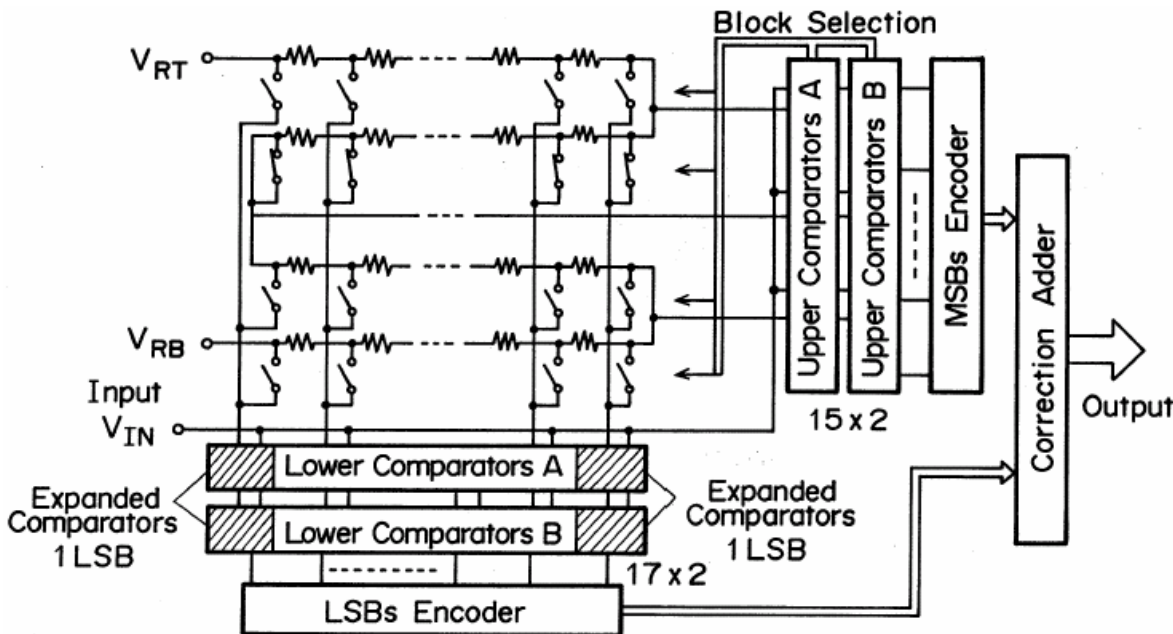


Input voltage

Interpolation method

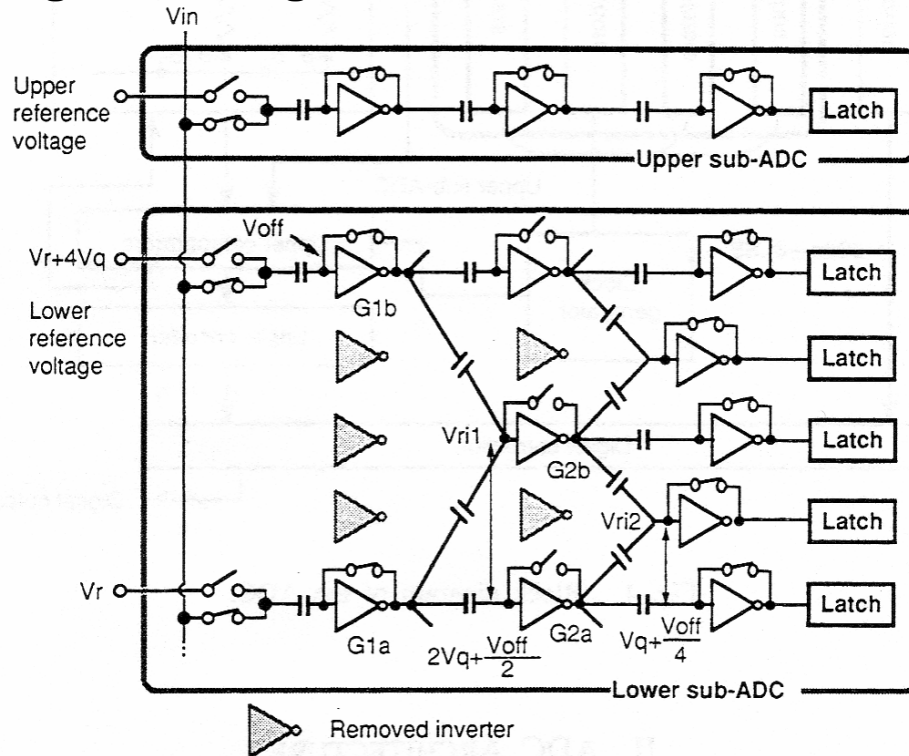Interpolation can generate accurate intermediate references which are between two references. Thus step sizes are almost equal, even though mismatch voltages are large.



 
K. Kusumoto and A. Matsuzawa
JSC, pp. 1200-1206, 1993.



Folding ADC

Input signal is folded to the compressed signals of which phases are different. Lower bits are obtained by comparing between these folded signals.

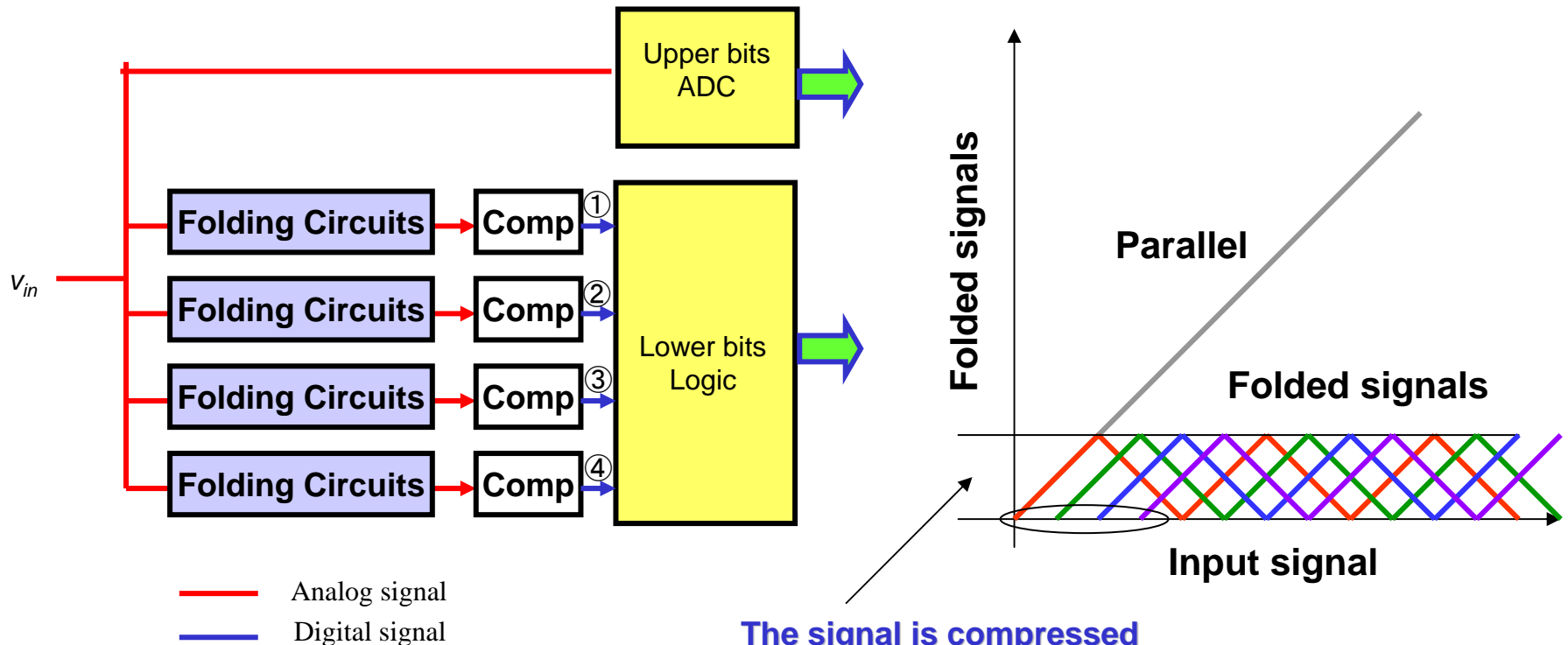
Low power and small size, yet still high speed.
However, not suitable for higher resolution. <10bit



The signal is compressed
→ The # of comparators can be reduced

Folding circuits

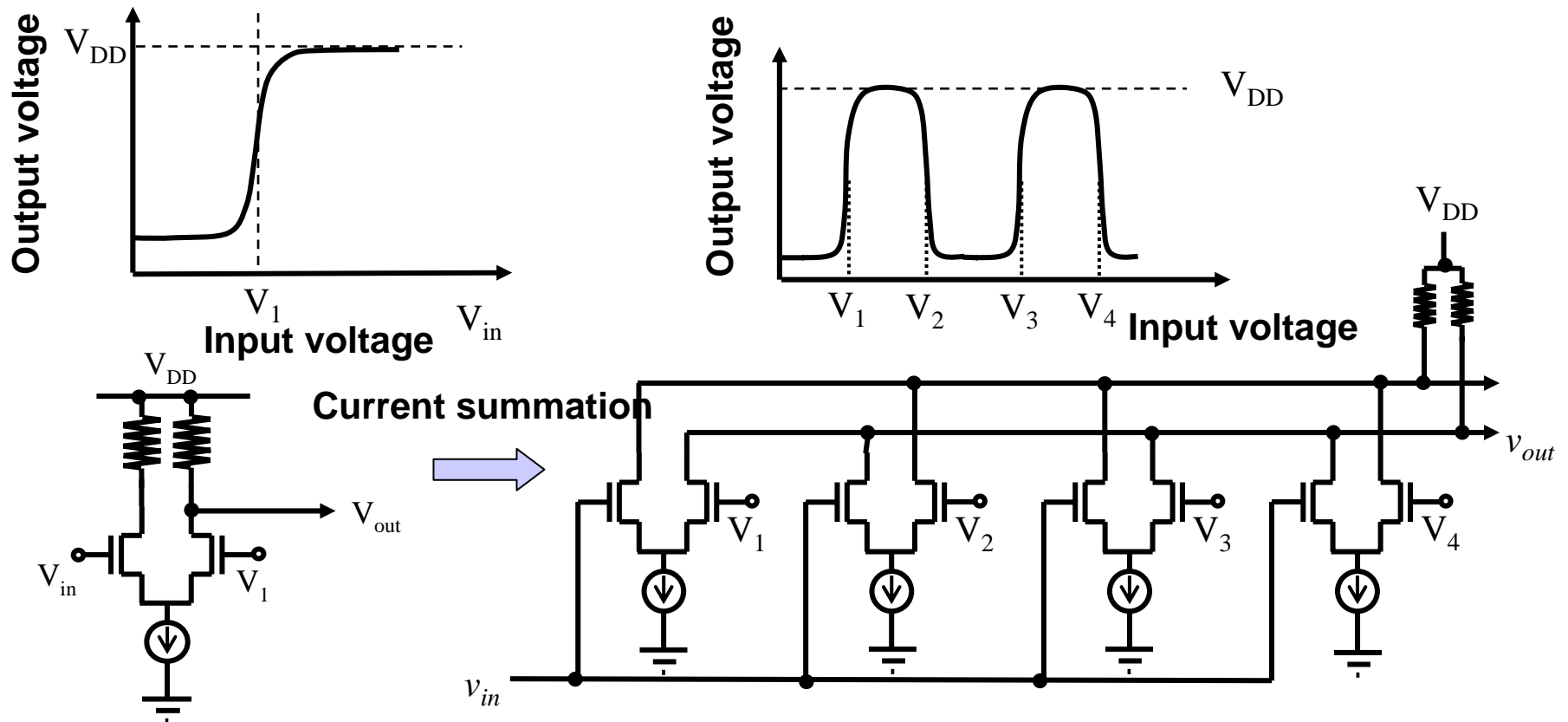Composing the folding characteristics by the summation of currents from differential transistor pairs.



Pipelined ADC

Pipelined ADC is the centerpiece of embedded ADCs for many applications, such as digital cameras, digital TVs, ADSLs, VDSLs, and wireless LANs.



Suitable for CMOS

Switched capacitor operation

High resolution (<15bit)

Moderate speed (<200MHz)


Low power consumption

 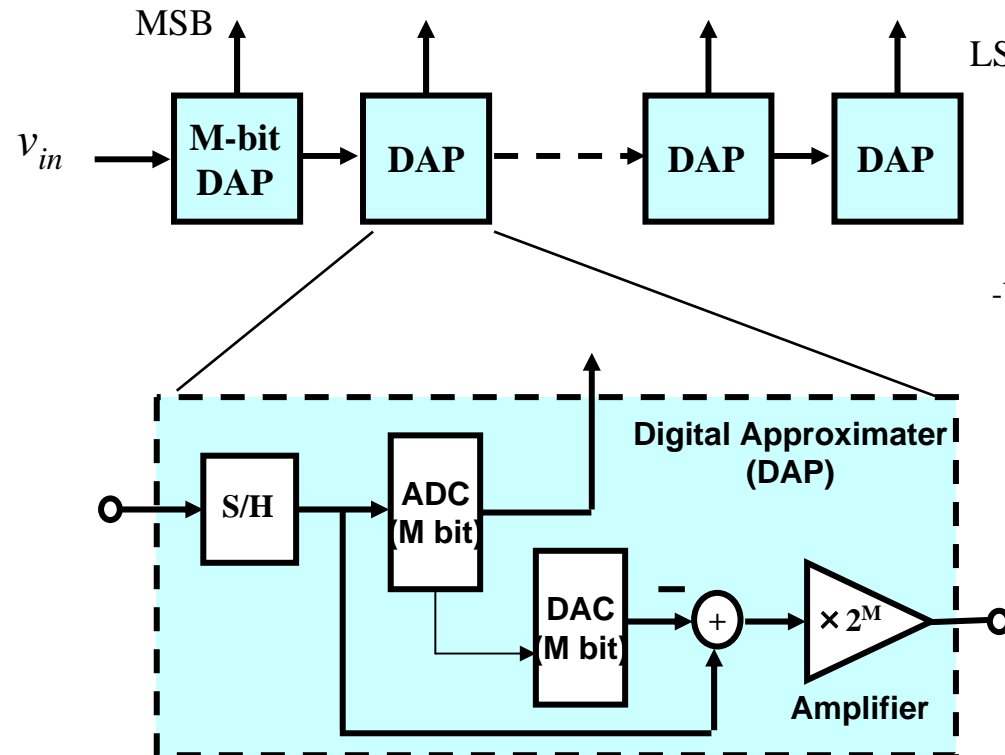


Conventional M is 1 or 1.5

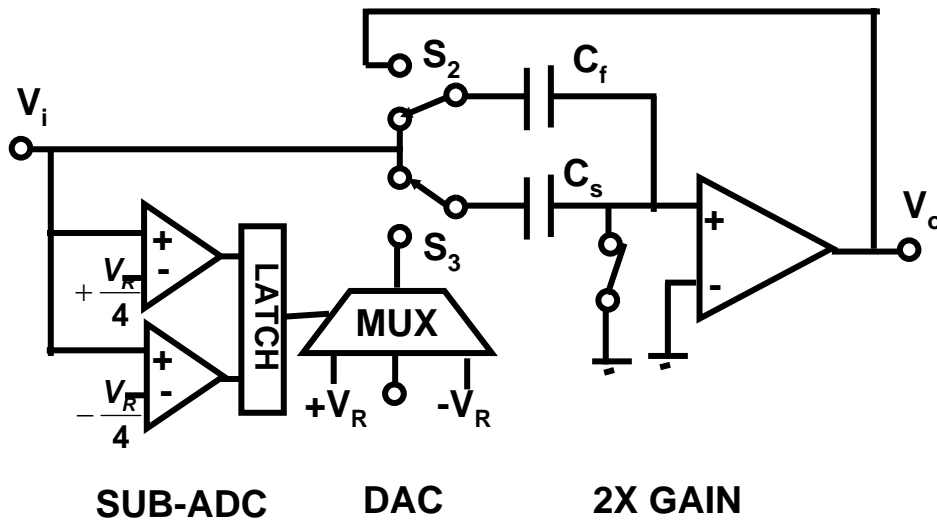1.5-bit/stage Pipeline ADC

Amplification at each stage reduces the input referred thermal noise.
 1.5b/stage architecture reduces the requirement for the comparator offset drastically.



Transfer characteristics

 


Unit conversion stage
 for 1.5-bit/stage pipeline ADC

$$V_o = \begin{cases} \left(1 + \frac{C_s}{C_f}\right) V_i + \frac{C_i}{C_f} V_{ref} & \text{if } V_i < -\frac{V_{ref}}{4} \\ \left(1 + \frac{C_s}{C_f}\right) V_i & \text{if } -\frac{V_{ref}}{4} \leq V_i \leq \frac{V_{ref}}{4} \\ \left(1 + \frac{C_s}{C_f}\right) V_i - \frac{C_i}{C_f} V_{ref} & \text{if } V_i > \frac{V_{ref}}{4} \end{cases}$$

Pipelining

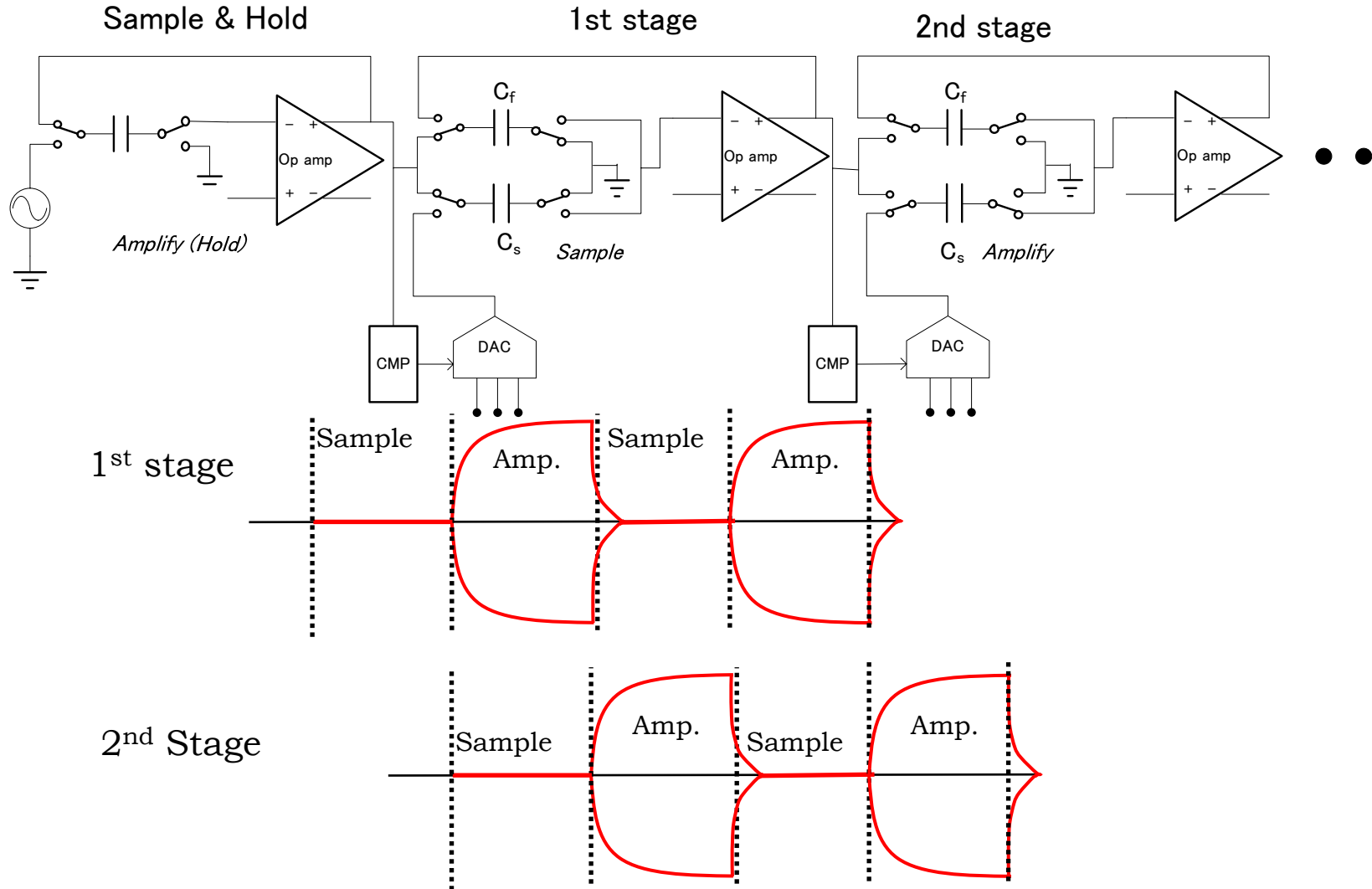Pipeline action relaxes settling time requirement.



4. Overview of high-speed D/A converters


- **Basic two concepts of DAC**
- **Binary method**
 - R-2R based DAC
 - Capacitor array DAC
- **Decoder method**
 - Resistor string DAC
 - Current steering DAC

Basic two concepts of DAC

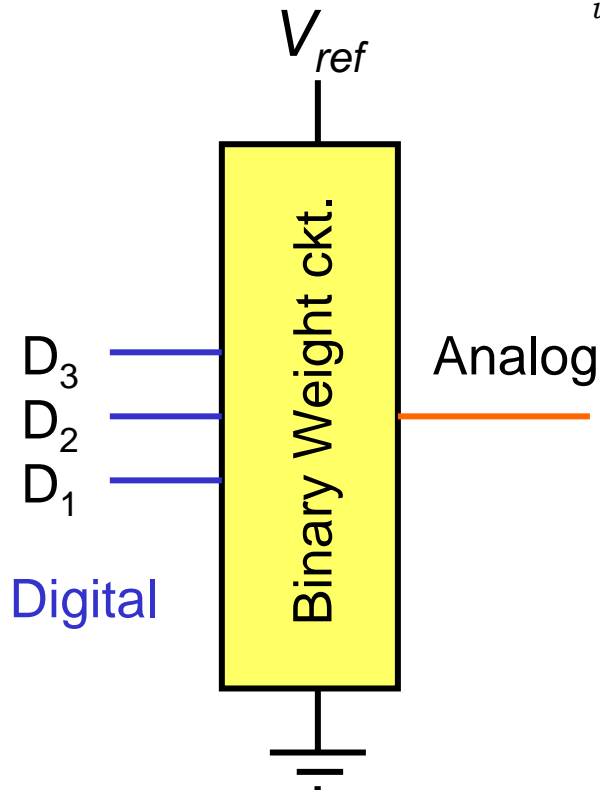1. Binary method

Not small DNL
Large glitch
Small area


$$V_{analg} = V_{ref} \sum_{i=1}^N \frac{1}{2^i} \cdot D_i$$



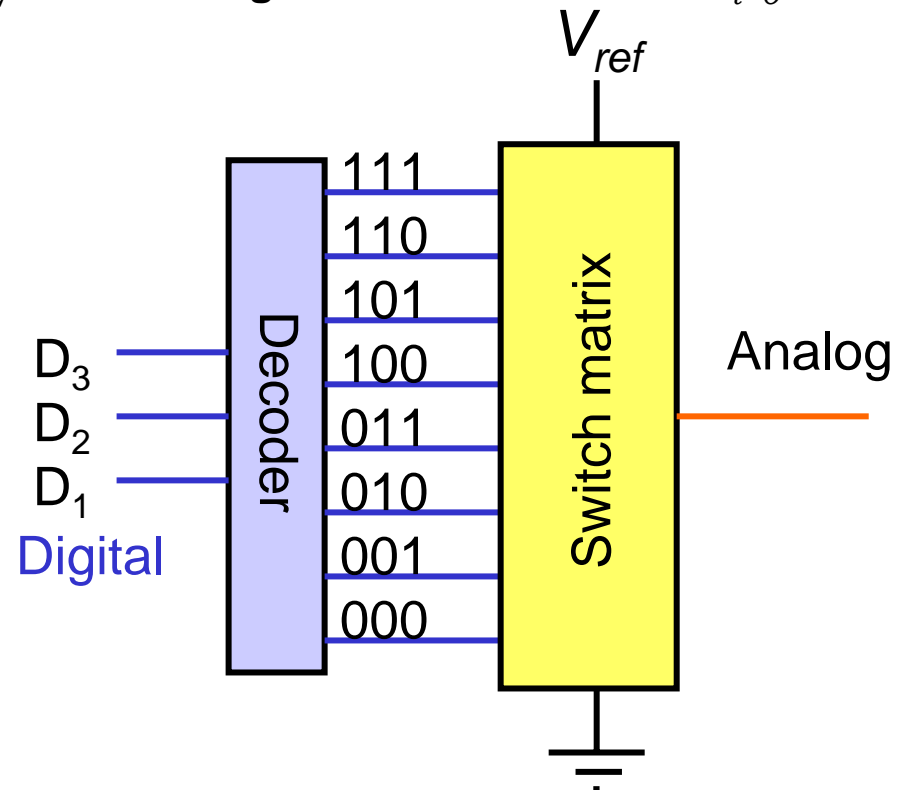2. Decoder method

Small DNL
Small glitch
Large area

$$V_{analg} = V_q \cdot \sum_{i=0}^{N-1} 2^i \cdot D_i$$



R-2R resistor ladder can generate binary weighted current easily.


Resolution: 12b

Large DNL

Small area at high resolution

Moderate speed

Large power consumption

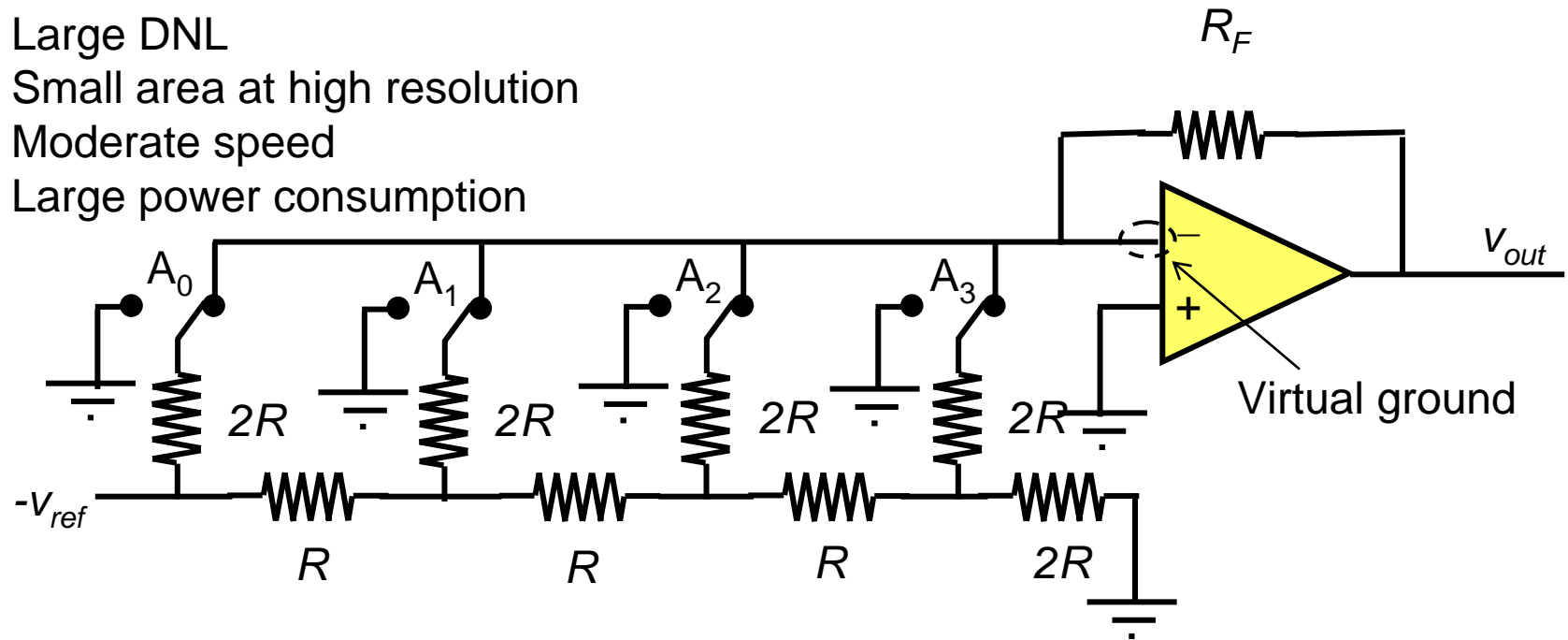

$$v_{out} = R_F \left(I_r \cdot A_0 + \frac{I_r}{2} \cdot A_1 + \frac{I_r}{2^2} \cdot A_1 + \frac{I_r}{2^3} \cdot A_1 \right)$$

$$I_r = \frac{v_{ref}}{2R}$$


Capacitor array DAC

Capacitor array DAC is widely used in CMOS technology.

Low power and no sample & Hold


$$Q = v_{ref} [C \cdot A_0 + 2C \cdot A_1 + 4C \cdot A_2 + 8C \cdot A_3] \quad A_i = 0 \text{ or } 1$$

$$v_{out} = -\frac{Q}{16C}$$

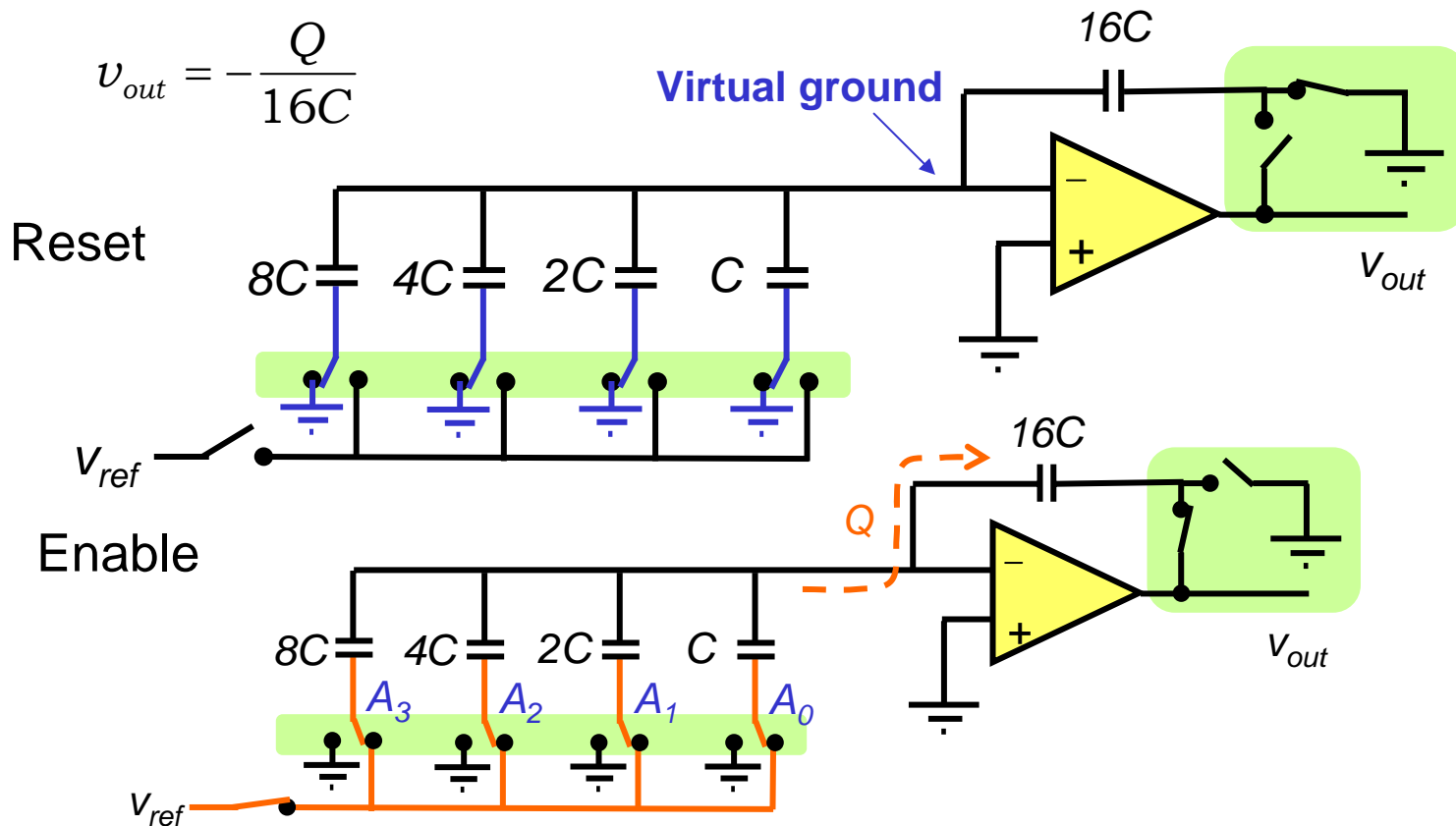

Resistor string DAC

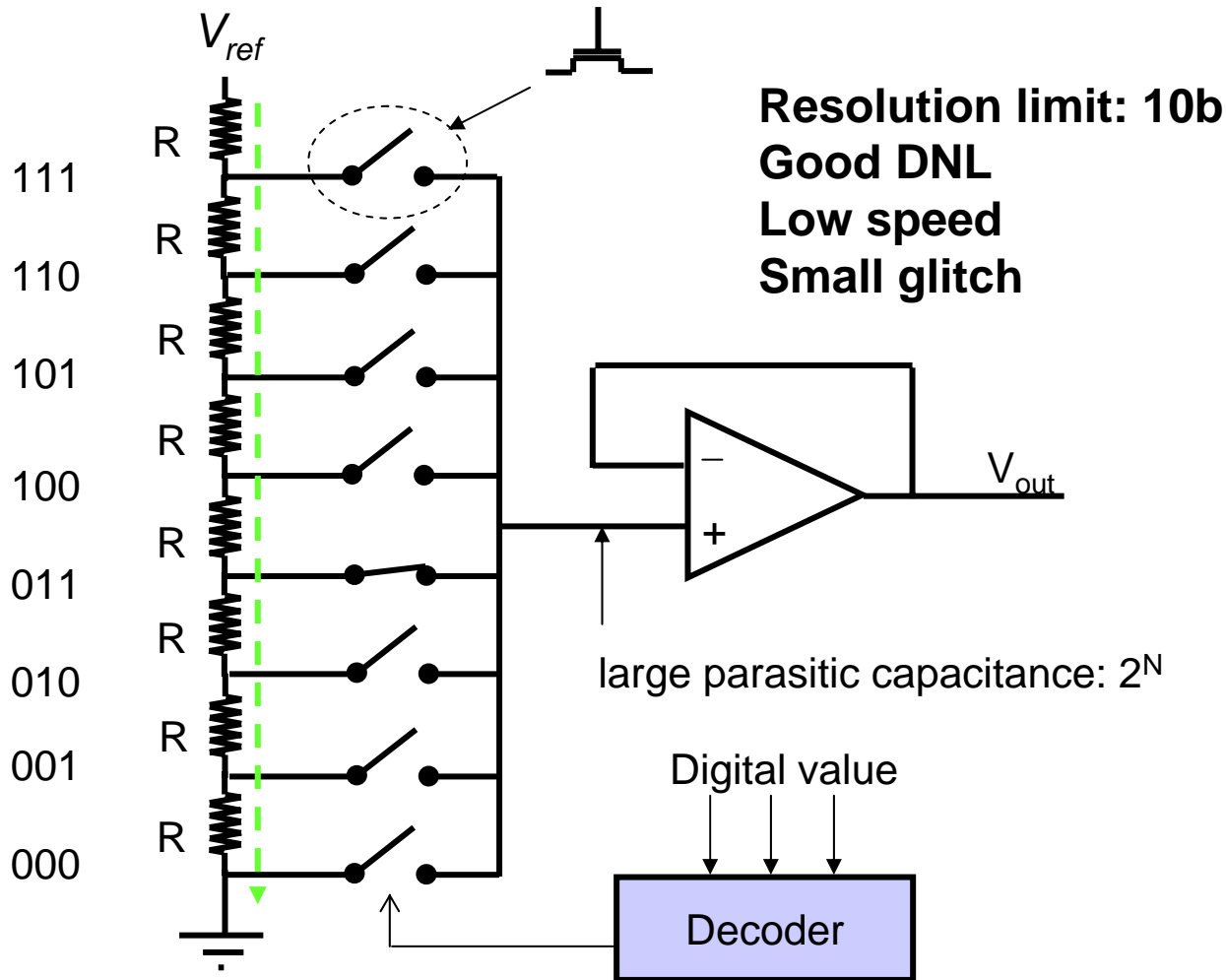Decoder method can realize small DNL, however needs large area at high resolution.




Current steering DAC



Widely used for high speed DAC. Graphics, communications, etc.

High speed, -- 1 GHz
 Resolution – 14 b
 Small DNL
 Small glitch

Conventionally large area

 

Current cell with switch

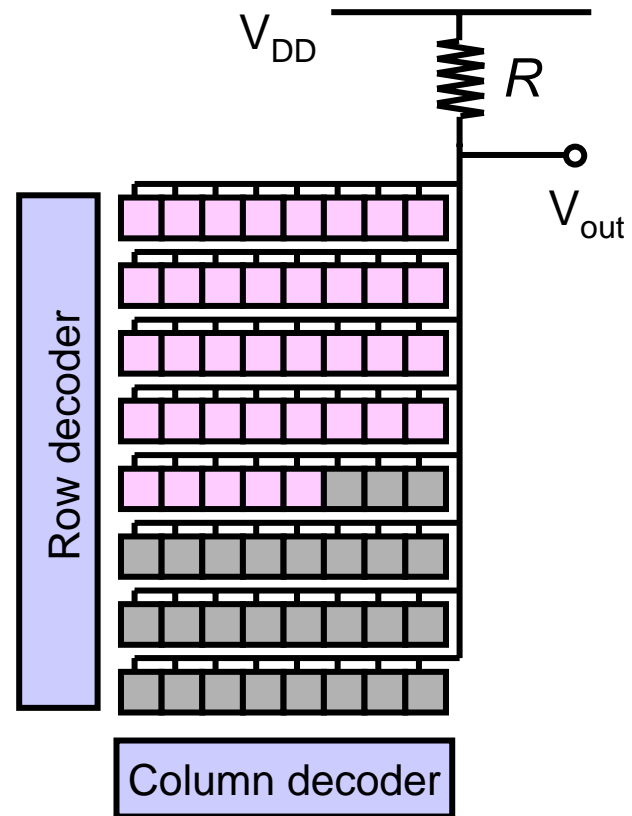 


5. Overview of over-sampling sigma-delta data converters

- **Sigma-delta modulation method**
 - Over sampling
 - Noise shaping
 - Sigma-delta modulator
 - SNR
 - Higher order system
 - Feed forward and feed back compensation
 - MASH (Multi-stage noise shaping)



Sigma-delta ADC, DAC

Sigma delta ADC and DAC are widely used in high resolution (14b-24b) and not high speed (<1MHz) applications.

Sigma delta ADC

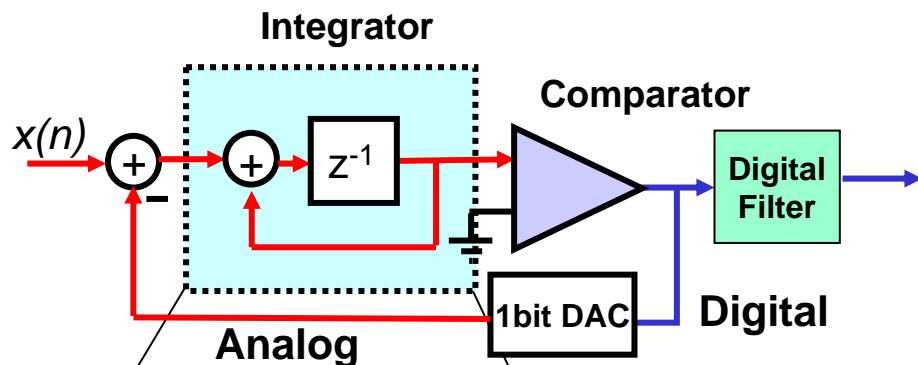


Sigma delta DAC

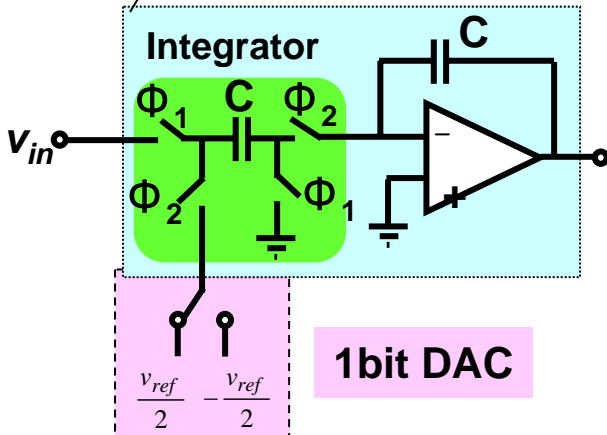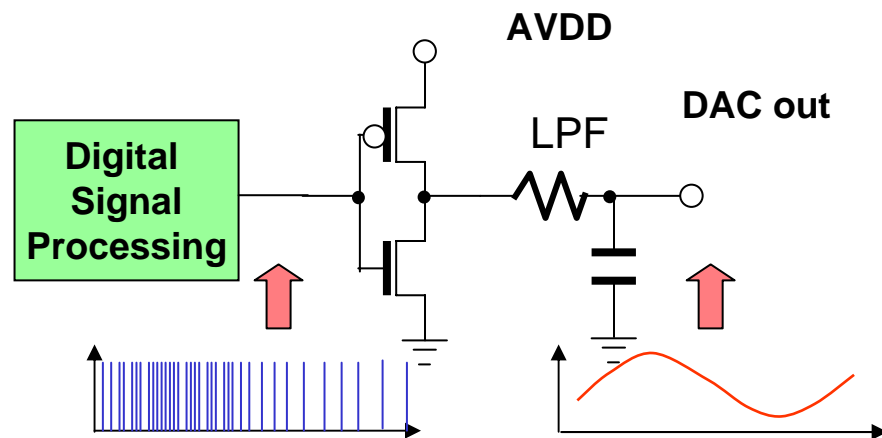

Implemented in CMOS, easily.


Over sampling

 Over sampling can reduce effective quantization noise.



Quantization noise power


$$P_e = \int_{-f_s/2}^{f_s/2} S_e^2(f) |H(f)|^2 df = \int_{-f_b}^{f_b} \frac{\Delta^2}{12} \cdot \frac{1}{f_s} df = \frac{\Delta^2}{12} \cdot \left(\frac{2f_b}{f_s} \right) = \frac{\Delta^2}{12} \cdot \frac{1}{OSR} \quad OSR \equiv \frac{f_s}{2f_b}$$

 

Reduction of bandwidth by filter → Reduction of effective noise power

Noise shaping

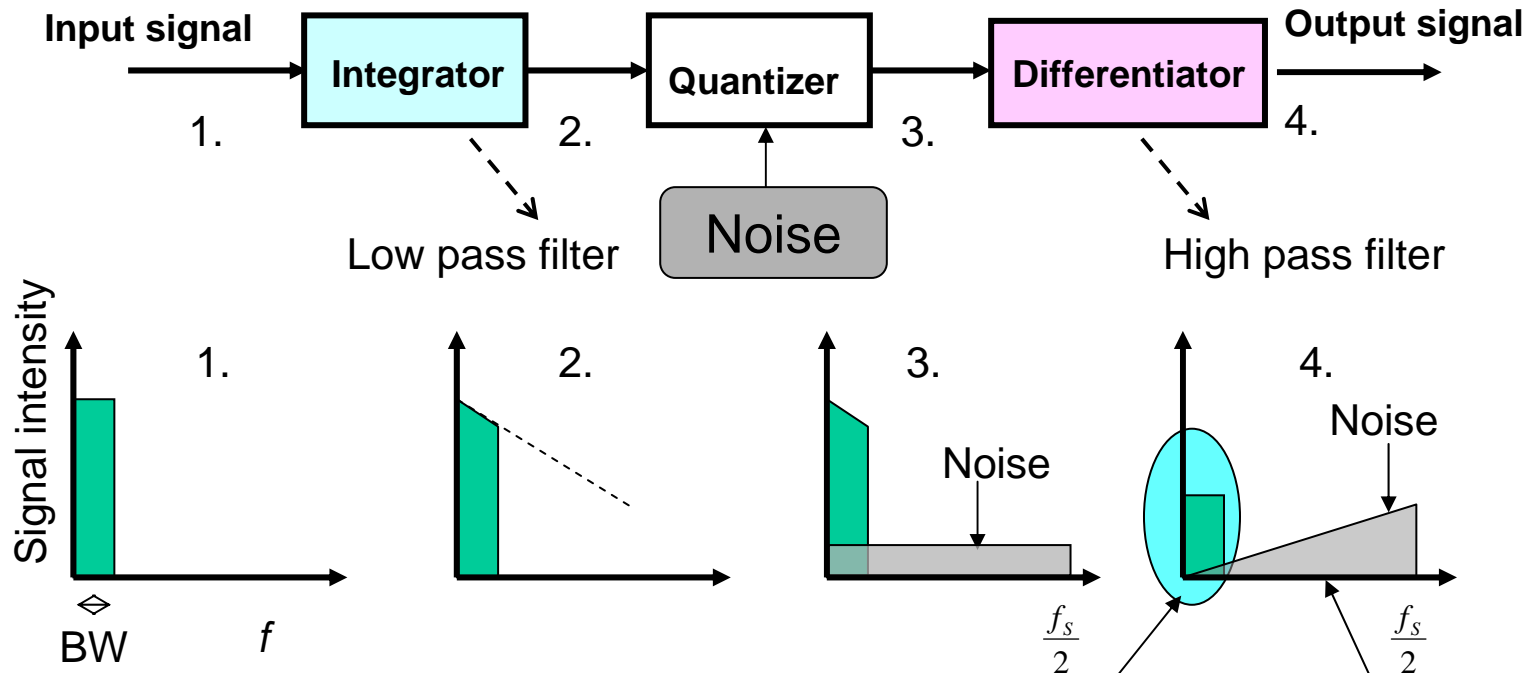Spectrum of quantization noise is shaped by differentiator.
In-band noise can be reduced.



Signal: Low pass filter x High pass filter \rightarrow Flat

In-band noise is reduced

Quantization noise: High pass filter \rightarrow Lower in low frequency


The spectrum of the quantization noise increases with frequency increase.

Only quantization noise is shaped in frequency characteristics

Sigma-delta modulator

Sigma-delta modulator shapes the frequency characteristics of the quantization noise


The signal will overflow

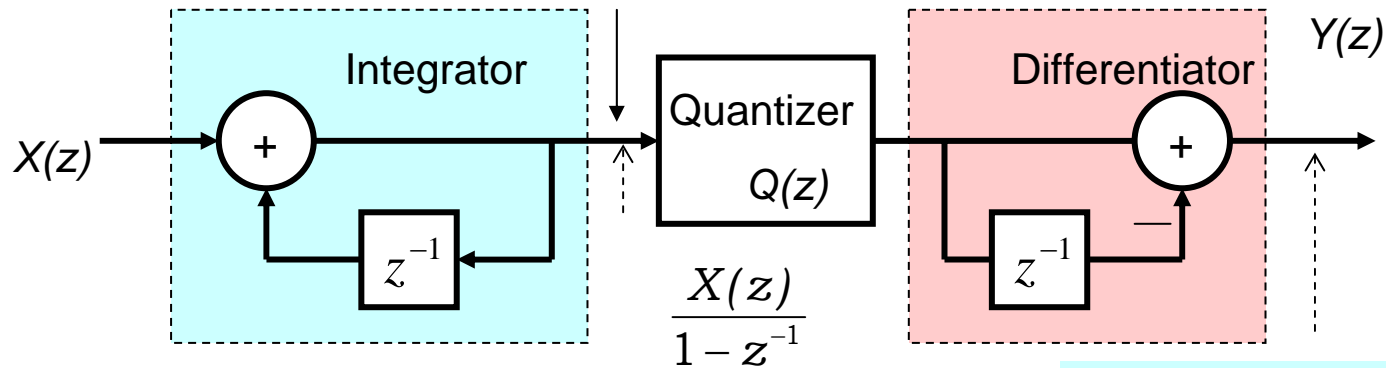

$$\frac{X(z)}{1 - z^{-1}}$$

$$Y(z) = X(z) + (1 - z^{-1})Q(z)$$

Equivalent transform

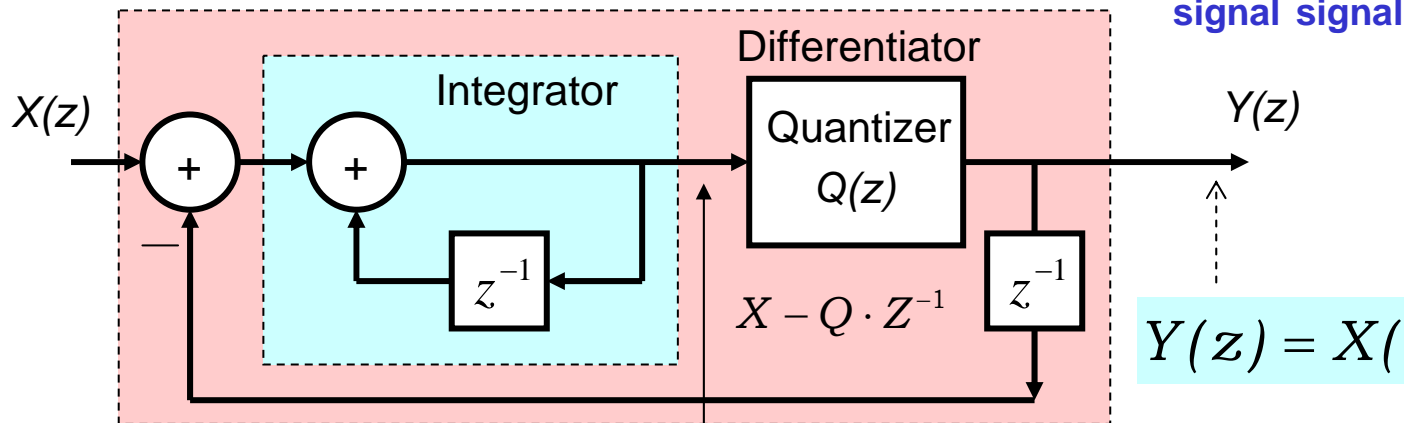

Output Input
signal signal

Quantization
noise


Differentiator
(High pass filter)

$$Y(z) = X(z) + (1 - z^{-1})Q(z)$$

No overflow

Generic expression of sigma-delta modulator

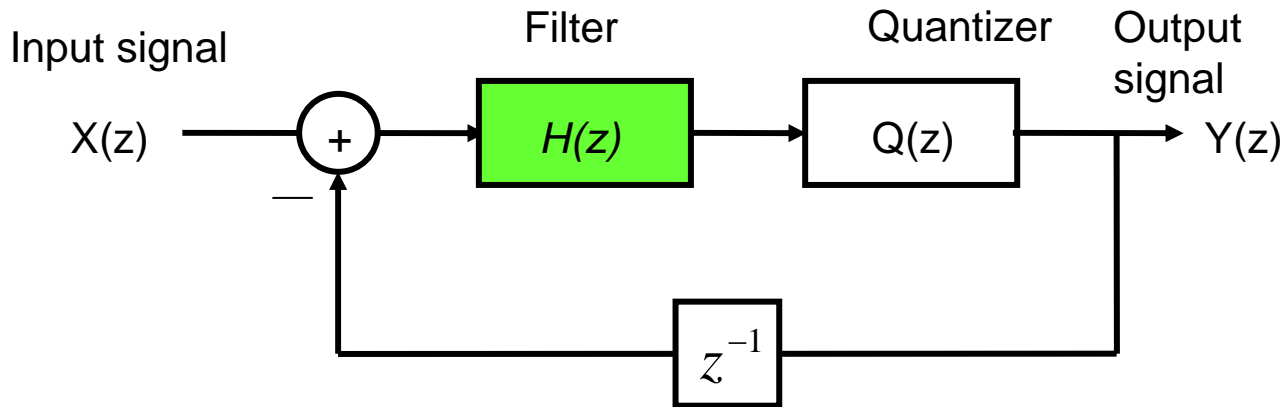We can use not only LPF but also BPF and complex BPF.
This gives us an excellent opportunity for wireless applications.



$$Y(z) = \frac{H(z)}{1 + H(z)z^{-1}} X(z) + \frac{1}{1 + H(z)z^{-1}} Q(z)$$

STF (Signal Transfer)

NTF (Noise transfer)

Ex.

$$H(z) = \frac{1}{1 - z^{-1}} \quad STF(z) = 1, \quad NTF(z) = \underline{1 - z^{-1}}$$

No filter

High pass filter

Noise power in sigma-delta modulator


L^{th} order filter

$$Y(z) = X(z) + (1 - z^{-1})^L Q(z)$$



$$h_q^2(f) = \frac{\Delta^2}{12f_s}$$

$$N_q = \int_{-f_b}^{+f_b} h_q^2(f) |1 - z^{-1}|_{z=e^{j2\pi f/f_s}}^{2L} df$$

$$\approx \int_{-f_b}^{+f_b} \frac{\Delta^2}{12f_s} \left| \frac{j2\pi f}{f_s} \right|^{2L} df = \left(\frac{\Delta}{2} \right)^2 \frac{1}{3\pi(2L+1)} \left(\frac{\pi}{OSR} \right)^{2L+1}$$

 


2nd order sigma-delta ADC

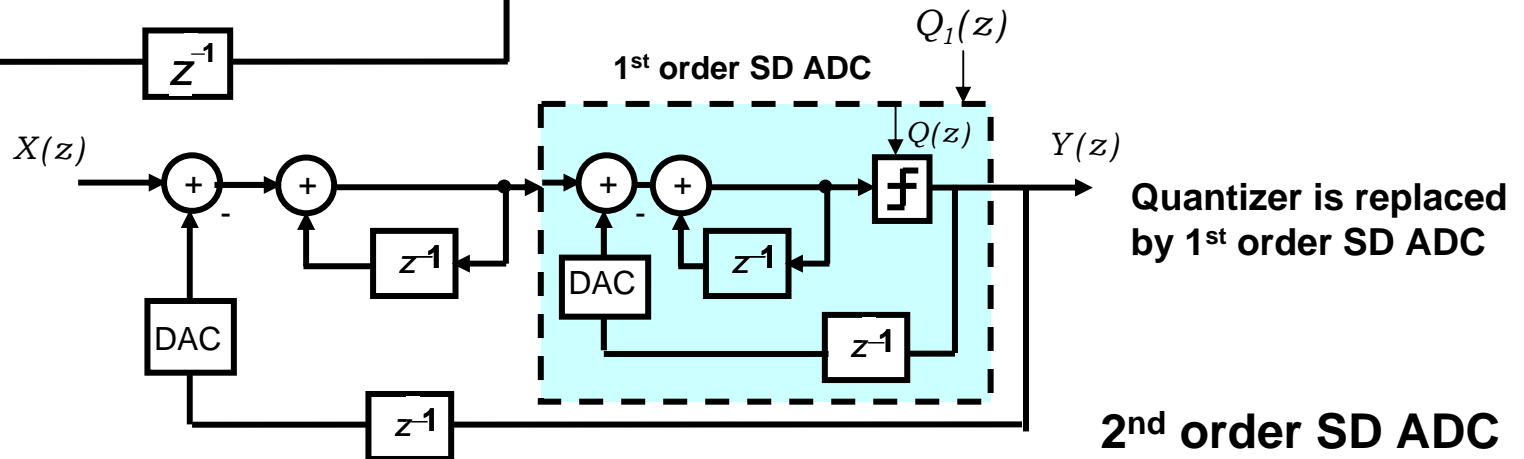 


$$Y(z) = X(z) + (1 - z^{-1})Q_1(z)$$

$$Q_1(z) = (1 - z^{-1})Q(z)$$


$$Y(z) = X(z) + (1 - z^{-1})^2 Q(z)$$

 

Multi bit sigma-delta ADC

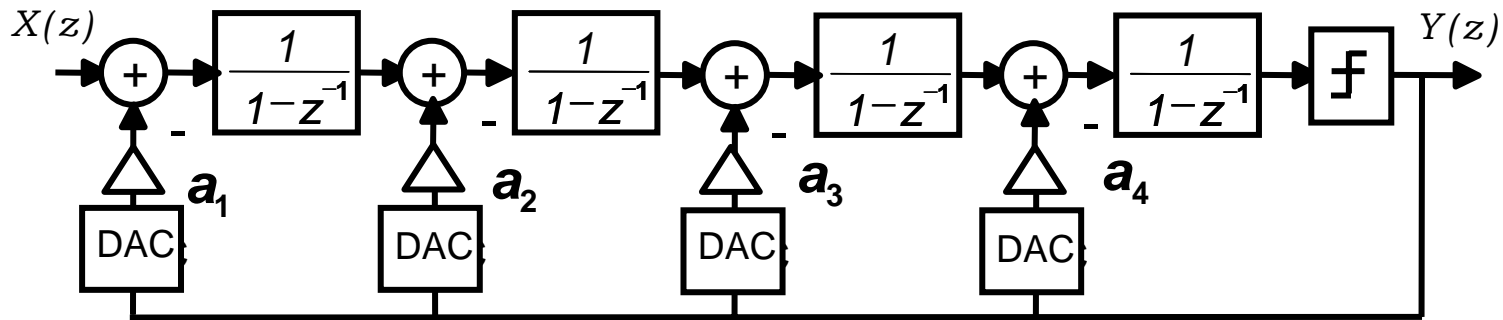

Feedback type

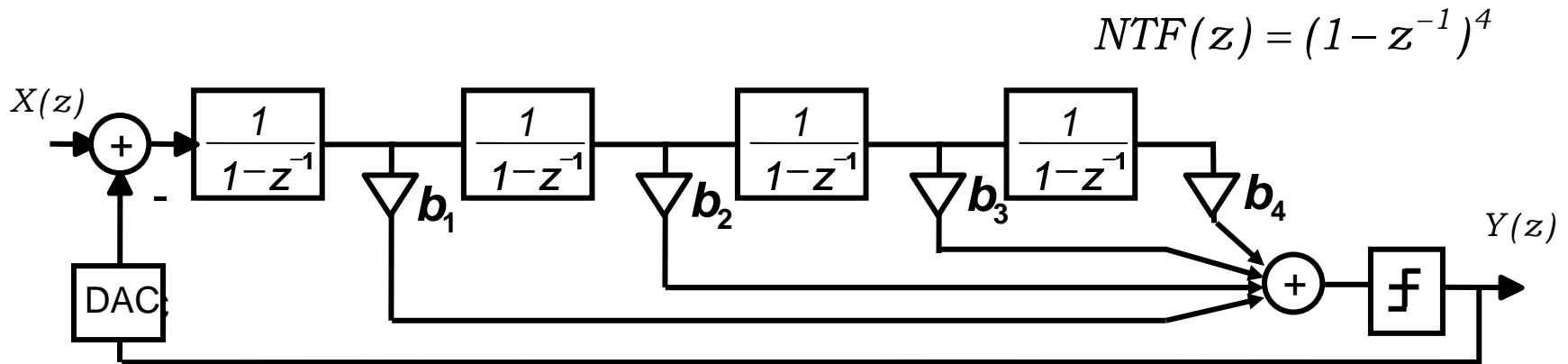


$$NTF(z) = (1 - z^{-1})^4$$

Feedforward type

Dynamic range of sigma-delta ADC



Higher order SD modulator seems effective to increase the dynamic range. However it is not easy, because of instability, signal saturation, and thermal noise.
 
$$DR = \frac{3\pi}{2} (2^N - 1)^2 (2L + 1) \left(\frac{OSR}{\pi} \right)^{2L+1}$$




Noise-shaping characteristics

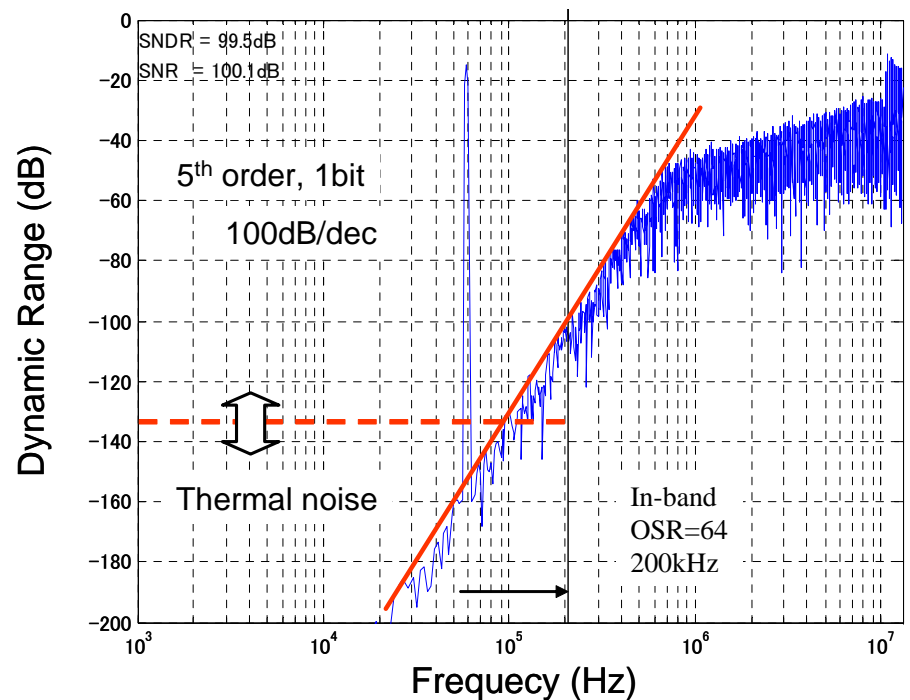 Higher order sigma-delta modulator can realize higher dynamic range, theoretically



Cascade (MASH) sigma-delta modulator

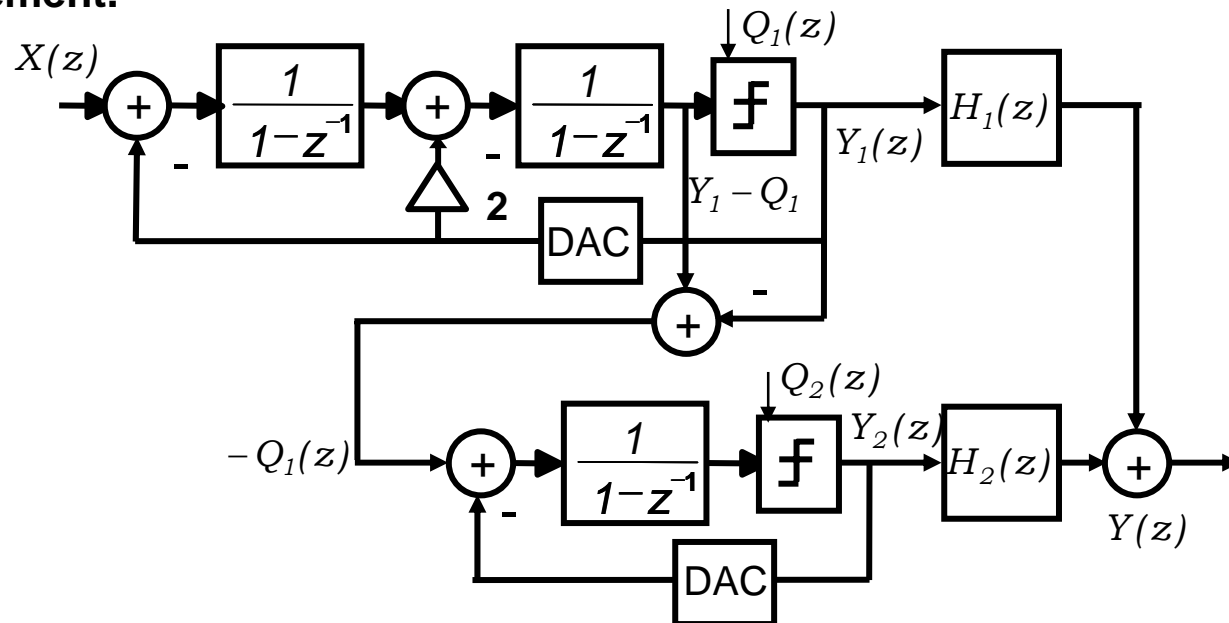Cascaded SD modulator can realize higher order noise shaping without stability issues. However, high dynamic range is difficult, due to severe mismatch requirement.



$$Y_1(z) = X(z) + (1 - z^{-1})^2 Q_1(z) \quad H_1(z) = 1$$

$$Y_2(z) = -Q_1(z) + (1 - z^{-1}) Q_2(z) \quad H_2(z) = (1 - z^{-1})^2$$

$$Y(z) = Y_1 H_1 + Y_2 H_2 = X(z) + (1 - z^{-1})^2 Q_1(z) - (1 - z^{-1})^2 Q_1(z) + (1 - z^{-1})^3 Q_2(z)$$


$$Y(z) = X(z) + (1 - z^{-1})^3 Q_2(z)$$

6. Basic design considerations

- **Accuracy**
 - Current mismatch and DAC accuracy
 - V_T mismatch
 - Capacitor mismatch
- **Comparator**
 - Offset compensation
- **Op-Amp**
 - Gain and GBW
 - kT/C noise

Current mismatch and DAC accuracy

 Larger resolution requires smaller mismatch.




$$\frac{\sigma(I)}{I} \approx \frac{1}{2C\sqrt{2^N}}$$

N: resolution


C: constant determined by INL yield

 - sigma (3.0, N)
- sigma (2, N)
- sigma (1.3, N)
- sigma (0.8, N)



V_T mismatch

 Larger gate area is needed for smaller V_T mismatch.
Technology scaling reduces V_T mismatch if the gate area is equal.



Mismatch current and transistor size

Smaller mismatch requires larger L and W.

$$I_{ds} = K' \frac{W}{L} (V_{gs} - V_T)^2$$

$$\Delta I_{ds} = \frac{\partial I_{ds}}{\partial V_T} \Delta V_T + \frac{\partial I_{ds}}{\partial K'} \Delta K' + \frac{\partial I_{ds}}{\partial \left(\frac{W}{L}\right)} \Delta \left(\frac{W}{L}\right)$$

$$\frac{\Delta I_{ds}}{I_{ds}} = \frac{-2 \Delta V_T}{V_{gs} - V_T} + \frac{\Delta K'}{K'} + \frac{\Delta \left(\frac{W}{L}\right)}{\left(\frac{W}{L}\right)}$$

$$\left(\frac{\Delta I_{ds}}{I_{ds}}\right)^2 = \frac{4K' A_{VT}^2}{L^2 I_{ds}} + \frac{A_K^2}{WL} + A_{WL}^2 \left(\frac{1}{W^2} + \frac{1}{L^2}\right)^2$$

Mismatch

$$\Delta V_T \approx \frac{A_{VT}}{\sqrt{LW}}$$

$$\frac{\Delta K'}{K'} \approx \frac{A_{K'}}{\sqrt{LW}}$$

$$\frac{\Delta \left(\frac{W}{L}\right)}{\left(\frac{W}{L}\right)} = A_{WL} \sqrt{\frac{1}{W^2} + \frac{1}{L^2}}$$


$$V_{gs} - V_T = \sqrt{\frac{I_{ds}}{K' \left(\frac{W}{L}\right)}}$$

Capacitor mismatch

Smaller capacitor mismatch requires larger capacitance


$$\frac{\Delta C}{C}(3\sigma) = \frac{6 \times 10^{-4}}{\sqrt{C(\text{pF})}}$$

Coefficient depends Fab.

 


CMOS comparators

 
There are many types of comparator circuits




(a)

 

(c)

 

(b)

 


(d)

Low power CMOS comparators

CMOS comparator are low power because of the lack of static current.

No static current
 Differential comparison
 Interpolation action
 High speed

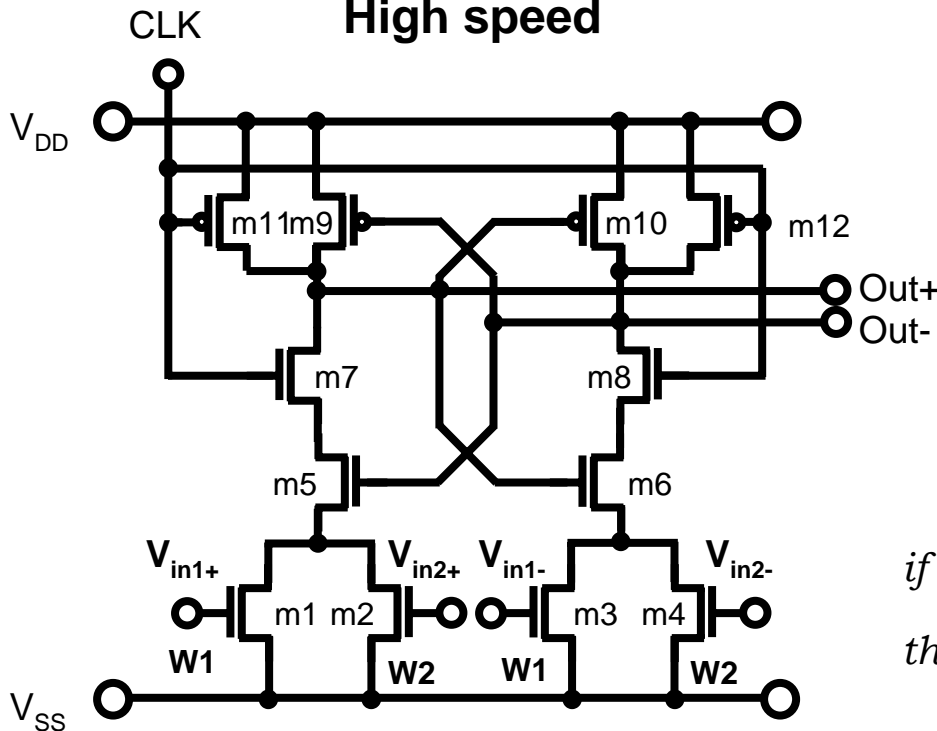T.B.Cho., et al., J.S.C., Vol.30,
 No.30, pp.166-172, Mar. 1995.



Interpolation action

$$G_1 = K_p \left[\frac{W_1}{L} (V_{in1+} - V_{th}) + \frac{W_2}{L} (V_{in2+} - V_{th}) \right]$$

$$G_2 = K_p \left[\frac{W_1}{L} (V_{in1-} - V_{th}) + \frac{W_2}{L} (V_{in2-} - V_{th}) \right]$$

$$\text{if } W_1 : W_2 = \frac{m-n}{m} : \frac{n}{m}$$

$$\text{then, } (m-n)V_{in1+} + nV_{in2+} = (m-n)V_{in1-} + nV_{in2-}$$



Design rule and Speed in Comparator

Gain bandwidth (=Speed) is inversely proportional to the L^2 (channel length).
Technology scaling is still effective in increasing the comparator speed,
if we are not concerned with the signal's dynamic range.

$$GBW = \frac{g_m}{2\pi \left(WC_j + \frac{2}{3} C_{ox} LW \right)} = \frac{I_{sink}}{2\pi \left(WC_j + \frac{2}{3} C_{ox} LW \right) V_{eff}}$$

$$I_{sink} = \frac{\mu C_{ox}}{2} \frac{W}{L} V_{eff}^2 \quad C_{ox} = \frac{\kappa}{L}$$

  
$$GBW = \frac{\mu V_{eff}}{2\pi L^2 \left(\frac{2}{3} + \frac{C_j}{k} \right)}$$



Offset compensation

Two ways for suppressing offset voltage.

 Store the offset voltage in capacitors and subtract it from the signal.



Feedback= High gain type


$$(V_a - V_{osA})(-A) = V_o = V_a$$

$$\therefore V_o = V_a = \frac{A}{1 + A} V_{osA}$$

V_{osA} : Offset of the amplifier

V_{osL} : Offset of the latch

a) Offset cancel at input nodes

 

Feed forward =Low gain type

$$V_{os_in} = \frac{V_{osl}}{A}$$


b) Offset cancel at output nodes

Operational amplifier


Higher resolution requires higher open loop gain.

Higher conversion frequency requires higher closed loop GBW.


Sampling

 

Amplify

 

Equivalent circuit

 

DC gain

$$G_{error} \approx -\frac{1}{G} \left(2 + \frac{C_p}{C_f} \right) \approx -\frac{1}{G\beta} \quad \beta \equiv \frac{1}{\left(2 + \frac{C_p}{C_f} \right)}$$

$$\frac{1}{G} \leq \frac{\beta}{2^{N-M+1}}$$

N: ADC resolution
M: Stage resolution

$$G (dB) > 6N + 10 \quad \text{for 1.5b pipeline ADC}$$

Closed loop gain-bandwidth



$$GBW_{close} = \frac{g_m \beta}{2\pi C_L} > \frac{N \cdot fc}{3}$$

$$\beta = \frac{C_f}{C_f + C_s + C_{pi}}$$

$$C_L = C_{po} + C_{oL} + \frac{C_f (C_s + C_{pi})}{C_f + C_s + C_{pi}}$$

kT/C noise

  
Larger SNR requires larger capacitance and larger signal swing.
Low signal swing increases required capacitance.



$$\langle v_n^2 \rangle = 4kTR \int \frac{1}{1 + (\omega CR)^2} \frac{d\omega}{2\pi} = \frac{kT}{C}$$

$$v_n^2 = \frac{nkT}{C} \quad n: \text{configuration coefficient}$$
 
$$SNR(dB) = 10 \log \left(\frac{CV_{FS}^2}{8nkT} \right)$$



Basic design consideration

Very tough tradeoffs, so let's keep up the design effort.

Small mismatch

$$\frac{\Delta C}{C} \text{ or } \frac{\Delta V_{\text{off}}}{V_{\text{FS}}} \propto \frac{1}{2^N}$$

Increase Capacitance

$$\frac{\Delta C}{C} \propto \frac{1}{\sqrt{C}} \text{ or } \Delta V_{\text{off}} \propto \frac{1}{\sqrt{LW}} \propto \frac{1}{\sqrt{C_g}}$$

$$C \propto 2^{2N} \text{ Results in}$$

Decrease speed and Increase Power

$$f_s \propto GBW \propto \frac{g_m}{C} \propto \frac{g_m}{2^{2N}} \quad GBW \propto \frac{I_d}{C} \propto \frac{I_d}{2^{2N}}$$

$$P_d \propto V_d I_d \propto f_s \cdot C \propto f_s \cdot 2^{2N}$$

$$f_s \propto \frac{I_d}{2^{2N}}$$

$$P_d \propto f_s \cdot 2^{2N}$$

Solutions

- 1) Architecture
Pipeline, Parallel
- 2) Redundancy
- 3) Error compensation
- 4) Circuit design

However, kT/C issue remains

$$SNR \propto CV_{\text{sig}}^2 \propto 2^{2N}$$

$$C \propto \left(\frac{2^N}{V_{\text{sig}}} \right)^2$$

Solutions

- 1) Increase signal swing
- 2) Increase OSR

$$SNR \propto OSR$$

Acknowledgement

- **The author thanks Mr. T. Matsuura from Renesas for some slides provision.**

Study-aid books

- **B. Razavi, “Data conversion system design,” IEEE press.**
- **P. E. Allen and D. R. Holberg, “ CMOS Analog Circuit Design,” 2nd Edition, OXFORD University Press.**
- **D. A. Johns and K. Martin, “Analog integrated circuit design,” John Wiley & Sons.**
- **R. J. Baker, “ CMOS mixed-signal circuit design,” IEEE Press.**
- **R.van de Plassche, “CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters,” 2nd Edition, Kluwer Academic Publishers.**
- **M. Gustavsson, J. J. Wikner and N. N. Tan, “CMOS data converters for communications,” Kluwer Academic Publishers.**
- **C. Shi and M. Ismail, ”Data converters for wireless standards,” Kluwer Academic Publishers.**
- **A. Rodriguez-Vazquez, F. Mederio, and E. Janssens, “CMOS Telecom Data Converters,” Kluwer Academic Publishers.**