

Current status and future prospect of analog and RF VLSI design

Akira Matsuzawa

Tokyo Institute of Technology

O-Okayama, Meguro-ku, Tokyo 152-8552, Japan


- **RF IC design**
 - 60GHz CMOS transceiver
 - Essence of millimeter wave IC design
- **ADC design**
 - Flash ADC with dynamic comparator
 - SAR ADC with dynamic comparator
 - Interpolated pipeline ADC
- **Discussion and summary**

RF IC design

60GHz CMOS transceiver

Usage model

 **Giga bit ultra-fast data transfer systems around 60GHz.
4 ch. 1.8GHz BW provides 3.5—7.0 Gbps data transfer.
Low power and small size are required**



Kiosk download



BW: 1.8GHz, 4 channels

IEEE 802.15.3c



Equipment image

Two chips solution on one PCB with antenna

Low cost system

  


Gain: 5.6 dBi

  

60GHz Transceiver: Block Diagram


6

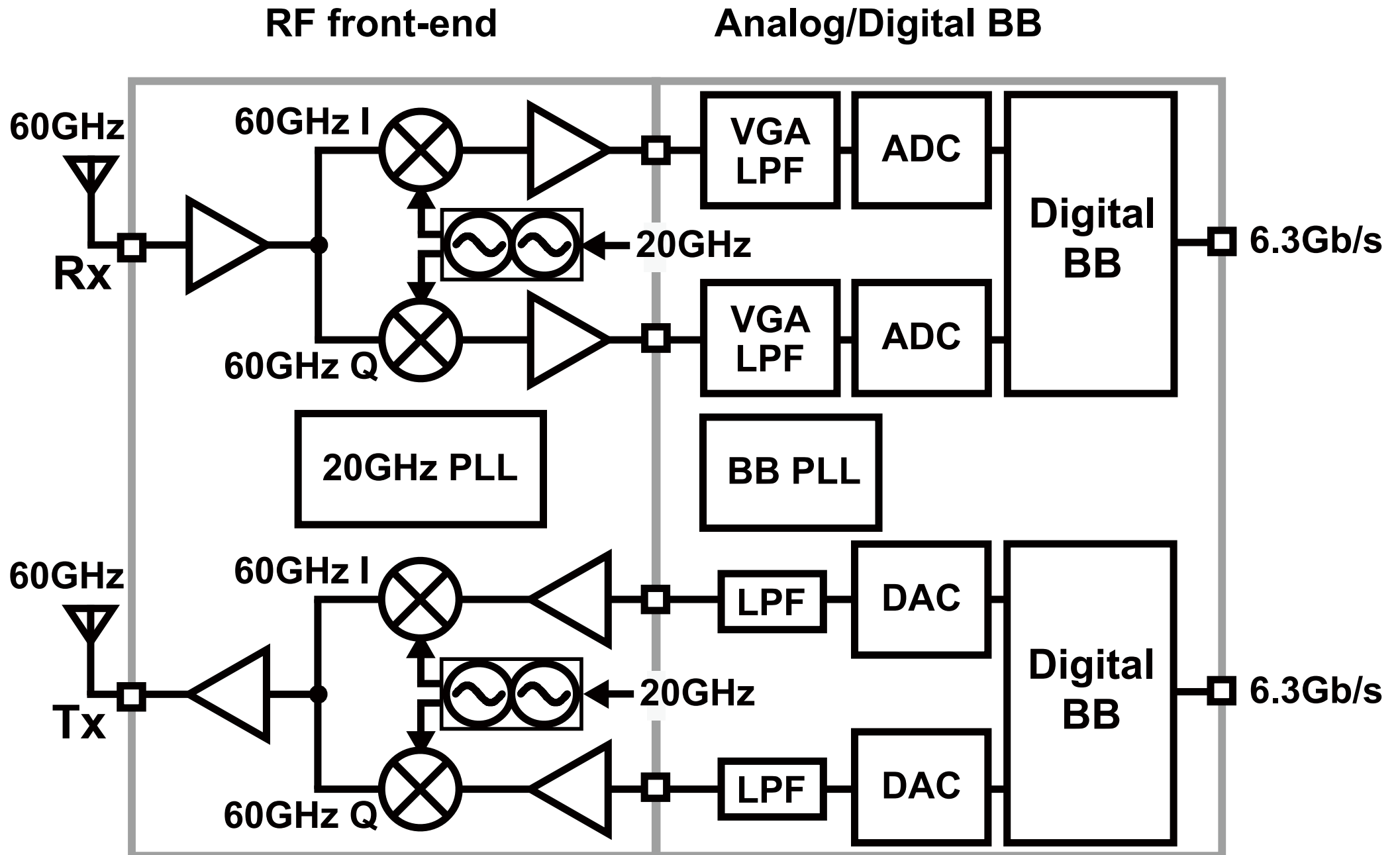


Die Photo

K. Okada and A. Matsuzawa, et al.,
ISSCC 2012

65nm CMOS (RF)

 


40nm CMOS (BB)


 


Chip with antenna in package

 The 60GHz RF chip are mounted on the antenna in package



RF+BB Measurement Setup

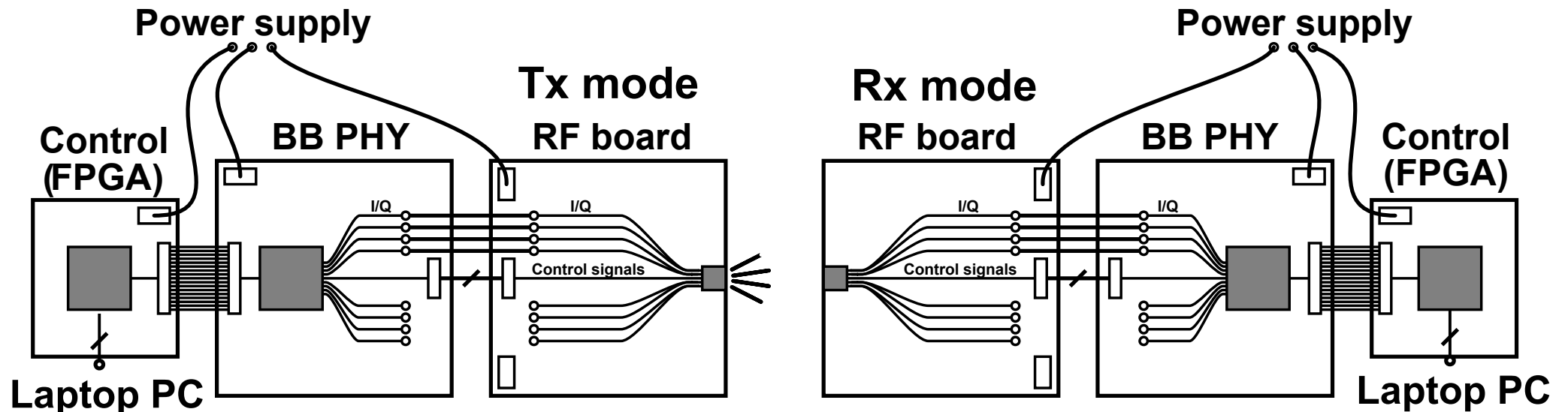 






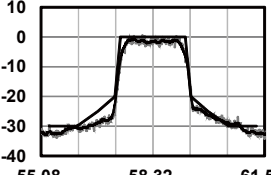
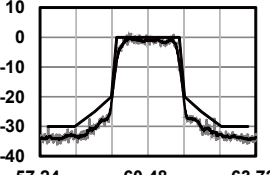
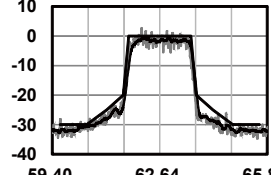
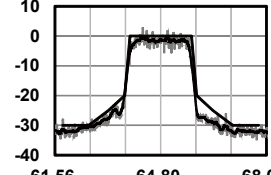
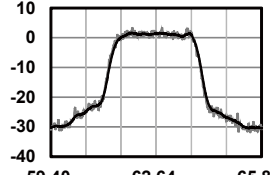
3.5Gb/s QPSK (max 8Gb/s)

Channel	ch.1	ch.2	ch.3	ch.4	Max rate
Constellation					
Spectrum					
Back-off	3.8dB	3.9dB	4.4dB	5.0dB	4.4dB (ch.3)
Data rate*	3.5Gb/s	3.5Gb/s	3.5Gb/s	3.5Gb/s	8.0Gb/s (ch.1-ch.4)
EVM	-21.2dB	-21.6dB	-21.4dB	-20.1dB	-17.3dB (ch.3)
Distance**	1.3m	1.4m	1.6m	1.6m	>0.01m (ch.3)

*The roll-off factor is 0.25. The bandwidth is 2.16GHz except for Max rate.

**Maximum distance within a BER of 10^{-3} . The 6-dBi antenna in the package is used.

7.0Gb/s 16QAM (max 10Gb/s)

Channel	ch.1	ch.2	ch.3	ch.4	Max rate
Constellation					
Spectrum	 55.08 58.32 61.56	 57.24 60.48 63.72	 59.40 62.64 65.88	 61.56 64.80 68.04	 59.40 62.64 65.88
Back-off	4.4dB	4.6dB	5.0dB	5.7dB	5.0dB (ch.3)
Data rate*	7.0Gb/s	7.0Gb/s	7.0Gb/s	7.0Gb/s	10.0Gb/s (ch.3)
EVM	-23.0dB	-23.0dB	-23.3dB	-22.8dB	-23.0dB (ch.3)
Distance**	0.3m	0.5m	0.5m	0.3m	>0.01m (ch.3)

*The roll-off factor is 0.25. The bandwidth is 2.16GHz except for Max rate.

**Maximum distance within a BER of 10^{-3} . The 6-dBi antenna in the package is used.





Performance Comparison

	Integration	#ch.	Data rate (16QAM)	P _{DC} (Tx/Rx)
Tokyo Tech [1]	RF (Direct)	2	11Gb/s [1] 16Gb/s [4]	252mW / 172mW
CEA-LETI [5]	RF (Hetero)	4	3.8Gb/s	1,357mW / 454mW
SiBeam [6]	RF (Hetero)	2	3.8Gb/s	1,820mW / 1,250mW
Tokyo Tech (This work)	RF (Direct) + analog /digital BB	4	RF: w/ wider-BW 10Gb/s RF+BB: 6.3Gb/s	RF: 319mW / 223mW BB: 196mW / 398mW

[1] K. Okada, *et al.*, ISSCC 2011 [4] H. Asada, *et al.*, A-SSCC 2011 [5] A. Siligaris, *et al.*, ISSCC 2011 [6] S. Emami, *et al.*, ISSCC 2011


Recent measurement results

Attains **the world fastest data rate of 16Gbps** in wireless systems

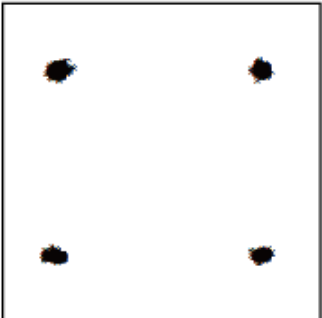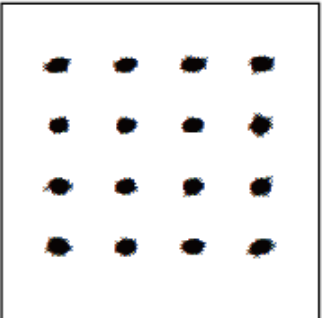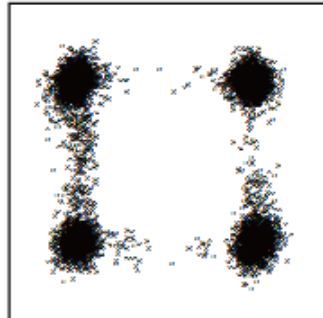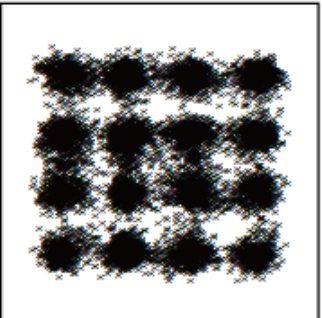Constellation	 9506 points	 19912 points	 13502 points	 42024 points
Modulation	QPSK	16QAM	QPSK	16QAM
Symbol rate	1.76GS/s	1.76GS/s	5.0GS/s	4.0GS/s
Data rate	3.52Gb/s	7.04Gb/s	10.0Gb/s	16.0Gb/s
EVM (withDFE)	-30.5dB	-28.2dB	-15.2dB	-16.1dB

Performance Comparison

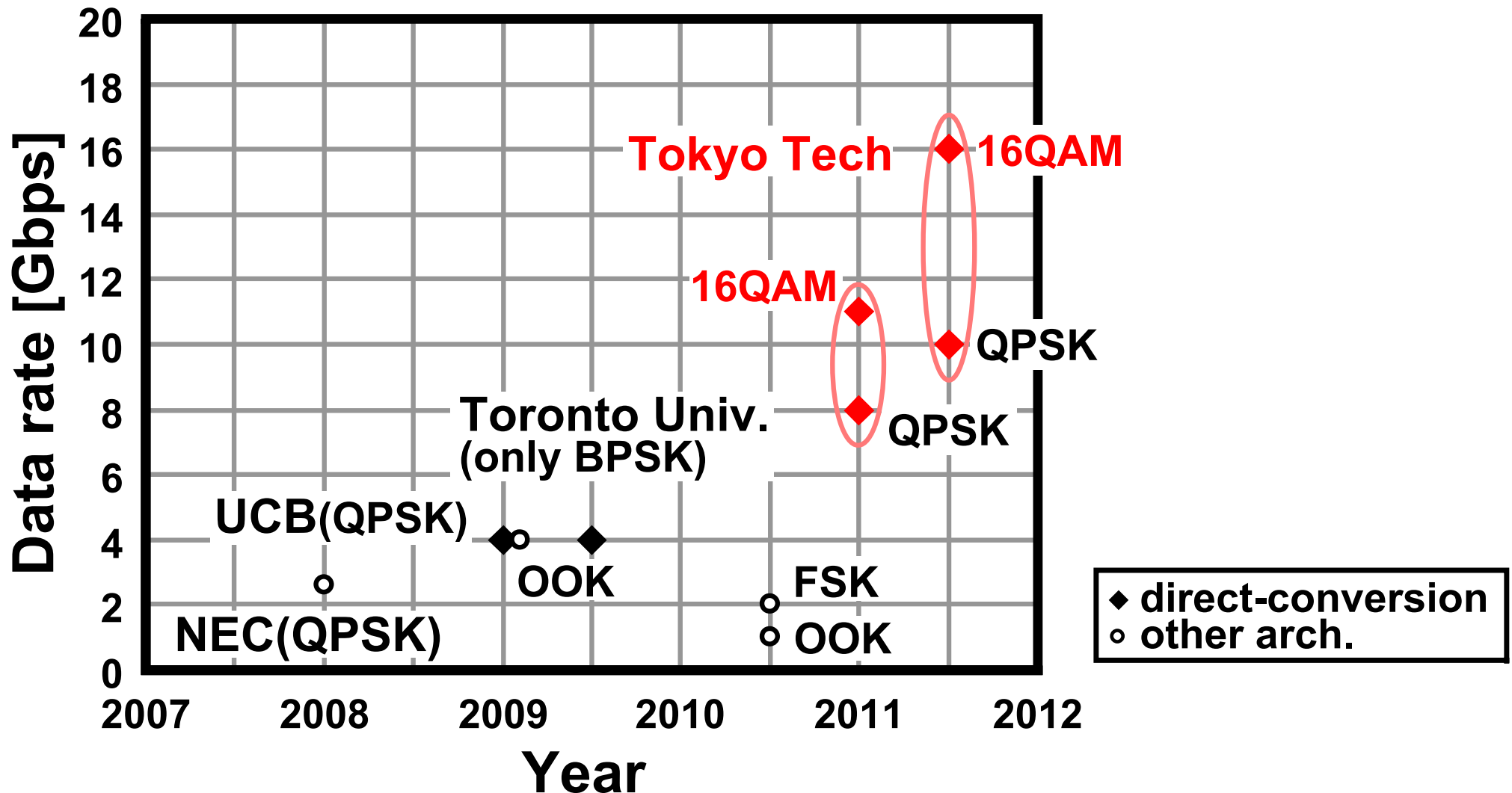
Attains the world fastest data rate of 16Gbps in wireless systems



Essence of millimeter wave IC design

Gain and noise are mainly determined by f_{\max} and f_T of Transistor

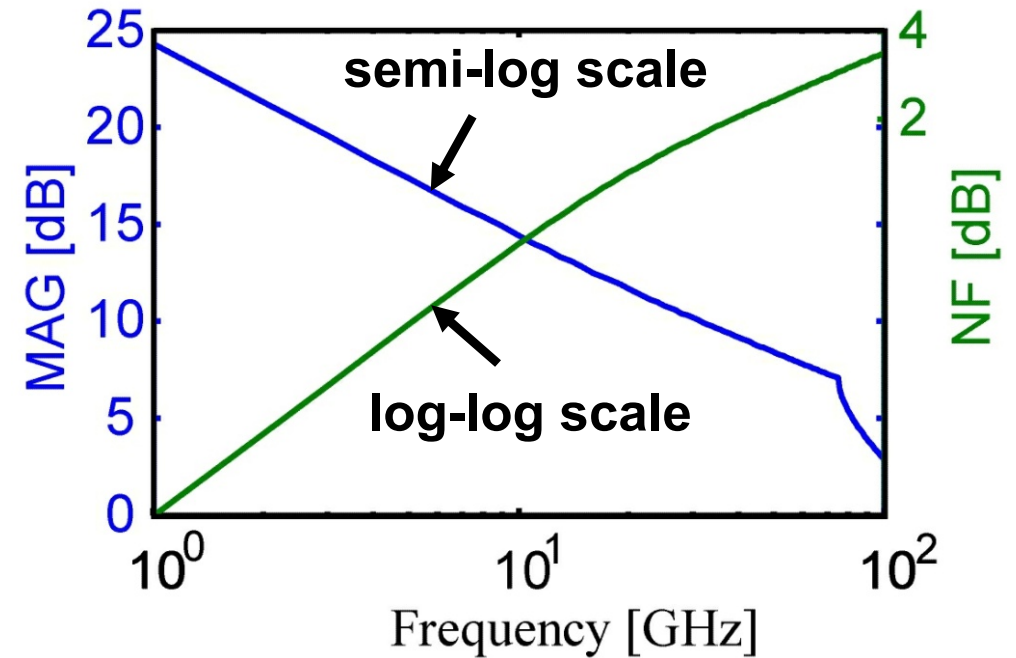- ☹ Lower gain
 - ☹ MAG is inversely proportional to the logarithm of the operating frequency f_c .
- ☹ Higher noise
 - ☹ NF_{\min} is proportional to the operating frequency f_c .



65nm NMOS


$W_f=2.5\mu\text{m}$, $N_f=32$, $V_{gs}=0.8\text{V}$ and $V_{ds}=0.8\text{V}$.

$$G_{\max} \approx \frac{f_{\max}}{f_c}$$

$$NF_{\min} \approx 1 + \left(\frac{f_c}{f_T} \right) \sqrt{1.3g_m(R_g + R_s)}$$

Expected f_{\max} and f_T

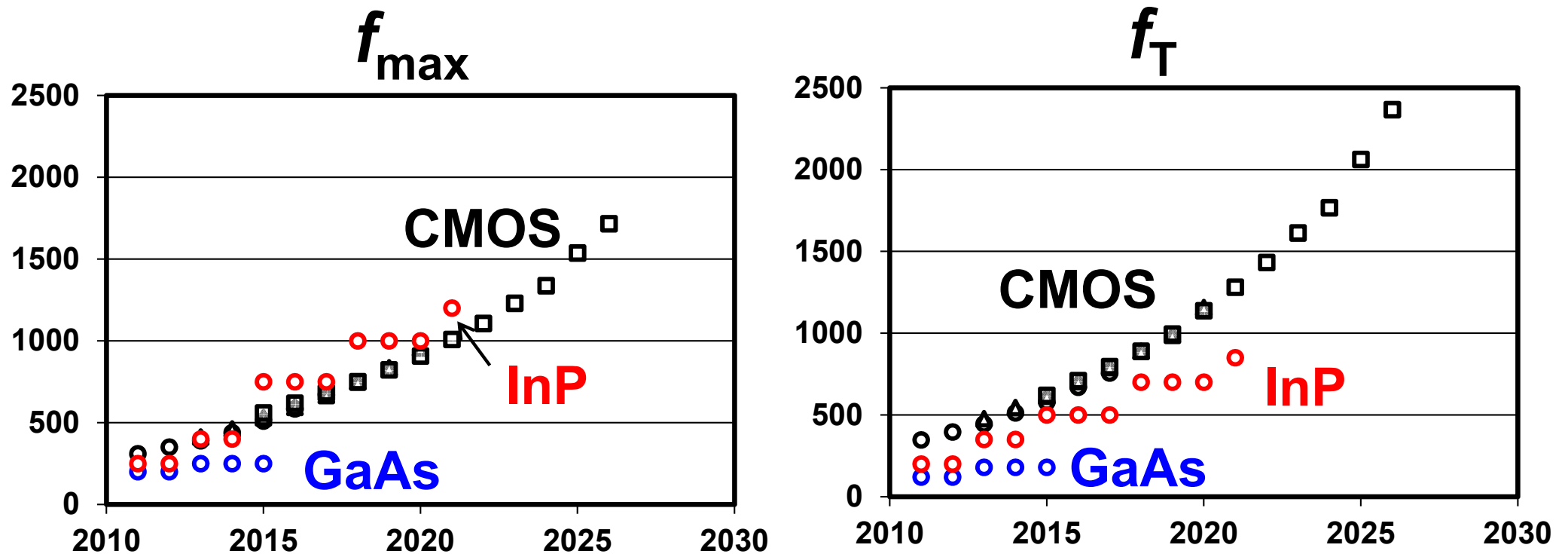f_{\max} and f_T of MOS transistor are expected to increase continuously




○ Bulk CMOS

△ Ultra-Thin-Body Fully-Depleted (UTB FD) SOI


□ Multi-Gate MOSFETs

Amplifier design

 Amplifier design;
accurate sizing, biasing, impedance matching and decoupling.



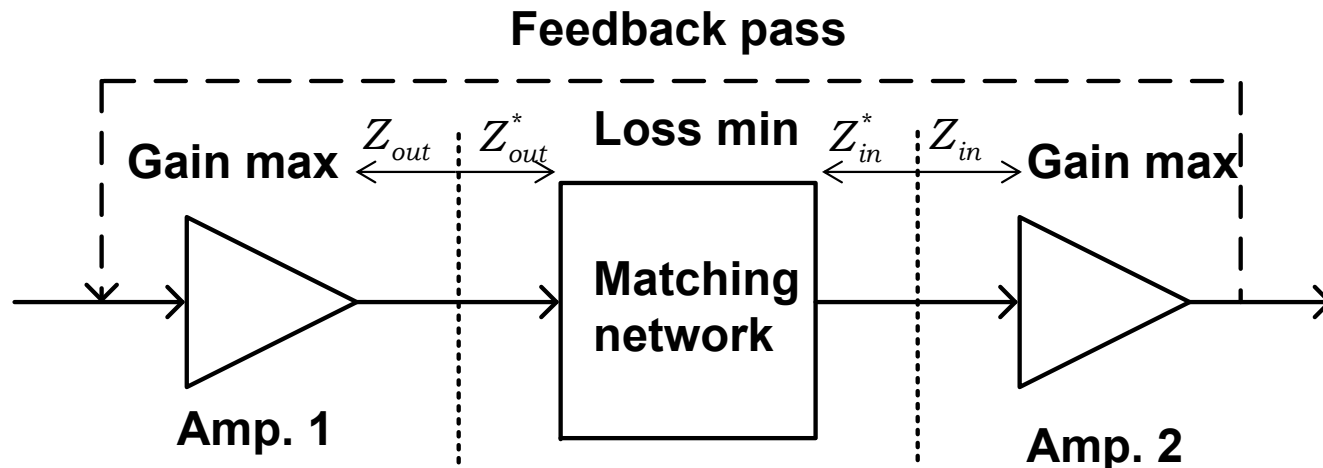A several GHz oscillation will occur, if the feedback passes are made.





Low loss TR line

Transmission line, transformer, and decoupling capacitor are developed.


Transmission line

0.8dB/mm


Manually-placed dummy metal

  

Transformer


 


Decoupling capacitor

 

Gain flatness

  A gain flatness causes ISI for QAM signal and results in increase of BER. Adjusting the impedance matching to reduce the gain flatness.




Gain Flatness	0dB	2dB	3dB
BER	~0	1.3e-5	3e-3
Constellation			

Modeling (De-embedding) technique

Through only method

Inaccurate due to interference between PADs

Measure the PAD and lead parts

 


L-2L Method

Thru (short line) structure

Pad model

Measure with L (200um) and 2L (400um) transmission lines

 No affect of interference from PADs and lead parts




A. M. Mangan, et al., IEEE Trans. on Electron Devices, vol. 53, no. 2, pp.235-241, Feb. 2006

N. Takayama, K. Okada, and A. Matsuzawa, et al., IEEE Asia-Pacific Microwave Conference (APMC), Singapore, Dec. 2009.


Measurement results

An accurate device modeling with proper measurement method is vitally important for very high frequency circuit design. The performance of millimeter wave circuits is mostly determined by The accuracy of modeling for passive and active devices.


Through only method

 

L-2L Method


 


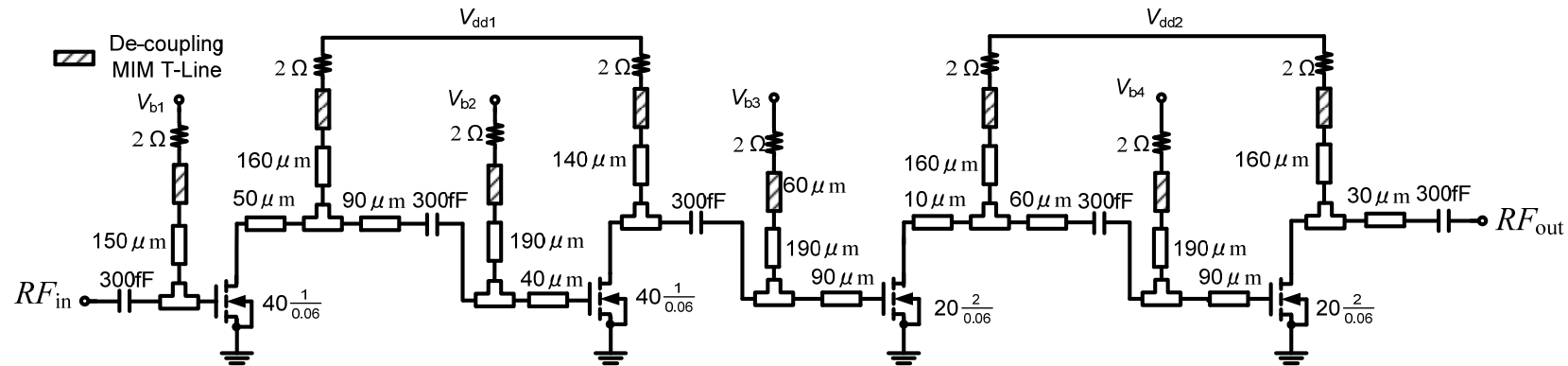A multi stage non-cascode CMOS LNA realizes wide gain flatness.



Four gain stages without cascodes

Gain flatness

 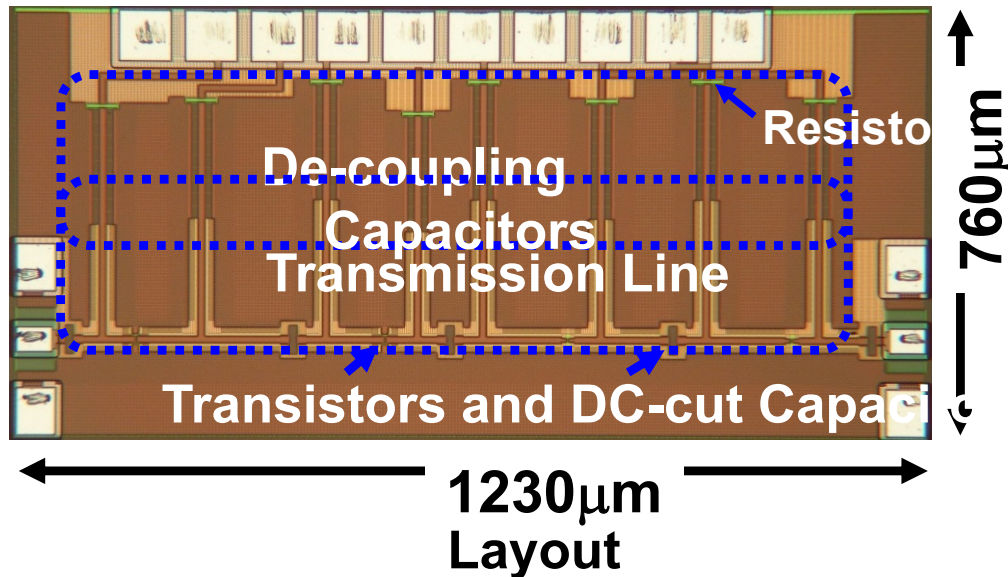


Comparison in LNA

	[1]	[2]	[3]	[4]	[5]	[6]	This work
Tech.	90nm	90nm	90nm	90nm	65nm	90nm	65nm
Topology	CS	Cas.	Cas.	CS	Diff. Cas.	Cas.	CS-CS
#Stage	3	2	2	2	3	3	4
BW [GHz]	5	6	8	-	7.7	14	17
Gain [dB]	15.0	14.6	15.5	12.2	19.3	20.0	24
NF [dB]	4.4	5.5	6.5	6.5	6.1	6.8	4.0-7.6
Power [mW]	3.9	24	86	10.5	35	36	30

[1] E. Cohen, *et al.*, *RFIC* 2008 [2] T. Yao, *et al.*, *JSSC* 2007 [3] S. Pellerano, *et al.*, *JSSC* 2008 [4] B. Heydari, *et al.*, *JSSC* 2007 [5] C. Weyers, *et al.*, *ISSCC* 2008 [6] Y. Natsukari, *et al.*, *VLSI Circuits* 2009

Cross coupled feedback capacitors

Differential circuit


 


Cross coupled feedback capacitors in a differential circuit can reduce the effective capacitance to increase the gain of 6dB at 60GHz.

$$f_{\max} = \frac{f_T}{2\sqrt{R_g g_m C_{gd} / (C_{gs} + C_{gd}) + (R_g + r_{ch} + R_s) g_{ds}}}$$

This term is reduced

Capacitance is cancelled

 
 


Y. Natsukari, et al., VLSI Circuits, Dig. Tech. Papers, pp. 252–253, June 2009.

W. L. Chan, et al., ISSCC. Tech. Dig., pp. 380–381, Feb. 2009.

Feedback signal and stability

  Feedback signal is suppressed by the cross coupled capacitors and this increase the stability of amplifier.




Required phase noise of IQ-VCO for 16QAM₂₇

A phase noise of LT. -90dBc/Hz@1MHz is required for 16QAM systems



A reported phase noise of 60GHz IQ VCO is -76dBc/Hz @1MHz at most

 K. Scheir, et al., ISSCC, pp. 494-495, Feb. 2009.




Key technology: Quadrature ILO

  Quadrature injection locked 60GHz oscillator with 20GHz PLL
Low phase noise of -96dBc/Hz @1MHz.



Best phase noise is achieved.


58-63GHz, -96dBc/Hz -1MHz offset

 

 
A. Musa, K. Okada, A. Matsuzawa., in A-SSCC Dig. Tech. Papers, pp. 101–102, Nov. 2010.

Injection locking method

Injection locking method is a very important circuit technique for high frequency signal generation and frequency divider. Phase noise of the oscillator is mandated by the injected signal.



Output

 

Injection signal

Phase noise $PN_{ILO} = PN_{INJ} + 20 \log(N)$

N: Multiple number

9.5dB @ N=3

Locking frequency range $f_L \approx \frac{f_o}{2Q} \cdot \frac{I_{inj}}{I_{OSC}}$


150GHz CMOS injection locked frequency divider 30

The injection locking method is useful for high frequency divider.



Technology	40nm 1P8M CMOS
Operating frequency	133.3GHz – 151.3GHz
Phase noise	-135.6dBc/Hz @1MHz offset
Power dissipation	12mW @ $V_{DD}=1.6V$
Circuit size	$8.8 \times 5.3\mu m^2$

Divide the pulses → control oscillation frequency


Free-running

 

Locked

  

M. Fujishima, et al., SSDM 2012

 


Further high frequency: CMOS Oscillator 31

Higher frequency can be obtained by CMOS oscillator, using push-push method.

410 GHz

 E. Seok, *et al.*, ISSCC 2008.


45nm CMOS Push-push Oscillator
205GHz oscillation with 410GHz
harmonic output. 11mA @ 1.5V




486 GHz

O. Momeni, *et al.*, JSSC 2011.

 65nm CMOS 486GHz
using Triple-Push oscillation
-7.9dBm from 61mW Pd.



 Fine frequency tuning is required to attain low phase error





$$I_T \sin \phi = I_{osc} \sin \theta$$

$$\frac{d\phi(t)}{dt} = (\omega_0 - \omega_{inj}) - \omega_L \sin\{\phi(t)\} \quad \omega_L \approx \frac{\omega_0}{2Q} \cdot \frac{I_{inj}}{I_{osc}}$$



Locked state
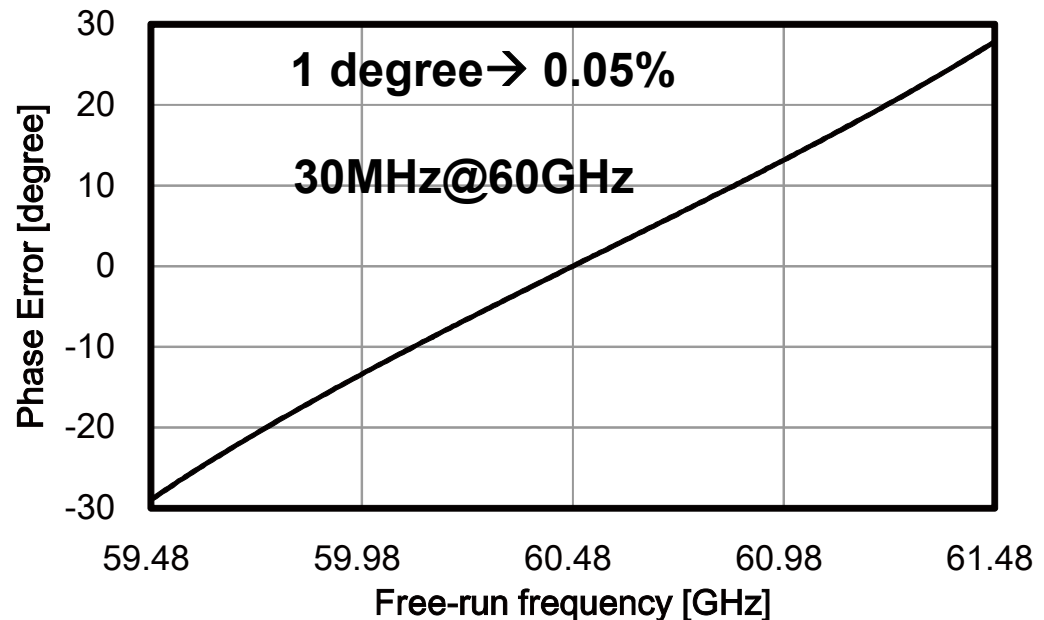 
$$\frac{d\phi(t)}{dt} = 0 \quad \phi(t) = \sin^{-1}\left(\frac{\omega_0 - \omega_{inj}}{\omega_L}\right) = \sin^{-1}\left\{2Q\left(\frac{\omega_0 - \omega_{inj}}{\omega_0}\right) \cdot \frac{I_{osc}}{I_{inj}}\right\}$$



Issue: Hot carrier Injection

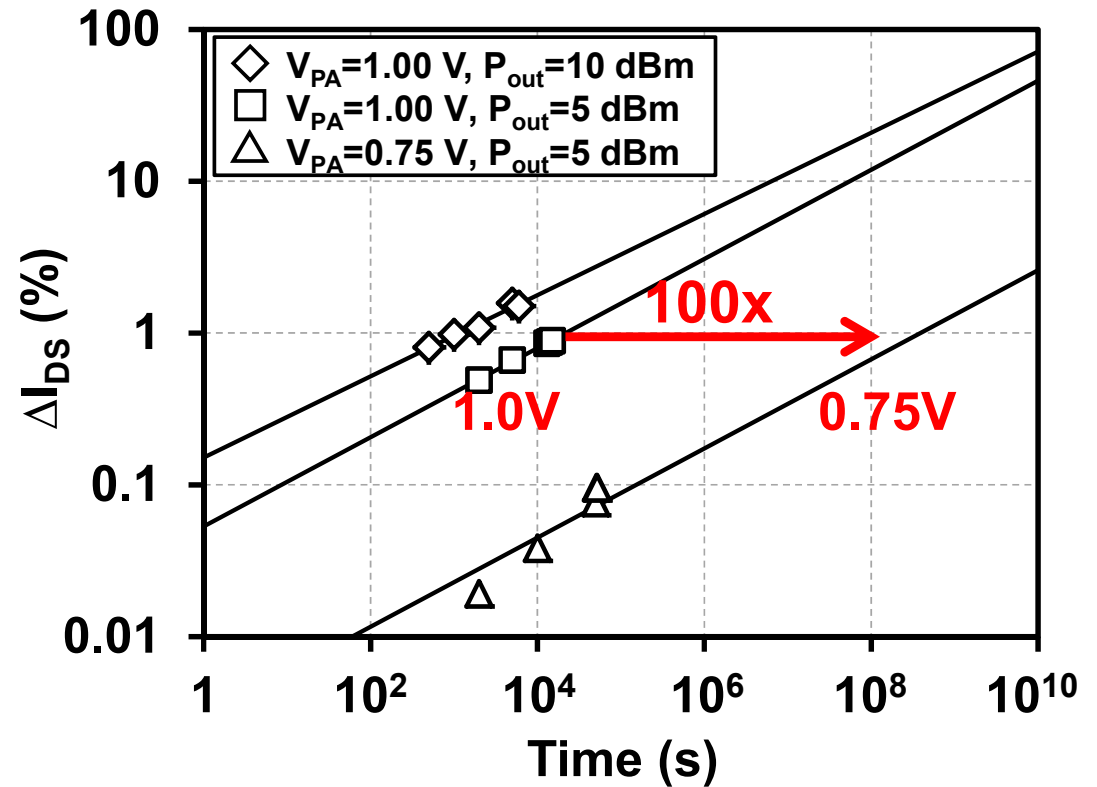 Power supply voltage control must be needed to increase the life time





[1] E. Takeda et al., IEDL 1983

Future issue: Loss in transmission line

Reducing the height of the top metal will increase the power loss in the transmission line.
  
$$\alpha \approx \frac{R}{2Z_0} = \frac{R_u}{2} \sqrt{\frac{C_u}{L_u}} \approx \frac{R_u C_u}{2\sqrt{\epsilon\mu}}$$



ADC design

Data rate is proportional to the product of f_s and N

$$D_{rate} \approx N \cdot f_s$$

If the signal bandwidth is fixed, increase of resolution is required to increase the data rate.

Shannon's theory to determine the communication capacity

$$C = BW \log_2 \left(1 + \frac{P_S}{P_N} \right)$$

Higher data-rate can be realized by higher multi-level modulation. It result in increase of ADC resolution.


BW and SNR of ADC are

$$BW < \frac{f_s}{2} \quad \left. \frac{P_S}{P_N} \right|_{ADC} = 1.5 \cdot 2^{2N}$$

Therefore

$$C \approx N f_s$$

f_s : Sampling frequency
 N : Resolution


 


Example: 38GHz 1Gbps fixed point wireless₃₇

38GHz 1Gbps fixed point wireless system has been developed.

Compatible with Gbit Ethernet

 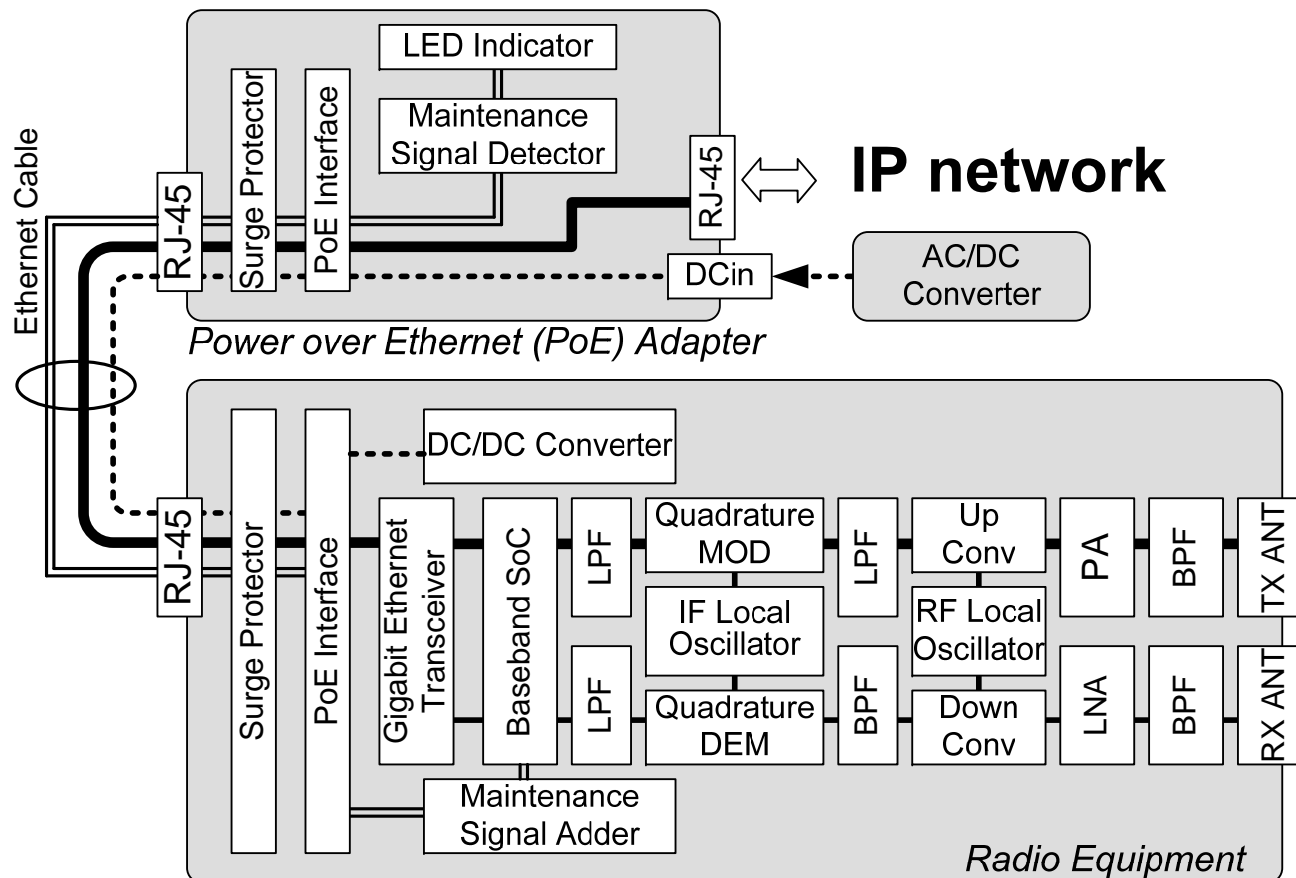
Hole system is integrated with planar antenna





Mixed signal BB SoC

38

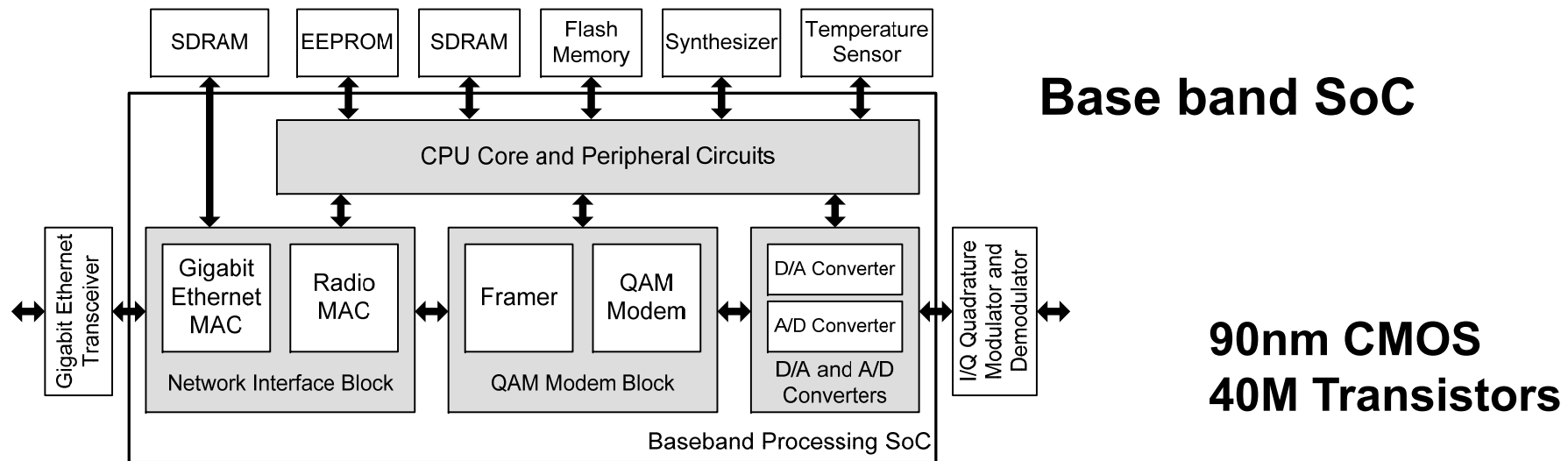A mixed signal SoC has been developed to realize 64QAM (1Gbps) with BW of 260MHz.




Our lab developed ADC & DAC

  


ADC performance and BER

Increase of ADC performance reduces BER of 64 QAM

 C/N vs 64QAM_BER on B-B pair **BW=260MHz**




64QAM

 


ADC architectures

 
Flash, SAR, pipelined, and sigma-delta are four major ADC architectures




(a) Flash

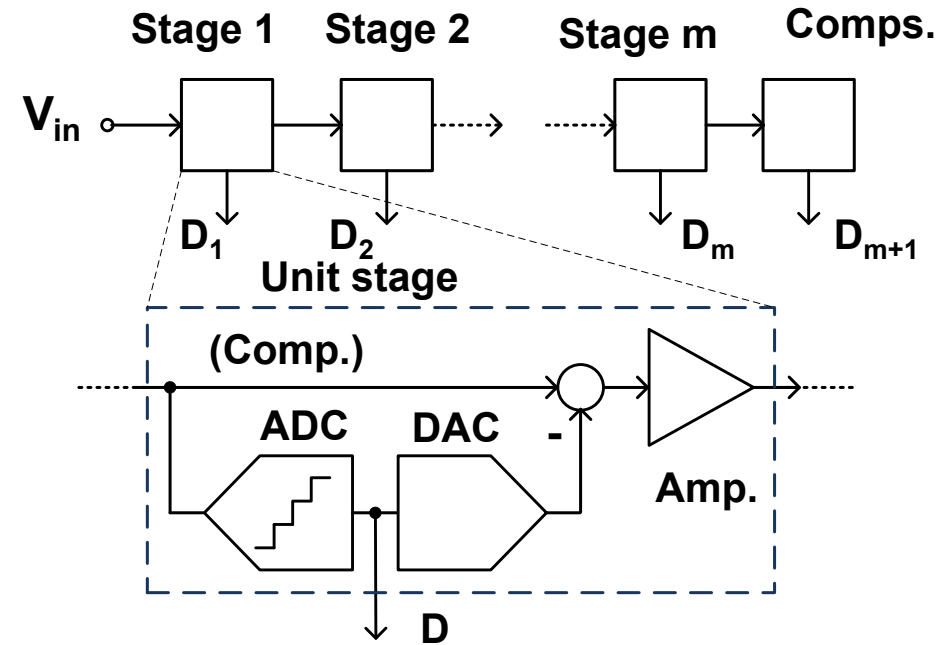

(c) Pipelined ADC

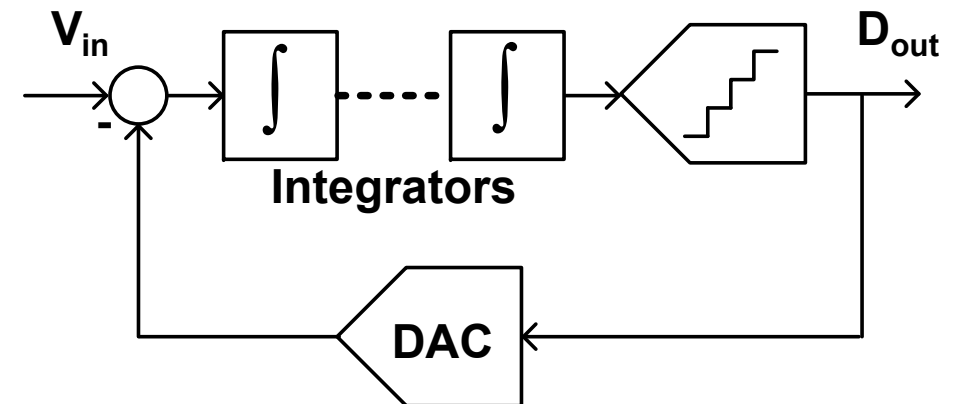


(d) Sigma-Delta

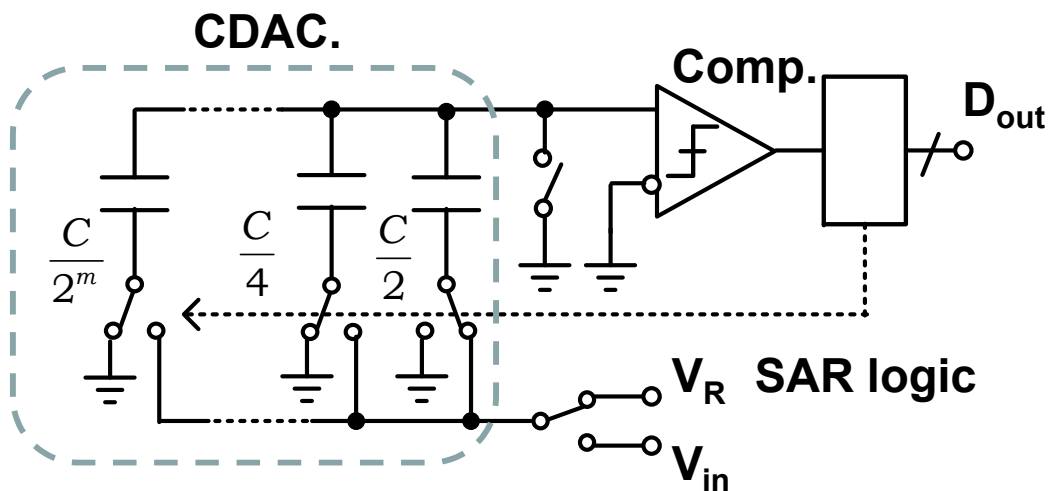

 (b) SAR

Covered performance area of comparator based ADCs have been increased. However OpAmp based ADCs are still needed for higher resolution.



Comparator based ADC design

Flash ADC

Developed baseband SoC and flash ADC 43

Baseband SoC for the 60GHz transceiver has been developed.
ADC, DAC, VGA, and PLL, are integrated in 40nm CMOS.



K. Okada and A. Matsuzawa, et al., ISSCC 2012

RX: 300mW, TX: 110mW
40nm CMOS technology

M. Miyahara and A. Matsuzawa, et al.,
RFIC 2012.


ADC 5b, 2.3GSps, 12mW/ch

Our lab. developed

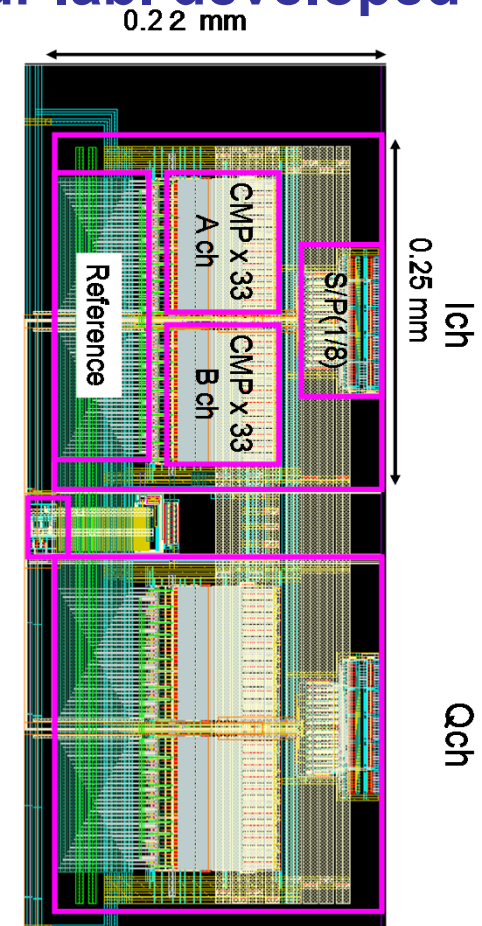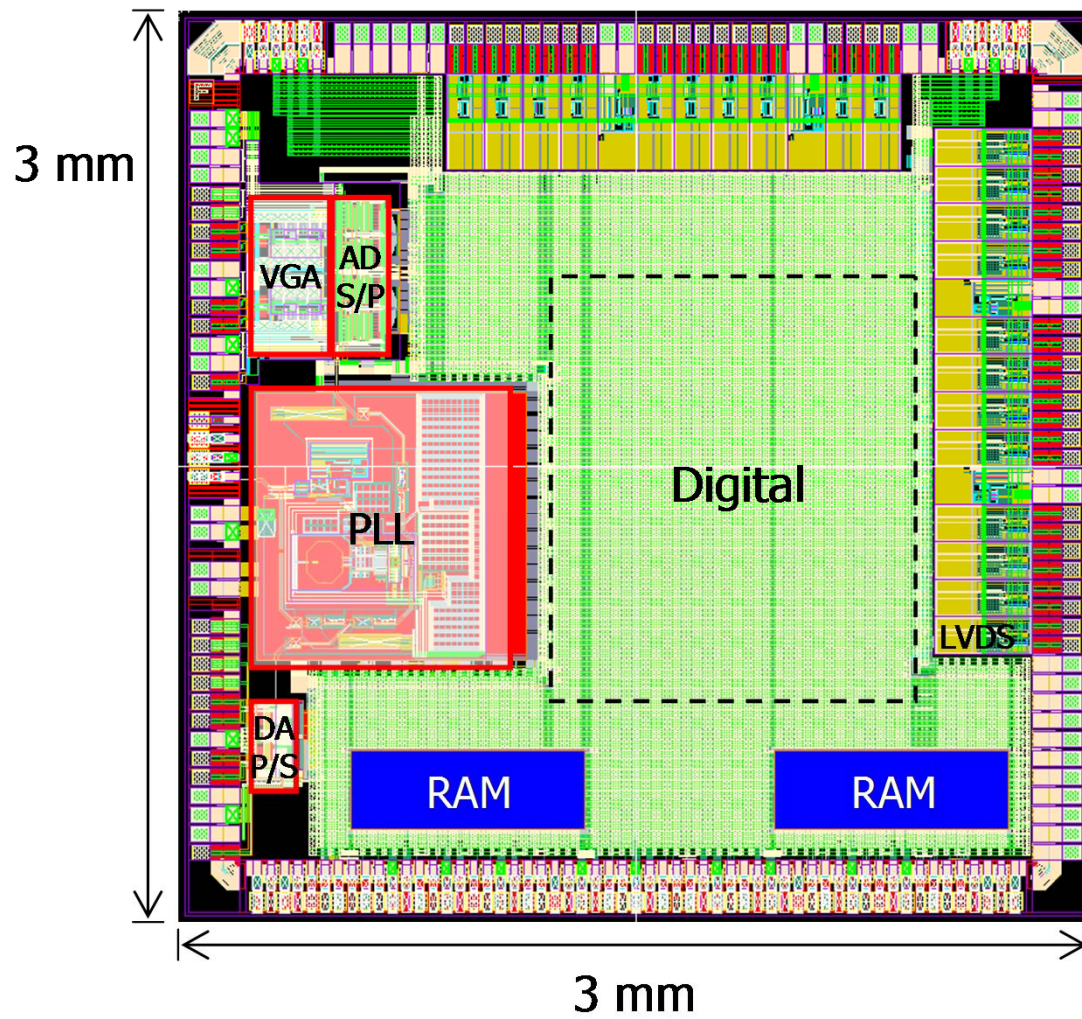


- Flash ADC is still reasonable for GHz and low resolution conversion.
- Comparator determines the ADC performance $N \leq 6$

 Offset mismatch mainly determines the effective resolution.



$$\Delta ENOB = \frac{1}{2} \log_2 \left(1 + 12 \left(\frac{V_{off}(\sigma)}{V_q} \right)^2 \right)$$


6bit : $V_{off} < 3\text{mV}$

 

The smaller is the better


Use smaller transistor to reduce energy and compensate mismatch digitally

 Larger transistor is required to reduce mismatch voltage and results in increase of gate area and consumed energy.




Only small ADCs attain low FoM

$$E_c \propto C \propto \text{Area}$$

 



Offset voltage can be corrected by changing the C_L and I_D

Equivalent circuit for the first stage

 

$$\Delta V_i = \frac{V_{eff}}{2} \left(\frac{\Delta C_L}{C_L} - \frac{\Delta I_D}{I_D} \right)$$

$$V_{eff} \equiv V_{GS} - V_T$$

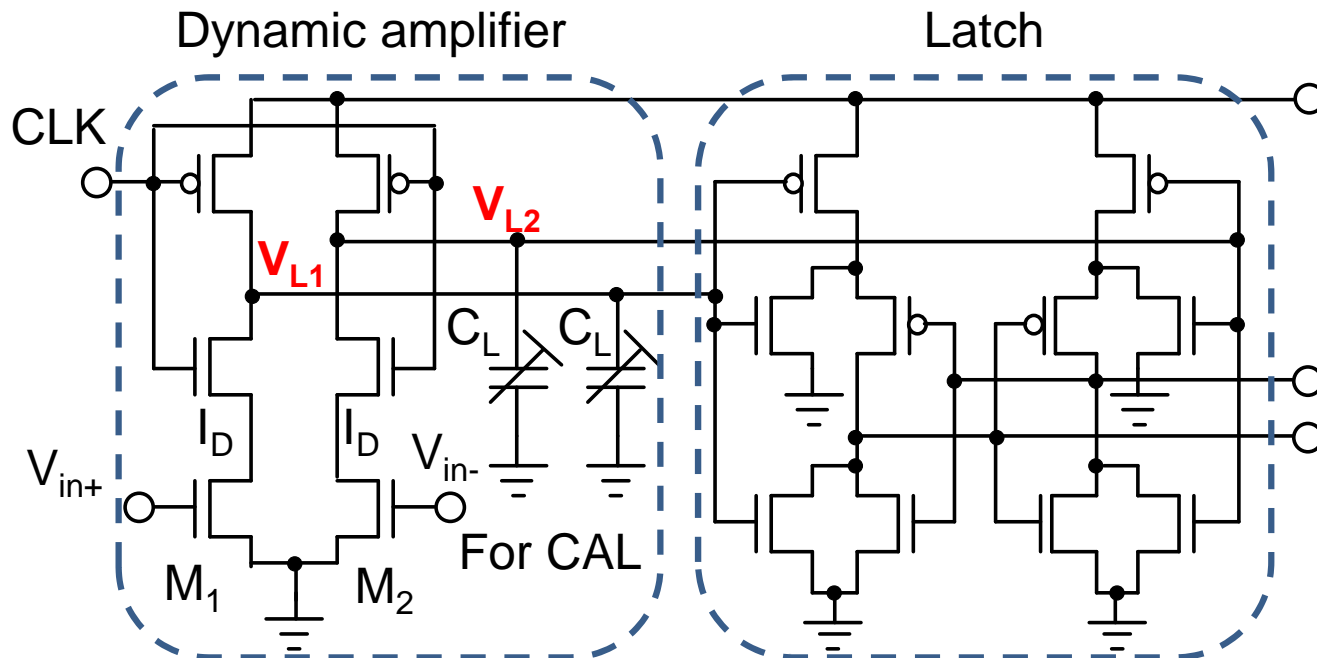 


Output

M. Miyahara and A. Matsuzawa, et al., A-SSCC, Nov. 2008.


Digital offset mismatch calibration methods⁴⁷

Resistor ladder type


 


Current calibration

Capacitor array type

 

Capacitance calibration

 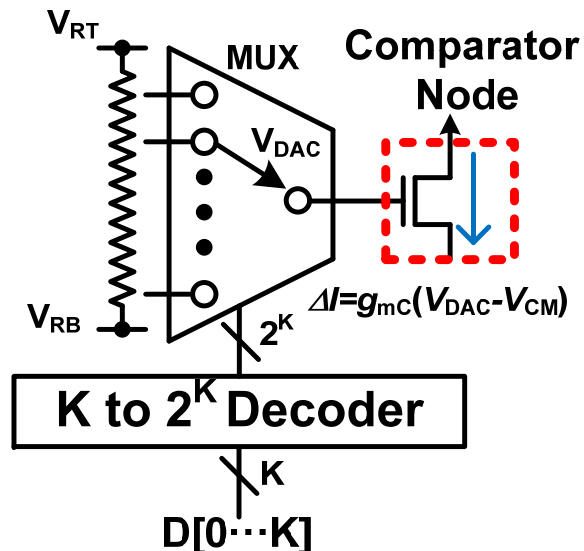


Binary weighted capacitor array

Y. Asada, K. Yoshihara, T. Urano, M. Miyahara and A. Matsuzawa,


“A 6bit, 7mW, 250fJ, 700MS/s Subranging ADC” A-SSCC, pp. 141-144, Nov. 2009.

 The mismatch voltage can be reduced from 14mV to 1.7mV.






Area comparison

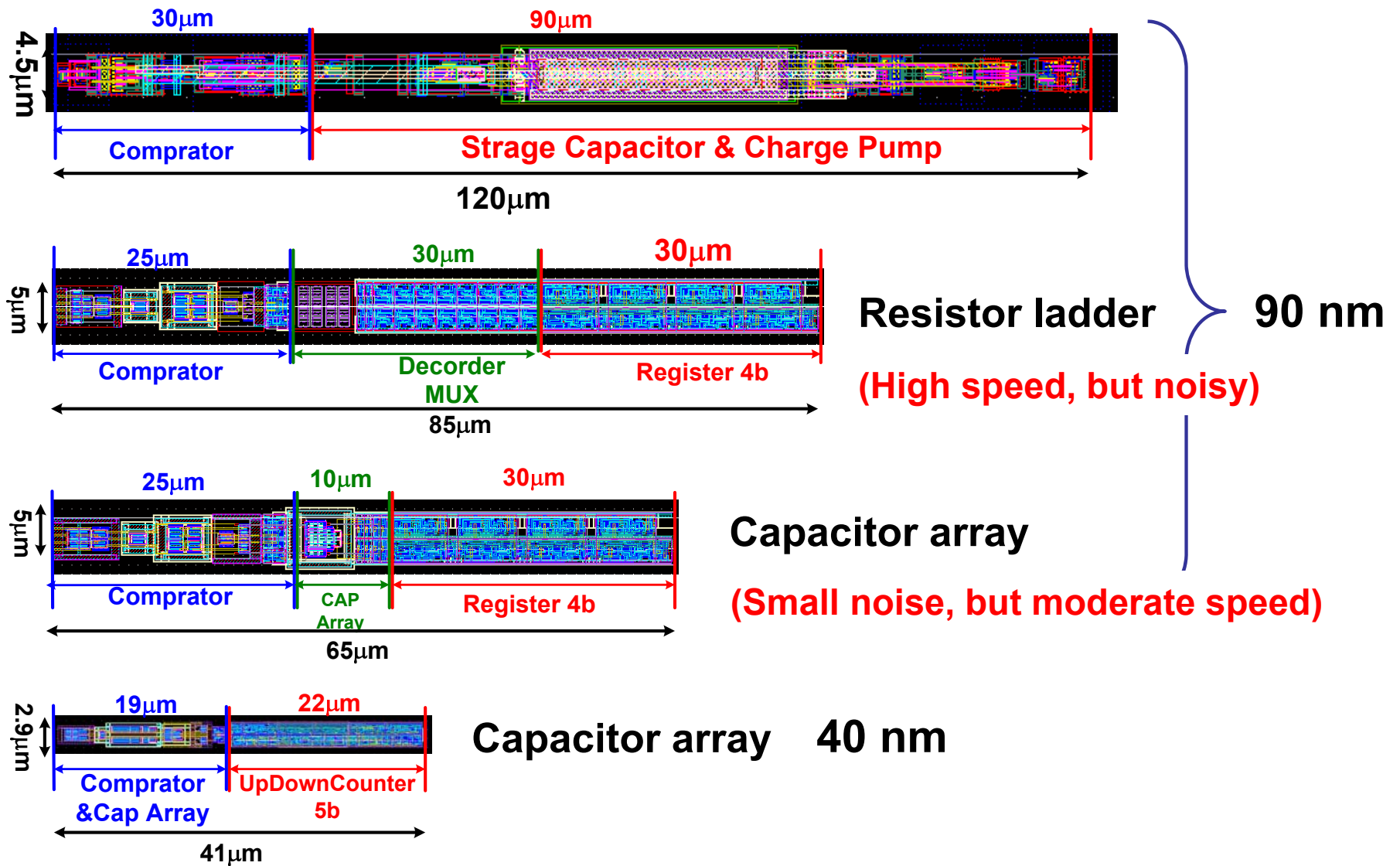Penalty area for digital compensation will be reduced with technology scaling.



Flash ADC for 60GHz transceiver

 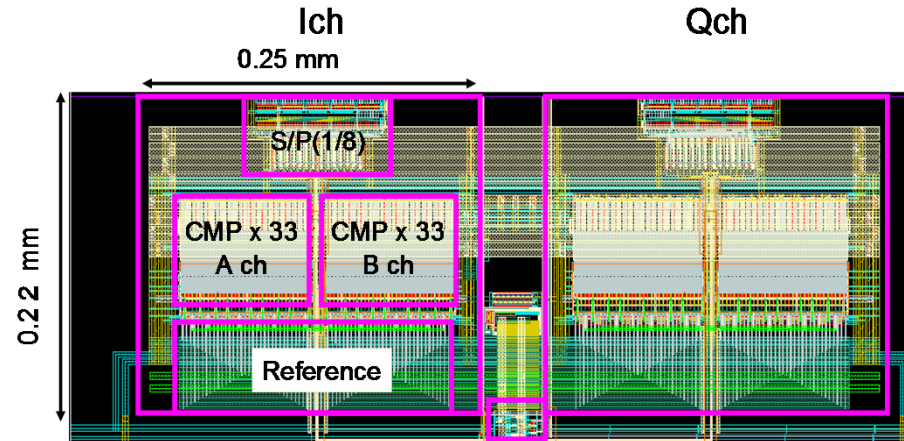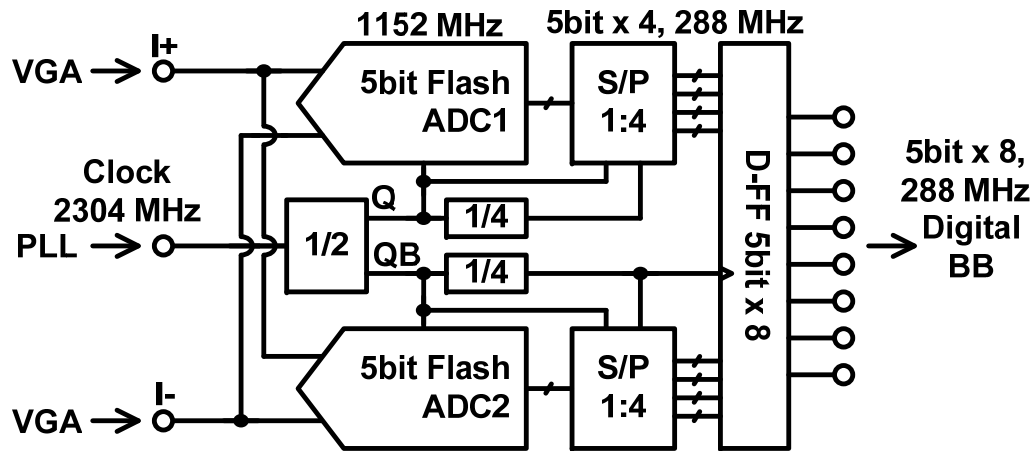M. Miyahara and A. Matsuzawa, et al.,
RFIC 2012.



VGA Gain range	0-40 dB
ADC Resolution	5 bit
Sampling rate	2304 MS/s
Power Consumption	VGA : 9 mW ADC : 12 mW*
DNL, INL	< 0.8 LSB
SNDR	26.1 dB
FoM of ADC	316 fJ/conv.-s

*single channel inc. S/P


ADC Comparison

Low power & small size ADC has been developed for 60GHz transceiver.

	Architecture	Cal.	fs [GS/s]	SNDR [dB]	Power [mW]	FoM [fJ/-c.s.]	Process [nm]	Area [mm ²]
[1]	Flash	-	3.5	31.2	98	946	90	0.149
[2]	SAR	Internal	2.5	34.0	50	489	45	1
[3]	Folding	Internal	2.7	33.6	50	474	90	0.36
[4]	Pipeline, Folding	External	2.2	31.1	2.6	40	40	0.03
[5]	Flash	Internal	2.88	27.8	36	600	65	0.25
This work	Flash	Internal	2.3	26.1	12	316	40	0.06

- [1] K. Deguchi, *et al.*, *VLSI Circuits* 2007 [2] E. Alpman, *et al.*, *ISSCC* 2009
[3] Y. Nakajima, *et al.*, *VLSI Circuits* 2007 [4] B. Verbruggen, *et al.*, *ISSCC* 2010
[5] T. Ito, *et al.*, *A-SSCC* 2010


0.5V Flash ADC

 

5bit 0.5V 600MSps Flash ADC has been developed.
S/H circuits use gate boosted switches.
Forward body bias is used to decrease gate delay.

M. Miyahara , J. Lin, K. Yoshihara, and A. Matsuzawa,
 "A 0.5 V, 1.2mW, 160fJ, 600 MS/s 5 bit Flash ADC"
 A-SSCC, pp. 177-180, Nov. 2010.

Reference #	[7]	[8]	[9]	[10]	This work
Resolution (bit)	5	5	5	5	5
fs (GS/s)	0.5	1.75	1.75	0.06	0.6
SNDR (dB)	26	30	30	26	27
Pd (mW)	5.9	2.2	7.6	1.3	1.2
Active area (mm ²)	0.87	0.017	0.03	-	0.083
Vdd (V)	1.2	1	1	0.6	0.5
FoM(fJ)	750	50	150	1060	160
CMOS Tech. (nm)	65	90	90	90	90
Architecture	SAR	Fold+Flash	Flash	Flash	Flash

 

FoM_{Fmax} = 160fJ @ 600MSps
FoM_{Best} = 110 fJ @ 360MSps

[7] B. P. Ginsburg, J. Solid-State Circuits 2007.
 [8] B. Verbruggen, ISSCC 2008.
 [9] B. Verbruggen, VLSI Circuits 2008.
 [10] J. E. Proesel, CICC 2008.

Comparator based ADC design


: SAR ADC

Basic idea for low energy analog design

Conventional analog circuit consumes larger energy.

Dynamic circuits doesn't consume larger energy.

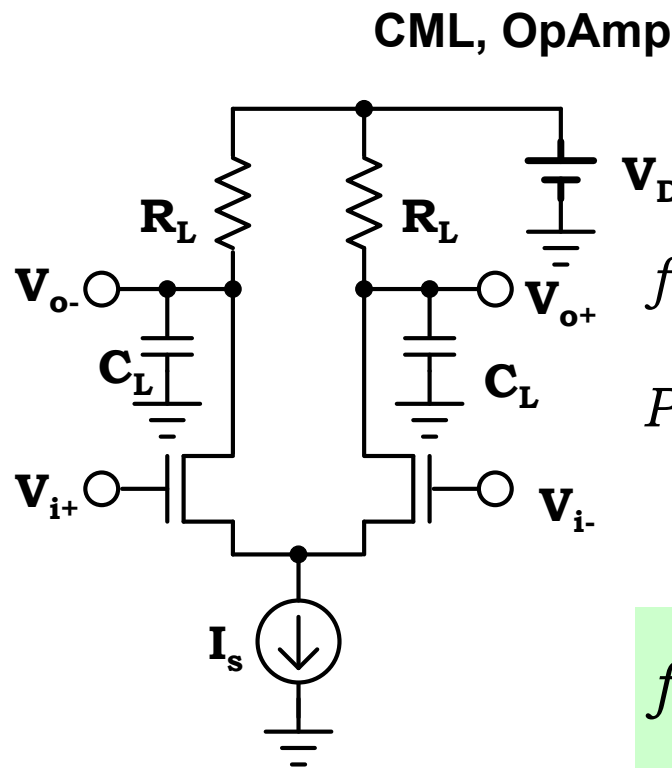
CMOS: Consumed energy is **independent** of the delay time.



$$f_{toggle} \propto \frac{I_s}{V_{DD} C_L}$$

$$P_d = V_{DD} I_s$$
 
$$f_{toggle} \propto \frac{P_d}{C_L V_{DD}^2}$$



$$f_{toggle} \propto \frac{1}{T_r} \propto \frac{1}{R_o C_L}$$

$$P_d = f E_d = \frac{1}{2} f C_L V_{DD}^2$$


$$E_d = \frac{1}{2} C_L V_{DD}^2$$

$$f_{toggle} \propto \frac{1}{R_o C_L}$$

SAR ADC


SAR can be designed to consume no static power.

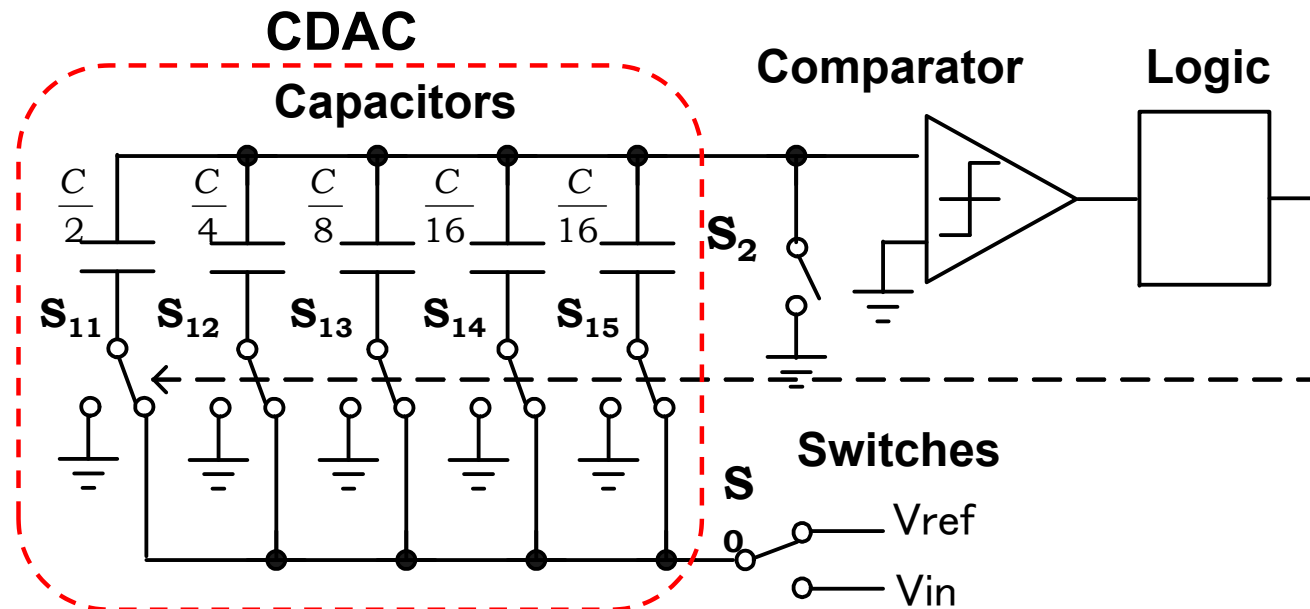SAR can realize larger signal swing compared with pipeline ADC.




Not OpAmp based,
but comparator based

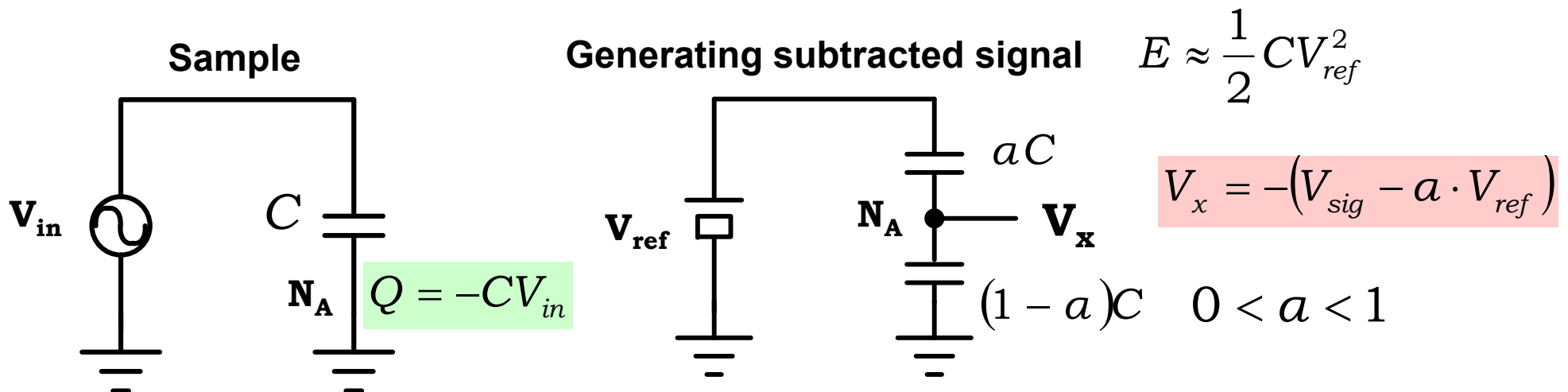No resistors
No static current !
Potentially full swing




 High SNDR over 70dB and low FoM of less than 50fJ looks not easy.



FoM LT. 10fJ is possible, however its SNDR is < 60dB

Low FoM, if SNDR is > 70dB is not easy.

 

FoM2 is supported by theory and show the energy trend more clearly.

$$FoM = \frac{P}{2^{(SNDR - 1.76)/6.02} \cdot F_S}$$

$$FoM2 = \frac{P}{2^{2 \cdot (SNDR - 1.76)/6.02} \cdot F_S}$$


Linearity of SAR ADC

Non-linearity is caused by CDAC, and it can be calibrated digitally. Therefore, a small capacitance determined by noise can be used.


Capacitor mismatch CAL

Floating capacitor CAL


Sprir capacitor

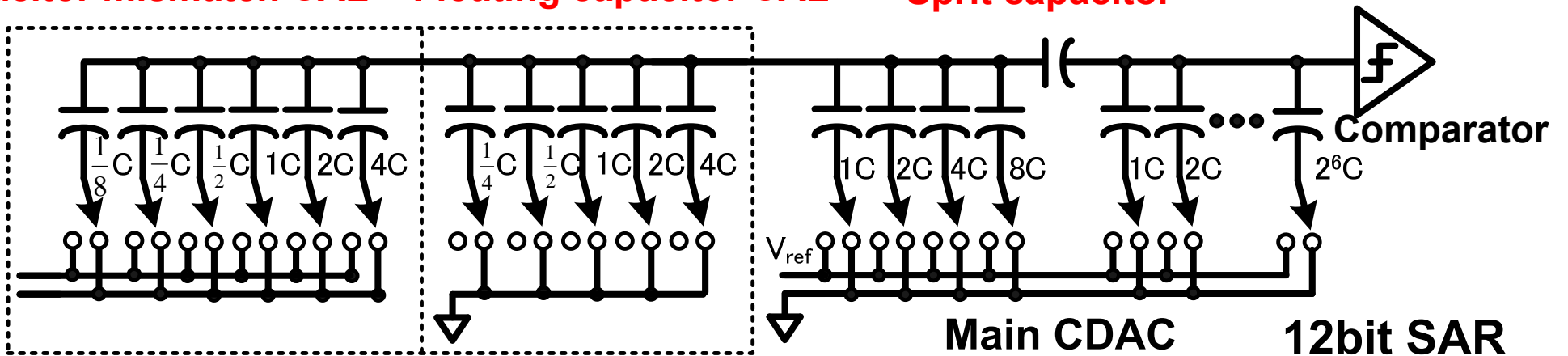

Capacitance mismatch CAL

 


Floating capacitor CAL

 



Noise of dynamic comparator

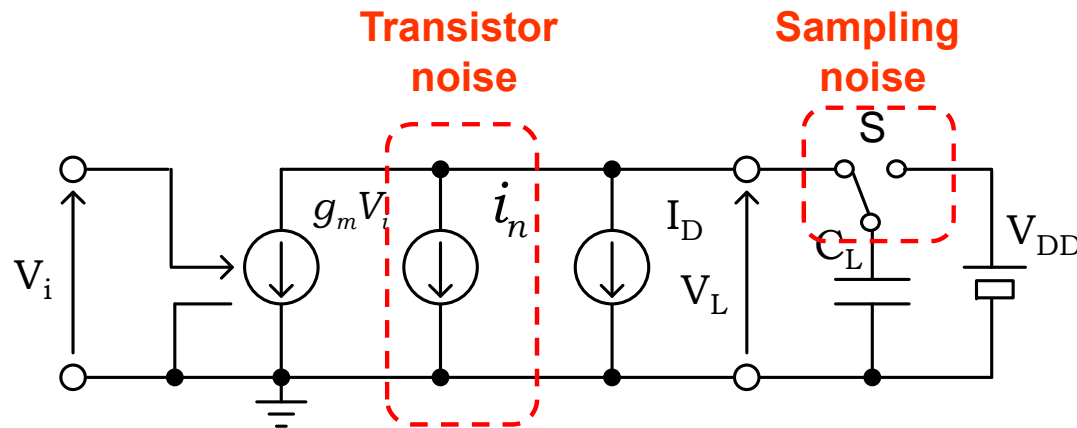Basic noise of the dynamic comparator is determined by load capacitor




Obtained noise equation

 
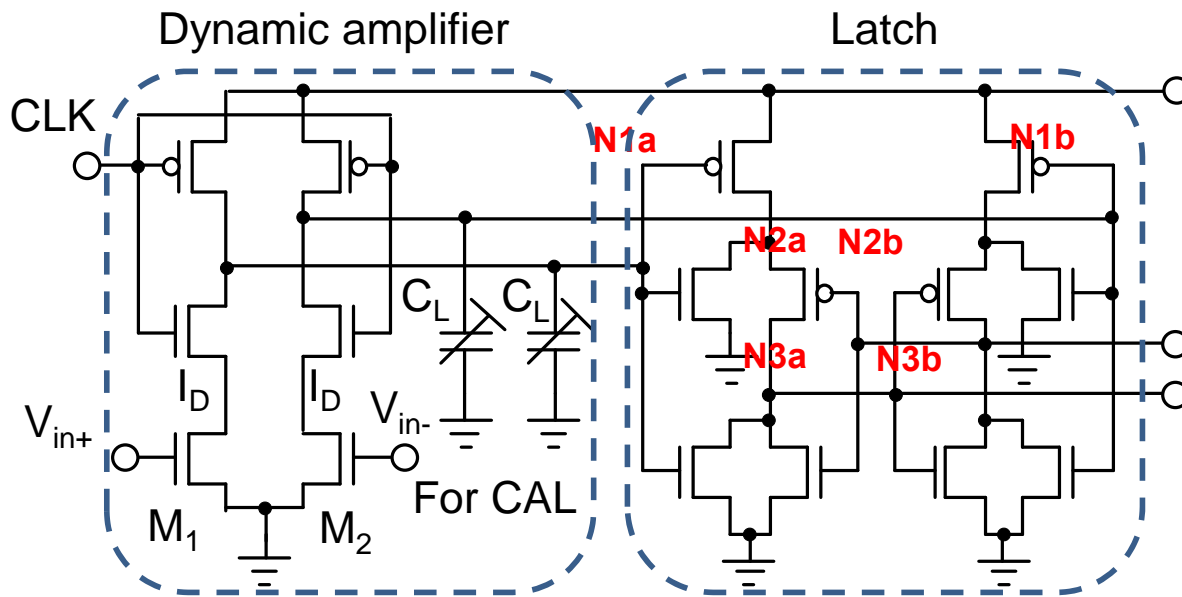
$$\delta V_{in}^2 = \frac{kTV_{eff}^2}{C_L V_{dd}^2} \left(2\gamma \frac{V_{dd}}{V_{eff}} + 1 \right)$$



 Gain and noise of the dynamic amplifier 59



  The larger gain requires the larger voltage swing




(1) Gain
$$\Delta V_o = -\frac{g_m \Delta V_{in}}{C_L} T_d$$

(2) Noise
$$G = -\frac{g_m}{I_D} V_{os} \approx -\frac{2V_{os}}{V_{eff}} \quad T_d = \frac{V_{os} C_L}{I_D}$$

$$\begin{aligned} \overline{i_{n0}^2} &= \int_0^\infty \left(\frac{i_{no}^2}{\text{Hz}} \right) |H(f)|^2 df = \frac{i_{no}^2}{\text{Hz}} \int_0^\infty T_d^2 \sin^2(fT_d) df \\ &= \frac{i_{no}^2}{\text{Hz}} \frac{T_d^2}{T_d} \int_0^\infty \sin^2(x) dx = \frac{i_{no}^2}{\text{Hz}} \frac{T_d}{2} \end{aligned}$$
 
$$\overline{v_{ni}^2} = \frac{\overline{v_{n0}^2}}{G^2} = \frac{V_{eff}^2}{4V_{os}^2} \times \frac{4kT\gamma g_m T_d}{C_L^2} = \frac{2kT\gamma}{C_L} \frac{V_{eff}}{V_{os}} = \frac{2kT\gamma}{g_m T_d}$$





$$H(f) = \frac{2}{2\pi f} \sin(\pi f T_d) = T \cdot \text{sinc}(fT_d)$$

Node capacitances should be increased to realize higher ADC resolution. This results in increase of consumed energy of the dynamic comparator.

$$\overline{V_n^2} = \frac{V_{n_latch}^2}{G^2} = \frac{V_{eff}^2}{4V_{os}^2} V_{n_latch}^2$$

  A dynamic amplifier with CMOS amplifier suppresses the noise from the latch




Fundamental Energy of sampling circuit 61

Fundamental energy of sampling is often used.

However this neglects the power for comparison.

$$E_s = 24kT2^{2N}$$

Sampling circuit

 

Electrical energy=Thermal energy

$$\frac{1}{2}CV_n^2 = \frac{1}{2}kT \quad \therefore V_n^2 = \frac{kT}{C}$$

Quantization voltage

$$V_{qn} = \frac{V_{FS}}{2^N}$$

Quantization noise power

$$P_{qn} = \frac{V_{qn}^2}{12} = \frac{V_{FS}^2}{12 \cdot 2^{2N}}$$

Noise balance

$$V_n^2 = P_{qn}$$

Capacitance


$$C = 12kT \frac{2^{2N}}{V_{FS}^2}$$

P_d of sampling circuit

$$E_d = 2CV_{FS}^2 = 24kT2^{2N}$$

Energy consumption of ADC

 Consumed energy of ADC is mainly determined by the resolution.
 Energy of ADC is reaching 100x of the fundamental sampling energy,
 and **10x** of the fundamental ADC energy consumption.



Conventional fundamental sampling energy

$$E_{ADC} \quad E_s = 24kT_s 2^{2N}$$

$$E_s \quad E_s = 2^{2N} \times 10^{-19}$$


Fundamental ADC conversion energy involving energy consumption of comparato

$$E_{ADC} \approx N \cdot E_s$$

$$E_{ADC} = N \times 2^{2N} \times 10^{-19}$$

Noise in comparison phase


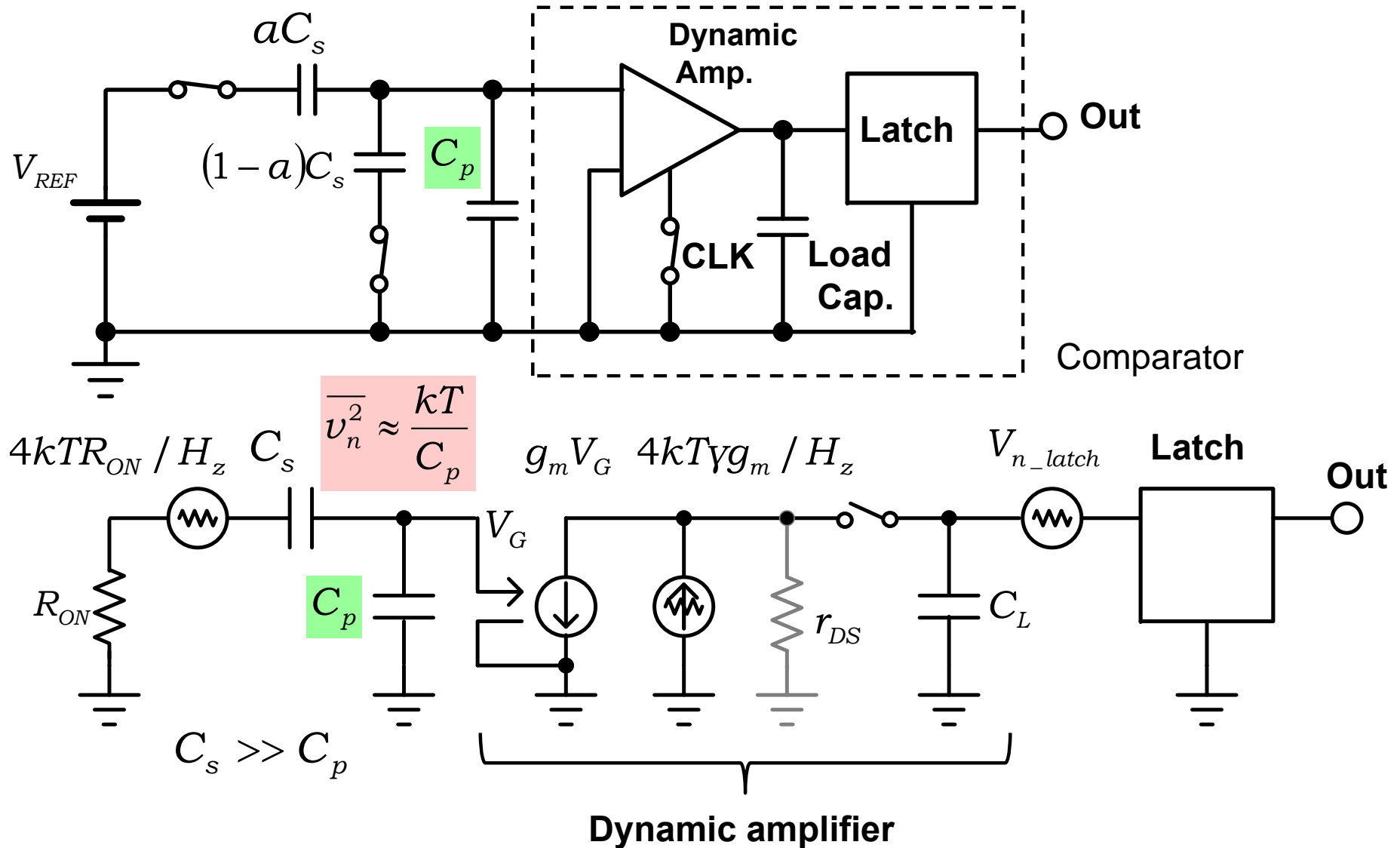
The switch resistance generates the noise and the noise voltage at the comparator is large due to the small parasitic capacitance.





Transient noise simulation

Input noise is increased with frequency bandwidth, if C_p is very small.
If C_p exists, it determines noise voltage.

$C_p=0$

  

$C_p=100fF$

  

Clear tradeoff between noise, speed and energy.

For low noise voltage

- 1) Large sampling capacitance
- 2) **Small switch resistance**
- 3) **Long integration time**
- 4) **Large Load capacitance**
- 5) Small latch noise
- 6) Large voltage swing
- 7) Small gate effective voltage

1) Sampling noise of C_s

$$\overline{V_{n1}^2} = \frac{2kT}{C_s}$$

2) Effective noise caused by the switch

$$\overline{V_{n2}^2} = \frac{4kTR_s}{\left(1 + \frac{C_p}{C_s}\right)^2} T_d$$

3) Noise by the dynamic amplifier

$$\overline{V_{n3}^2} = \frac{4kT\gamma}{C_L} \frac{V_{eff}}{V_{os}} = \frac{4kT\gamma}{g_m T_d}$$

4) Noise by from the latch


$$\overline{V_{n4}^2} = \frac{V_{n_latch}^2}{G^2} = \frac{V_{eff}^2}{4V_{os}^2} V_{n_latch}^2$$

Dynamic response of reference circuit

Dynamic response of the reference circuit affects the linearity of the ADC.

Large decoupling capacitance is required to suppress this effect.

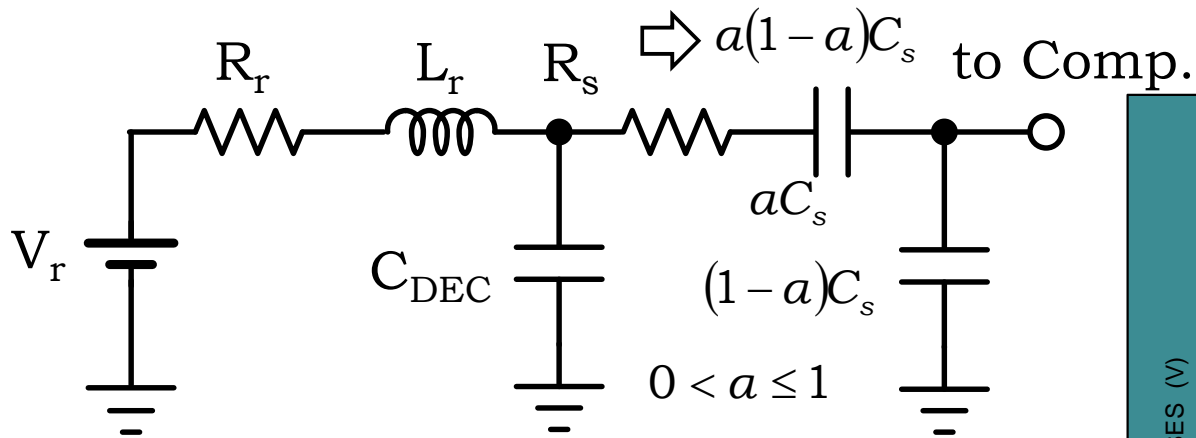Impedance design (IC, bonding, package, board, etc.) becomes important.



1LSB: 0.5mV @12bit

$$C_s = 4\text{pF}$$

$$a = 0.5$$

$$R_s = 20\Omega$$

$$R_r = 30\Omega$$

$$L_r = 5\text{nH}$$


$$V_r = 1.0\text{V}$$

$$\Delta V_r \approx \frac{(1-a)C_s}{C_{DEC}} (V_R - V_{int})$$

V_{int} : Initial voltage of C_s


$$\Delta V_r(t) \approx \Delta V_r(0)e^{-\frac{t}{\tau}}$$

$$\tau \approx R_r C_{DEC}$$

 


MOM capacitance

 MIM capacitance has a good matching, MOM is not so,,,.
However matching issue can be solved by digital mismatch compensation.
Capacitor density is increased by technology scaling.
Very small capacitance ($<0.1\text{fF}$) is available and useful for the mismatch comp.



MOM capacitance

 

OpAmp based ADC design

Interpolated pipeline ADC



Conventional Pipelined ADC

Pipelined ADCs are still needed for high resolution and high speed ADC.

However, conventional pipelined ADC requires accurate MDAC

$$N \geq 10\text{bit}$$

$$f_s > 200\text{MSps}$$

 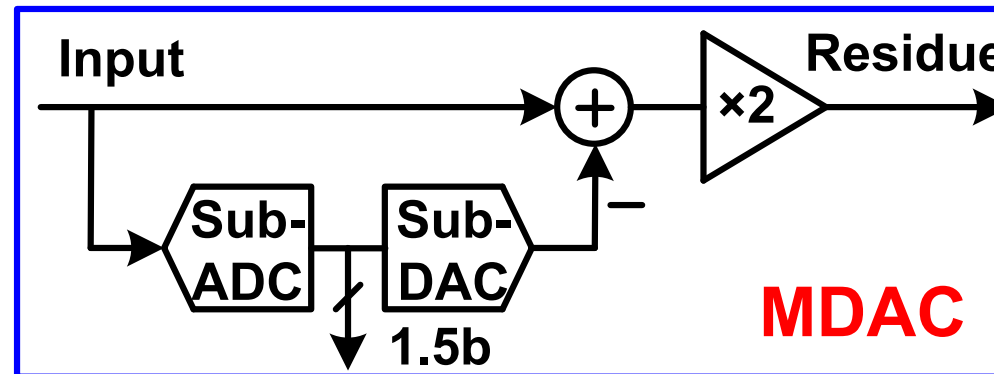

OpAmp gain and conversion error


$$\varepsilon_{(LSB)} = \frac{3 \times 2^N}{G} \quad G > \frac{3 \times 2^N}{\varepsilon_{(LSB)}}$$

$$G > 6N + 10 \text{ (dB)}$$


Gain > 70dB

10bit ADC

Large error occurs

 

40dB gain

 


Developed new 10b ADC to address 64 QAM.

Interpolated pipeline scheme
No need of high gain OP amps

10b, 320 MSps, 40mW ADC


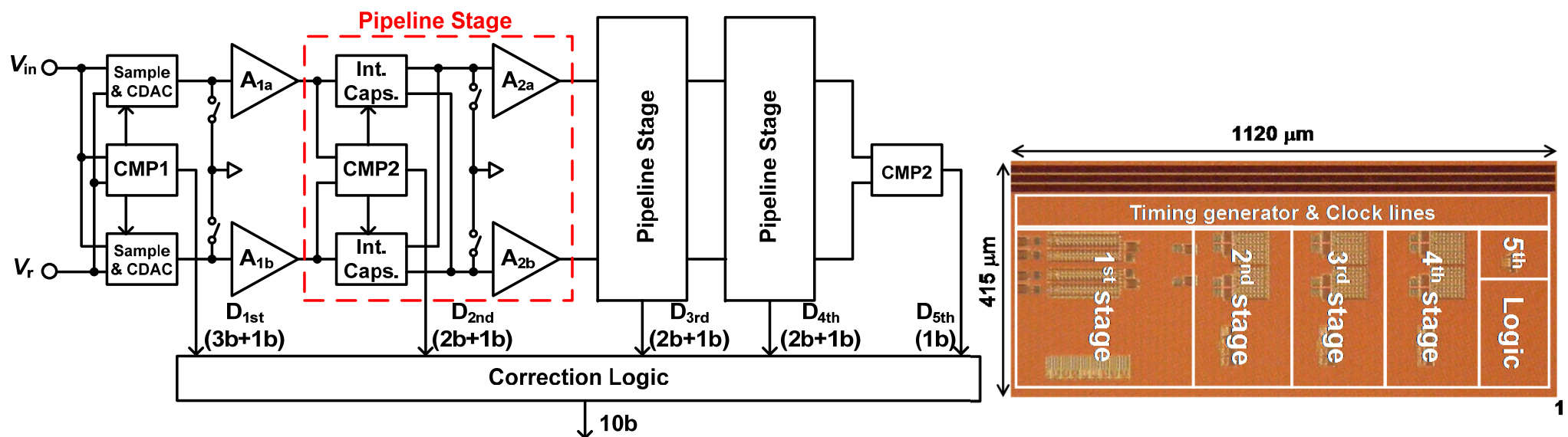
Suitable for low gain and low V_{DD} scaled CMOS



Pipelined interpolation

The interpolation can realize the fine A/D conversion.
No accurate absolute gain is required.

 
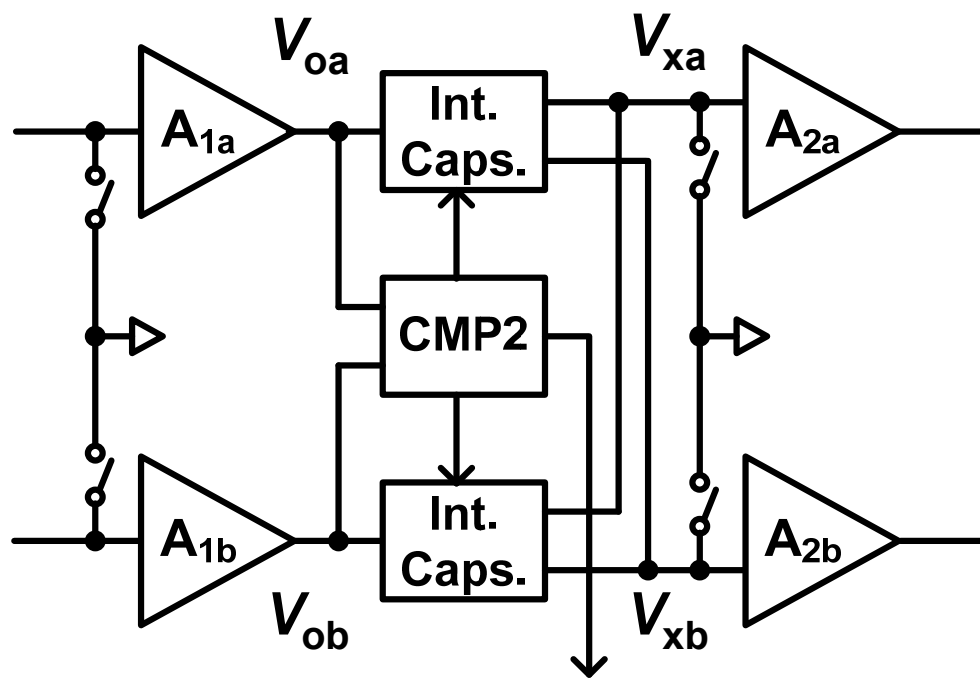
The accuracy of cross points depends the gain mismatch,
and does not depend the absolute gain



Gain of amplifiers is about 4

Proposed weight controlled capacitor array realizes accurate interpolation. Furthermore, the offset voltages of amplifiers are cancelled.
 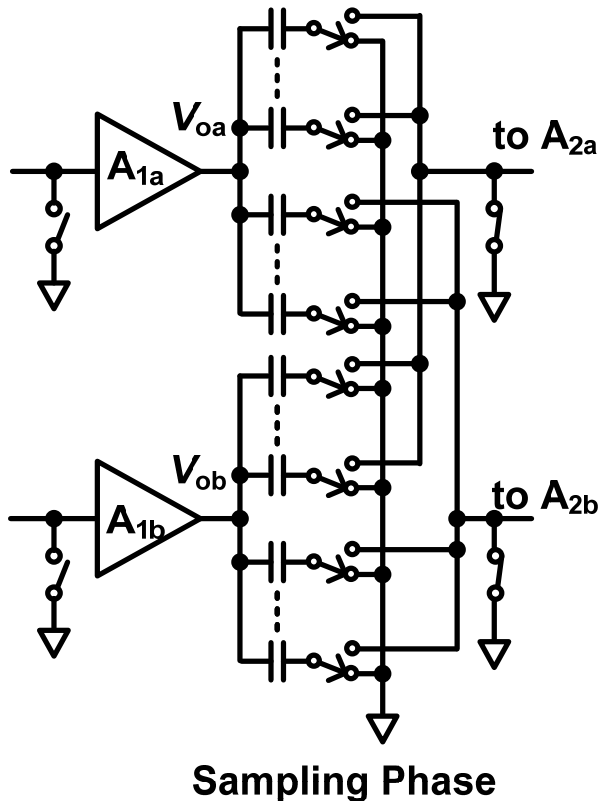
$$V_x = - \left\{ \frac{m}{m+n} G_a (V_{in} - V_{ra}) + \frac{n}{m+n} G_b (V_{in} - V_{rb}) \right\}$$




$$V_{oa} = G_a (V_{in} - V_{ra} - V_{off_a})$$

$$V_{ob} = G_b (V_{in} - V_{rb} - V_{off_b})$$

$$V'_{oa} = G_a (-V_{off_a})$$

$$V'_{ob} = G_b (-V_{off_b})$$

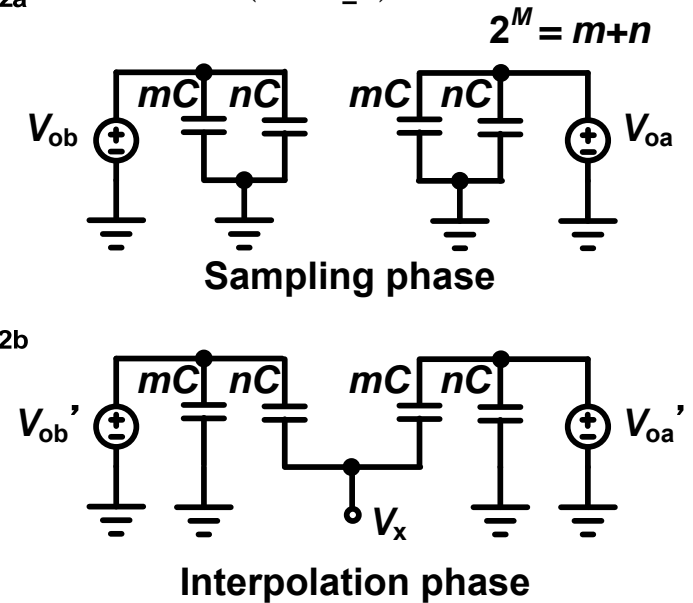



Low gain Amplifier

74

1st stage amplifier require good linearity
=>CMOS input with source degenerations

$$G = 4$$
  
$$\text{Gain mismatch} < 2.1\%(3\sigma)$$



Performance summary

	This Work	[2]	[6]	[7]
Resolution (bit)	10	10	10	10
F_{sample} (MS/s)	320	500	205	320
V_{DD} (V)	1.2	1.2	1.0	-
Power (mW)	40	55	61	42
$\text{ENOB}_{\text{peak}}$ (bit)	8.5	8.5	8.7	8.7
$\text{FoM}_{\text{FS}} / \text{FoM}_{\text{ERBW}}$ (pJ/c.-s)	0.35 / 0.77	0.31	0.65	0.36/0.44
Technology (nm)	90	90	90	90
Active Area (mm ²)	0.46	0.5	1	0.21
Amplifier type	Open	Closed	Closed	Closed
Linearity Compensation	No	Yes	No	Yes


[2] A. Verma and B. Razavi, IEEE J. Solid-State Circuits, vol. 44, Nov., 2009.

[6] S. Lee, Y. Jeon, K. Kim, J. Kwon, J. Kim, J. Moon, and W. Lee, "ISSCC, 2007.

[7] H. Chen, W. Shen, W. Cheng, and H. Chen, A-SSCC, 2010.

Sigma-delta ADC

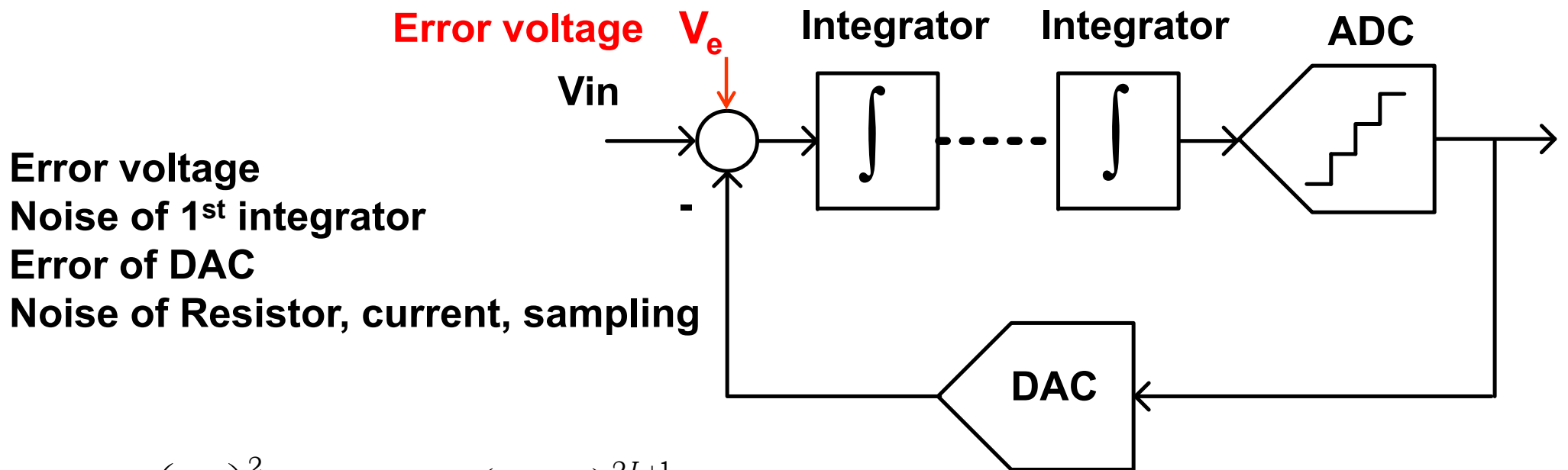**Sigma delta ADC can suppress only the quantization noise of ADC.
The performance is limited by the input error voltage.
For wide band signal, SD ADC may not be efficient architecture.**



**Error voltage
Noise of 1st integrator
Error of DAC
Noise of Resistor, current, sampling**


$$N_q = \left(\frac{V_q}{2}\right)^2 \frac{1}{3\pi(2L+1)} \left(\frac{\pi}{OSR}\right)^{2L+1}$$

Quantization noise can be suppressed so much

$$V_{e_eff} \approx \frac{V_e}{OSR}$$

Error voltage at input summing node can't be suppressed so much. Suppressed by only OSR.

 SNR and Power dissipation of wide band (multi-bit) SAR ADC are Not attractive. SAR ADC will reach the SNR and exhibit very low power consumption.




SAR Pipelined ADC



For wide fb and high SNDR ADC, SAR-Pipelined ADC is very attractive.

It can relax the requirement of settling time and noise of comparator

10bit, 500MSps, 8.2mW, FoM of 34fJ

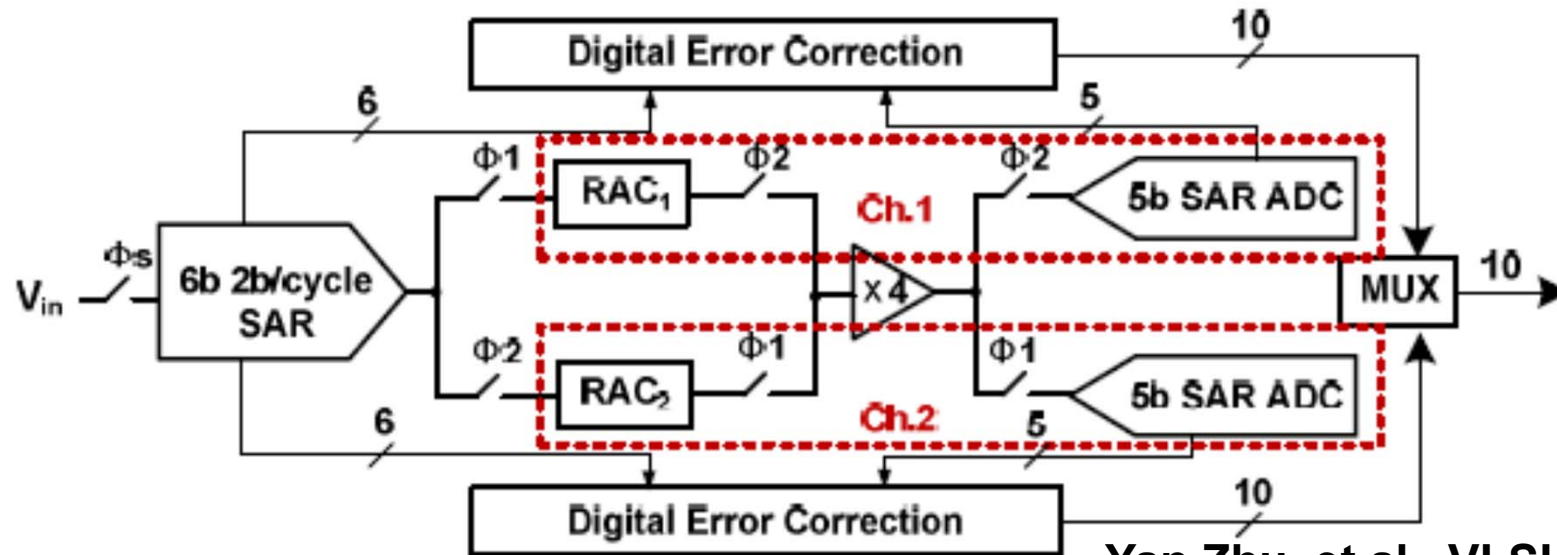

Yan Zhu, et al., VLSI Circuits, 2012

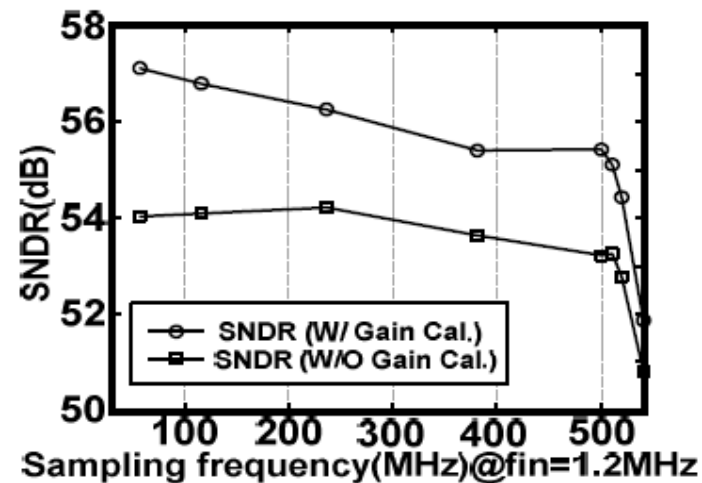 

Macau univ.

-
- **60GHz CMOS Transceiver has been realized**
 - **Technology scaling increases operation frequency to several 100GHz**
 - **Accurate device modeling is very important**
 - **Wide band width with proper matching and low phase noise of high frequency oscillator are required for high speed data transfer.**
 - **Injection locking method is very innovative method to generate low phase noise high frequency signals and to realize frequency divider.**
 - **Accurate phase control, address the HCI issue are next challenge.**

-
- **Flash ADC**
 - Smaller is the better for Low FoM
 - Digital mismatch compensation tech. should be used
 - **SAR ADC**
 - Concern the comparator noise
 - Remind the tradeoff (Noise, speed, power)
 - Take care of reference circuits
 - **Pipelined ADC**
 - Proposed interpolated pipeline ADC offers good solution
 - **Future of ADC**
 - ADCs will be unified by SAR ADC.