

Anatomy of Innovation: Bug or Feature?


“Interpolation techniques” in ADCs

Akira Matsuzawa

Tokyo Institute of Technology


Bug triggered to find the “interpolation”

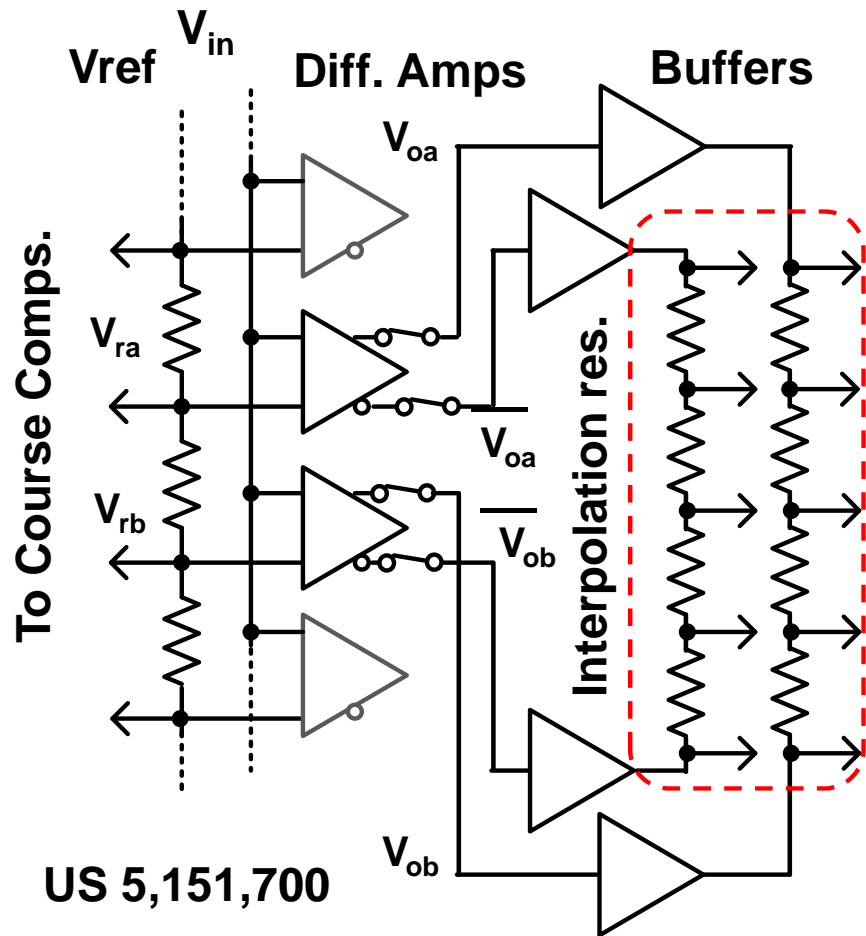Bug!! { I have **failed** to develop a sub-ranging ADC.
I had only **Three weeks** from idea to tape-out for the new ADC.
I founded the most **robust** ADC architecture; “Interpolation”



Compare the two signals (Reference is involved)

Free from the course-fine gain matching

 

A. Matsuzawa, et al., “A 10b 30MHz Two-Step Parallel BiCMOS ADC with Internal S/H,” ISSCC, pp.162-163, Feb. 1990.


The original interpolation technique in ADC must be R. E. J. Van de Grift, et al., J.S.C. pp. 944-953, Dec. 1987.

Feature reveals the essence of “interpolation”

The interpolation is **not the equal division** between the two voltages, but **the internal division; weight and sum** of the two values.

Many implementation methods are possible


Internal division method

 


Essence
weight and sum

$$x = \frac{na + mb}{m + n}$$



Capacitive method is possible

 

$$V_x = \frac{nV_a + mV_b}{m + n}$$

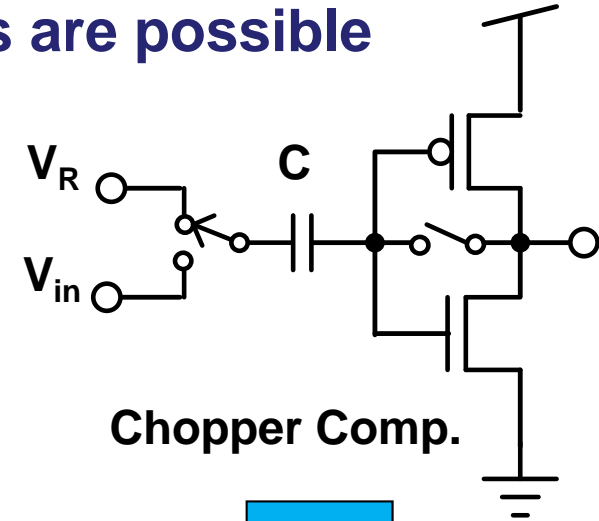


Chopper Comp.

  

Interpolated chopper Comp.

Invention of the capacitive interpolation

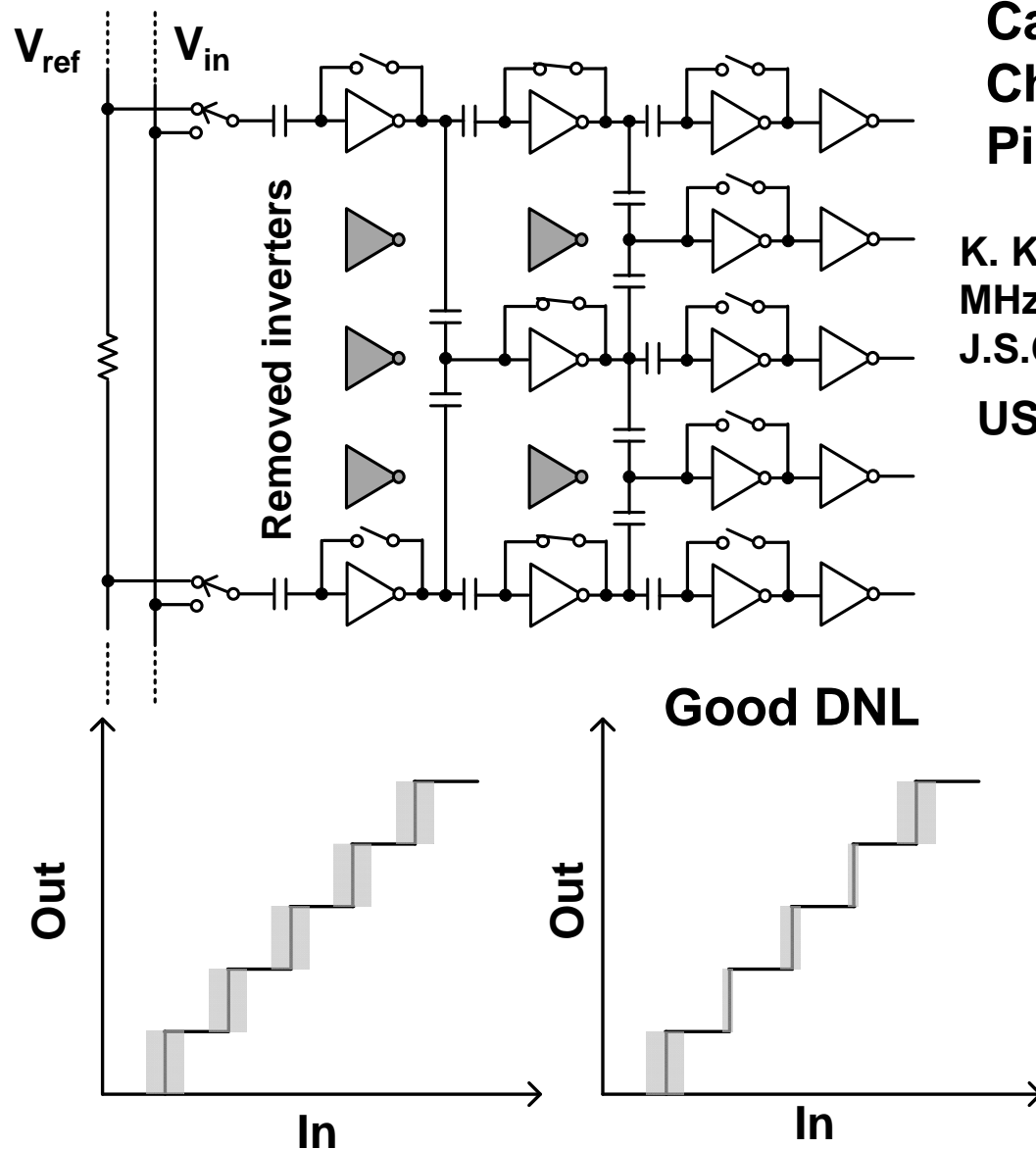An ultra-Low FoM CMOS 10b ADC (1/8 to others) has been realized.




Capacitive interpolation
 Chopper comparator
 Pipelining

K. Kusumoto, A. Matsuzawa, K. Murata, "A 10-b 20-MHz 30-mW Pipelined Interpolating CMOS ADC," J.S.C., pp.1200-1206, Dec. 1993. ISSCC 1993.

US 5,465,093

FoM of 10b ADC

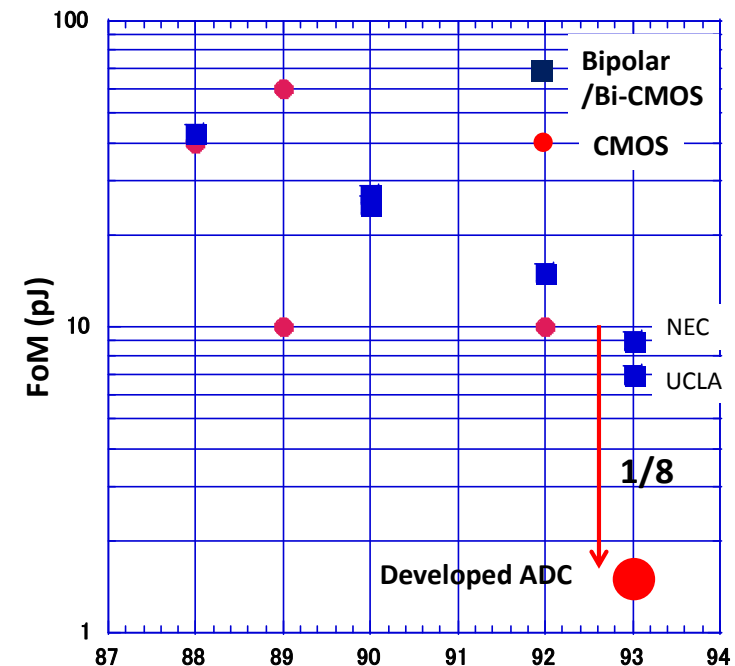

Gate-width weighted interpolation


Gate-width can be used for the weighting

Array of gate-width weighted dynamic comparators with preamplifiers realizes high speed and low power ADC

Effective threshold voltage condition


$$W_1 V_{o1} + W_2 V_{o2} > W_1 \bar{V}_{o1} + W_2 \bar{V}_{o2}$$

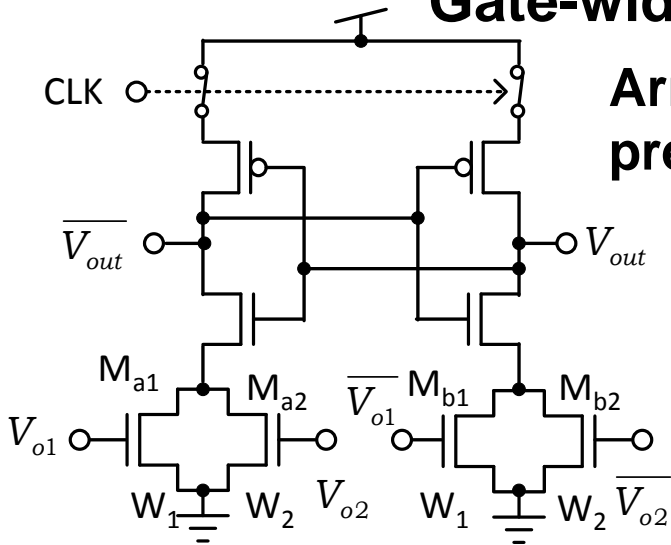An ultra-low power (1/10 to others) and high speed ADC




T. B. Cho and P. R. Gray, "A 10b 20 Msample/s, 35 mW Pipelined A/D Converter," J.S.C, pp166-172, March 1995.

But, no use for the interpolation

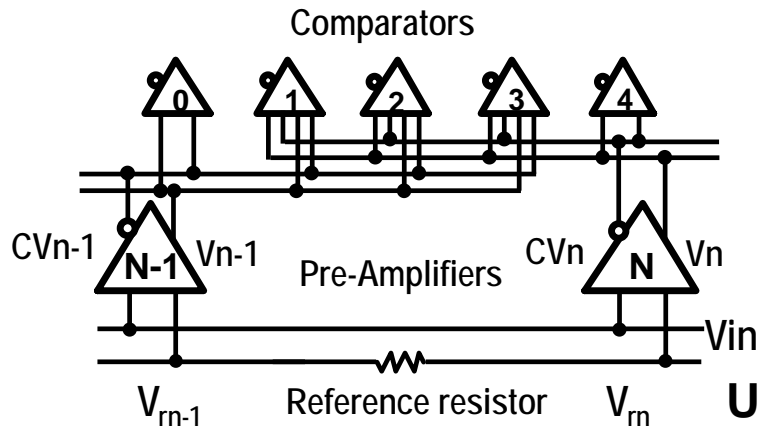

US 6,707,413 B2

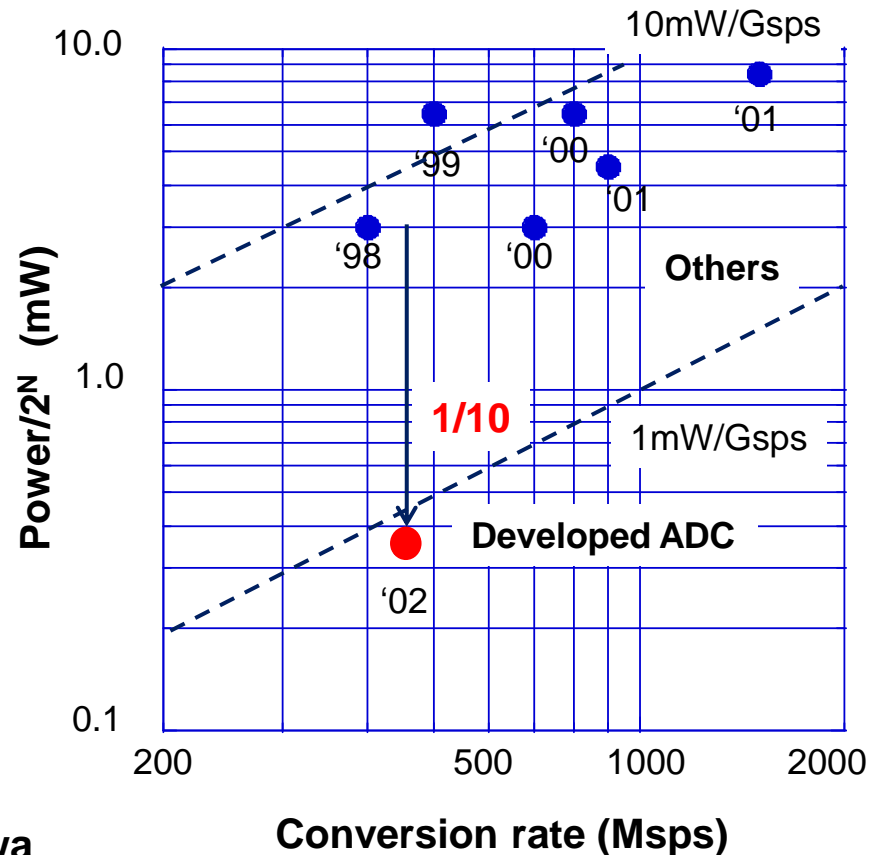K. Sushihara, A. Matsuzawa, "A 7b 450MSample/s 50mW CMOS ADC in 0.3mm²," ISSCC 2002.



- **Bugs** are always the **triggers** for innovative ideas.
 - unexpected bad result, a failure of development, a high pressure for development schedule, and tough performance targets
- The innovative ideas are **created from the logical thinking**. Seeking the **essence** of technology leads us to the novel view.
 - What is an analog to digital conversion?
 - Why a reference voltage is needed?
 - What is an interpolation?
- High level **abstraction** of the system, such as mathematical model sometimes **reveals the essence**. If we can find it, we can create many implementation methods easily.
- The other important factor is a **sense of beauty**. I believe an essential feature is always beautiful.