 


Digitally Assisted Wireless Transceivers and Synthesizers

Kenichi Okada

Tokyo Institute of Technology




Outline

- ➔ • **Analog to Digital**
 - **Digitization of Wireless TRX**
- **Digital Assistance**
 - **Wireless Transceiver**
 - **Frequency Synthesizer**
- **Future Analog Design**
 - **Synthesizable Analog**

Analog to Digital

Digitization

- Scalability
- Portability

 


Digital Assistance

- Robustness
- Less redundancy

Further Digitization

Digitization

- Scalability
- Portability

 

Massive Digital Assistance

- Robustness
- Less redundancy

Case Study

**Partially replaced by pure digital-domain “calculation”
(NOT time-domain analog processing)**


- Filter: LPF in AD-PLL, LPF in wireless TX
- Equalizer: FIR in wireless, OFDM
- PLL: carrier and timing recovery in wireless RX
- Mixer: Low-IF transceiver

Only analog-domain

- Oscillator: Clock generation
- Data converter: V-to-D, D-to-V, D-to-I, C-to-D,..
- Analog amplifier: voltage-to-voltage

↓
Difficult for digitization


History of Timing Recovery

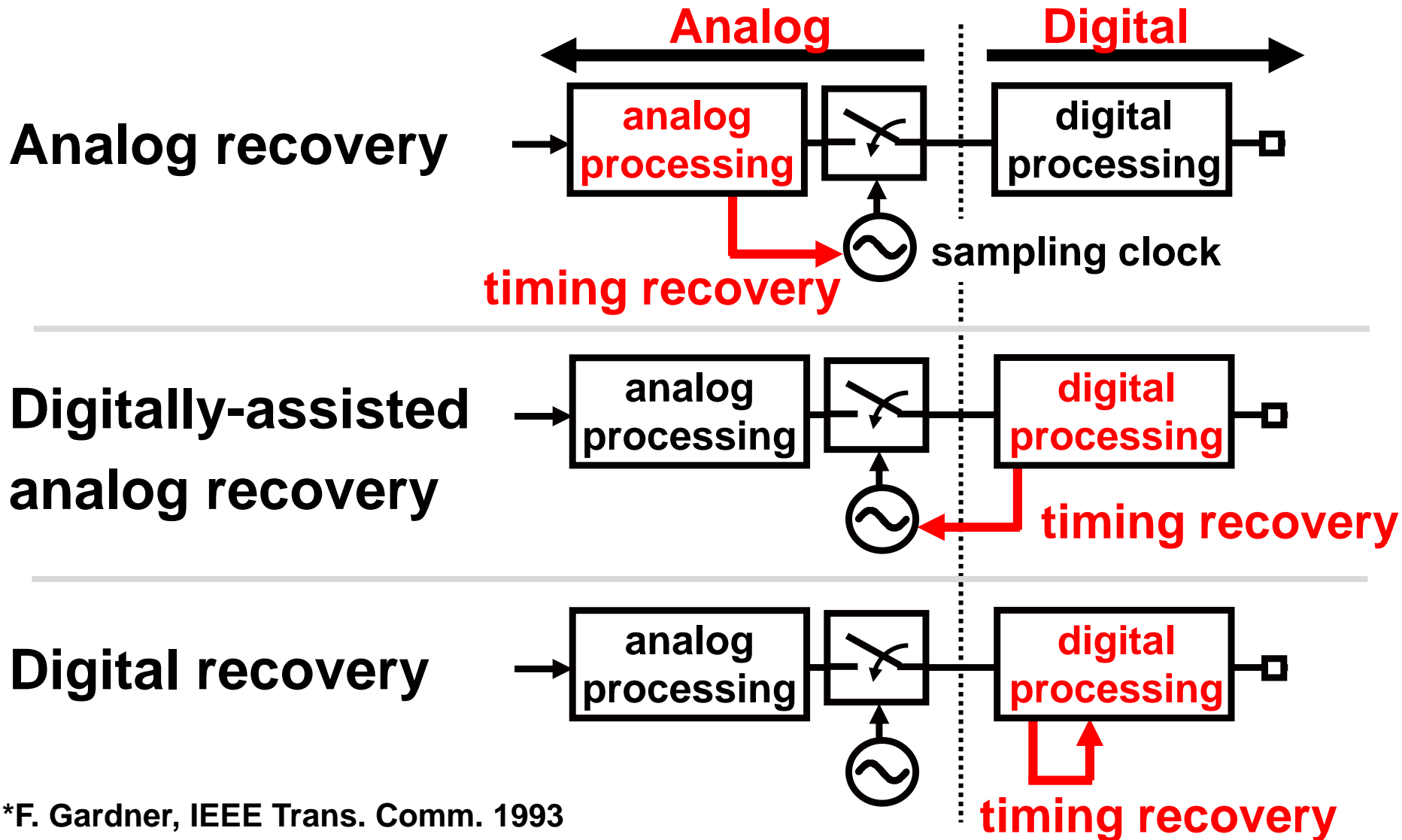

*F. Gardner, IEEE Trans. Comm. 1993

Analog Demodulator

Costas-loop for BPSK

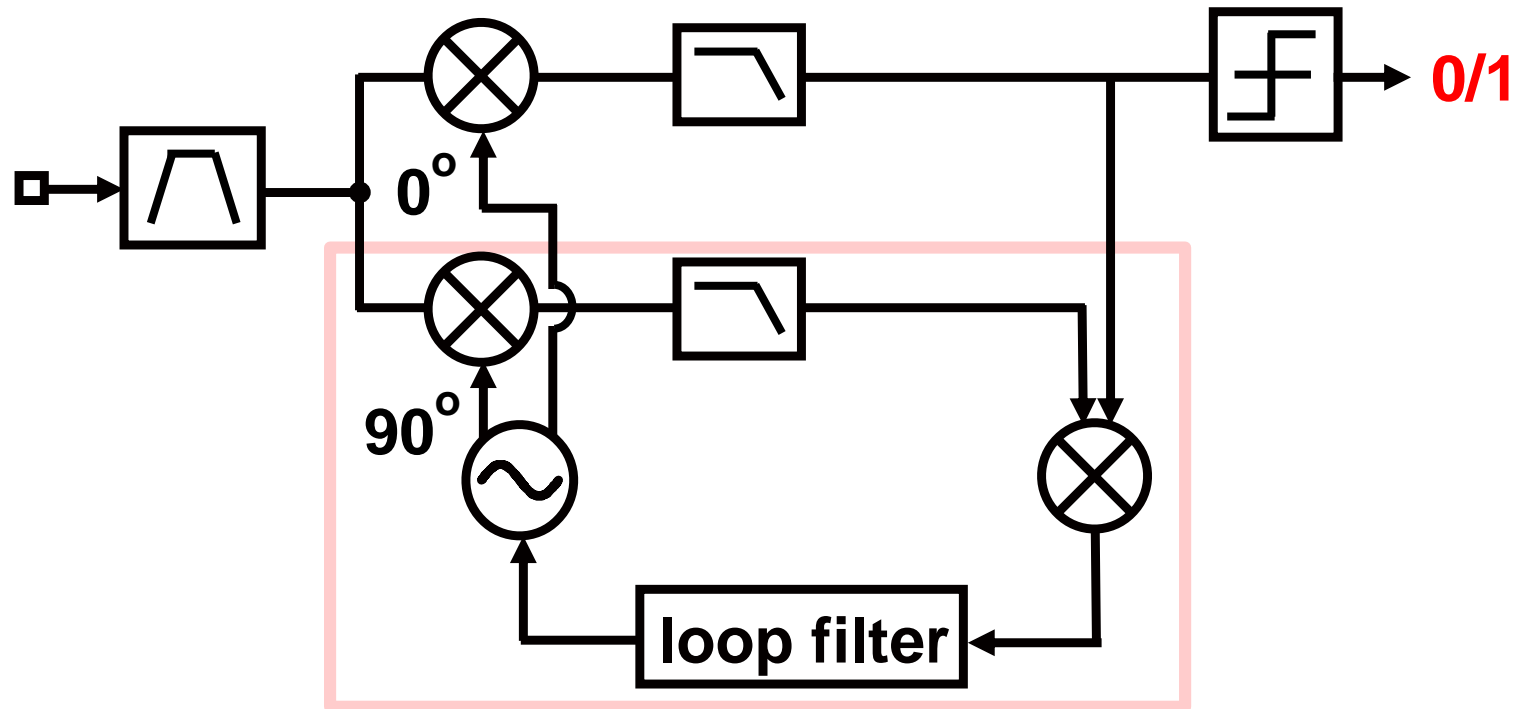

timing recovery loop (carrier & phase)


*H. Suzuki, *et al.*, IEEE Trans. VT 1985

Digital Carrier and Timing Recovery

Everything is implemented in digital domain.

timing recovery (phase)

carrier recovery (freq.)

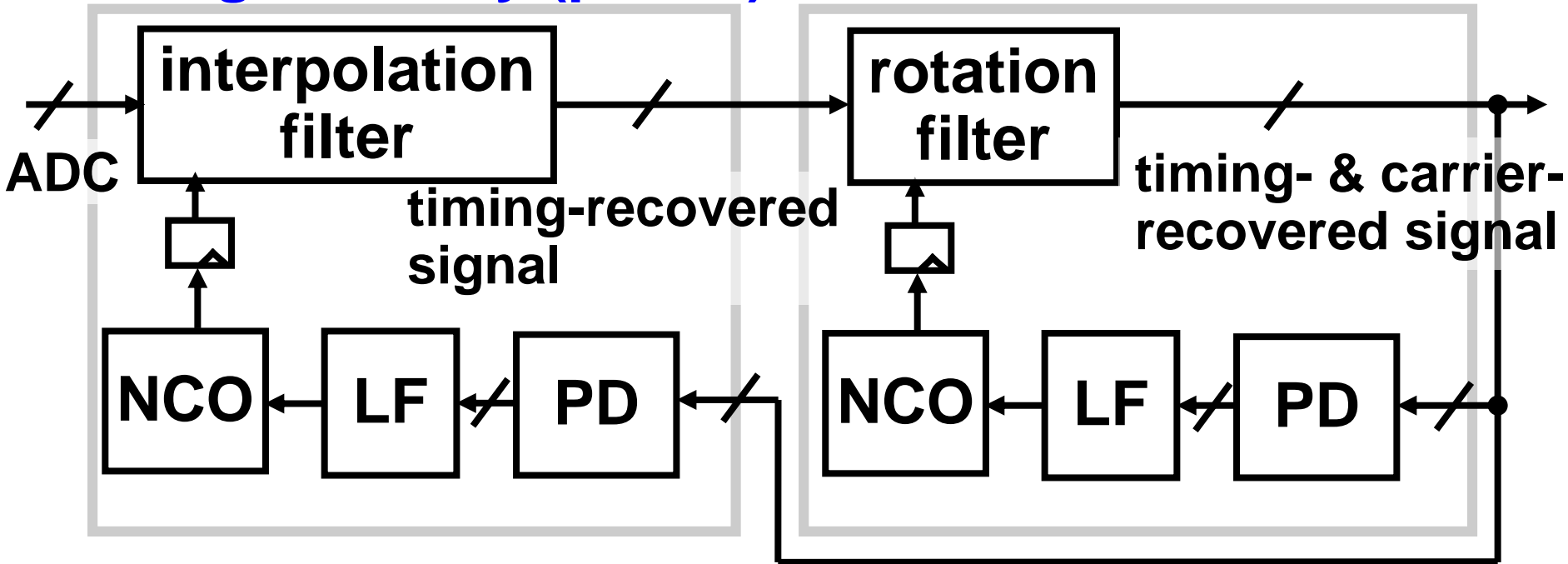


NCO: Number-Controlled Oscillator
LF: Loop Filter
PD: Phase Detector

*F. Gardner, IEEE Trans. Comm. 1993

Recent Digital Transceiver

Analog

Digital

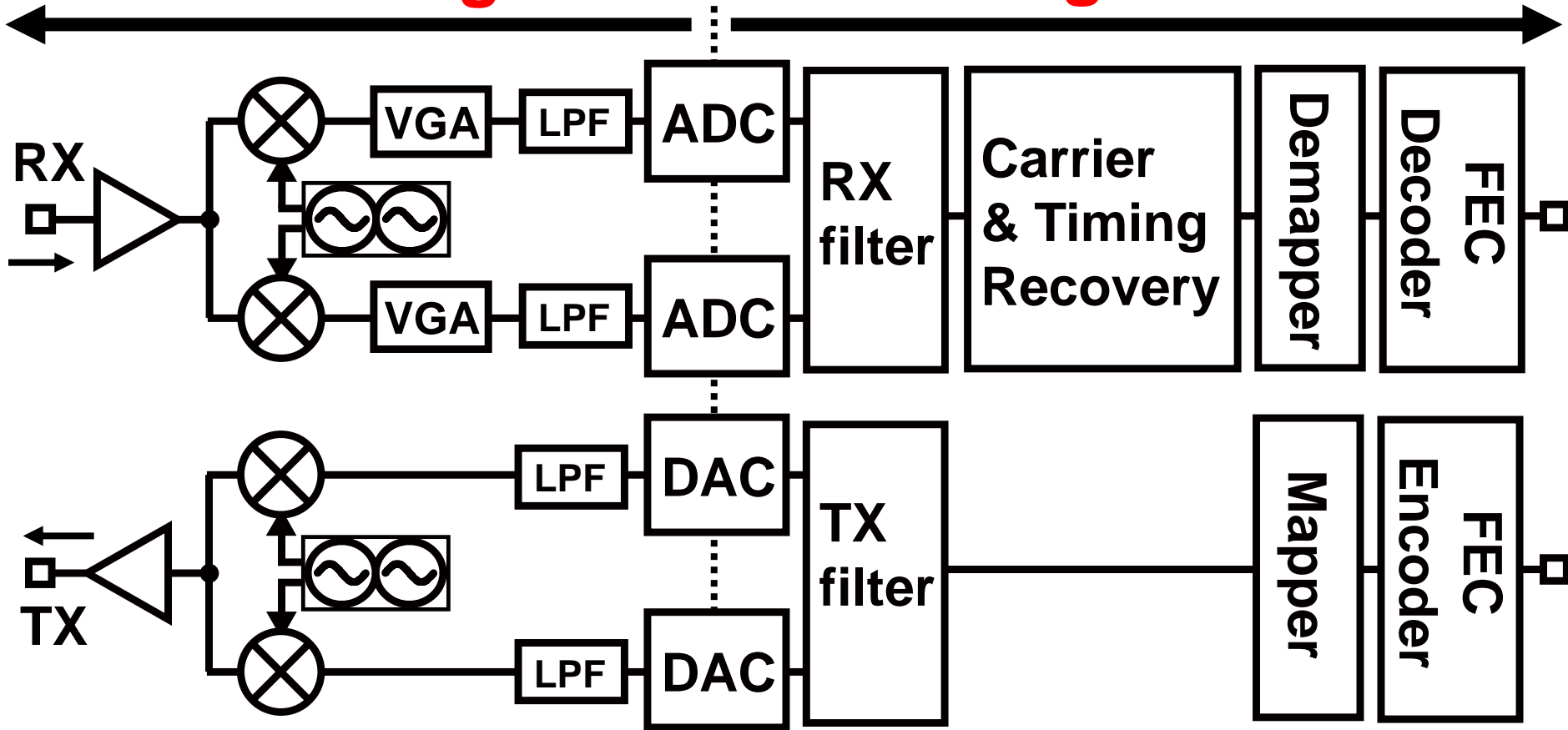


Zero-IF

Digital LPF in Wireless

Analog

Digital

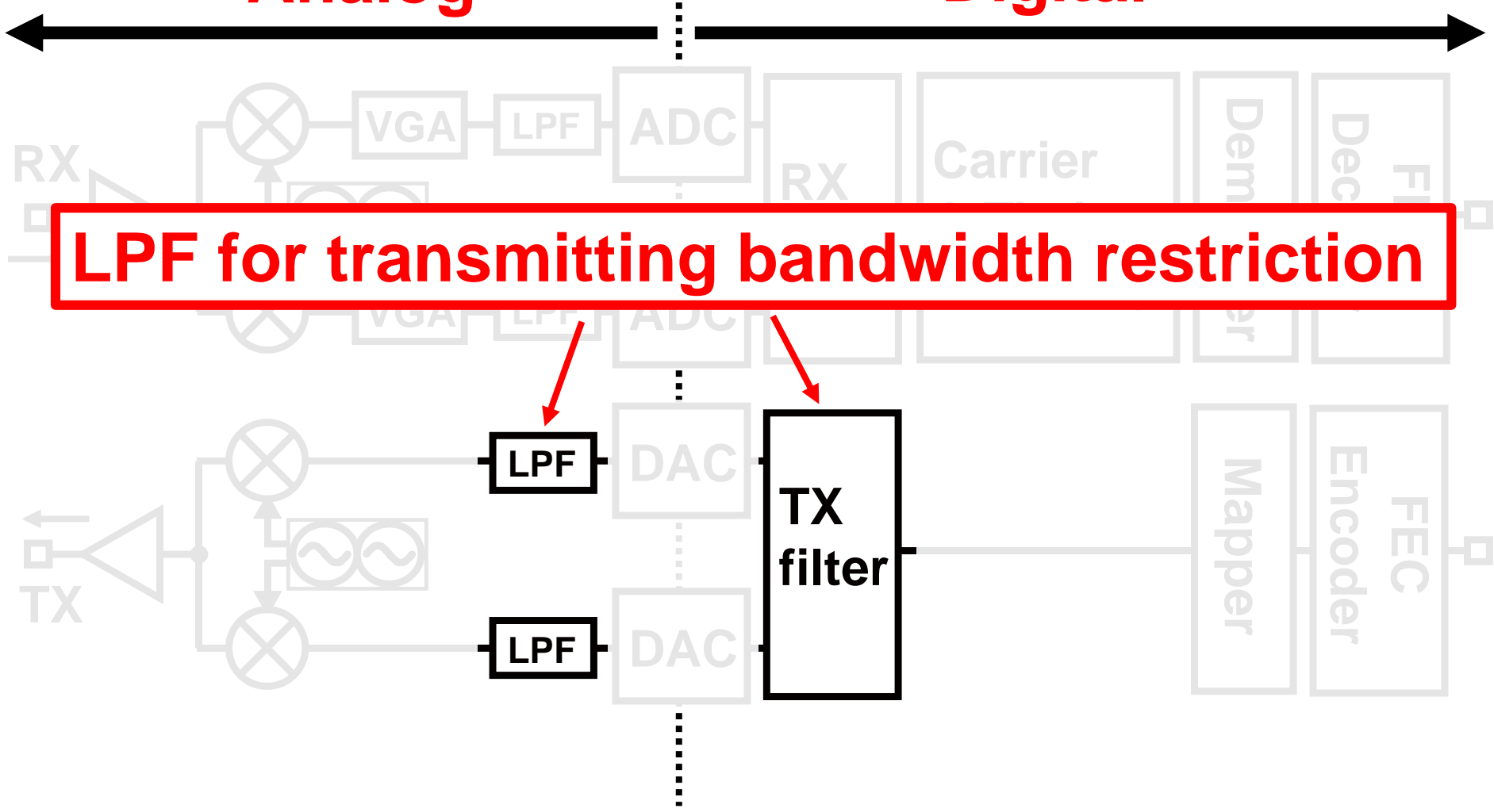


LPF for transmitting bandwidth restriction

Digital Equalizers in Wireless


Analog

Adaptive RF&BB equalizer

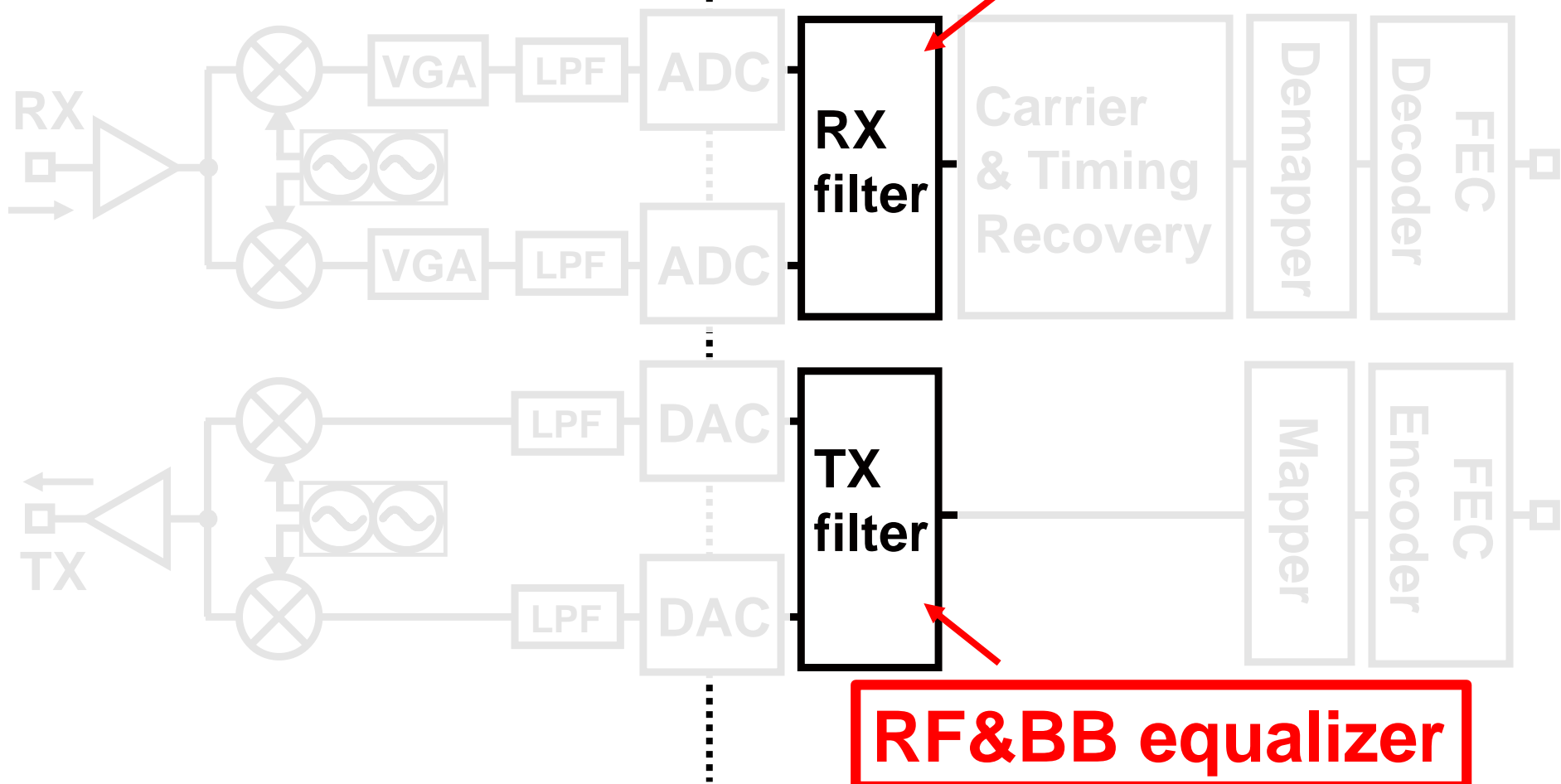


Digitization of IF Mixer

Hetero-dyne RX

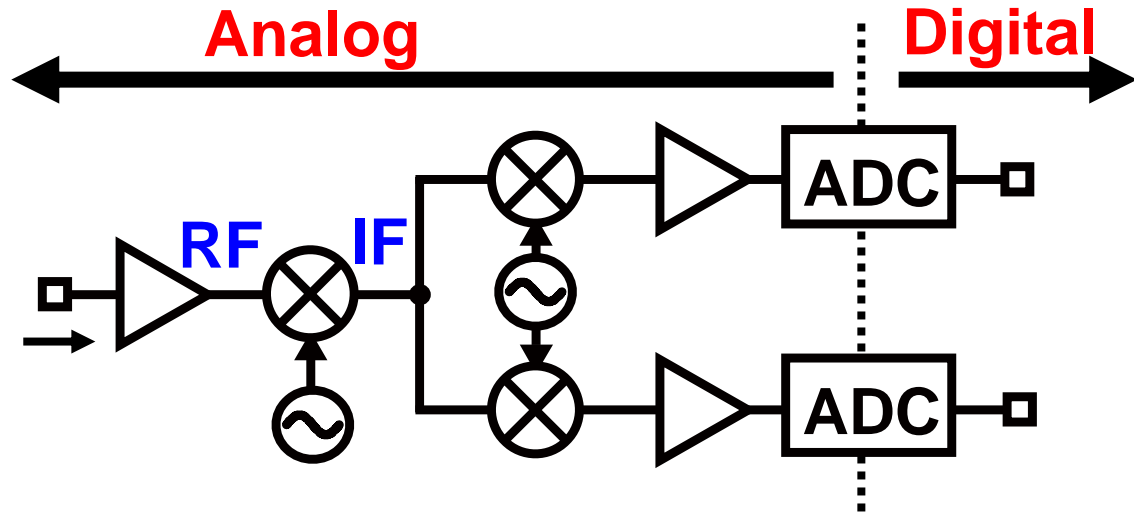

Low-IF RX

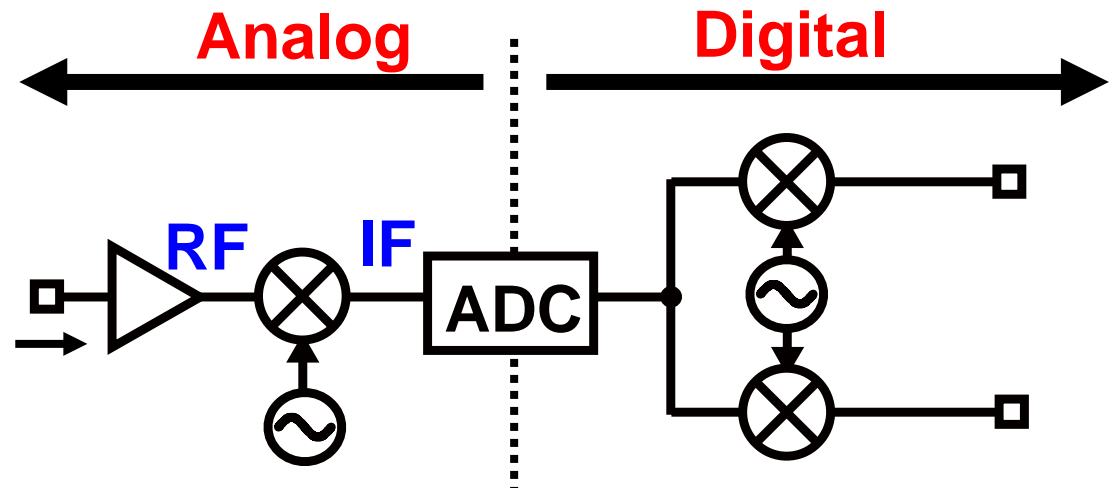Very common for BT
1/f noise
Overhead for ADC



Aim of This Talk

- **Digitization**

- Wireless transceiver is a good example of digitized analog circuit. (for hinting)

- **Digital assistance**

- Digital calibration/compensation is implemented in a system level to satisfy complicated requirements for wireless system.
- Mutual re-use of TX and RX for calibration

- **Digitally-designed analog**

- **Toward “Synthesizable Analog Circuit”**

Outline

- **Analog to Digital**
 - **Digitization of Wireless TRX**
- **Digital Assistance**
 - ➔ • **Wireless Transceiver**
 - **Frequency Synthesizer**
- **Future Analog Design**
 - **Synthesizable Analog**

Impairments in Wireless Transceiver

Mismatch in differential block

- DC offset in RX
- IIP2 in RX
- LO leakage in TX

Mismatch btw I and Q blocks

- Image signal
- Analog filter BW (LPF)

Non-linearity

- IMD in PA

PVT variation

- Gain control
- Power control
- VCO LC tank
- ILFD/ILO

Environmental variation

- TX-to-RX distance
- Fading
- Antenna reflection

*A. Jerng, "Digital Calibration for RF Transceivers," ISSCC 2012, Tutorial 9

Digital Equalizers

Analog

Adaptive RF&BB equalizer

Environmental Variation
Fading by multi-path
flat or frequency selective

RX filter

TX filter

RF&BB equalizer

Carrier & Timing Recovery

Demapper


Decoder

FEC

Mapper

Encoder


FEC

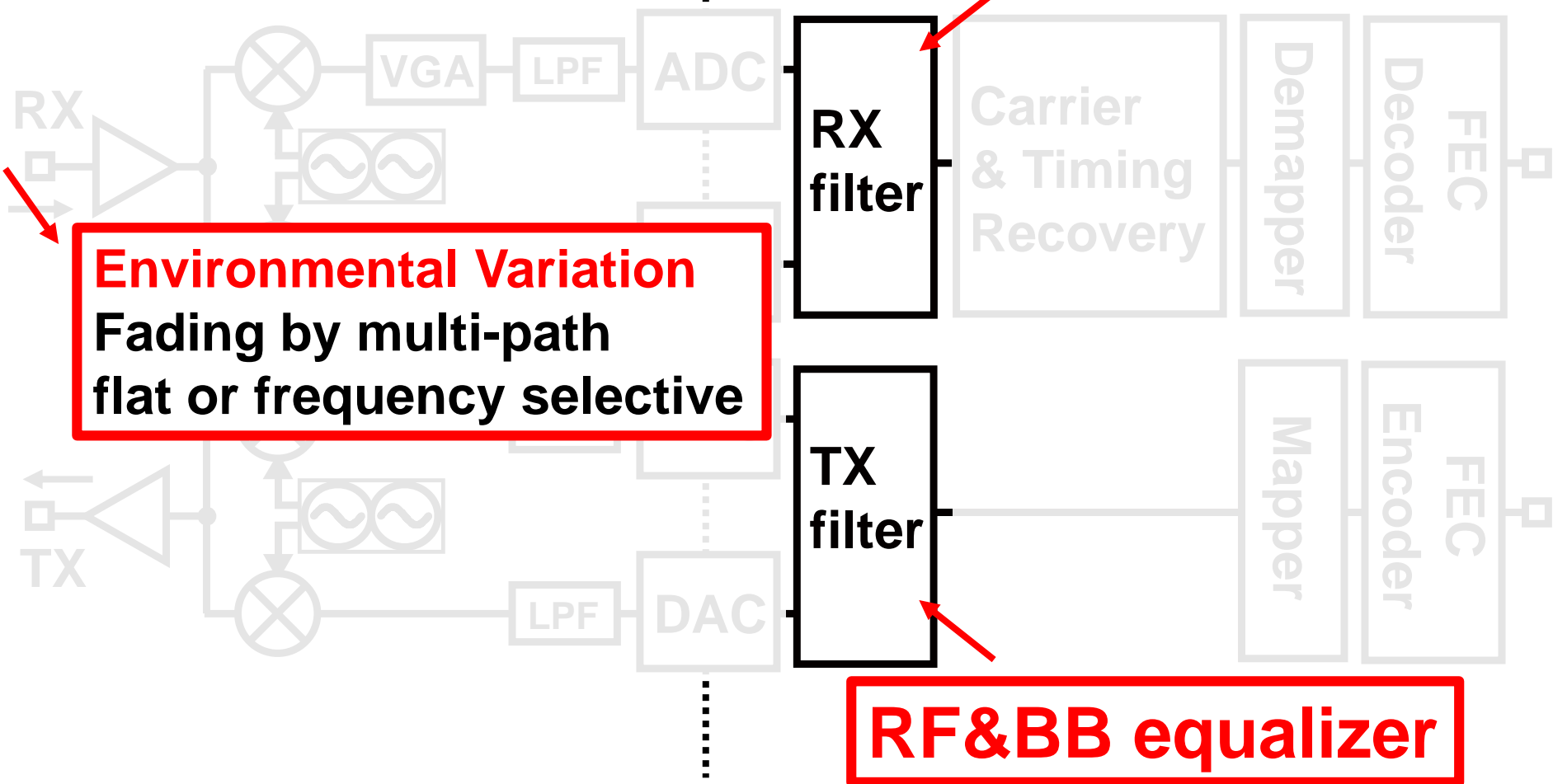

Automatic Gain Control (AGC)

Analog

Digital

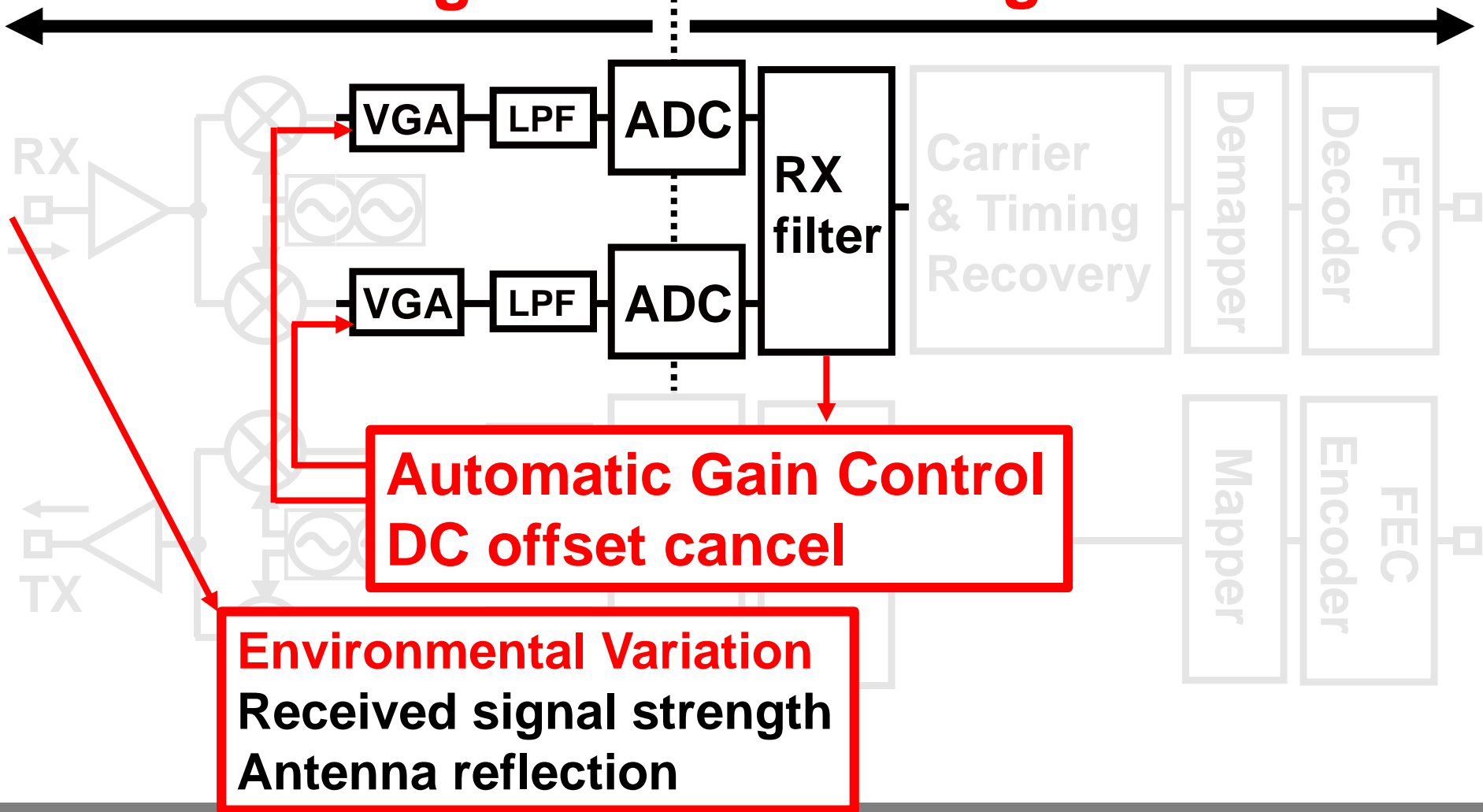

**Automatic Gain Control
DC offset cancel**

**Environmental Variation
Received signal strength
Antenna reflection**

I/Q Mismatch

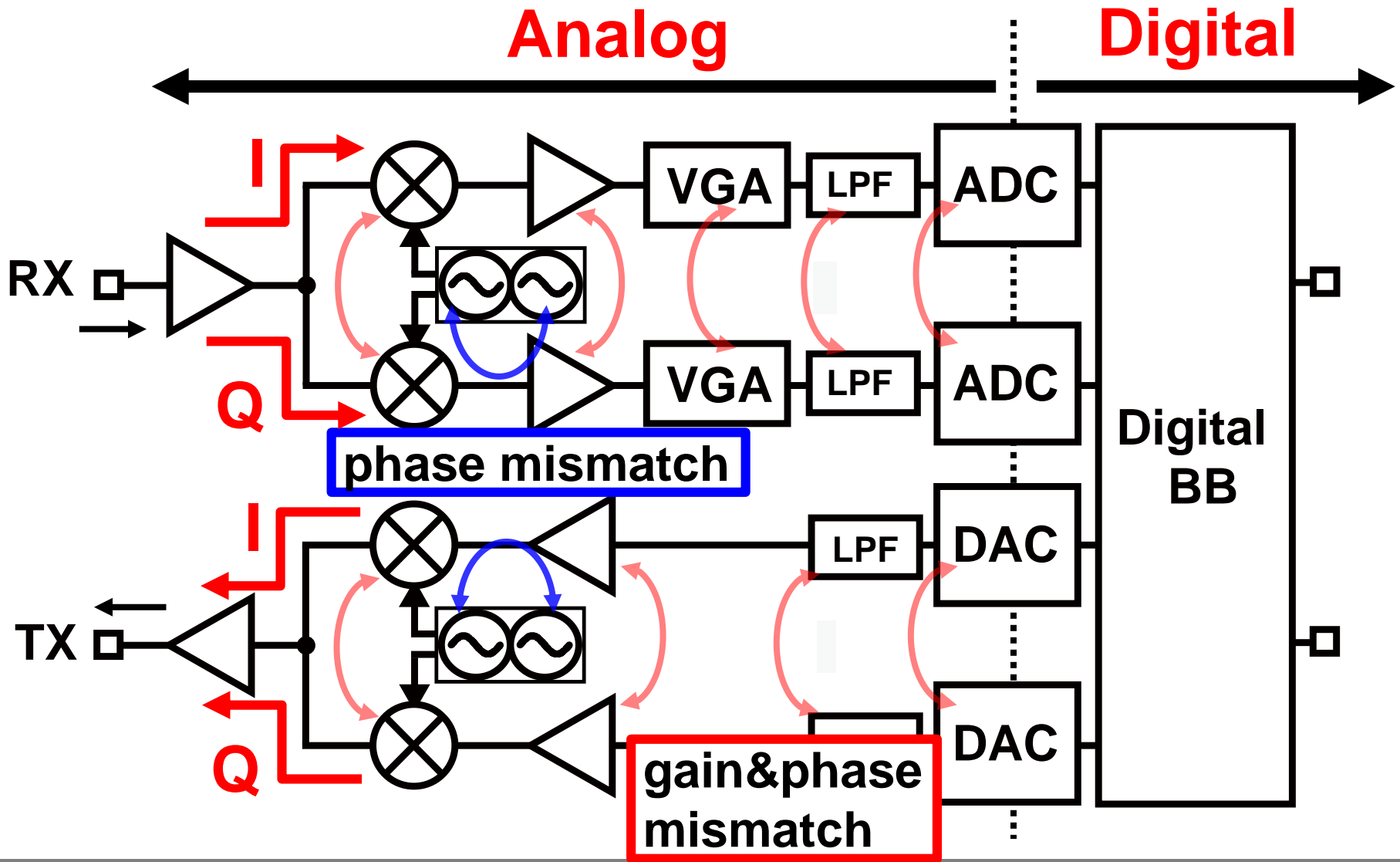


Image Rejection Ratio (IMRR)

e.g. $\omega_{\text{BB}} = 10\text{MHz}$

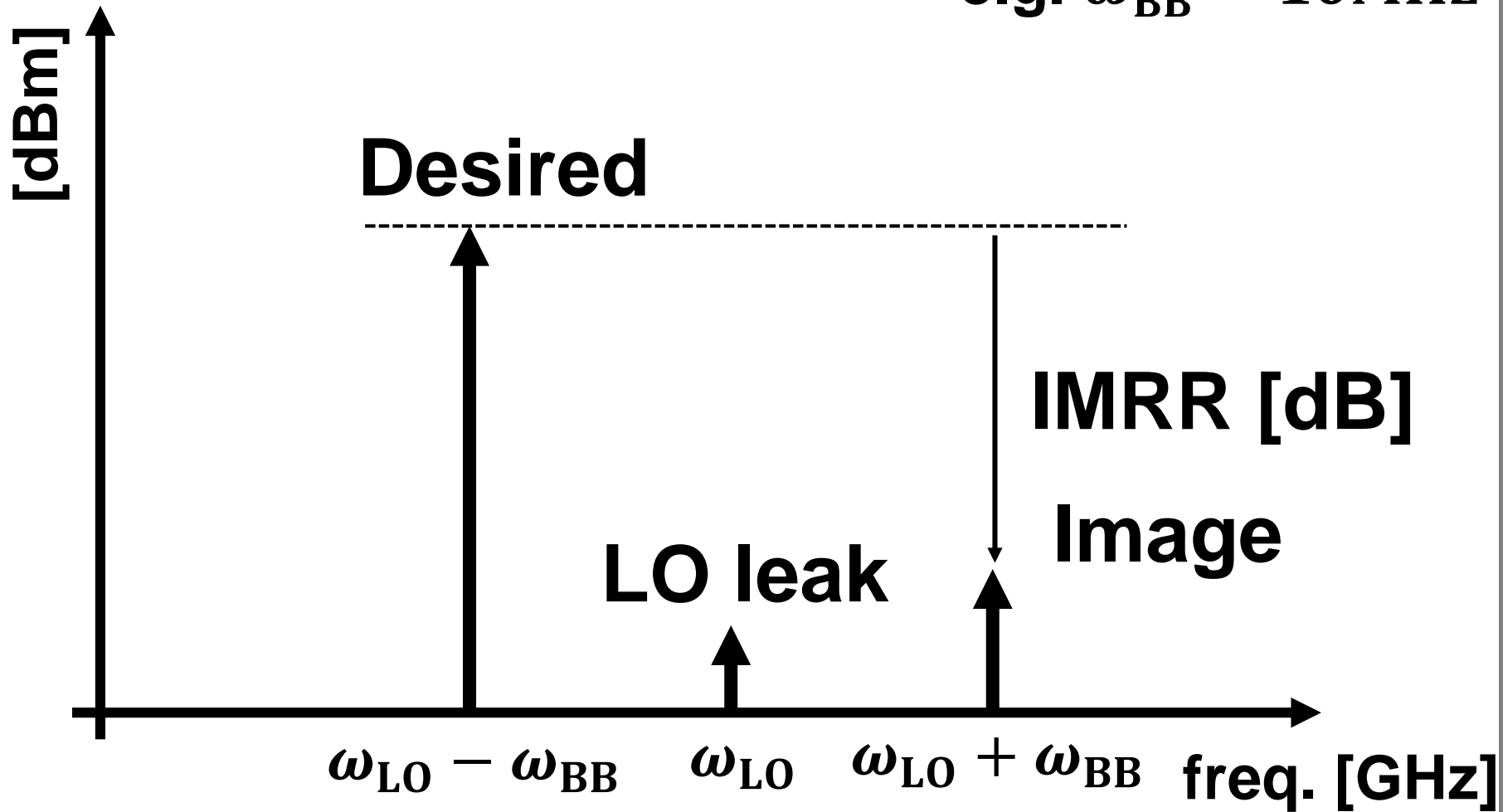


Image for Modulated Sig.

I/Q mismatch degrades SNR.


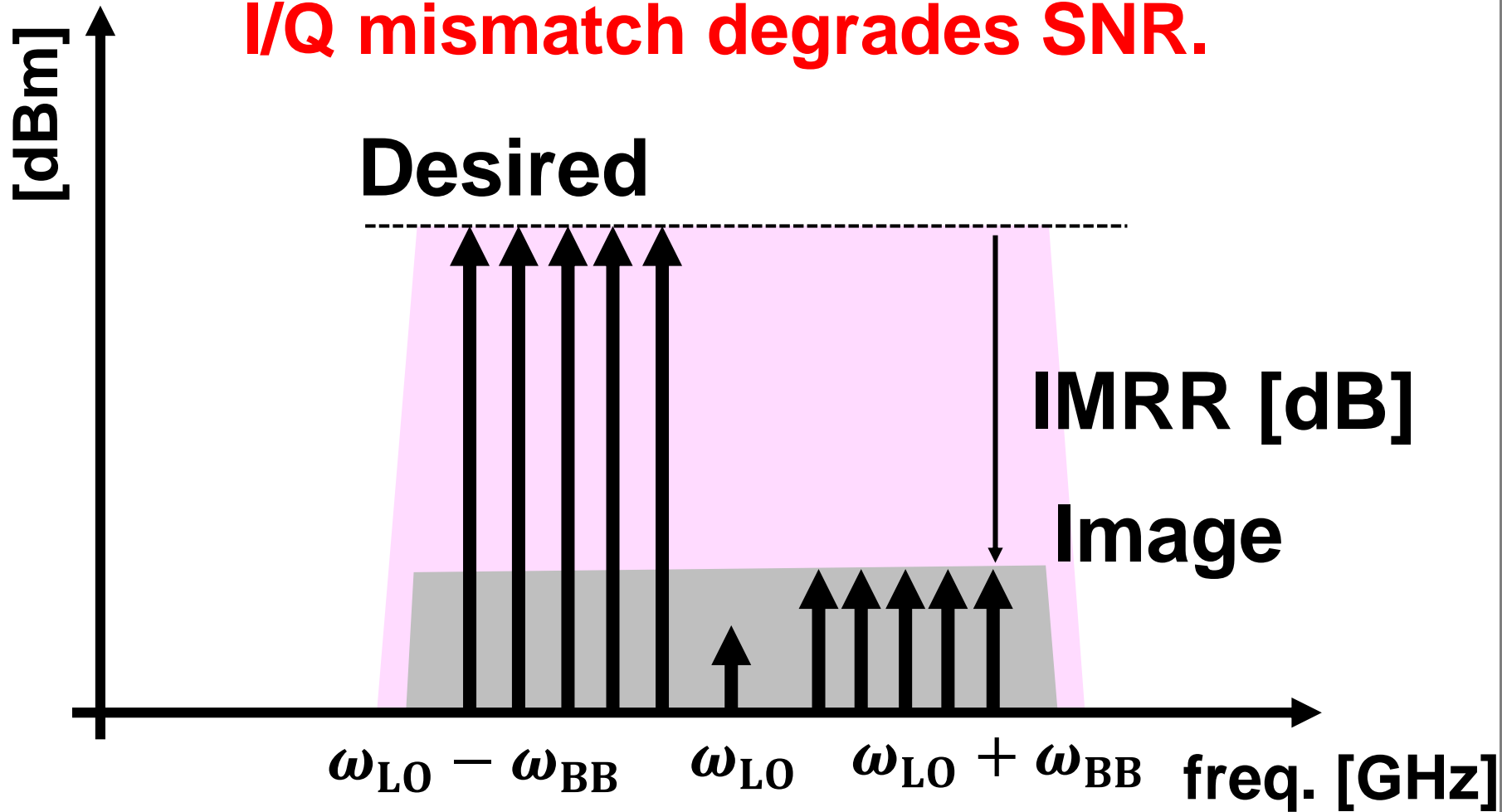


Image Rejection Ratio (IMRR)


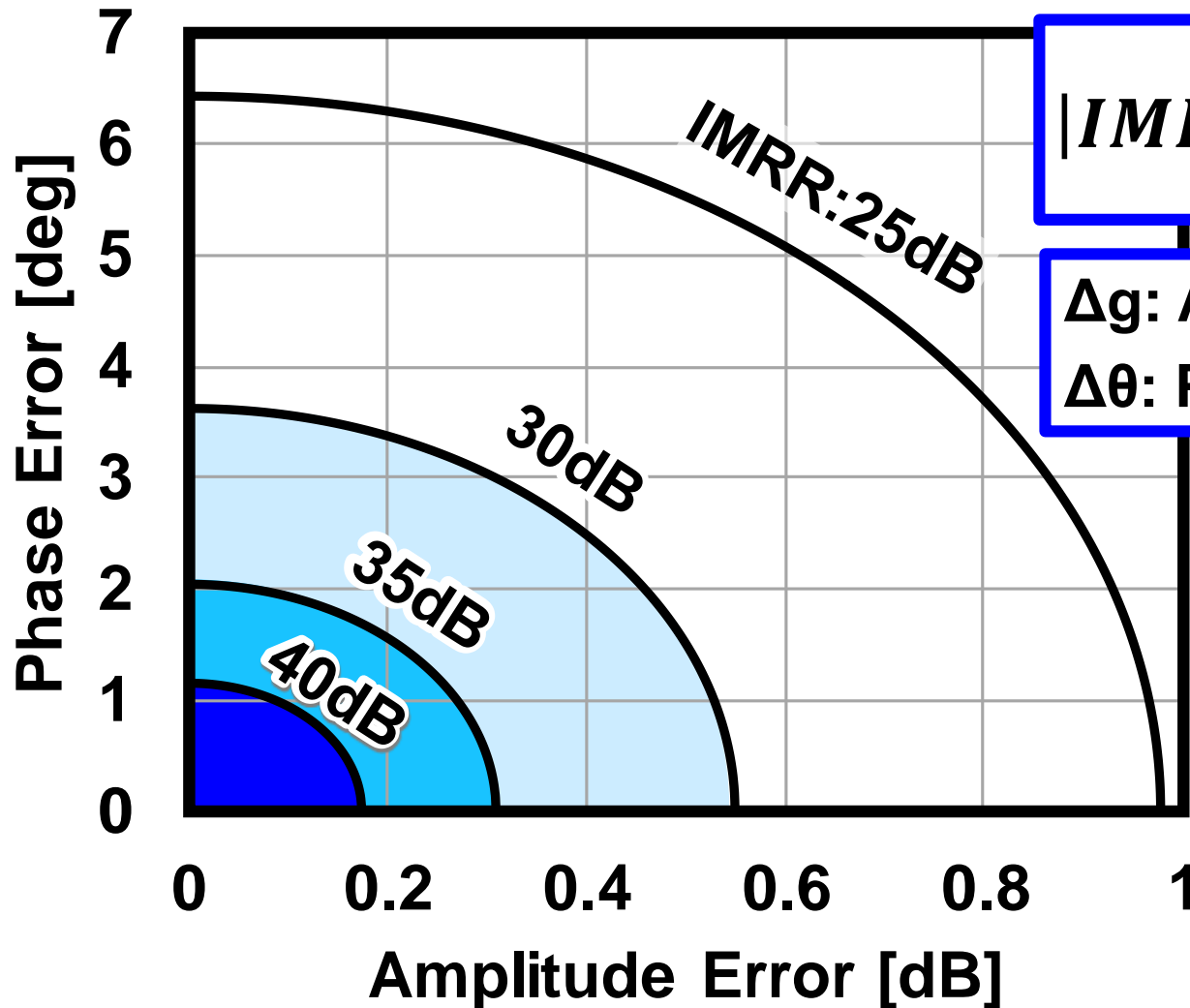


$$|IMRR| \approx \frac{|\Delta g^2 + \Delta \theta^2|}{4}$$


Δg : Amplitude error ratio
 $\Delta \theta$: Phase error

Target:
0.2dB, 1.0degree
for IMRR of 35dB

TX IMRR Calibration

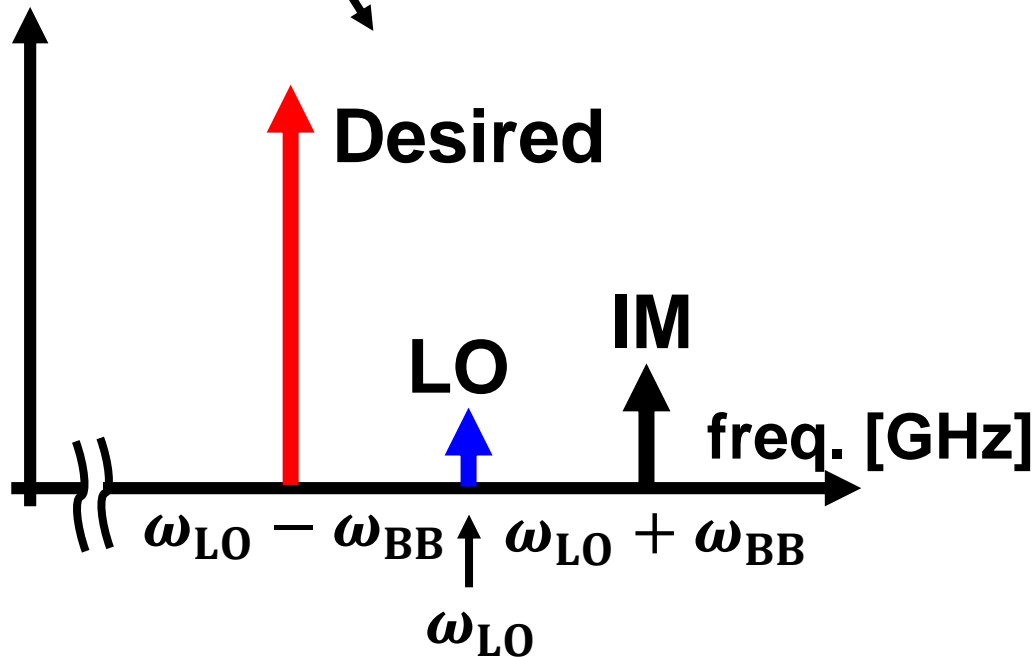 


Down-conversion is required.

 


Detector can be used.
(2nd-order distortion)


TX IMRR Calibration

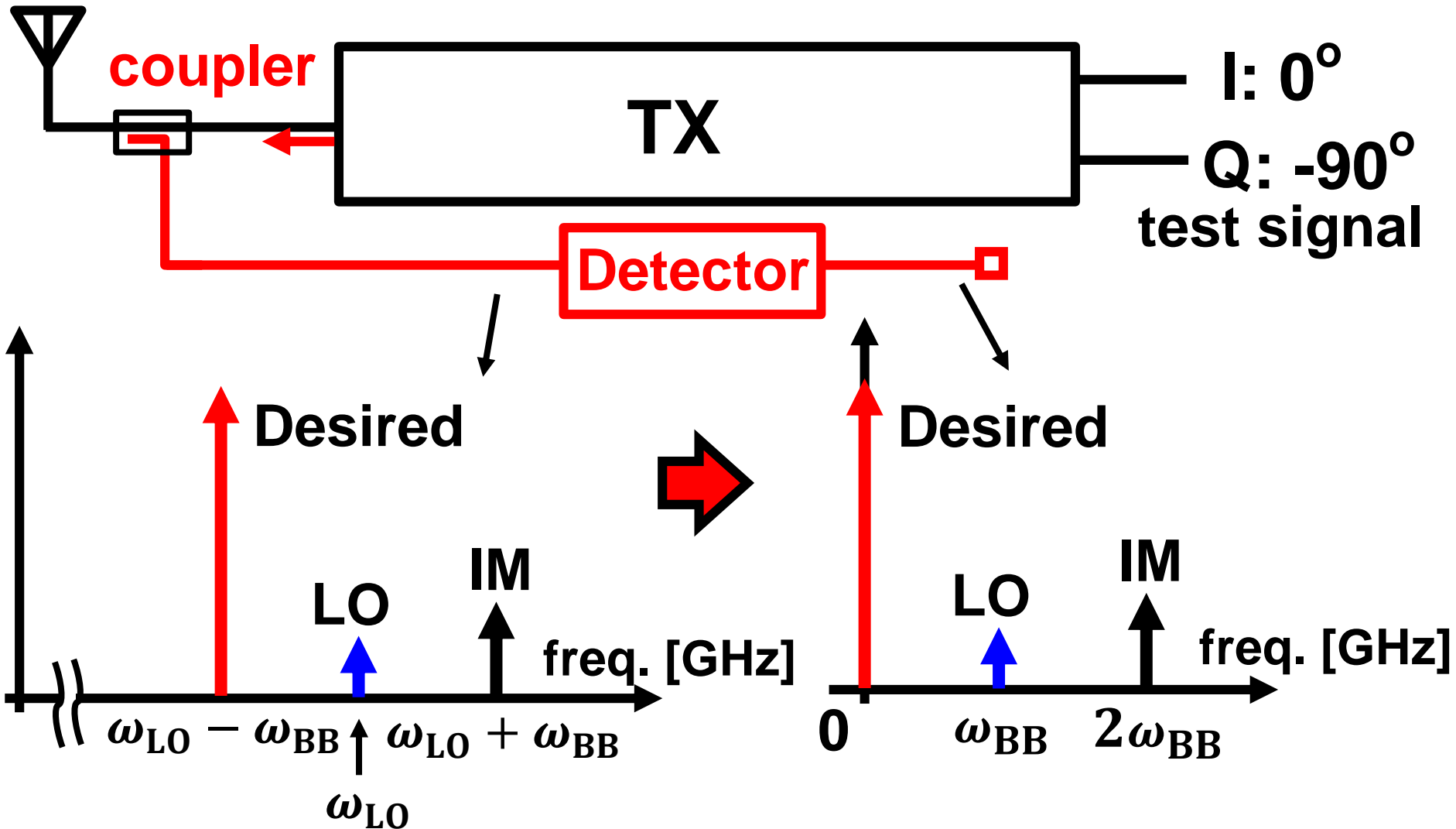

Detector

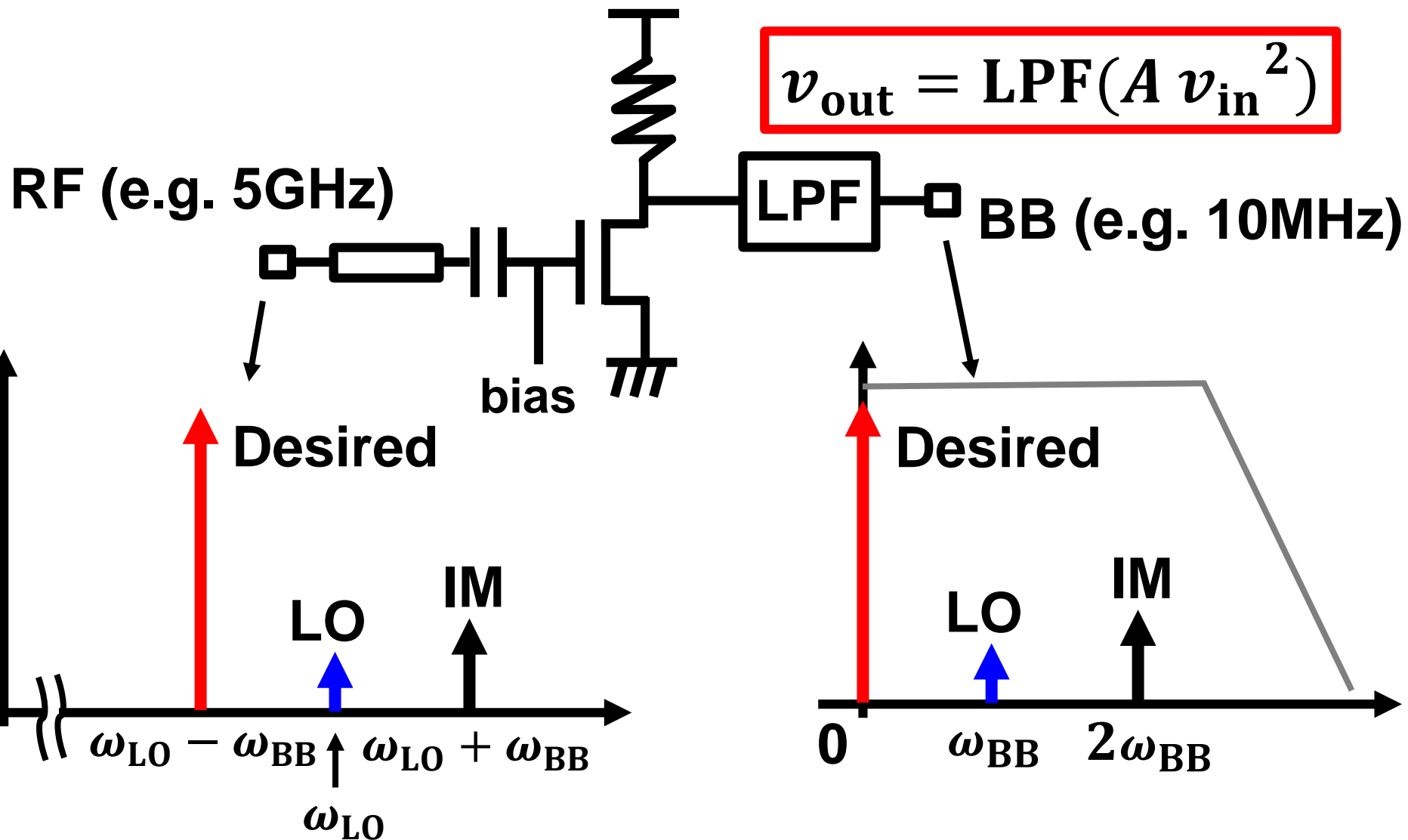


I/Q Mismatch Calibration by Loop-back

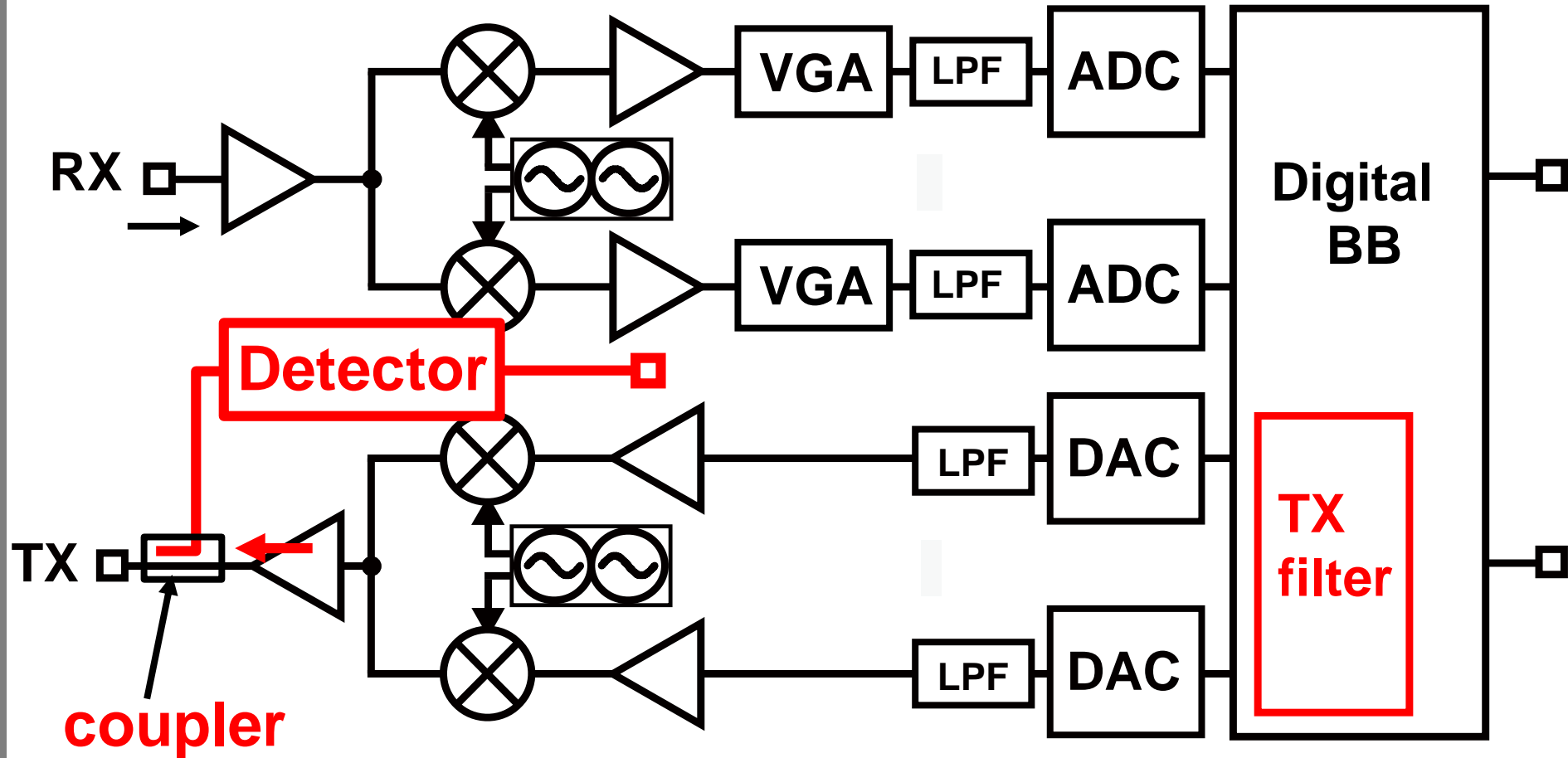

- I/Q Amplitude offset
- I/Q Phase offset



I/Q Mismatch Calibration by Loop-back

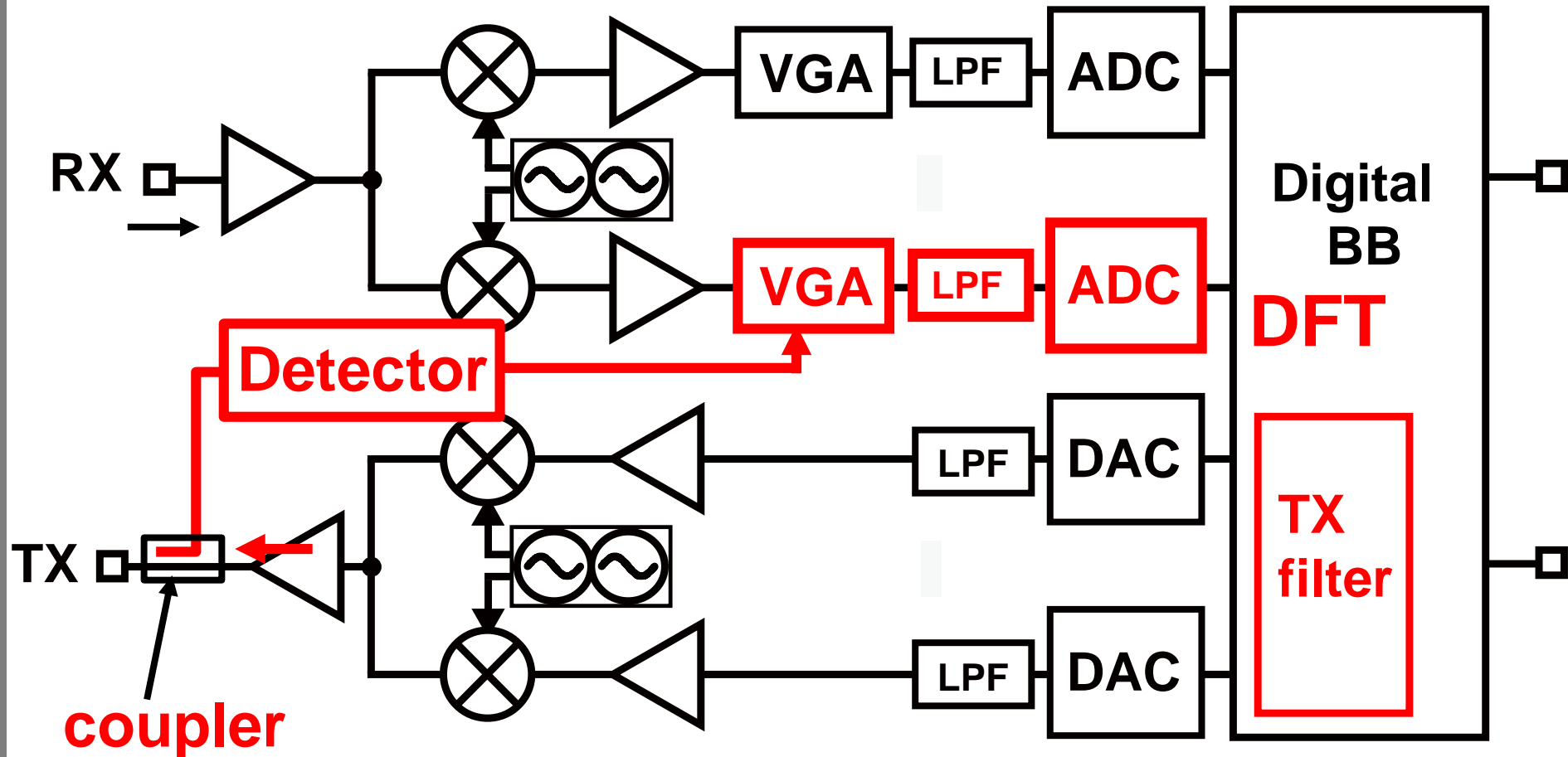

- I/Q Amplitude offset
- I/Q Phase offset

*Iason Vassiliou, et al., IEEE JSSC 2003.



Frequency-Dependent I/Q Mismatch

  

5% cut-off mismatch causes a serious frequency-dependent I/Q mismatch.

Frequency-Dependent IMRR

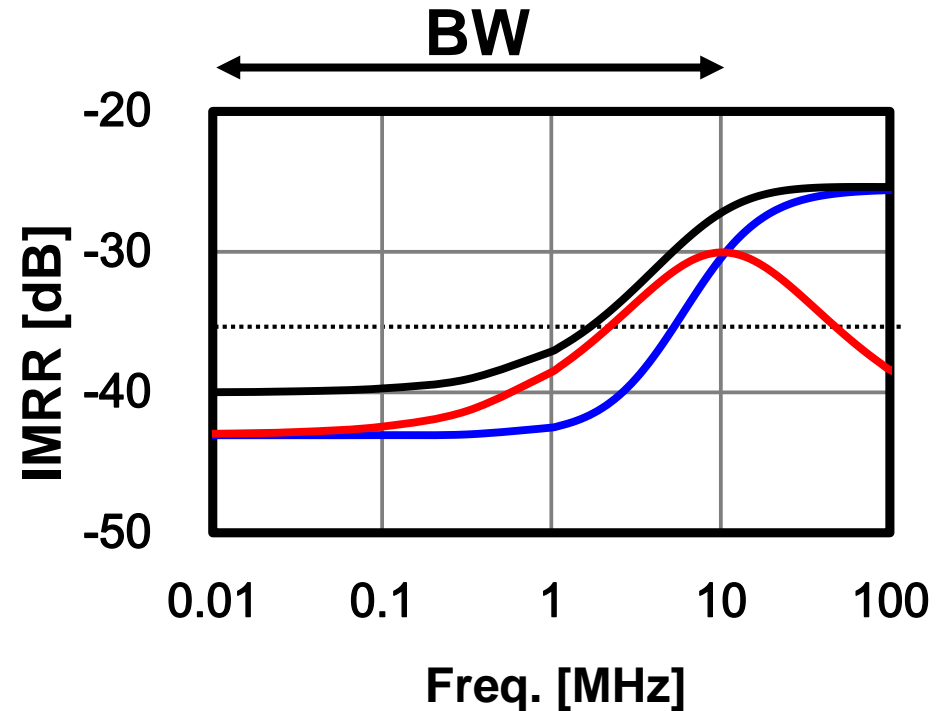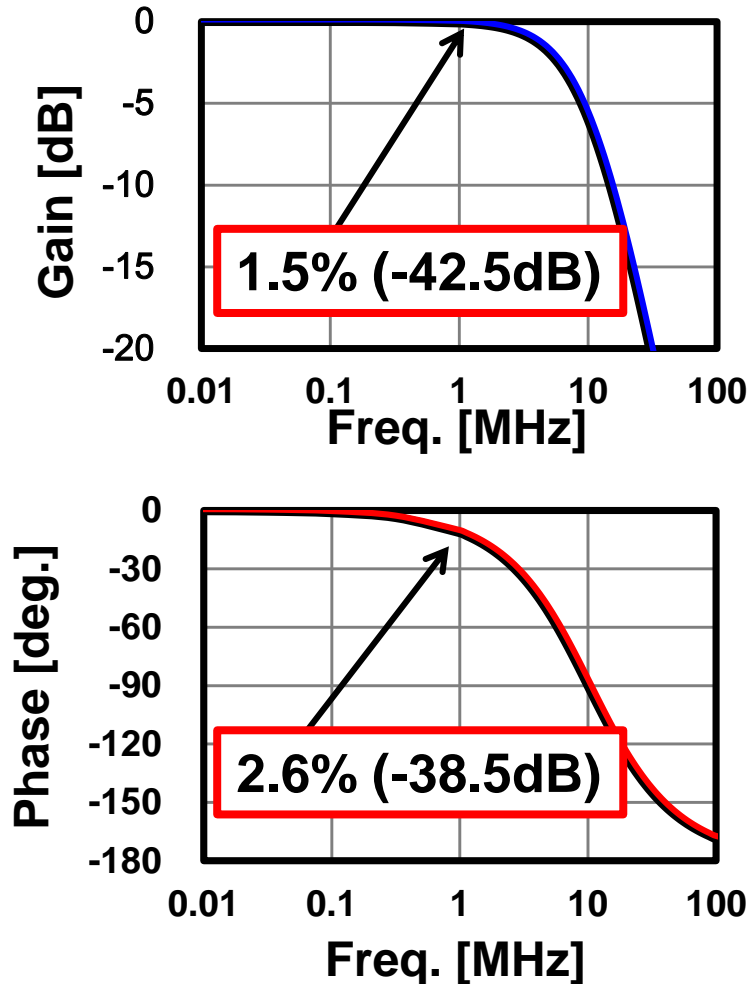Gain/phase mismatch can be frequency-dependent.



5% cut-off frequency mismatch
-37dB @ 1MHz, -27dB @ 10MHz

Key Idea of Wireless Calibration

Self-calibration with less additional blocks

Reuse of TRX each other


TX = Signal Generator for RX calibration

RX = Spectrum Analyzer for TX calibration

Overall Procedure of TRX Calibration


- 1. RX BB LPF Calibration (using TX BB)**
 - I/Q gain mismatch
 - LPF cut-off mismatch (including VGA and ADC)
- 2. TX BB LPF Calibration (using RX BB)**
 - I/Q gain mismatch
 - LPF cut-off mismatch
- 3. TX I/Q Calibration (using detector and RX BB)**
 - Impairments of mixer, LO, RF I/Q amps., etc
 - compensated by **digital BB**
- 4. RX I/Q Calibration (using TX)**
 - Impairments of mixer, LO, RF I/Q amps., etc
 - compensated by **digital BB**

RX Filter Calibration (BB loopback)

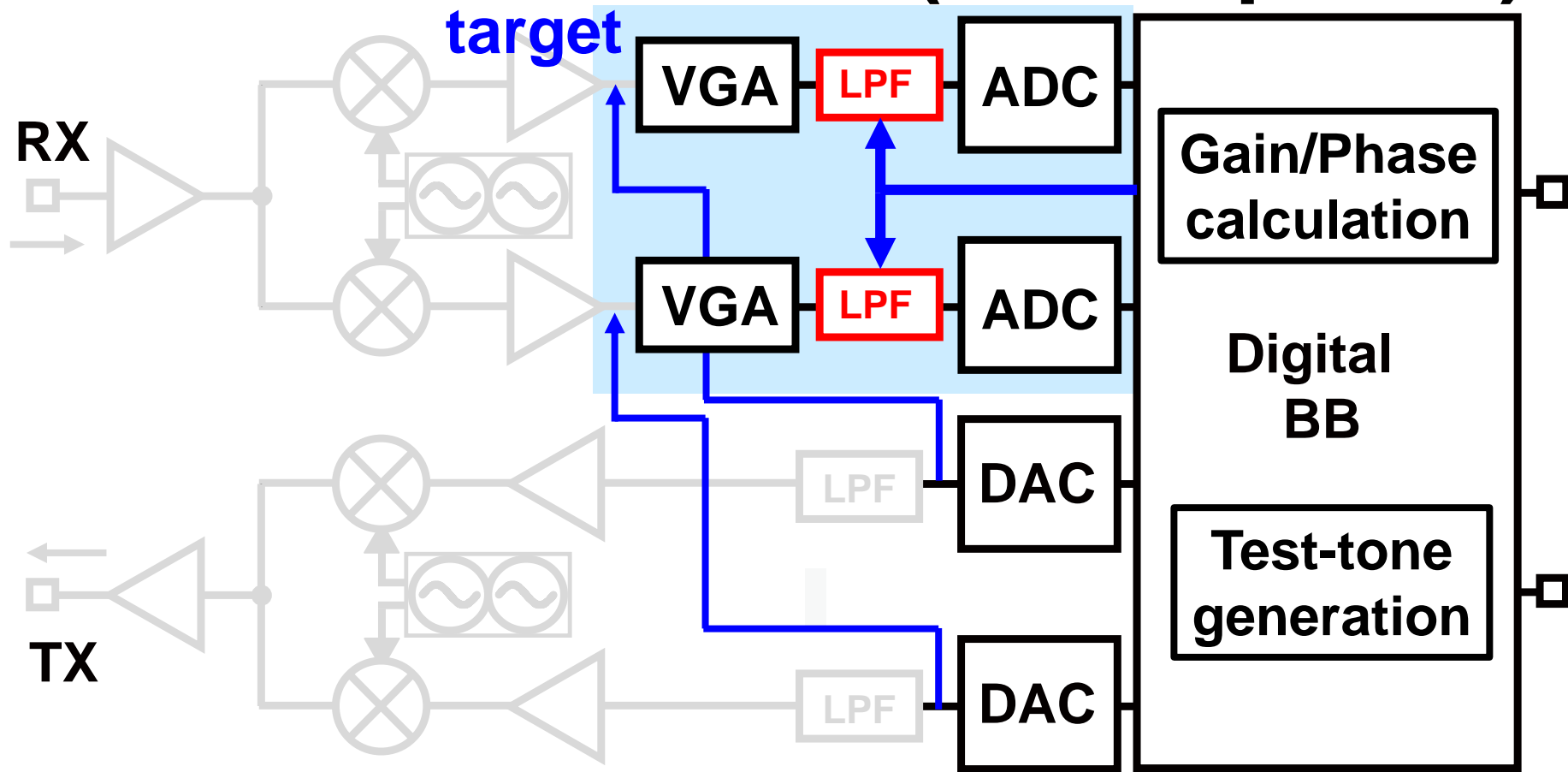

VGA and ADC are also included in RX BB calibration.


TX Filter Calibration (BB loopback)

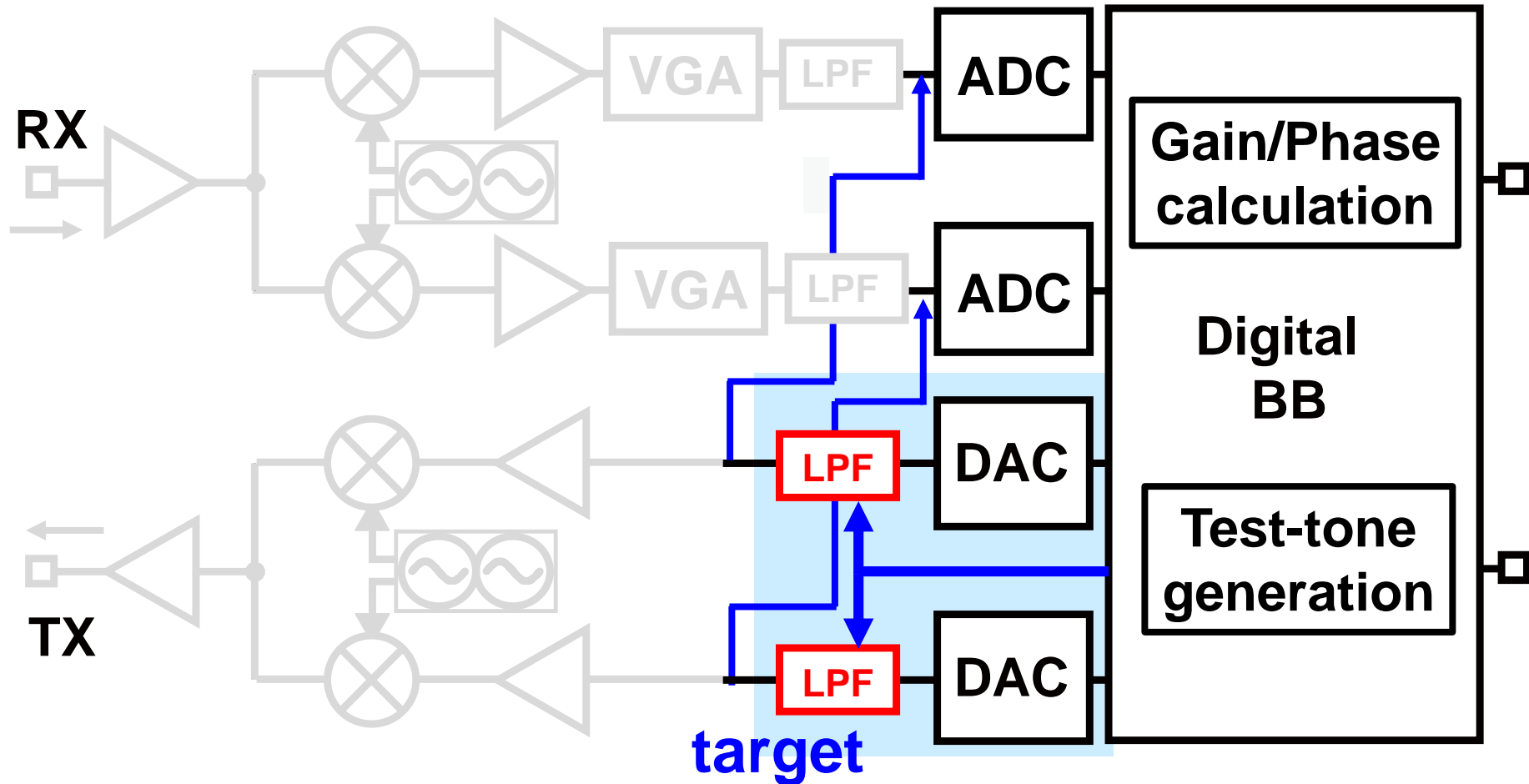

LPF gain/cut-off mismatch between I/Q paths are calibrated.


RF Loop-Back Calibration for TX

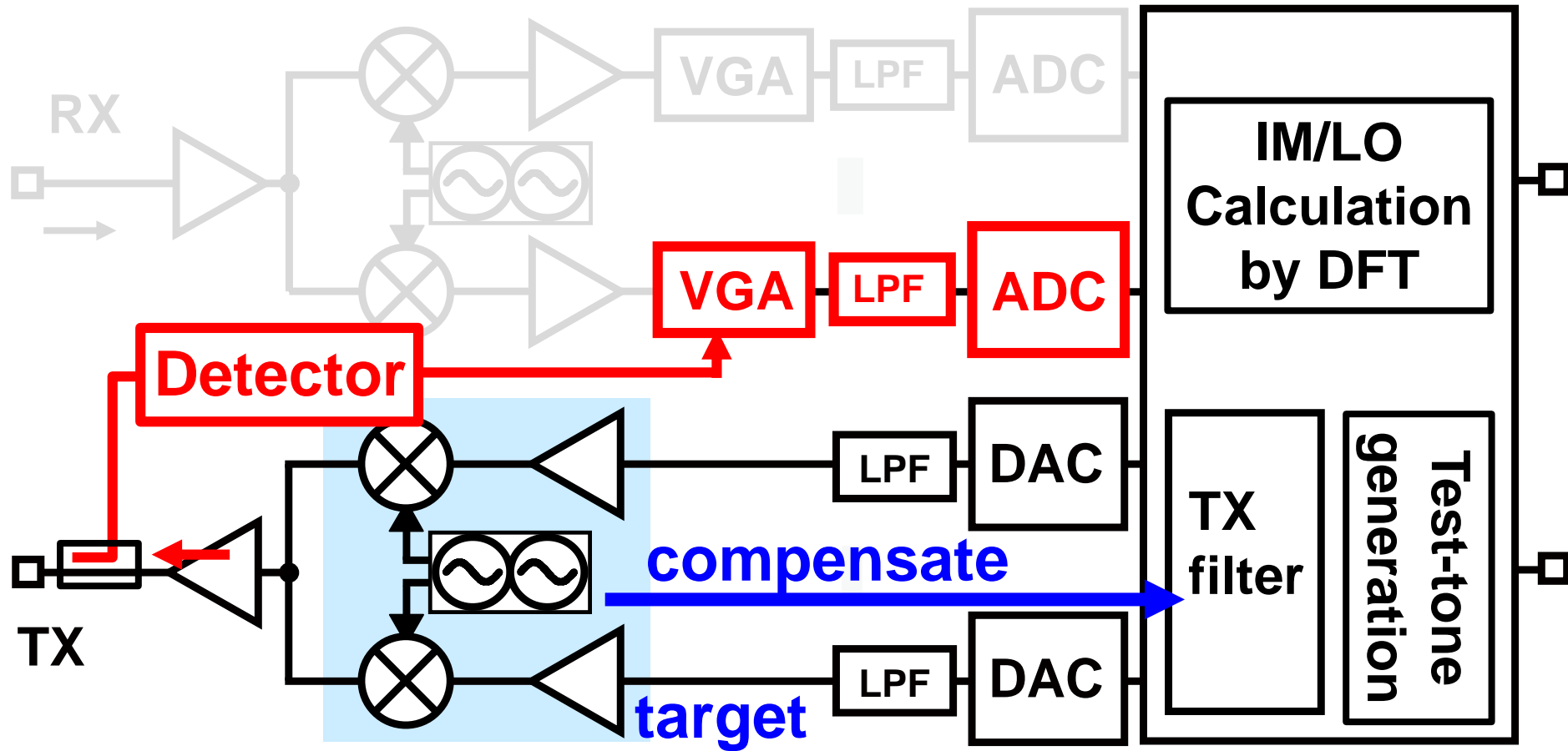ADC is re-used for IM/LO calculation with DFT in BB.



*Iason Vassiliou, et al., IEEE JSSC 2003.


RF Loop-Back Calibration for TX

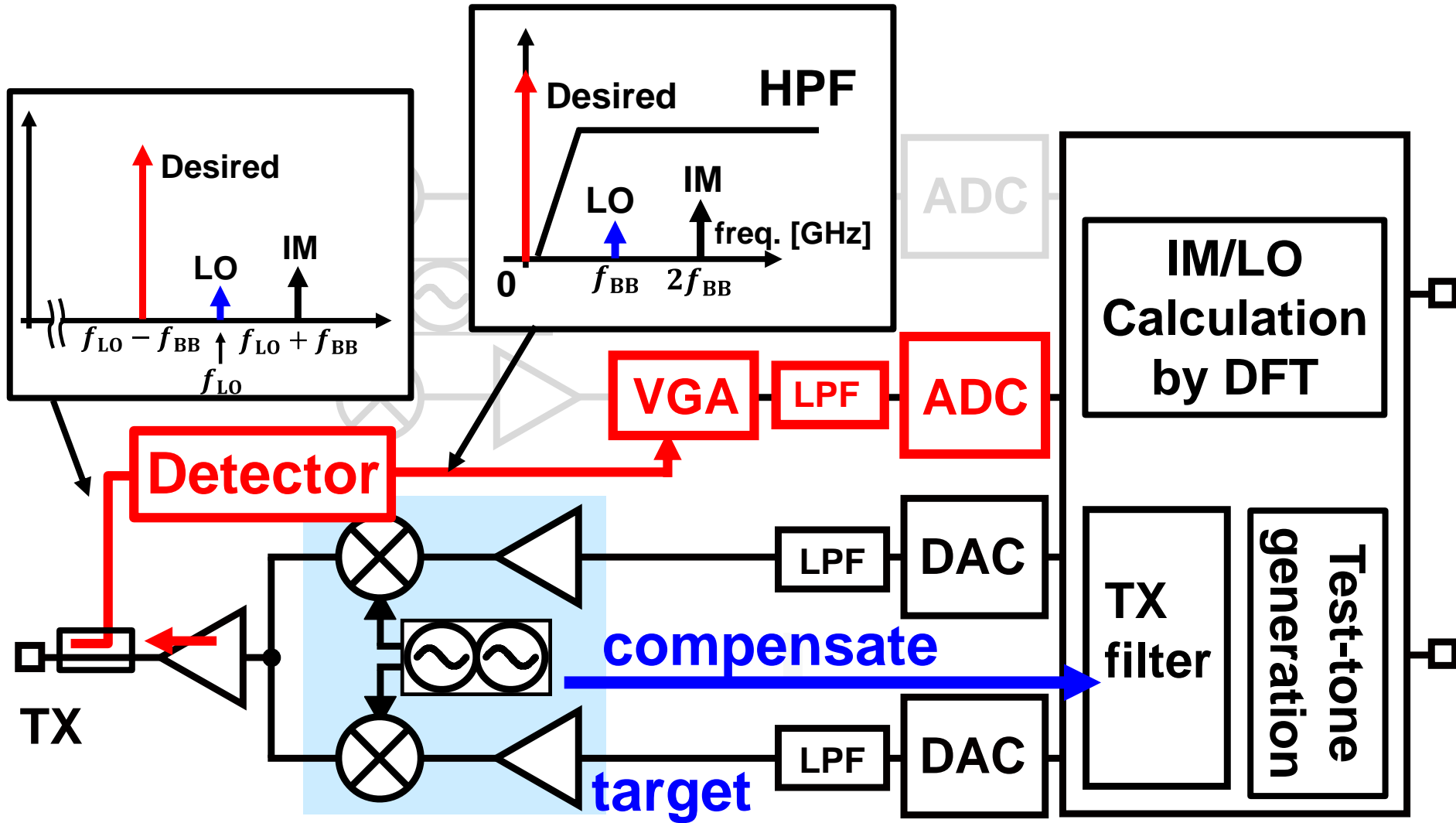

*Iason Vassiliou, et al., IEEE JSSC 2003.

RF Loop-Back Calibration for RX



TX is used for a test-tone generator.

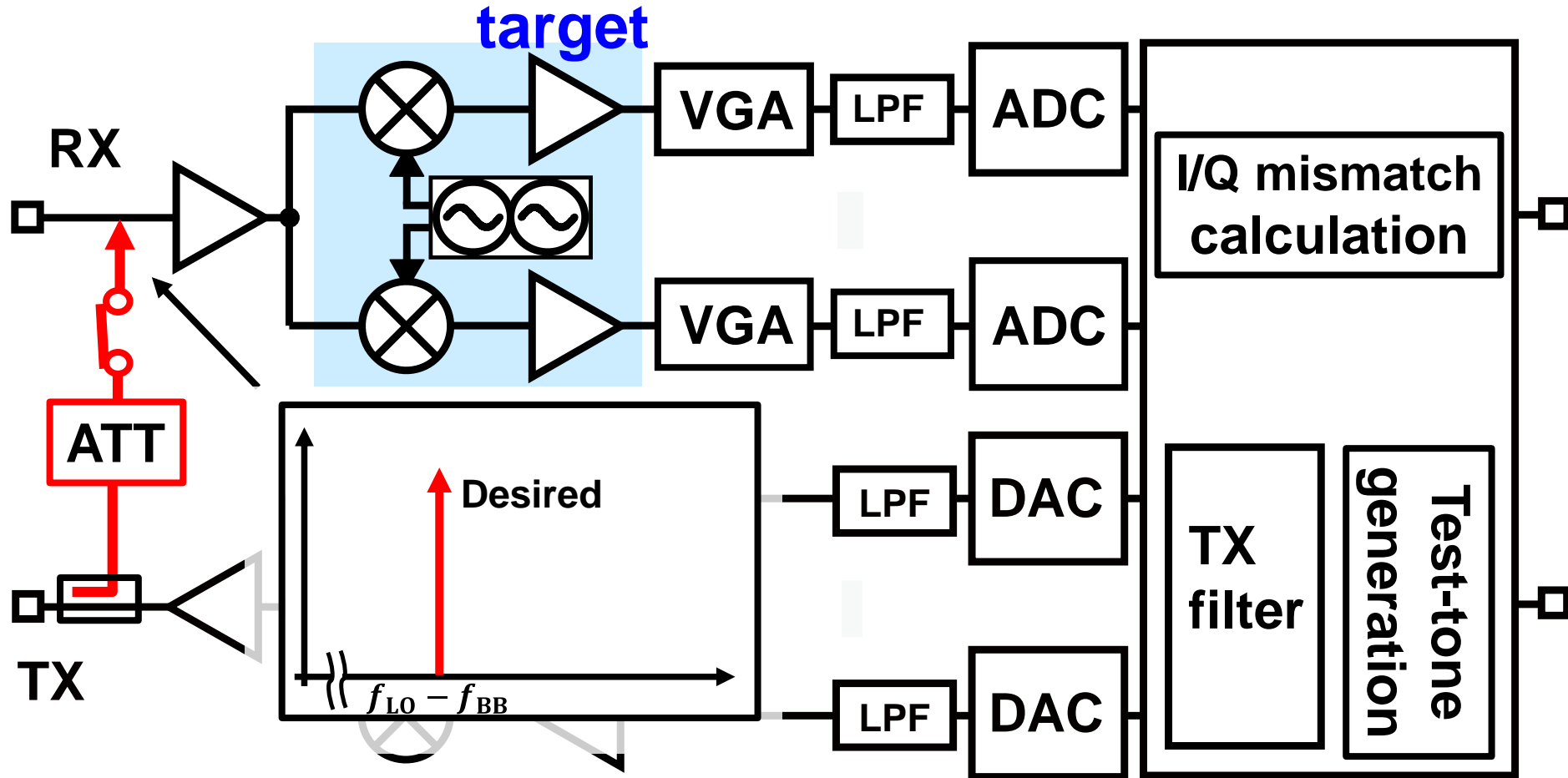

*Iason Vassiliou, et al., IEEE JSSC 2003.

I/Q Gain/Phase Mismatch Calculation

  At least, a **10-bit ADC** is required for a IMRR of 40dB.



$$\text{LPF}(I^2 + Q^2)$$

RSSI → AGC

$$\text{LPF}(I^2 - Q^2) \cong \Delta g$$


$$\text{LPF}(I * Q) \cong -\Delta\theta/2$$

Modulated signal can be used.

→ Background calibration

*S. Lerstaveesin, et al., IEEE JSSC 2006.

RF Loop-Back Calibration for RX

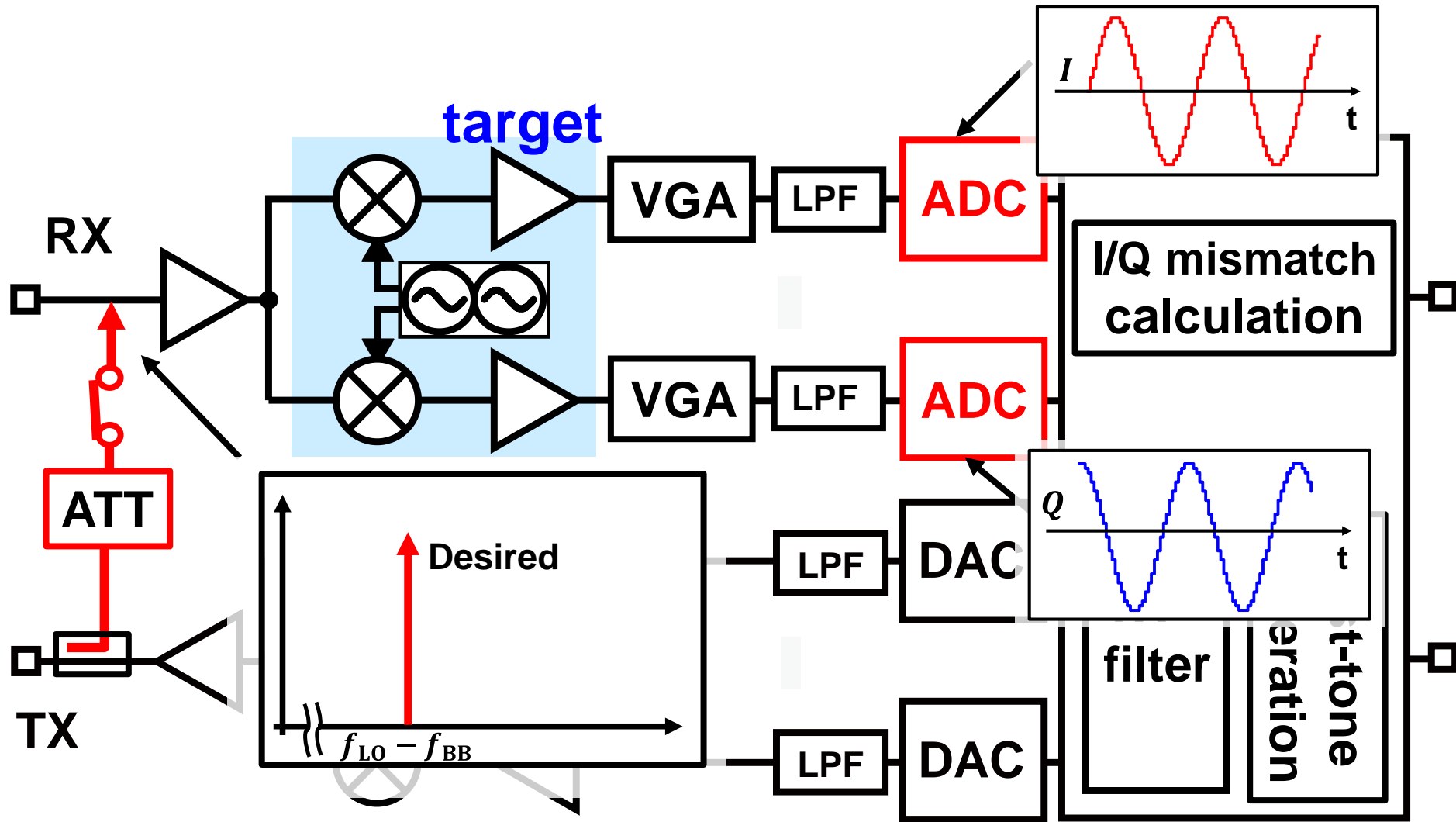

*Iason Vassiliou, et al., IEEE JSSC 2003.

Calibration vs Compensation

Frequency independent (RF)

TX I/Q mismatch(RF) → Digital compensation (BB TX filter)

RX I/Q mismatch(RF) → Digital compensation (BB RX filter)

FDE/OFDM

Frequency independent (BB)

TX I/Q mismatch(BB) → Digital compensation

RX I/Q mismatch(BB) → Digitally-calibrated analog (AGC)
/ Digital compensation

Frequency dependent (BB)


TX I/Q mismatch(BB) → Digitally-calibrated analog

RX I/Q mismatch(BB) → Digitally-calibrated analog
/ Digital compensation

as a typical case


60GHz Transceiver Calibration

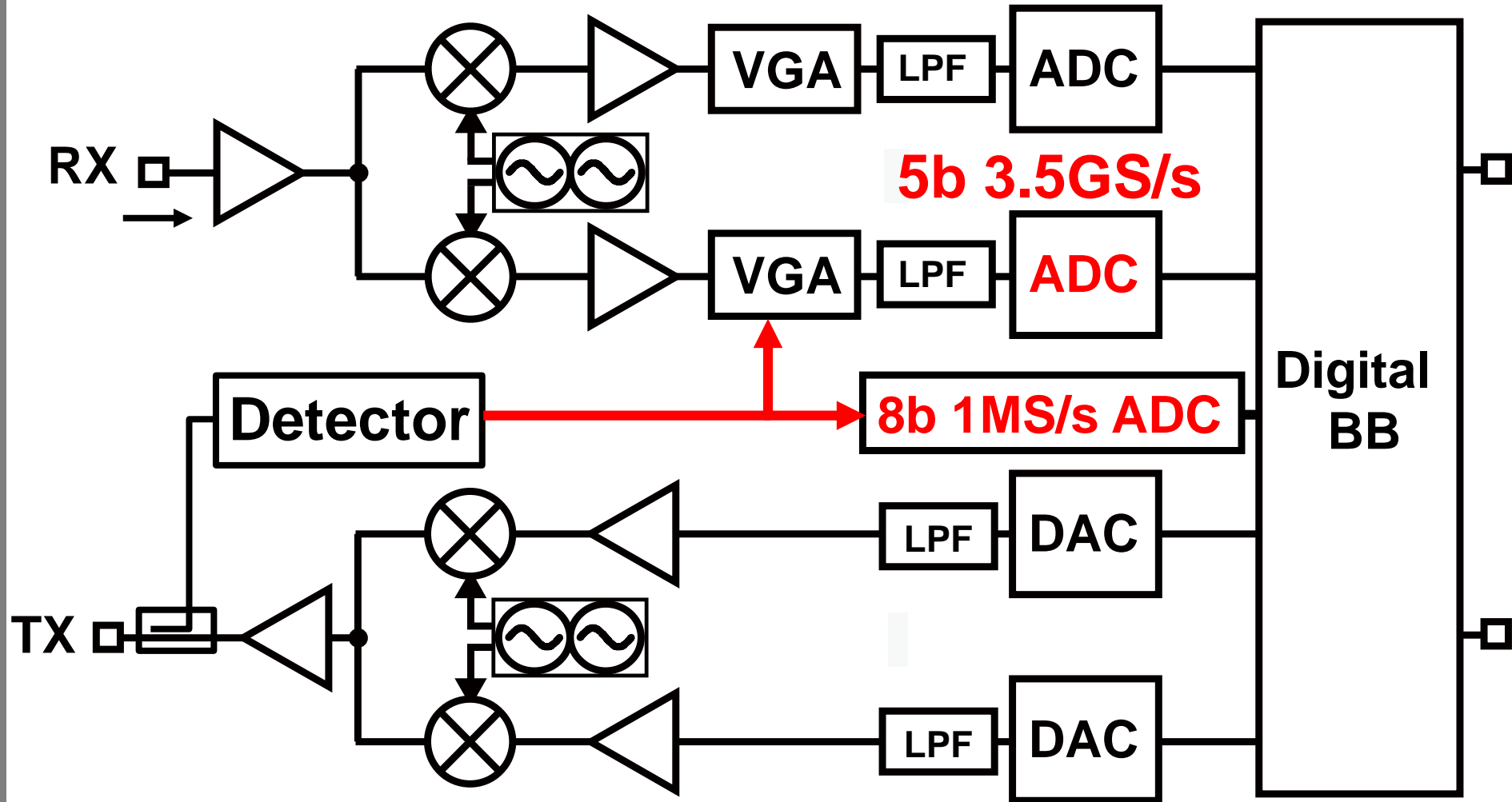One additional ADC is used for a fine resolution.



*T. Tsukizawa, *et al.*, ISSCC 2013

Outline

- **Analog to Digital**
 - **Digitization of Wireless TRX**
- **Digital Assistance**
 - **Wireless Transceiver**
 -  • **Frequency Synthesizer**
- **Future Analog Design**
 - **Synthesizable Analog**

Calibration in Frequency Synthesizer

- AFC for capacitor-bank in LC-VCO
- ILFD/ILO Calibration
- Linearity calibration/compensation
 - Loop-BW, Quantization noise, FM/Polar-TX

VCO: frequency \leftarrow voltage (varactor, C-bank)

DCO: frequency \leftarrow **code** (C-bank, I-control)

TDC: **code** \leftarrow delay (PVT, noise, layout, etc)

(ADC: **code** \leftarrow voltage)

(DAC: voltage \leftarrow **code**)

(Amp: voltage \leftarrow voltage)

AFC: Automatic Frequency Calibration



ILFD: Injection-Locked Frequency Divider

ILO: Injection-Locked Oscillator (Multiplier)

ILFD Calibration

Locked*/Free-run** frequency is used.

60GHz PLL

 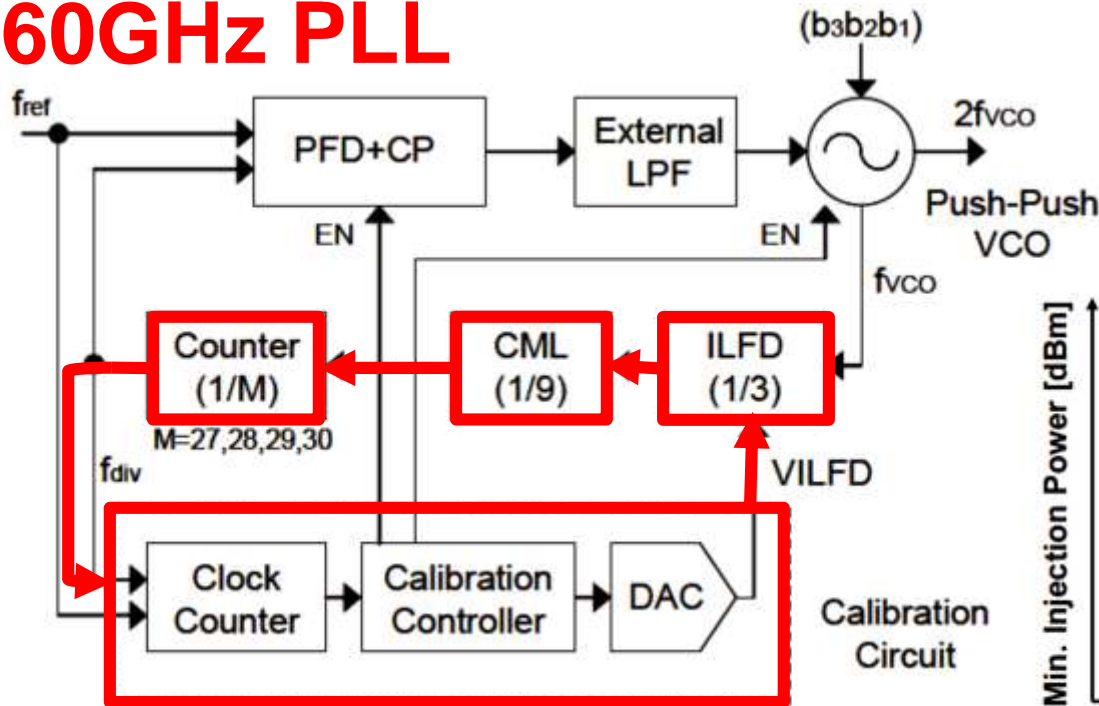


*S. Pellerano, *et al.*, ISSCC 2008 **T. Shima, *et al.*, APMC 2011

***W. Deng, *et al.*, A-SSCC 2012

Summary of Transceiver Calibration

- **Wireless transceiver is a big system.**
- **Historically, architecture-level digitization has been applied with system-level calibration and compensation for PVT and environmental variations.**
- **Re-use of counter-part block for calibration**

Outline

- **Analog to Digital**
 - **Digitization of Wireless TRX**
- **Digital Assistance**
 - **Wireless Transceiver**
 - **Frequency Synthesizer**
-  • **Future Analog Design**
 - **Synthesizable Analog**

Issues of Analog Circuit Design

Why is the simulated performance degraded?

Imperfection caused by physical implementation

PVT

layout non-ideality

- **mismatch**
- **isolation/coupling**


**Compensated by
digital assistance**

Layout Design Issues beyond 20nm

Transistor matching cannot be expected any more.

Double patterning

Well proximity effect

 


- Larger R_d , R_s , R_g
- Fixed fin height (for FinFET)
- Self-heating
- No body effect


STI stress (LOD)

Scaled CMOS Layout

65nm layout style

 

32nm layout style

 

- **Uni-directional features**
- **Uniform gate dimension**
- **Gridded layout**

*M. Bohr, ISSCC 2009

Massive Digital Assistance

PVT

layout non-ideality

- **mismatch**
- **isolation/coupling**


**Compensated by
digital assistance**

Delay and linearity in delay can be calibrated easily in time-domain analog circuits, e.g. AD-PLL.

Further Analog Circuit

Digitization


- Scalability
- Portability

 

Massive Digital Assistance

- Robustness
- Less redundancy

Outline

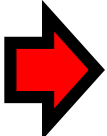- **Analog to Digital**
 - **Digitization of Wireless TRX**
- **Digital Assistance**
 - **Wireless Transceiver**
 - **Frequency Synthesizer**
- **Future Analog Design**
 -  • **Synthesizable Analog**

Synthesizable Analog Circuits

HDL


```
module PLL  
(CLK, ..., OUT)  
...  
endmodule
```

Digital design flow




Commercial P&R tools...

GDS

 

**with a standard-cell library
without any custom-designed cells
without manual placement**


Analog Synthesis by Digital Tools

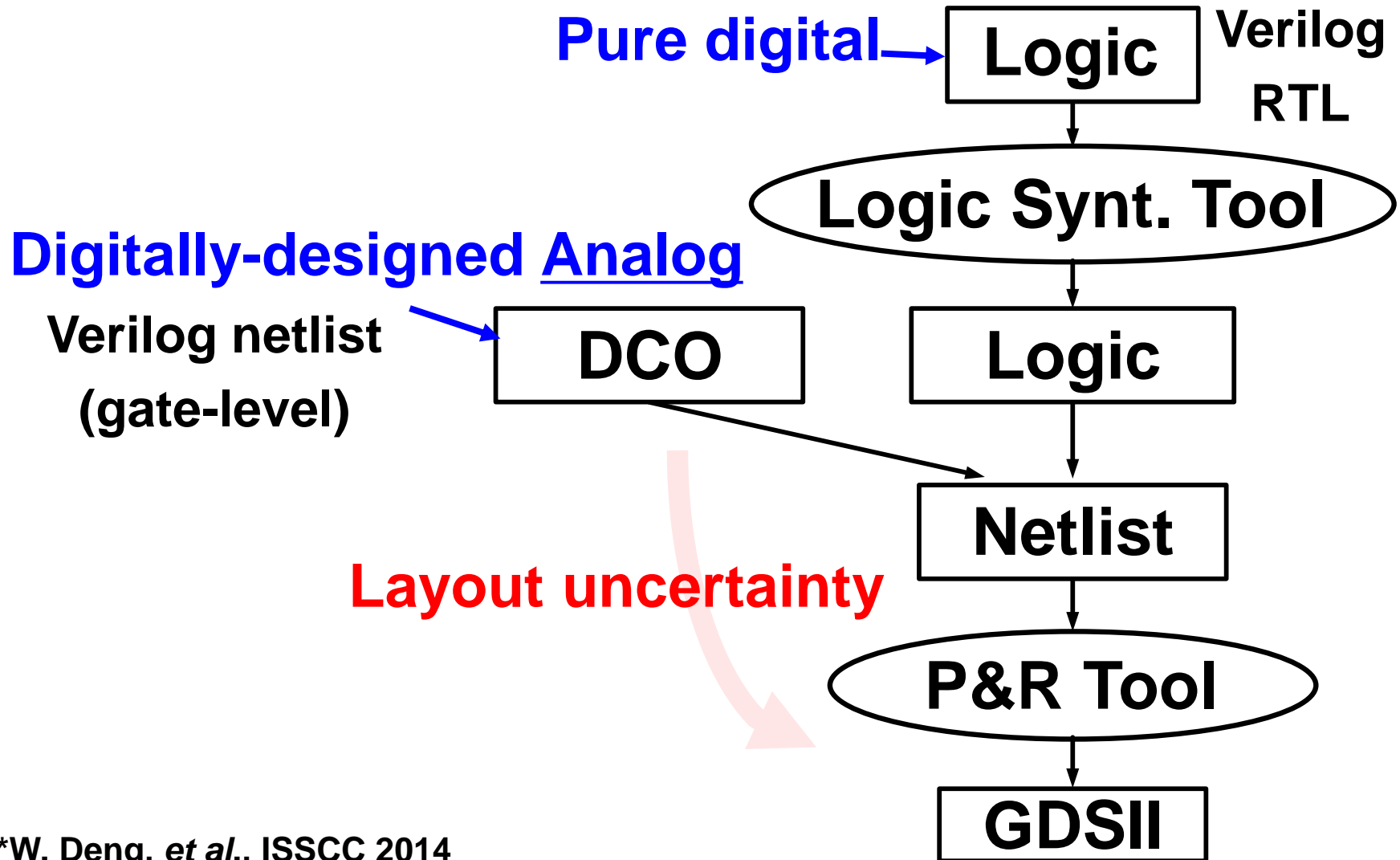


*W. Deng, et al., ISSCC 2014

Issue: Layout Uncertainty

 Massive digital assistance can overcome the layout uncertainty issue.



Ideal placement

 

Actual placement

→ Unbalanced loading
No layout symmetry

e.g., DCO & TDC linearity



Synthesizable Analog Circuits

only by standard cells

- **Synthesizable PLL***
- **Synthesizable DCO**
- **Synthesizable DAC**
- **Synthesizable TDC**
- **Synthesizable ADC****

*W. Deng, *et al.*, ISSCC 2014 **S. Weaver, *et al.*, IEEE TCAS-I 204

Synthesizable ADC

 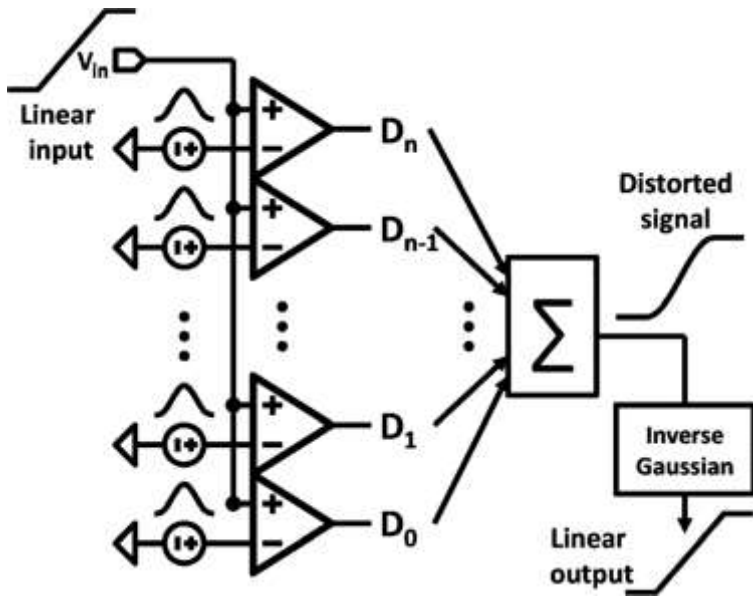

ADC architecture

SNDR of 35.9dB, 210MS/s


Linearity compensation by inverse Gaussian

Comparator by NAND3


Gaussian offset distribution

*S. Weaver, *et al.*, IEEE TCAS-I 2014

Synthesizable DCO

 

MUX and varactor*

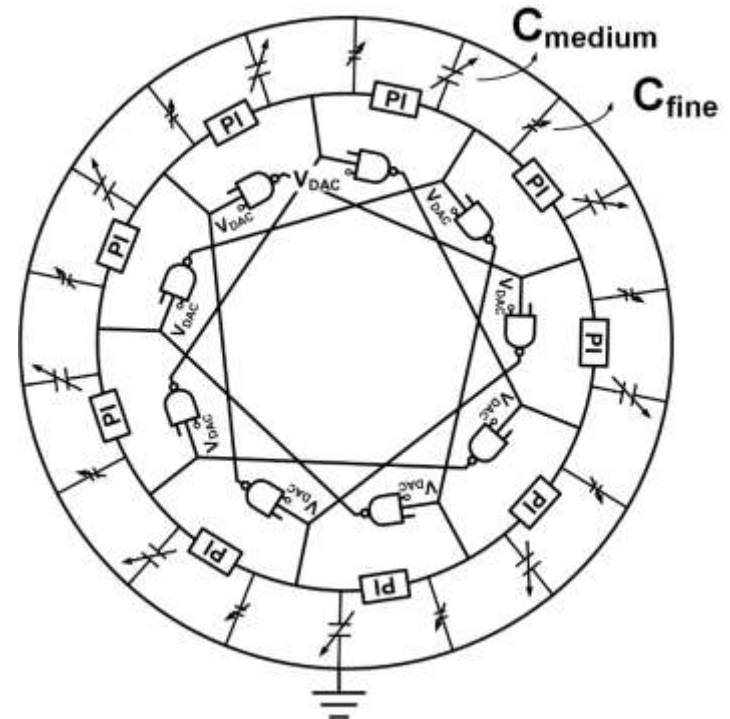


Phase-Interpolator**, I-DAC***, and fine varactor***

*D. Sheng, *et al.*, IEEE TCAS-II 2007

A. Matsumoto, *et al.*, JSSC 2008 *W. Deng, *et al.*, ISSCC 2014

Synthesizable DAC

Only standard cell

 


$$D_0 = 0$$

$$V_{\text{out}} = 1V$$

$$D_0 = 1$$

$$V_{\text{out}} = 0V$$

 

$$D_0 D_1 = 11$$

$$V_{\text{out}} = 0V$$

$$D_0 D_1 = 10$$

$$V_{\text{out}} = 0.5V$$

$$D_0 D_1 = 01$$




$$V_{\text{out}} = 0.5V$$

$$D_0 D_1 = 00$$



$$V_{\text{out}} = 1V$$

Synthesizable I-linear DAC

Only standard cell

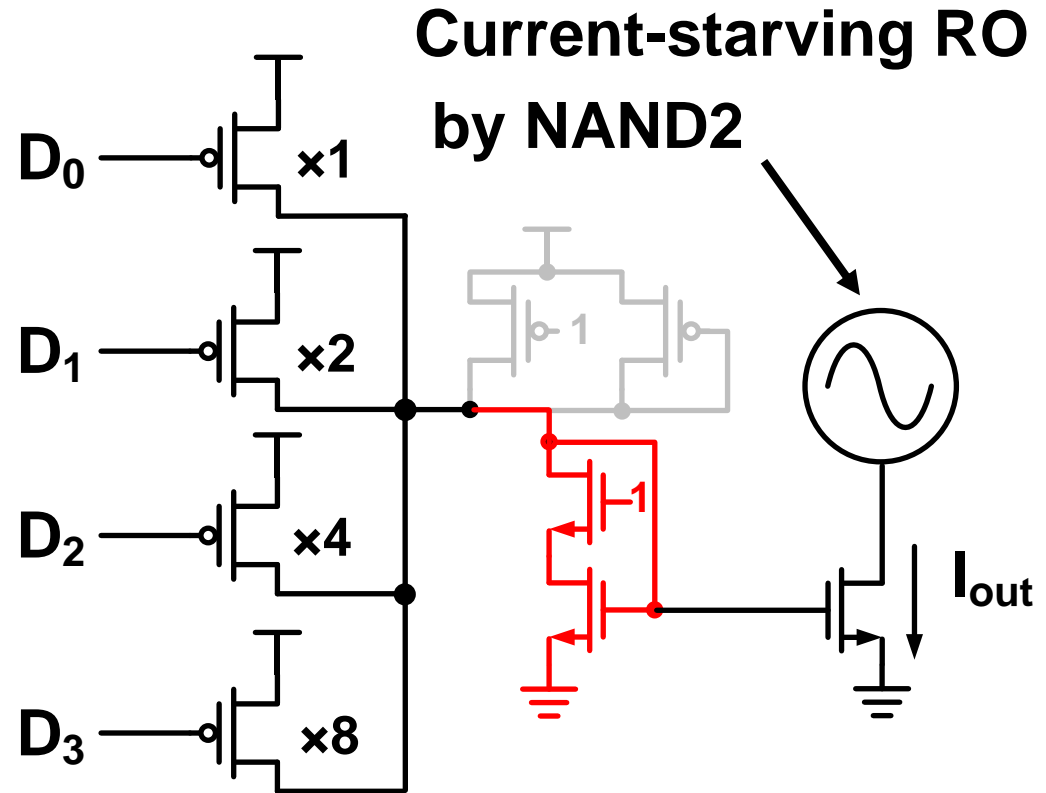 
 


V-linear DAC vs I-linear DAC

  


Stdcell Varactor

1.55ps @200MHz

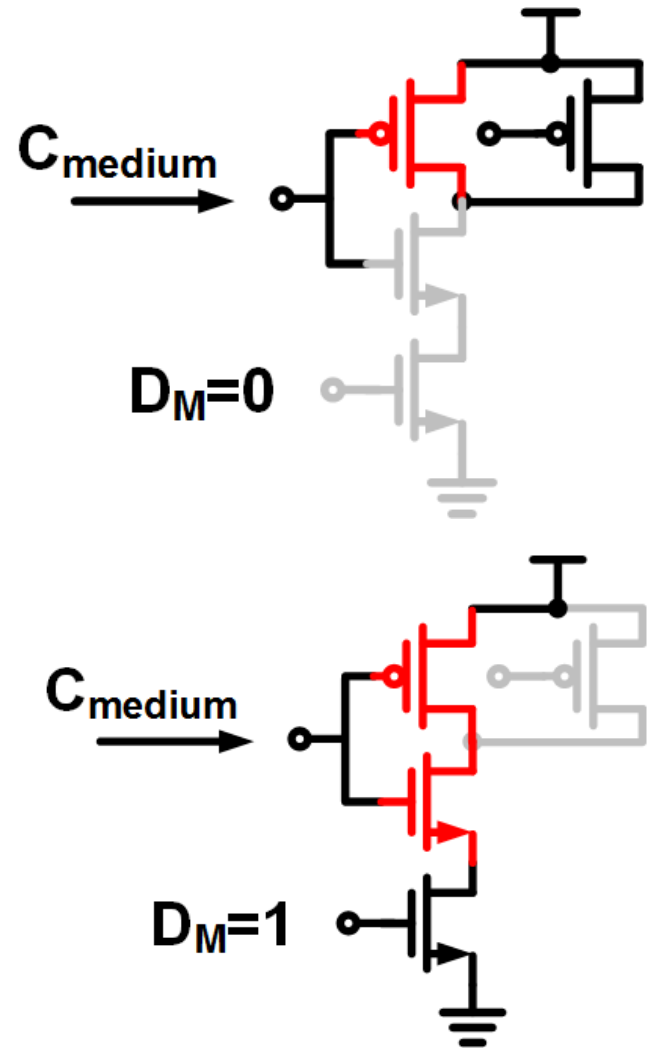 


*P. L. Chen, *et al.*, TCAS II 2005

Performance Trade-off

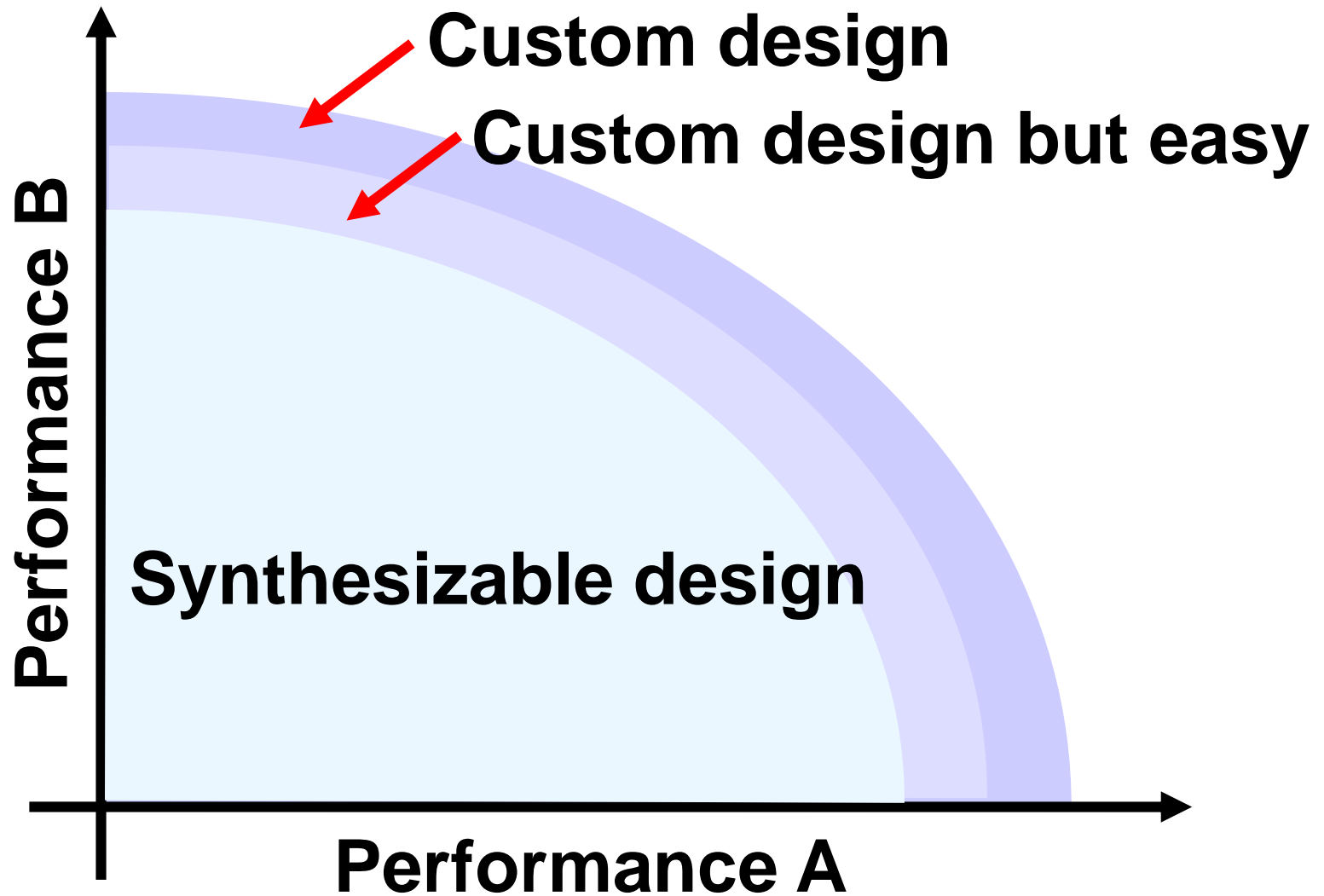

Performance Trade-off

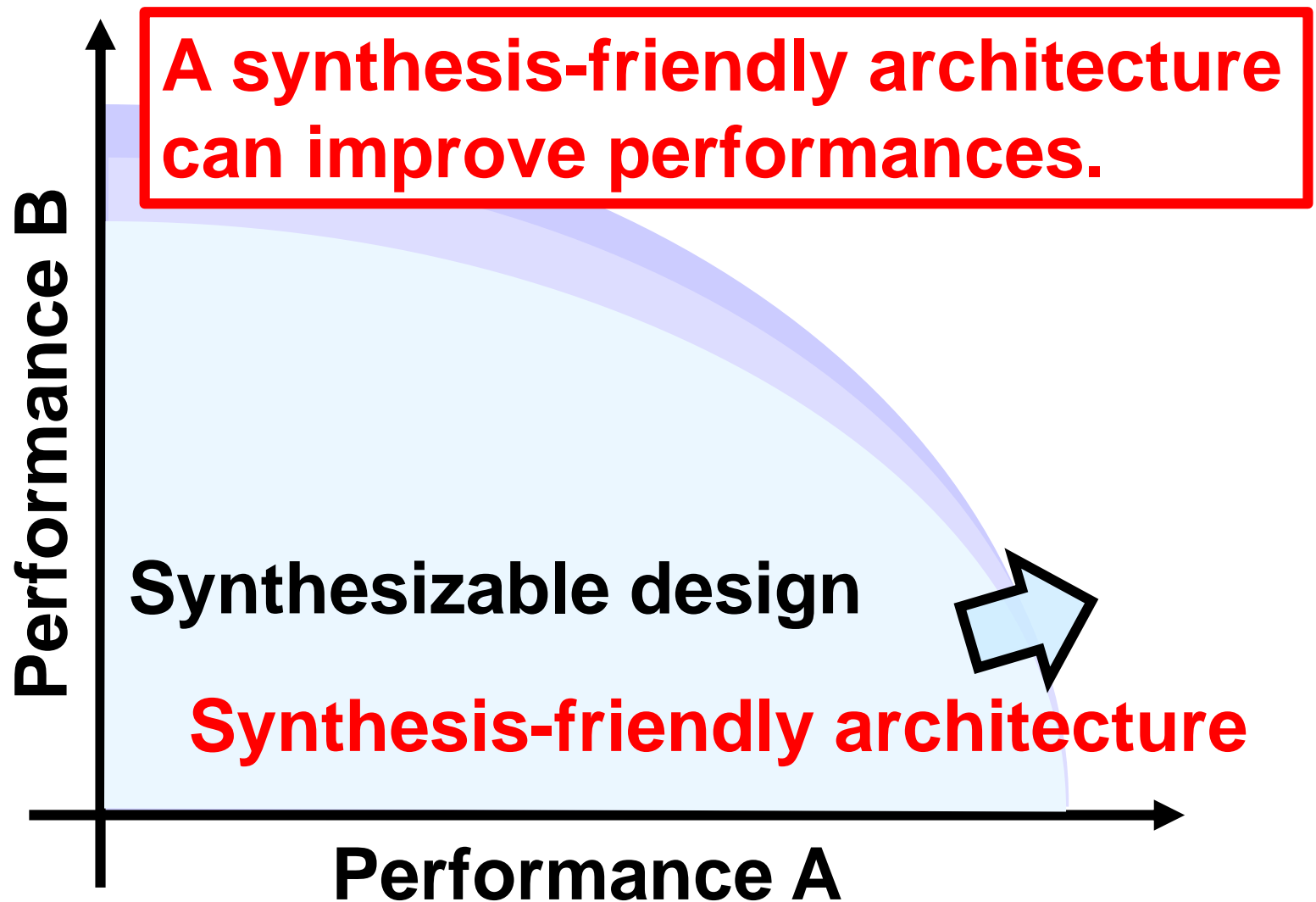

Injection-Locked PLL (IL-PLL)

Conventional CP-PLL and TDC-PLL (AD-PLL)

- Phase lock: feedback
- Frequency lock: feedback

Injection-Locked PLL (IL-PLL)


- Phase lock: **feed-forward** ← Injection-lock
- Frequency lock: feedback ← Counter



The fine timing feedback is not required.


→ **Synthesis-friendly**

Injection-Locked PLL

 

*S. Ye, et al., IEEE JSSC 2002 **N. D. Dalt, IEEE TCAS-II 2014

Synthesizable IL-PLL


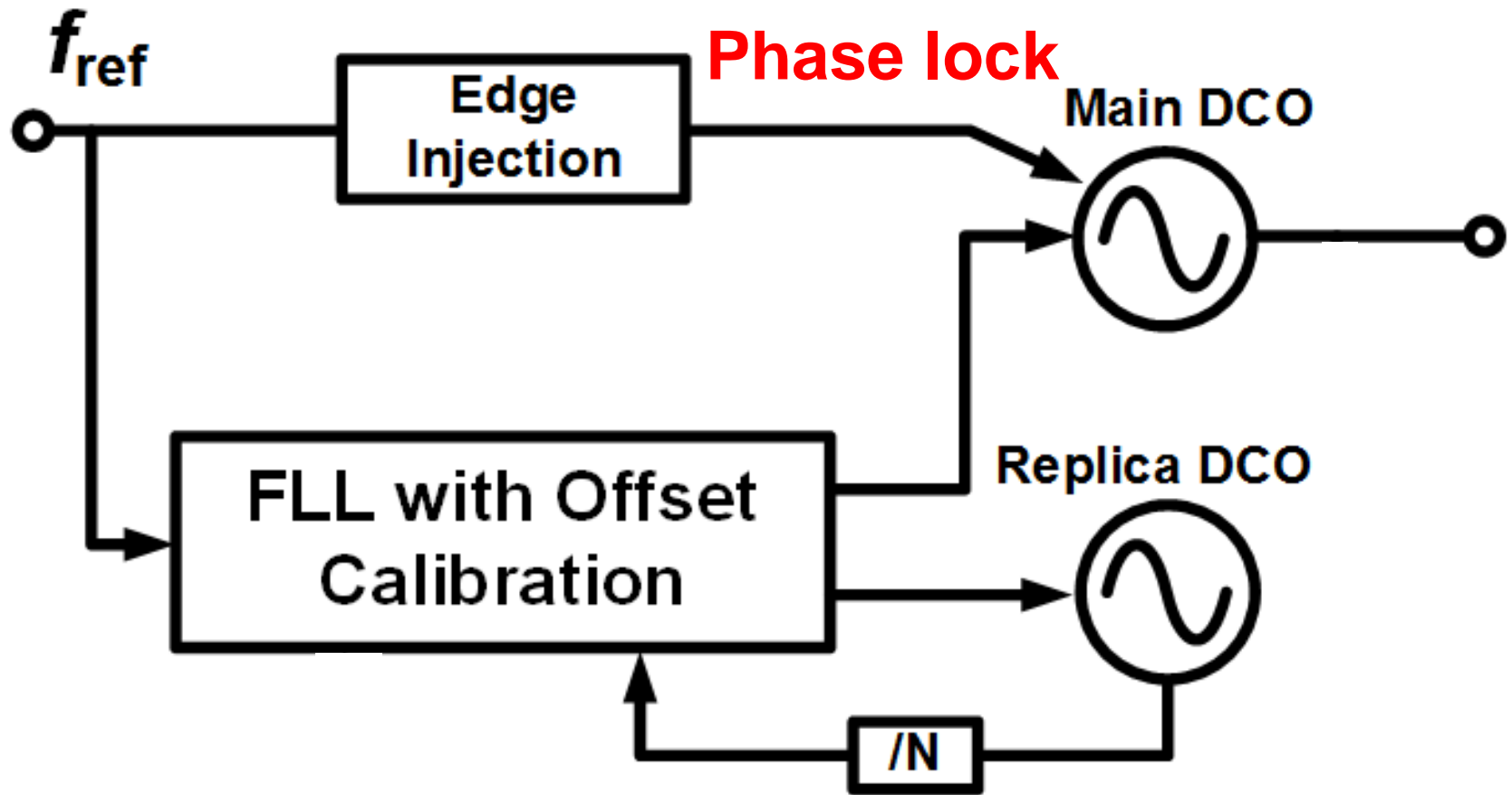


Frequency tracking with very narrow BW

*W. Deng, *et al.*, ISSCC 2013 **A. Musa, *et al.*, JSSC 2014 ***W. Deng, *et al.*, ISSCC 2014


Gated Edge Injection

Severe timing design is NOT required.

 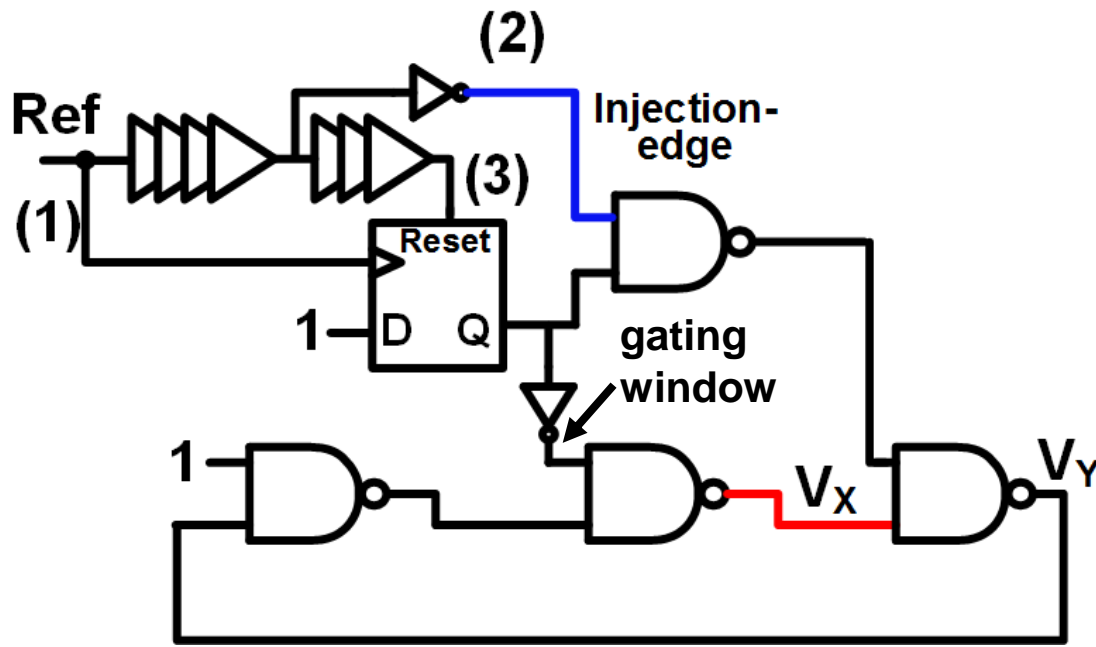

*W. Deng, *et al.*, ISSCC 2014 **D. Park, *et al.*, ISSCC 2012

Layout

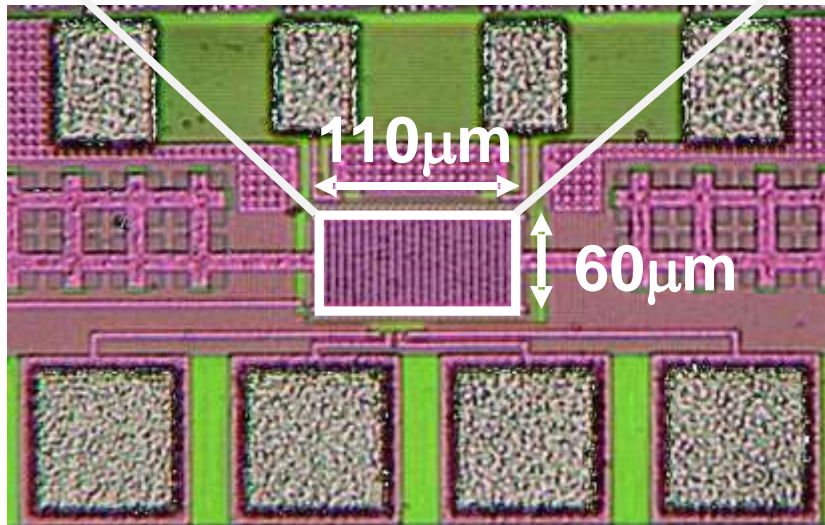

CMOS 65nm


Area: 0.0066mm²

Jitter: 1.7ps

P_{DC}: 780μW

FOM: -236.5 dB

Comparison of the state-of-the-art PLLs

 

*W. Deng, et al., ISSCC 2014

Comparison of Synthesizable PLL

	This work 65nm	[22] 28nm	[23] 65nm	[24] 65nm
Power [mW]	0.78 @900MHz	13.7 @2.5GHz	3.1 @250MHz	2.1 @403MHz
Area [mm ²]	0.0066	0.042	0.032	0.1
Integ. Jitter [ps]	1.7	N.A.	30	N.A.
RMS Jitter [ps]	2.8	3.2	N.A.	13.3
FOM [dB]	-236.5	-218.6*	-205.5	-214*
W/ custom cells?	No	No	Yes	Yes
Topology	IL-base	TDC-base	TDC-base	TDC-base

*FOM is calculated based on RMS jitter.

Conclusion

- **Digitization vs Digitally-Assisted Analog**
- **Digitally-Assisted Analog**
to **Digitally-Designed Analog**
e.g. **Synthesizable Analog Circuit**
portability, scalability, robustness,..

References

- [1] F. Gardner, "Interpolation in Digital Modems-Part I: Fundamentals," *IEEE Trans. on Communications*, Vol. 41, No. 3, pp. 501-507, Mar. 1993.
- [2] H. Suzuki, Y. Yamao, and H. Kikuchi, "A Single-Chip MSK Coherent Demodulator for Mobile Radio Transmission," *IEEE Trans. on Vehicular Technology*, Vol. VT-34, No. 4, pp. 157-168, Nov. 1985.
- [3] A. Jerng, "Digital Calibration for RF Transceivers," *ISSCC 2012, Tutorial 9*.
- [4] I. Vassiliou, *et al.*, "A Digitally Calibrated 5.15-5.825GHz Transceiver for 802.11a Wireless LANs in 0.18 μ m CMOS," *IEEE Journal of Solid-State Circuits*, Vol. 38, No. 12, pp. 2221-2231, Dec. 2003.
- [5] S. Lerstaveesin, *et al.*, "A Complex Image Rejection Circuit with Sign Detection Only," *IEEE Journal of Solid-State Circuits*, Vol. 41, No. 12, pp. 2693-2702, Dec. 2006.
- [6] T. Tsukizawa, *et al.*, "A Fully Integrated 60GHz CMOS Transceiver Chipset Based on WiGig/IEEE802.11ad with Built-in Self-Calibration for Mobile Applications," *ISSCC Dig. Tech. Papers*, pp. 230-231, Feb. 2013.
- [7] S. Pellerano, R. Mukhopadhyay, A. Ravi, J. Laskar, and Y. Palaskas, "A 39.1-to-41.6GHz $\Delta\Sigma$ Fractional-N Frequency Synthesizer in 90nm CMOS," *ISSCC Dig. Tech. Papers*, pp. 484-485, Feb. 2008.
- [8] T. Shima, J. Sato, K. Mizuno, K. Takinami, "A 60 GHz CMOS PLL Synthesizer Using a Wideband Injection-Locked Frequency Divider with Fast Calibration Technique," *APMC*, pp. 1530-1533, Dec. 2011.

References

- [9] W. Deng, A. Musa, K. Okada, and A. Matsuzawa, "A 0.38mm², 10MHz-6.6GHz Quadrature Frequency Synthesizer Using Fractional-N Injection-Locked Technique," A-SSCC Dig. Tech. Papers, pp. 353-356, Nov. 2012.
- [10] M. Bohr, "The New Era of Scaling in an SoC World," ISSCC Dig. Tech. Papers, pp. 23-28, Feb. 2009.
- [11] W. Deng, A. Musa, T. Siriburanon, M. Miyahara, K. Okada, and A. Matsuzawa, "A 0.0066-mm² 780- μ W Fully Synthesizable PLL with a Current Output DAC and an Interpolative-Phase Coupled Oscillator using Edge Injection Technique," ISSCC Dig. Tech. Papers, pp. 266-267, Feb. 2014.
- [12] S. Weaver, B. Hershberg, and Un-Ku Moon, "Digitally Synthesized Stochastic Flash ADC Using Only Standard Digital Cells," IEEE Transactions on Circuits and Systems-I, Vol. 61, No. 1, pp. 84-91, Jan. 2014.
- [13] P. M. Levine, and G. W. Roberts, "A High-Resolution Flash Time-to-Digital Converter and Calibration Scheme," IEEE International Test Conference, pp. 1148-1157, Oct. 2004.
- [14] D. Sheng, *et al.*, "An Ultra-Low-Power and Portable Digitally Controlled Oscillator for SoC Applications," IEEE Trans. Circuits and Systems-II, Vol. 54, No. 11, pp. 954-958, Nov. 2007.

References

- [15] A. Matsumoto, S. Sakiyama, Y. Tokunaga, T. Morie, and S. Dosho, "A Design Method and Developments of a Low-Power and High-Resolution Multiphase Generation System," *IEEE Journal of Solid-State Circuits*, Vol. 43, No. 4, pp. 831-843, Apr. 2008.
- [16] P. L. Chen, *et al.*, "A Portable Digitally Controlled Oscillator Using Novel Varactors," *IEEE Trans. Circuits and Systems-II*, Vol. 52, No. 5, pp. 233-237, May 2007.
- [17] S. Ye, L. Jansson, and I. Galton, "A Multiple-Crystal Interface PLL With VCO Realignment to Reduce Phase Noise," *IEEE Journal of Solid-State Circuits*, Vol. 37, No. 12, pp. 1795-1803, Dec. 2002.
- [18] N. D. Dalt, "An Analysis of Phase Noise in Realigned VCOs," *IEEE Transactions on Circuits and Systems-II*, Vol. 6, No. 3, pp. 143-147, March 2014.
- [19] W. Deng, A. Musa, T. Siriburanon, M. Miyahara, K. Okada, and A. Matsuzawa, "A 0.022mm² 970 μ W Dual-Loop Injection-Locked PLL with -243dB FOM Using Synthesizable All-Digital PVT Calibration Circuits," *ISSCC Dig. Tech. Papers*, pp. 248-249, Feb. 2013.
- [20] A. Musa, W. Deng, T. Siriburanon, M. Miyahara, K. Okada, and A. Matsuzawa, "A Compact, Low Power and Low Jitter Dual-Loop Injection Locked PLL Using All-Digital PVT Calibration," *IEEE Journal of Solid-State Circuits*, Vol. 49, No. 1, pp. 50-60, Jan. 2014.

References

- [21] D. Park, and S. Cho, "A 14.2mW 2.55-to-3GHz Cascaded PLL with Reference Injection, 800MHz Delta-Sigma modulator and 255fsrms Integrated Jitter in 0.13um CMOS," ISSCC Dig. Tech. Papers, pp. 344-345, Feb. 2012.
- [22] Y. Park, and D.D. Wentzloff, "An All-Digital PLL Synthesized from a Digital Standard Cell Library in 65nm CMOS," IEEE Custom Integrated Circuits Conf., Oct. 2011.
- [23] W. Kim, et al., "A 0.032mm² 3.1mW Synthesized Pixel Clock Generator with 30psrms Integrated Jitter and 10-to-630MHz DCO Tuning Range," ISSCC Dig. Tech. Papers, pp.250-251, Feb. 2013.
- [24] M. Faisal, and D.D. Wentzloff, "An Automatically Placed-and-Routed ADPLL for the MedRadio Band using PWM to Enhance DCO Resolution," IEEE Radio Frequency Integrated Circuits Symposium, pp.115-118, Jun. 2013.

Other example:


- [25] D. Kaczman, et al., "A Single-Chip 10-Band WCDMA/HSDPA 4-Band GSM/EDGE SAW-less CMOS Receiver With DigRF 3G Interface and +90 dBm IIP2," IEEE JSSC, Vol. 44, No. 3, pp. 718-739, March 2009.

Acknowledgement


This work was partially supported by MIC, SCOPE, MEXT, STARC, and VDEC in collaboration with Cadence Design Systems, Inc., and Agilent Technologies Japan, Ltd.

Appendix

Up-conversion by $\cos(\omega_{LO}t)$


 


Up-conversion by $\sin(\omega_{LO}t)$

 



Ideal I/Q Up-Conversion

Image signals are canceled.

  


I/Q Up-Conversion with Mismatch


Image signals are NOT canceled.

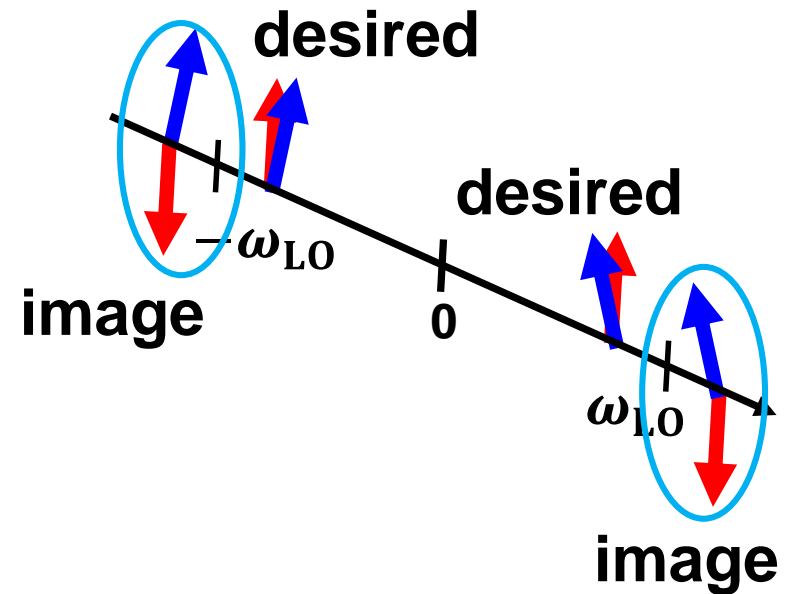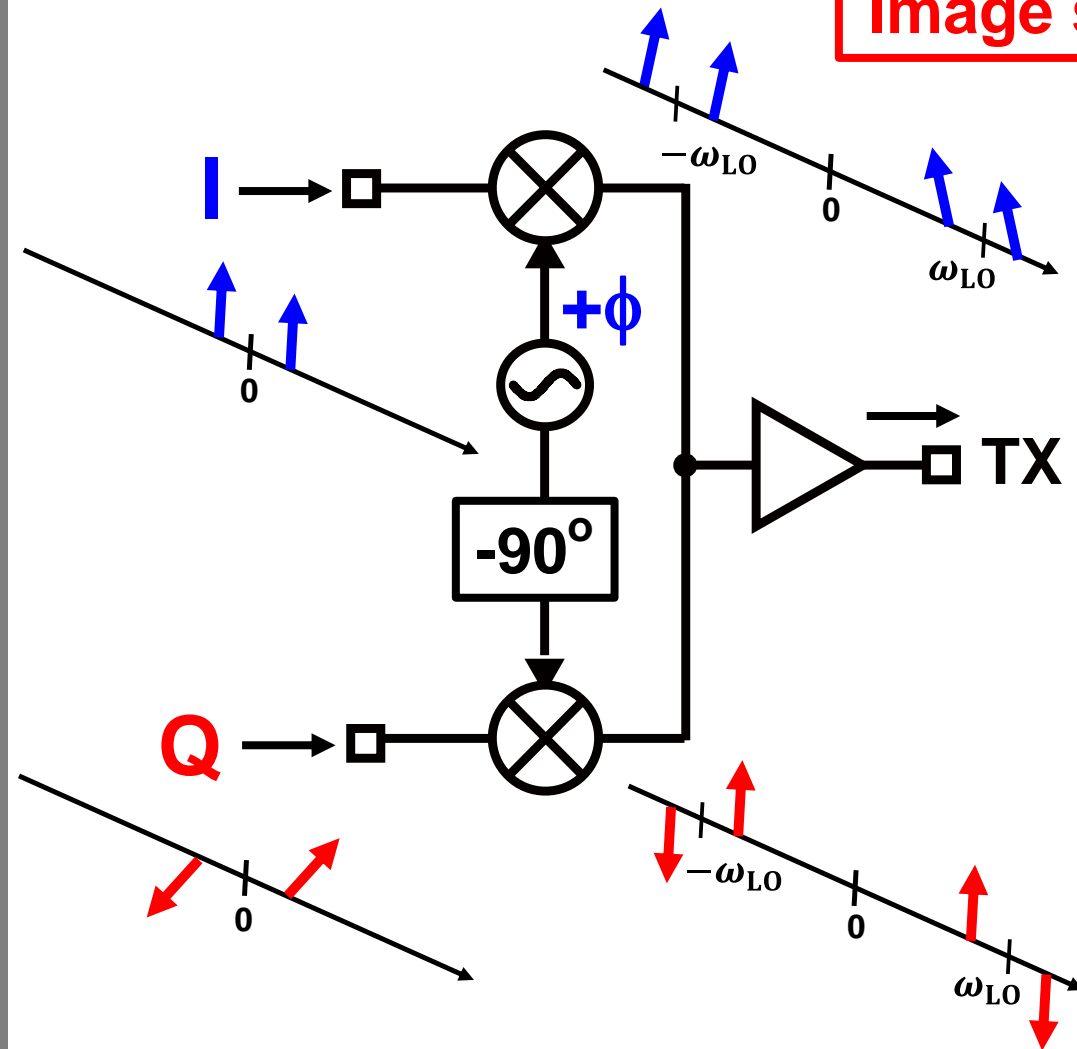


Stochastic TDC

 

Ideal condition (no noise, no PVT)

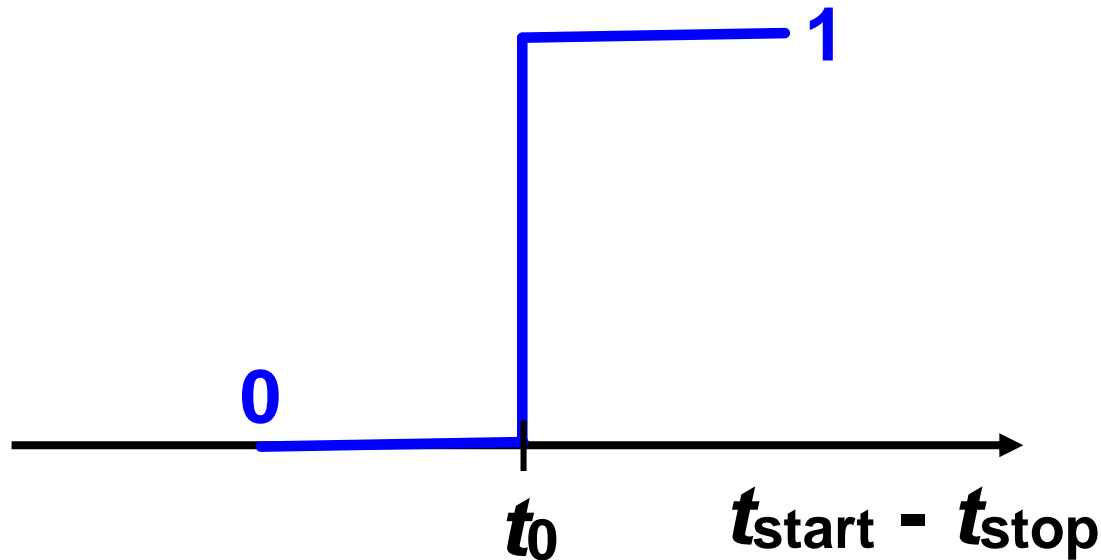


Stochastic TDC

 


Noise & Process variation

threshold distribution

 



Stochastic TDC

potentially synthesizable

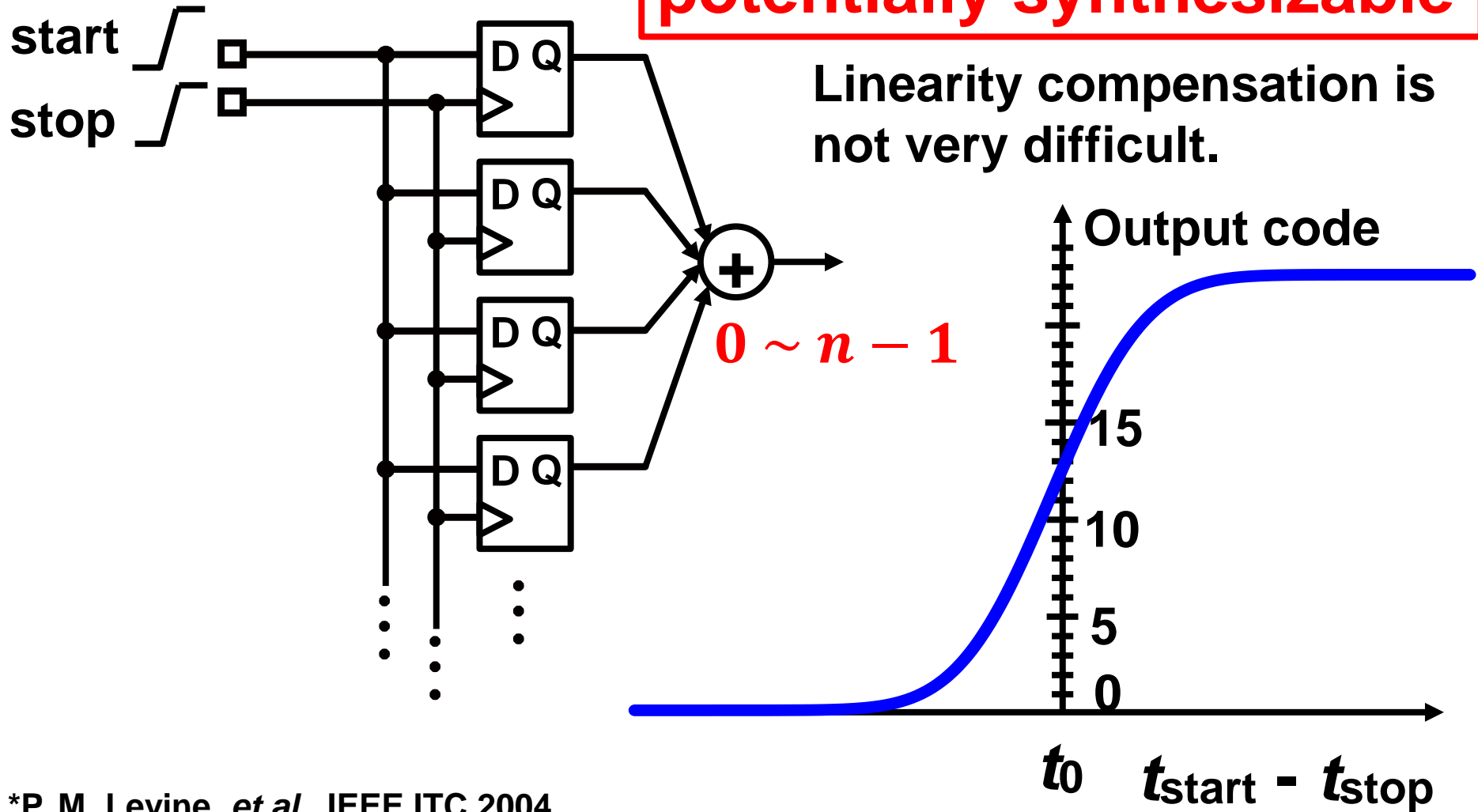

*P. M. Levine, et al., IEEE ITC 2004


Pulse Injection

  



- **Severe timing design** is required on the injection pulse width.

*B. Helal, *et al.*, JSSC 2009

Measured Phase Noise

 


Simulated C_{medium} against V_{in}

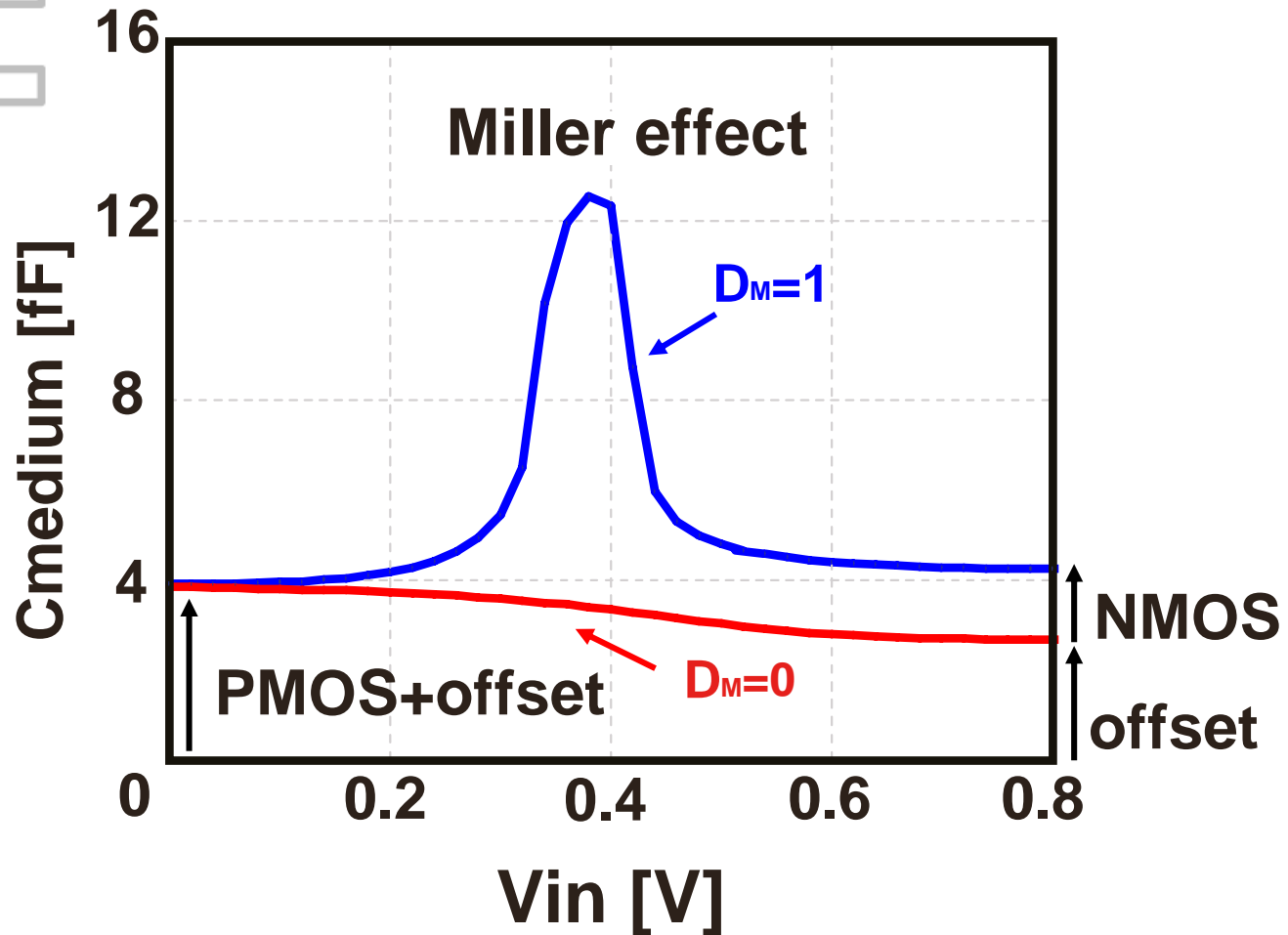 


Fine Varactor

Miller effect is gain-dependent.


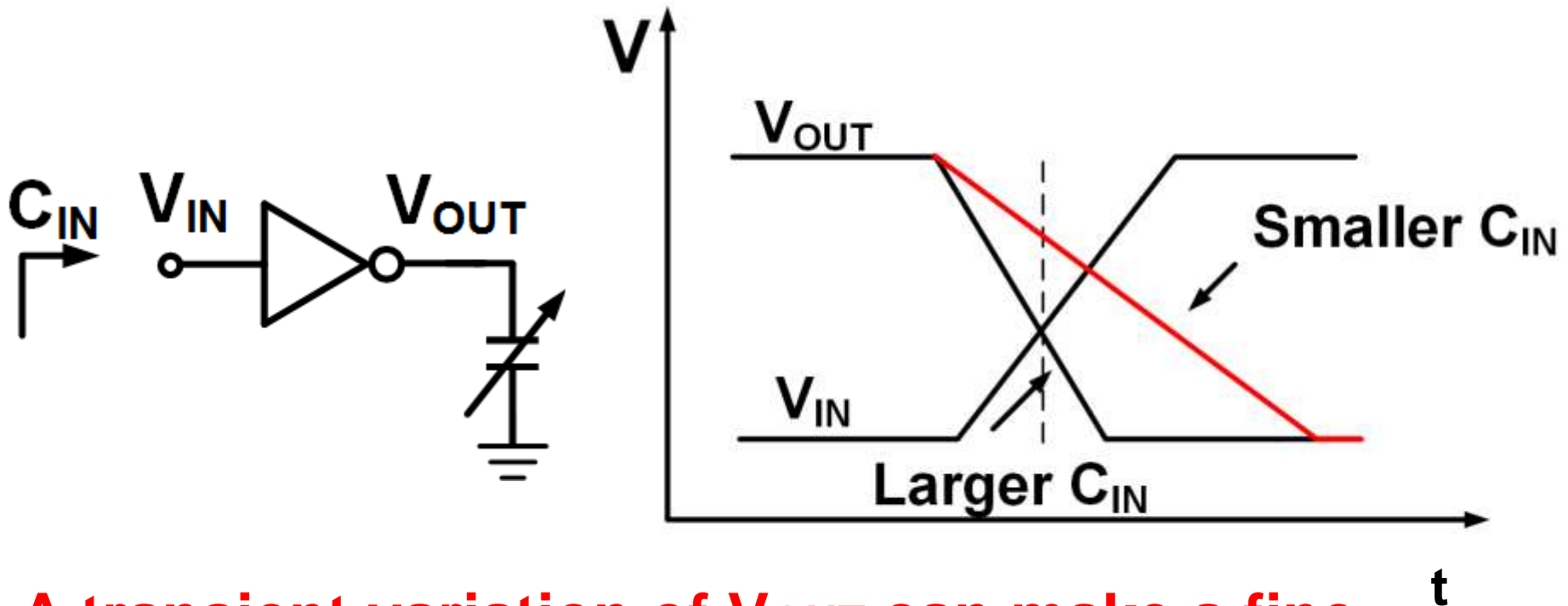


A transient variation of V_{OUT} can make a fine capacitance difference in C_{IN} .


Fine Varactor (cont.)

 

Medium resolution

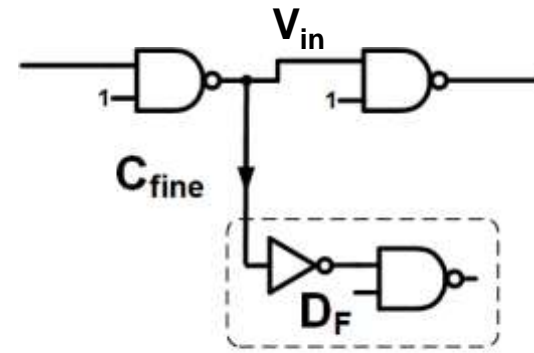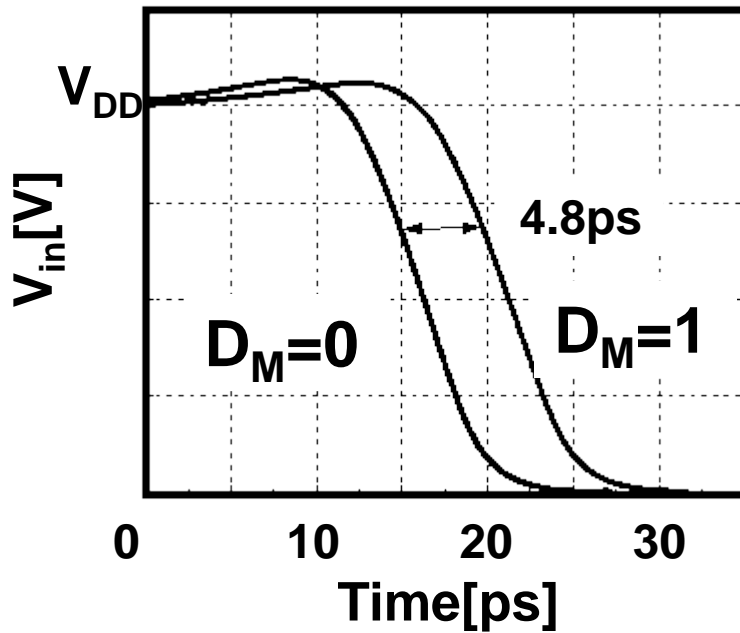

Fine resolution

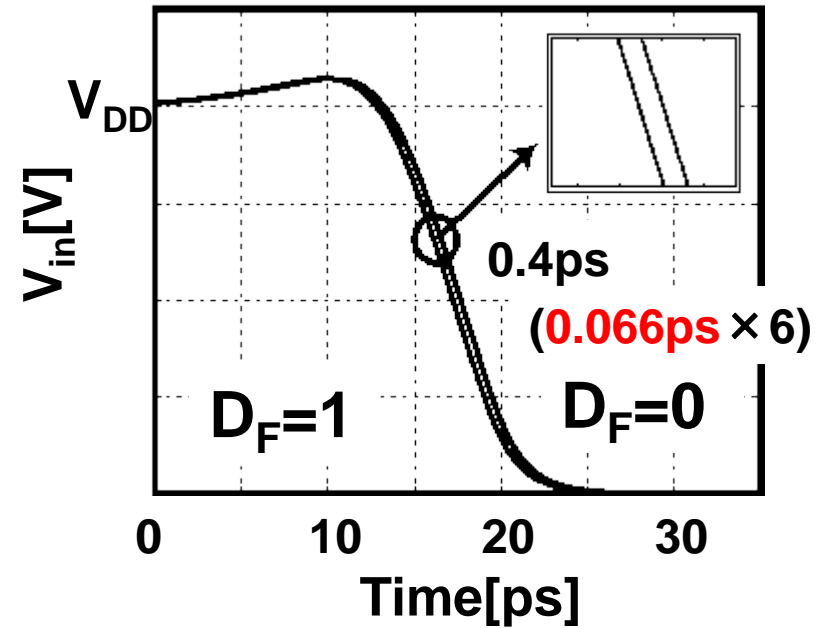


*W. Deng, et al., ISSCC 2014

Robust for Layout Uncertainty

Integrating Jitter: 1.7ps

P_{DC} : 780 μ W

FOM: -236.5 dB

 


**Fully synthesized
(proposed)**

Integrating Jitter: 2.32ps

P_{DC} : 640 μ W

FOM: -234.6 dB

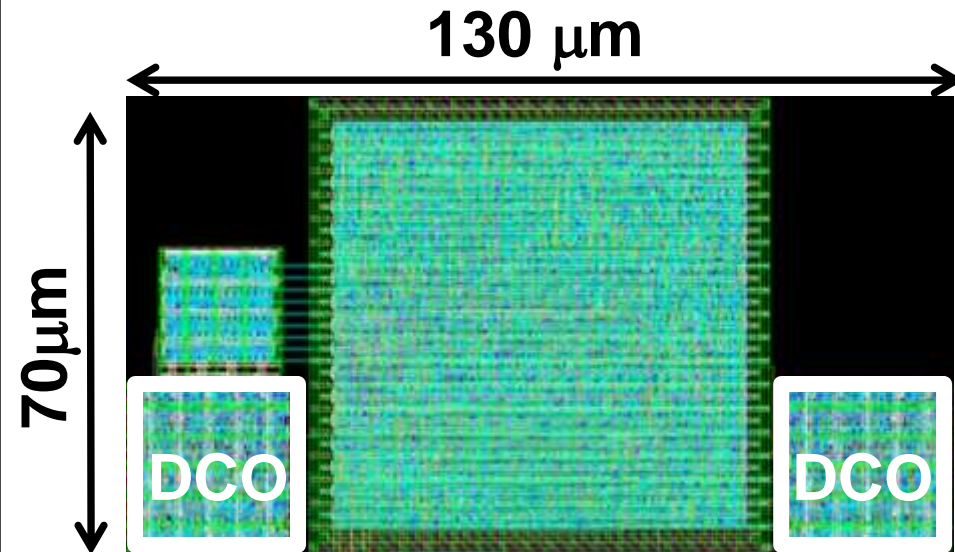

**Hierarchical P&R with
synthesized DCOs
(for comparison)**